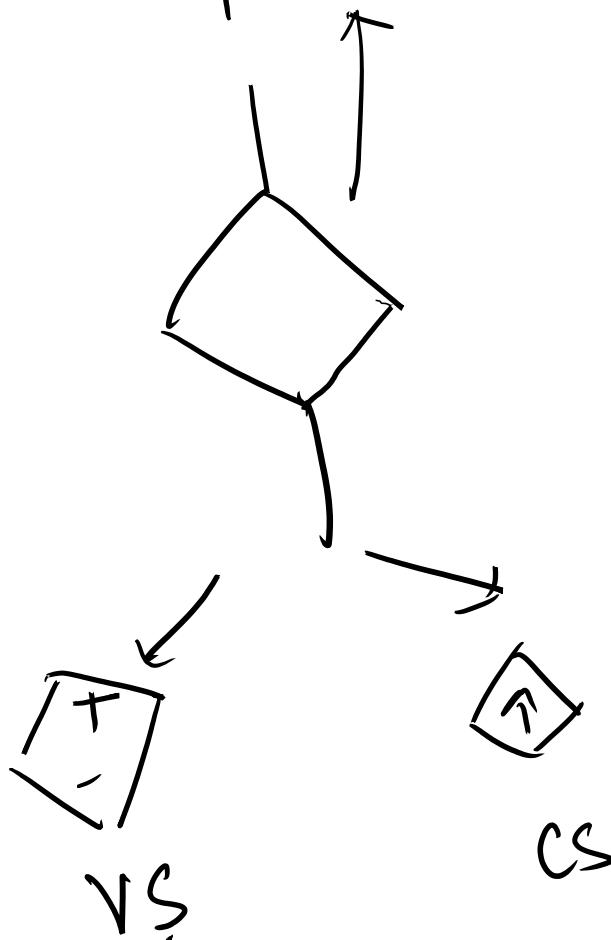


UES013 : Electrical & Elect Science


* Dependent & Independent Sources



CCVS



CCCS

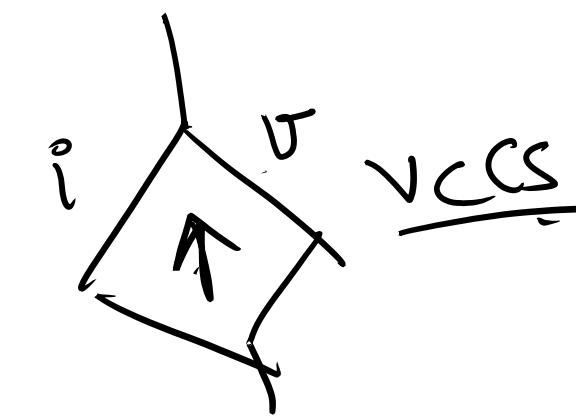

$H_3 \leftarrow CSE \rightarrow \checkmark \rightarrow \underline{UES013}$
 $\underline{H_1, H_2} CSE \rightarrow \cdot \rightarrow \underline{\underline{UES001}}$

* Kirchoff's Current Law (KCL)


→ Nodes

→ Branches

→ Loops

→ Mesh

→ Path

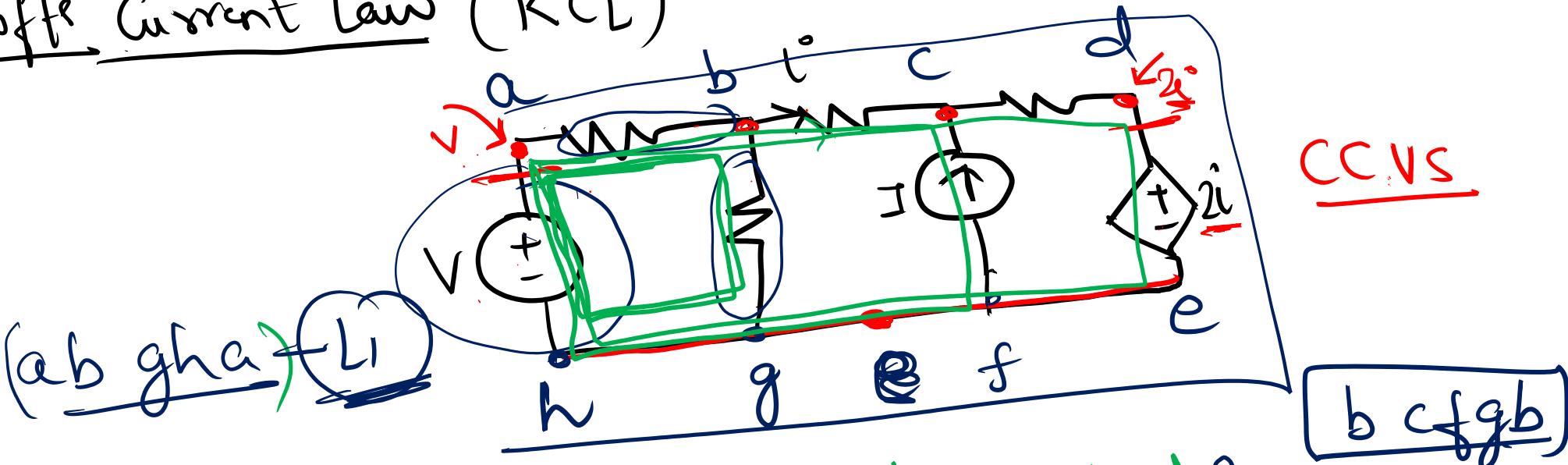

a b g h
a b c d
a b c d e f g h

a b c f g h a - loop 2


a b c d e f g h a - loop 3

Mesh → loop which does not have any other loops within it.

① KCL:

Algebraic sum of all currents at a node is zero
‘or’:

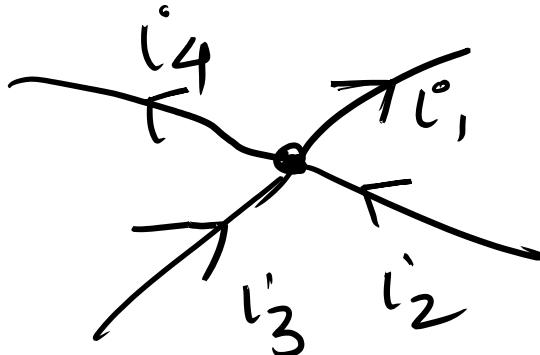Alg. sum of all currents entering a node =
“ “ “ “ leaving a node.




KCL at node;

$$i_1 + i_4 - i_3 - i_2 = 0$$

$$\underline{i_1 = -2A}$$

leaving the node as $(+)$

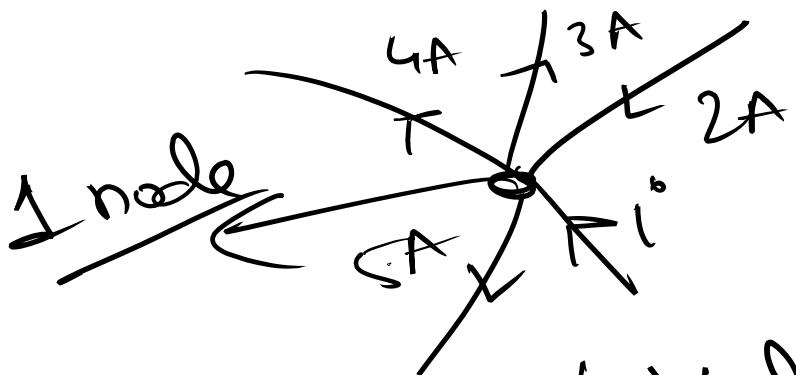


$$i^o = ?$$


$$3 + 4 + 5 - 2 - i^o = 0$$

② Kirchoff's Voltage law (KVL)

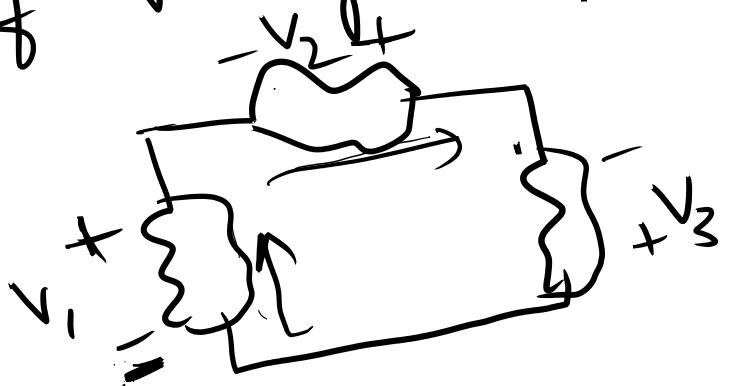Algebraic sum of voltage drops in a loop is zero



$$-V_1 - V_2 - V_3 = 0$$

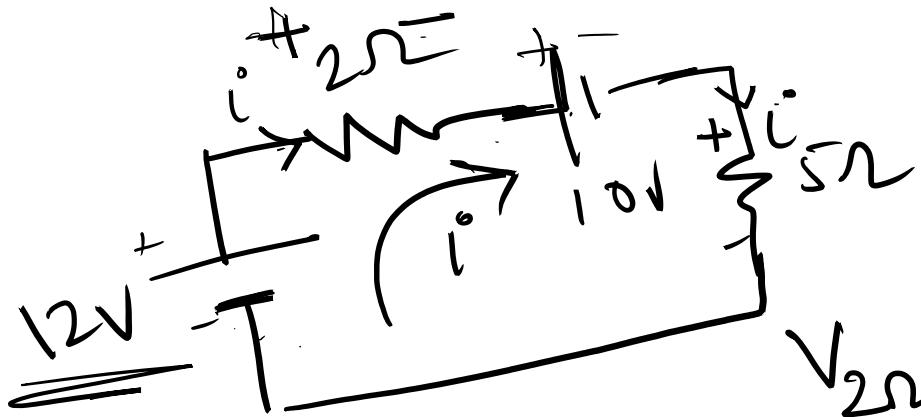

$$V_{2\Omega} = \frac{4}{7}V ; V_{10V} \Rightarrow \frac{10}{7}V$$

Applying KVL:

$$-12 + (i \cdot 2) + 10 + 5i = 0 \Rightarrow i = \frac{2}{7}A$$


$$V = iR \Rightarrow P = i^2 R \xrightarrow{\text{loss}}$$

$$\text{Power} \Rightarrow P = V \cdot i$$

$$P_{12V} = Vi = 12 \times \frac{2}{7} = \frac{24}{7}W \text{ (Delivery)} \quad P_{5\Omega} = \frac{10}{7} \times \frac{2}{7} = \frac{20}{49}W \text{ (absorbing)}$$

$$P_{2\Omega} = \frac{4}{7} \times \frac{2}{7} = \frac{8}{49}W \text{ (absorbing)} * \underline{\text{Note:}}$$
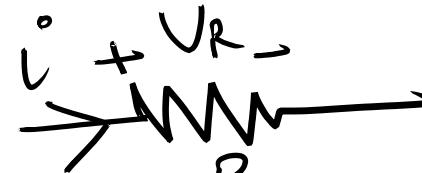
$$P_{10V} = 10 \times \frac{2}{7} = \frac{20}{7}W \text{ (absorbing)}$$




Absorbed

Delivered

12V → delivered
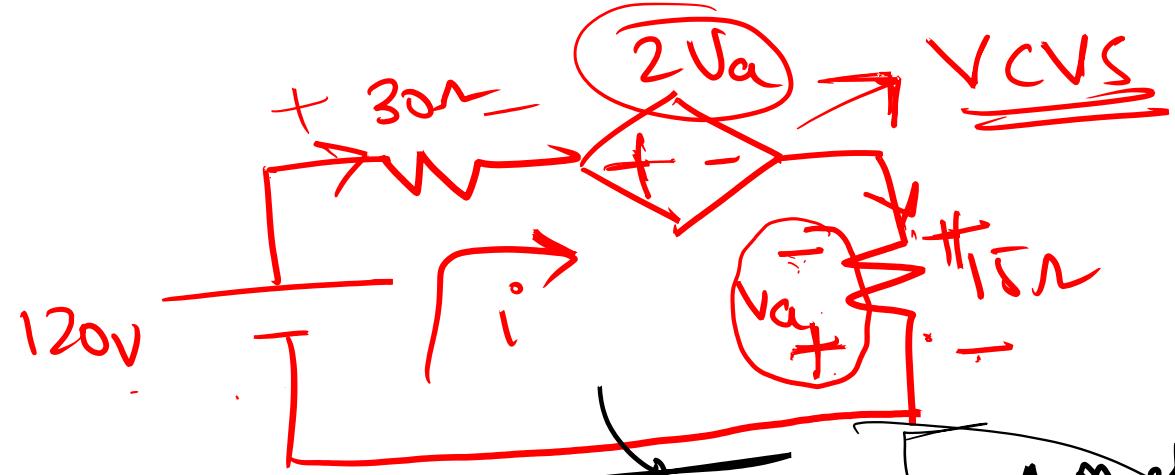
$$\left. \begin{array}{l} 2\Omega \\ 5\Omega \\ 10V \end{array} \right\} \text{Abs}$$



Applying KVL:

$$-120 + 30i + 2Va + 15i = 0 \quad (1)$$

$$i = ?$$



$$Va = ?$$

$$Va = 15i$$

Mechanical
Electrical
Model

Electri. \downarrow Analysis

Mathematical functions

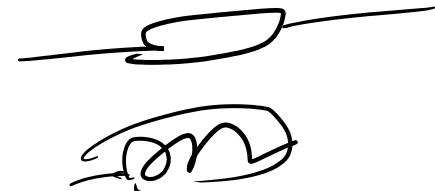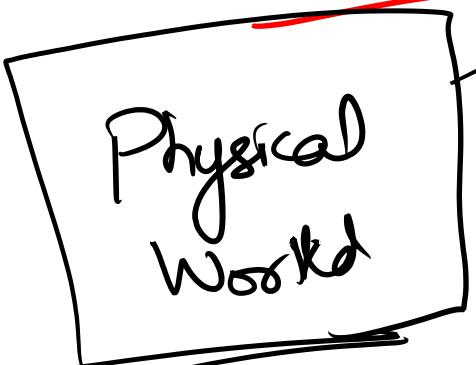

on



Analyse

\rightarrow KVL; KCL; Ohm's Law

* KVL \rightarrow Mesh Analysis


KCL \rightarrow Nodal Analysis

\rightarrow Analysis

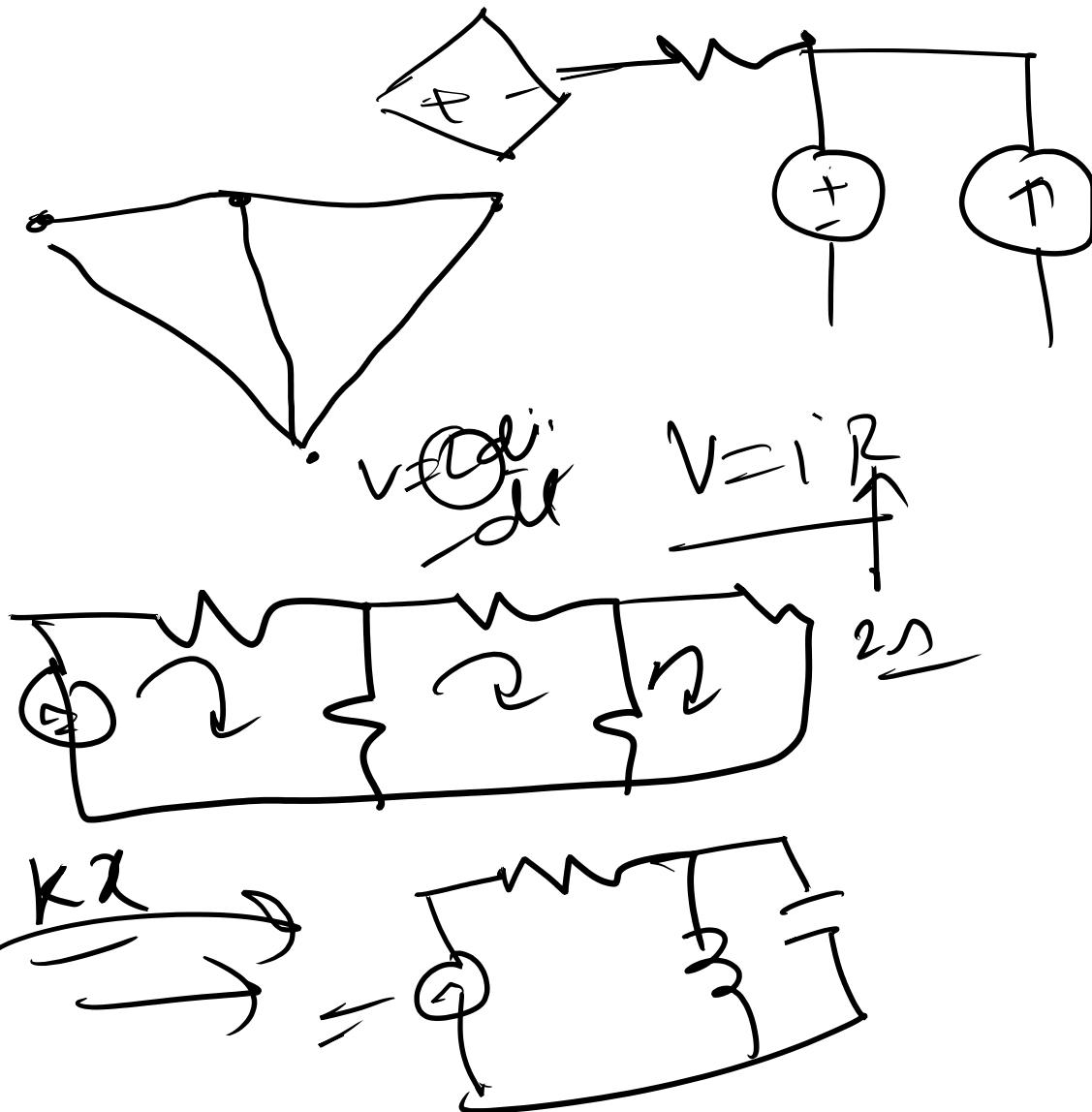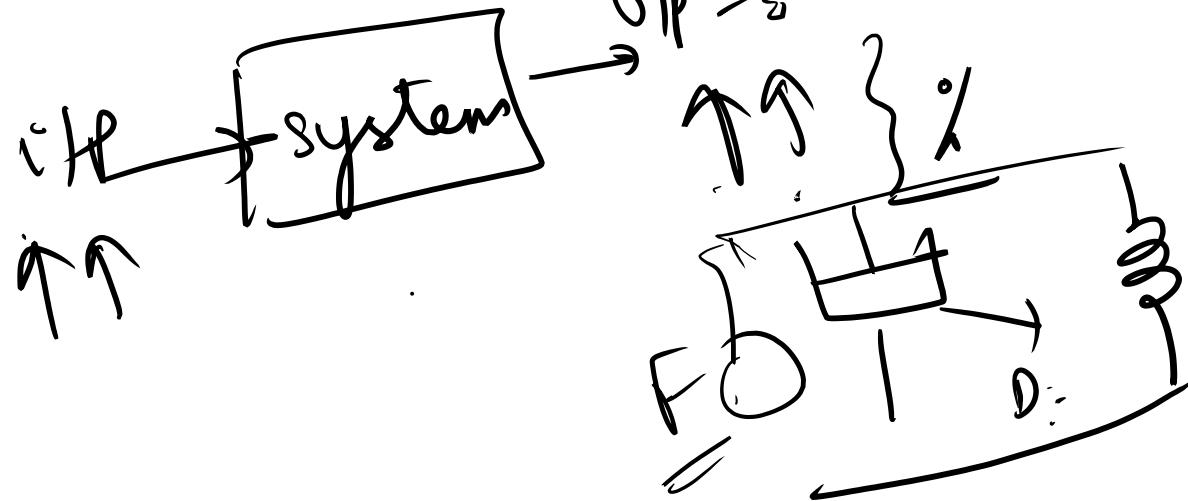

Node


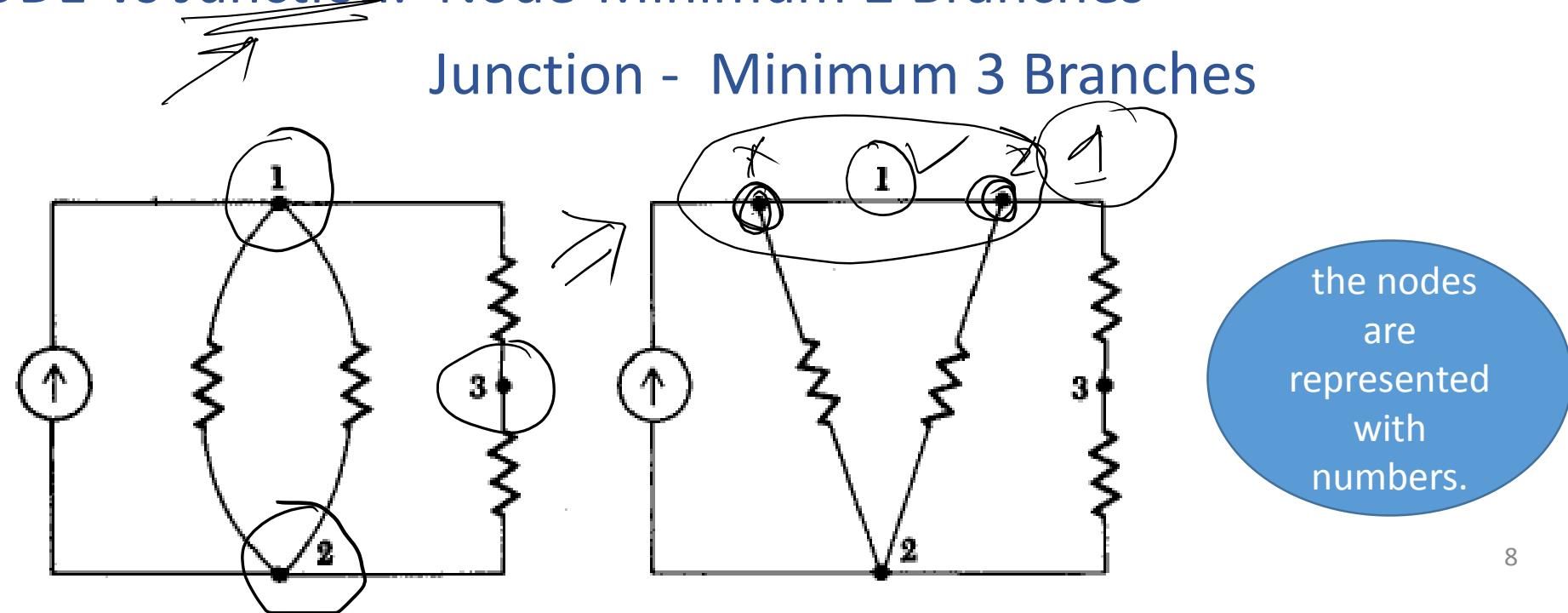
- A point at which two or more elements have a common connection is called a node.
- Two points connected through a zero resistance line will be considered as a same node.
- **NODE Vs Junction:** Node-Minimum 2 Branches



Loop, Node and Branch


Closed path

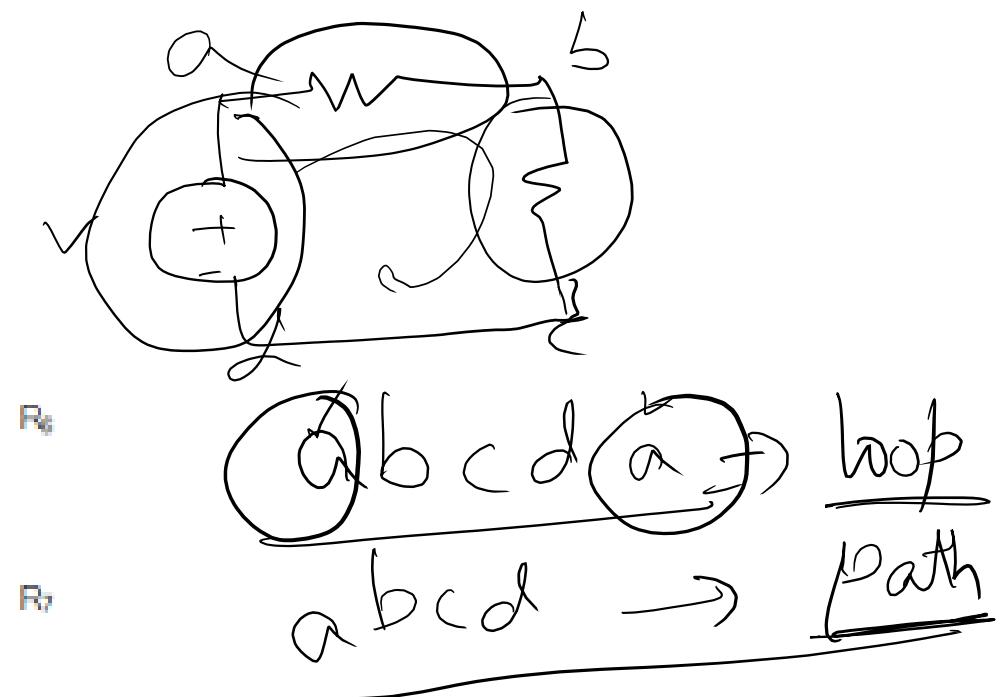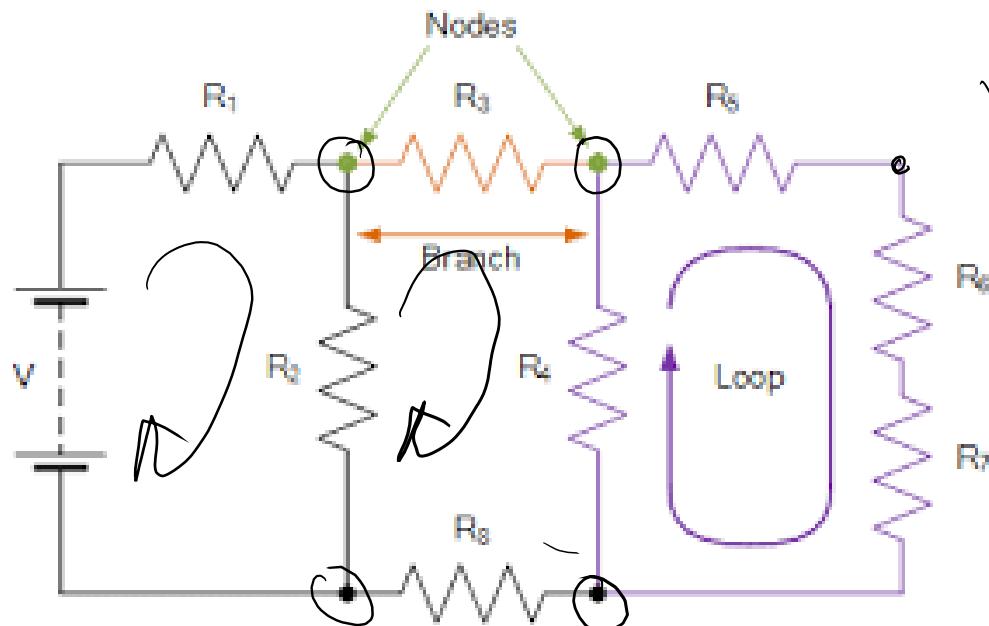- A branch is a single path in a network composed of simple element and one node at each end.




Mesh

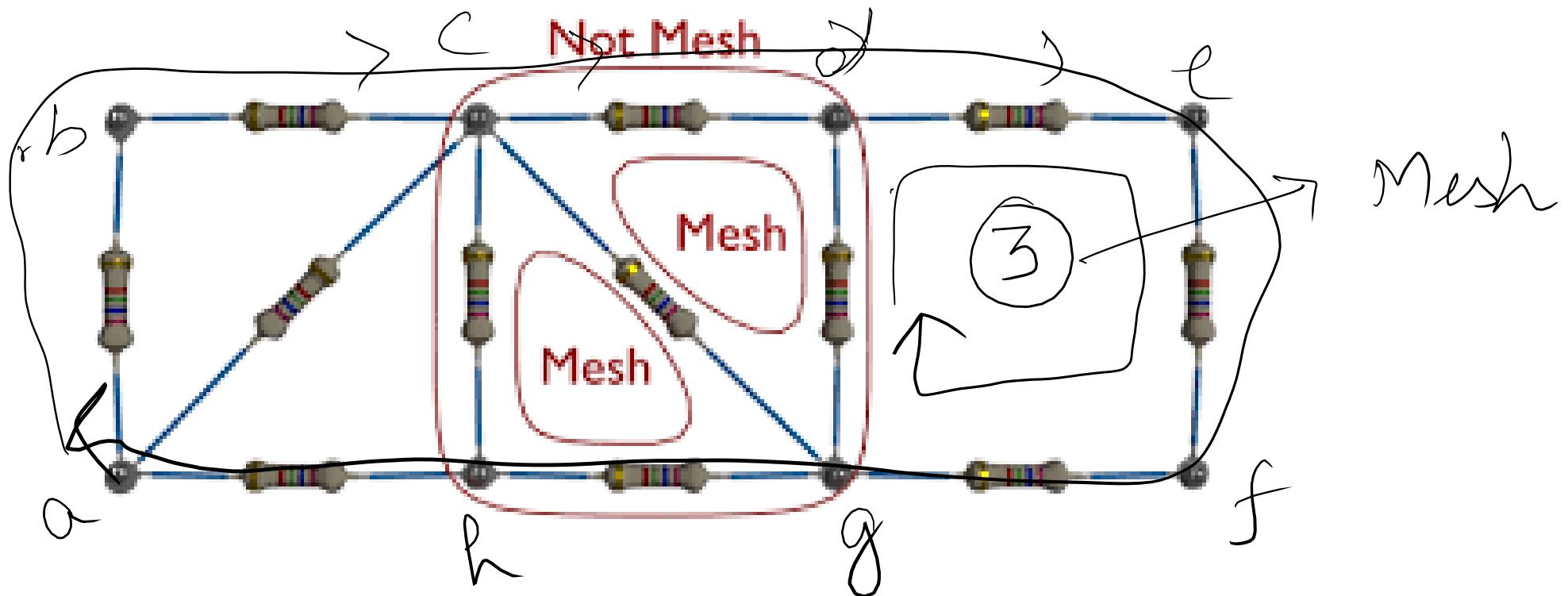- Mesh is a loop which does not contain any other loop within it.



Mesh

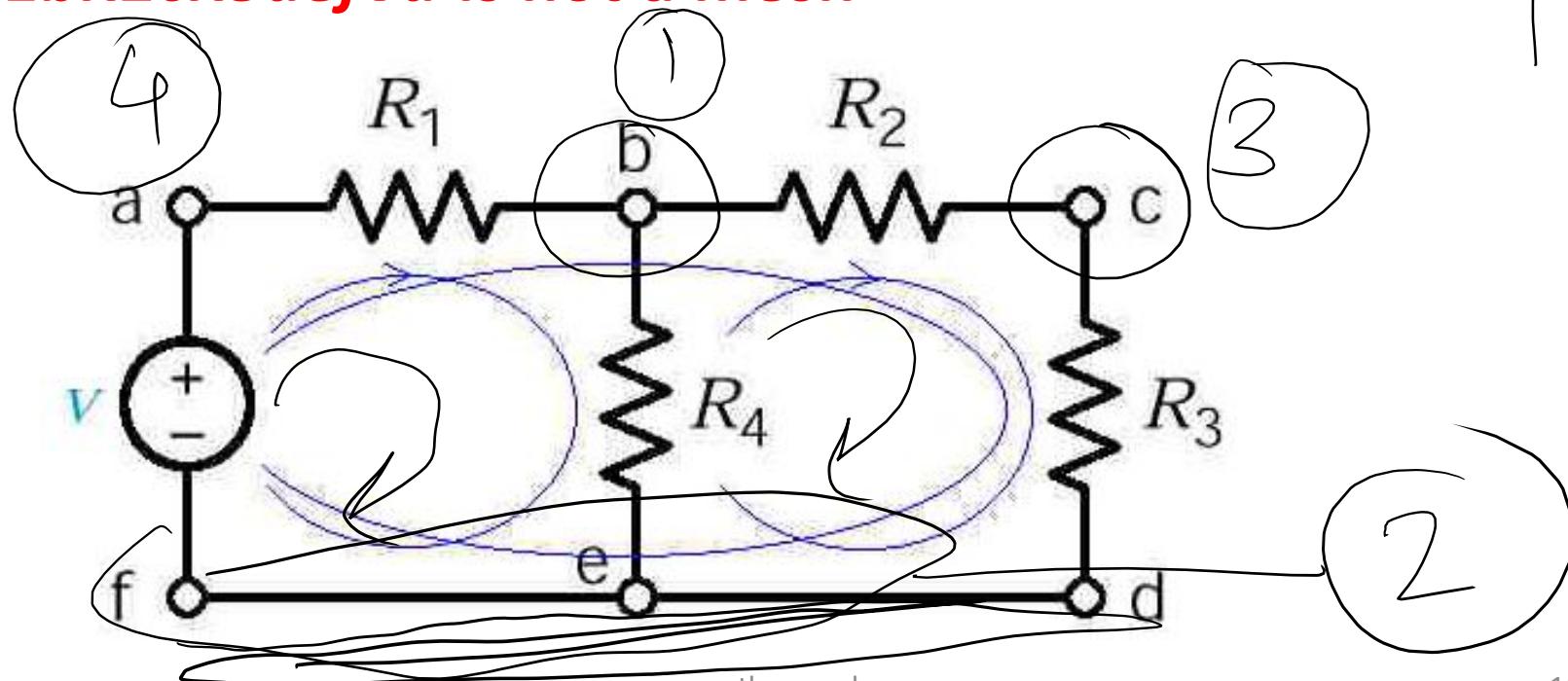- The circuit below has 4 nodes.
- The loops $aR1bR4efVa$ and $bR2cR3deR4b$ are mesh.
- **Loop $aR1bR2cR3defVa$ is not a mesh**




Branch, Loop and Nodes

- Relationship between branches, nodes and loops.

$$b = l + n - 1$$

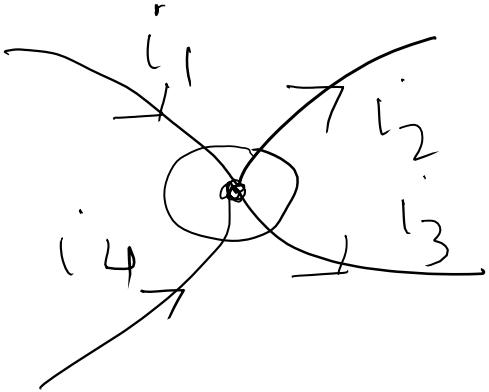
- *b – branches*
- *n - nodes*
- *l – independent loops*





Apply KCL at Node:

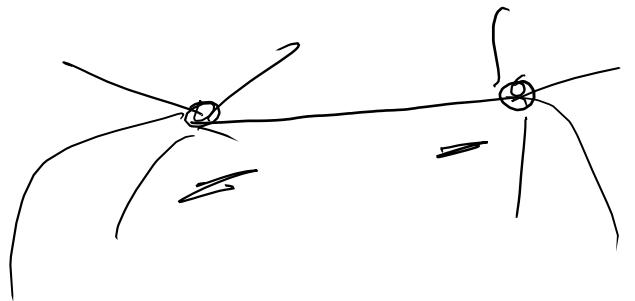* Convention → outgoing \oplus
 \rightarrow Uniform throughout




* Conservation of charge?

$$i_3 + i_2 - i_1 - i_4 = 0 \quad \rightarrow \text{no incoming } \oplus$$

$$i_1 + i_4 - i_3 - i_2 = 0$$

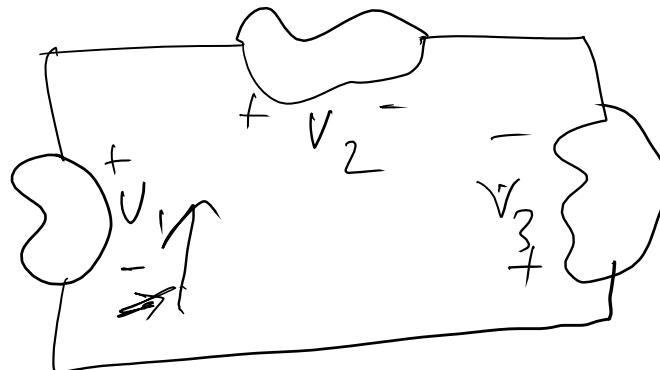KVL: The algebraic sum of voltages around any closed path in a circuit is zero.




Convention

$$-V_1 + V_2 - V_3 = 0$$

* KVL + KCL

KVL ; KCL

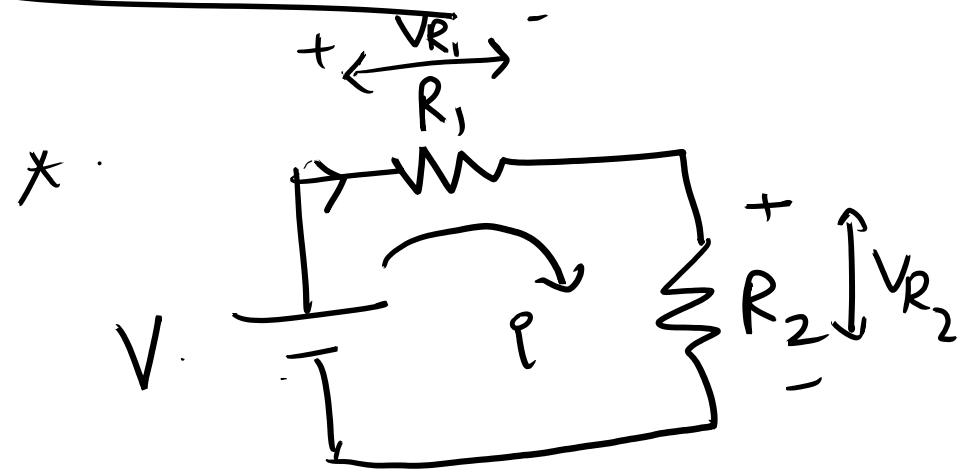

Apply KVL;

$$-V + iR_1 + iR_2 = 0$$

$$i(R_1 + R_2) = V$$

$$i = \frac{V}{R_1 + R_2} \quad \textcircled{1}$$


$$V_{R_1} = IR_1 = i \cdot R_1 = \frac{R_1 V}{R_1 + R_2} \quad \textcircled{2}$$

$$V_{R_2} = IR_2 = iR_2 = \frac{R_2 V}{R_1 + R_2} \quad \textcircled{3}$$

Eq \textcircled{2} & \textcircled{3} \implies \underline{\text{Voltage Division}}

$$V_{R_1} = R_1 \frac{V}{(R_1 + R_2)}$$


$$V_{R_2} = R_2 \frac{V}{(R_1 + R_2)}$$

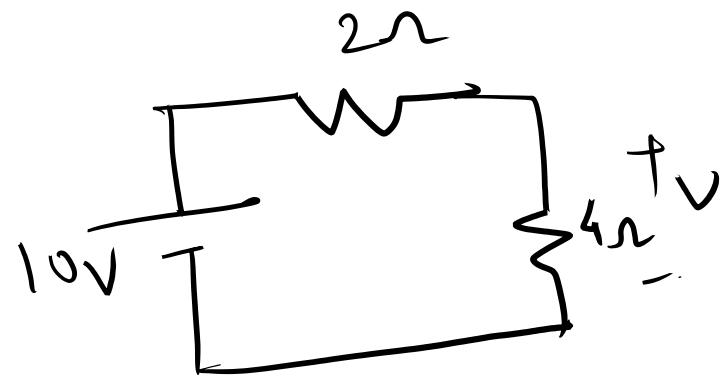

$$V = 4 \times \frac{10}{4+2} = \frac{40}{6} \text{ Volts}$$

Voltage Div. $\Rightarrow R \cdot \frac{V}{\text{Sum of } R}$

* Current Division

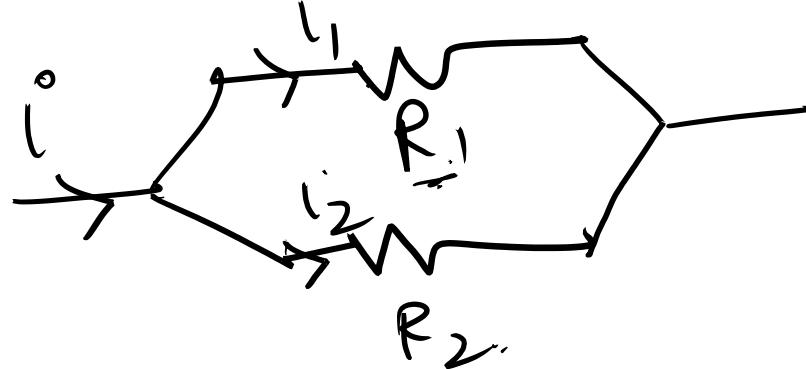

$$i_1 = \frac{i \cdot R_2}{R_1 + R_2}$$

$$i_2 = \frac{i \cdot R_1}{R_1 + R_2}$$

* Mesh Analysis

→ Identify Meshes & take some variables for mesh currents

→ Apply KVL in individual meshes.


Mesh ①

$$-10 + 2i_1 + 6(i_1 + i_2) = 0 \quad -①$$

Mesh ②


$$+4i_2 - 6 + 6(i_1 + i_2) = 0 \quad -②$$
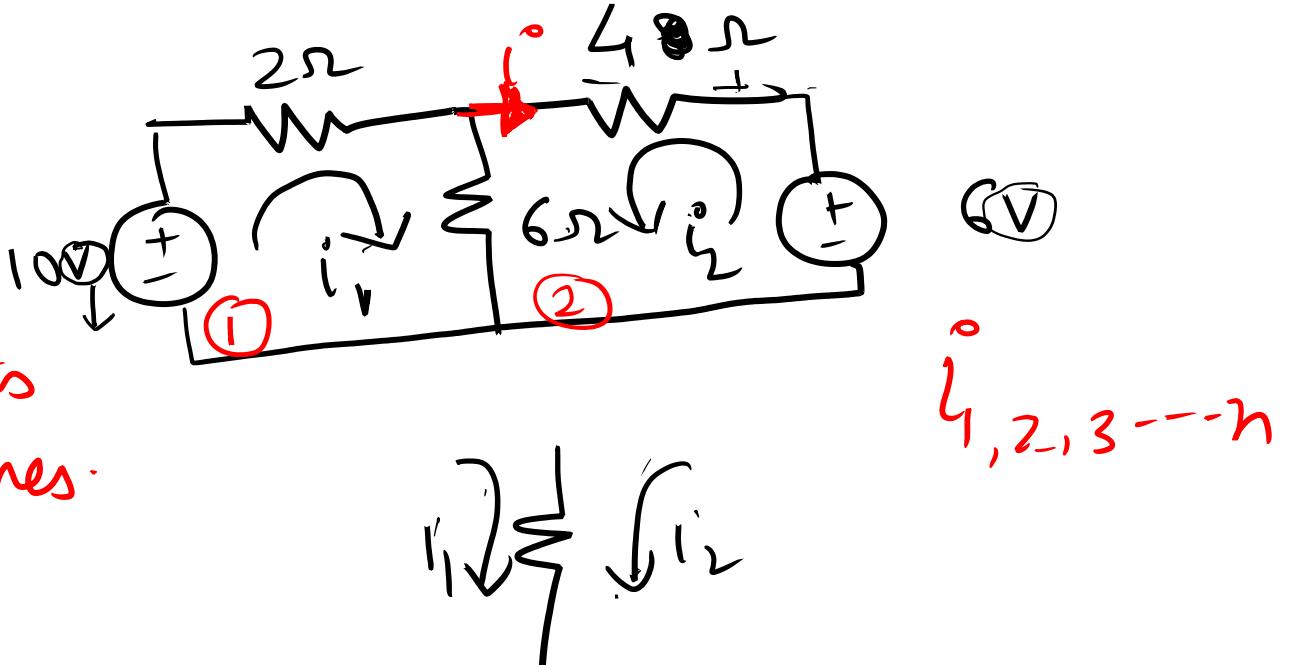
$$i_1 = \frac{16}{11} \text{ A} ; i_2 = -\frac{3}{11} \text{ A}$$



$$\begin{aligned} i_1 &\uparrow \\ &\left\{ \begin{array}{l} 2 \\ 6 \end{array} \right. \uparrow \quad \uparrow \quad \uparrow \\ &= 6(i_2 - i_1) \\ &6(i_1 - i_2) \end{aligned}$$

*

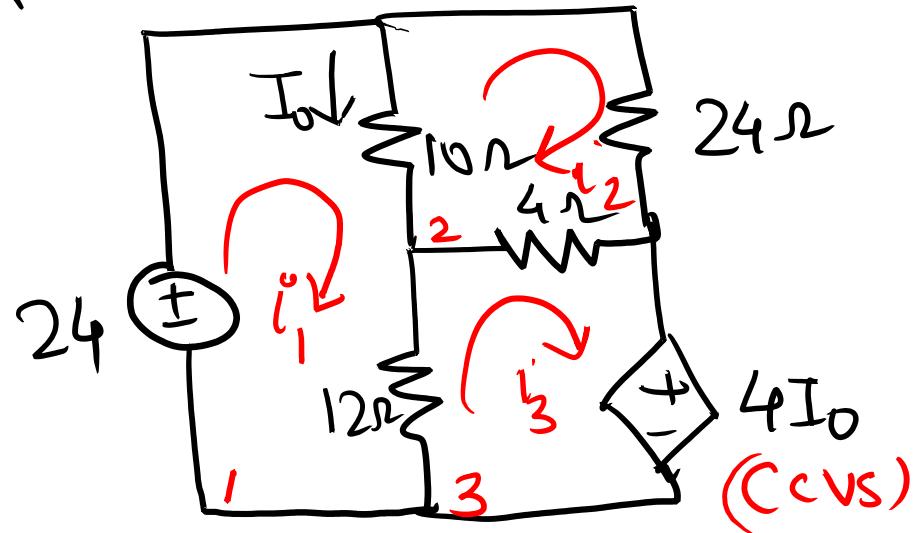

* Mesh 1

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0 \quad \text{--- (1)}$$


* Mesh 2

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0 \quad \text{--- (2)}$$

* Mesh 3

$$4(i_3 - i_2) + 4I_0 + 12(i_3 - i_1) = 0 \quad \text{--- (3)}$$

$$I_0 = i_1 - i_2 \quad \text{--- (4)}$$

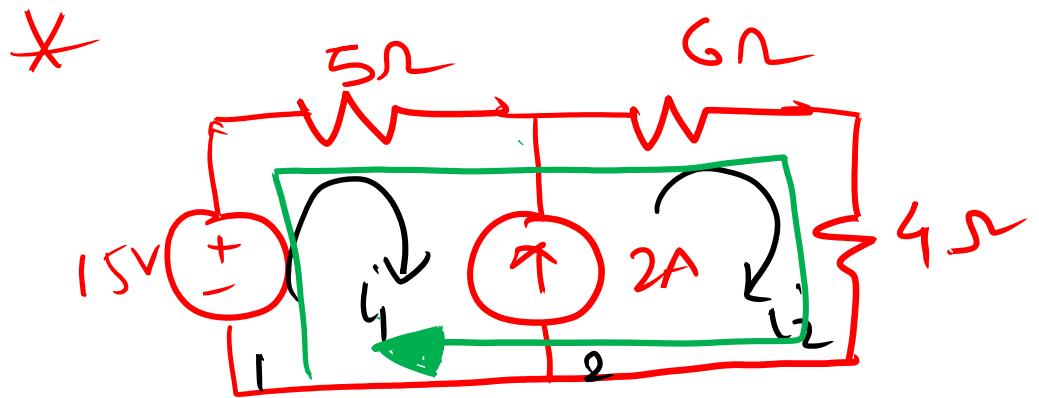


→ Super Mesh

$$-15 + 5i_1 + 6i_2 + 4i_2 = 0 \quad \text{---} ①$$

$$i_2 - i_1 = 2 \quad \text{---} ②$$

Mesh 1:


$$-15 + 5i_1 + ? = 0$$

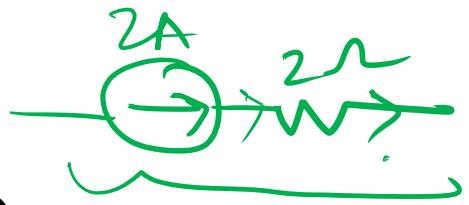

Mesh 2:

$$6i_2 + 4i_2 + ? = 0$$



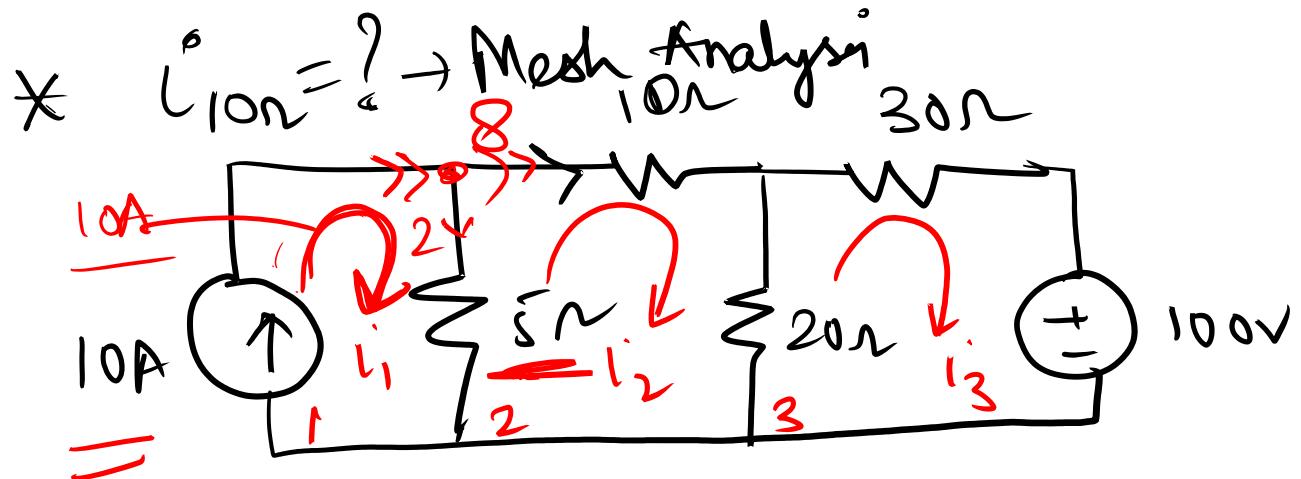

$$5(i_2 - i_1)$$

$$\underline{5(12 - 10) =}$$

20

Mesh 1: $\rightarrow i_1 = 10 \rightarrow 0$

Mesh 2: $10i_2 + 20(i_2 - i_3) + 5(i_2 - i_1) = 0$

2

Mesh 3:

$$\overline{30i_3 + 100 + 20(i_3 - i_2)} = 0$$

3

→ Mesh Analysis + Super Mesh

→ Nodal Analysis : (KCL)

① Identify nodes


② Mark the nodes
with unknown voltages

③ Take one node as a ref
with ($V=0$)


④ Take currents on all node

(outgoing current → +ive)

⑤ Finally write KCL eq. on each node

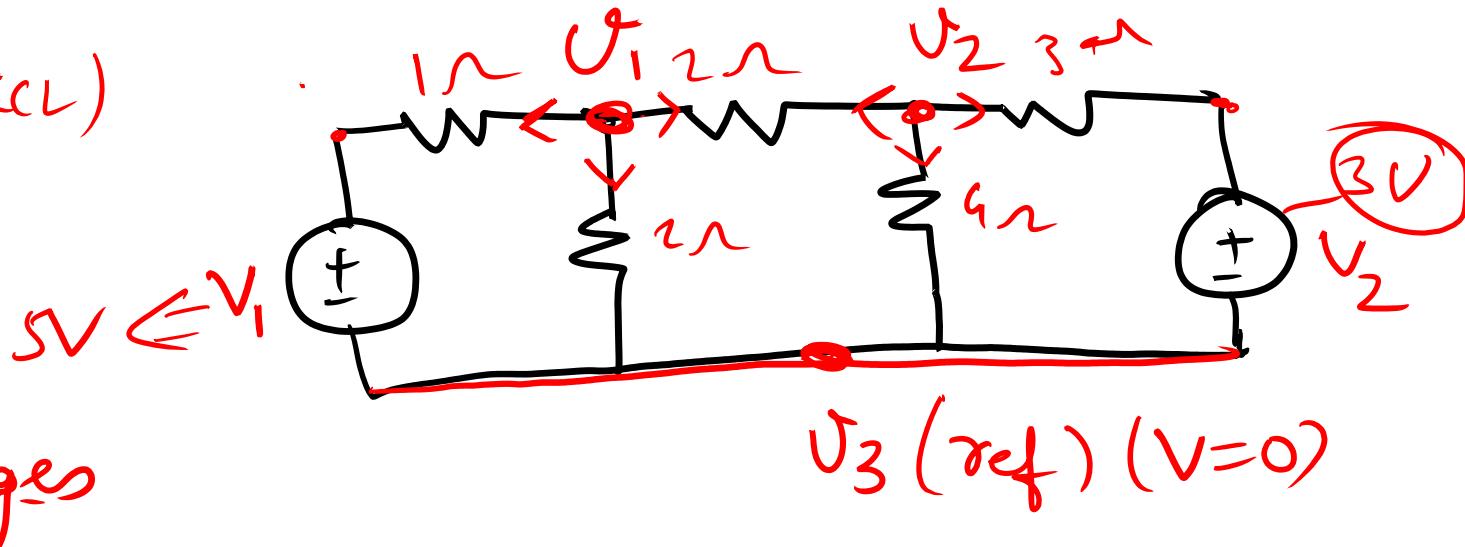

Q

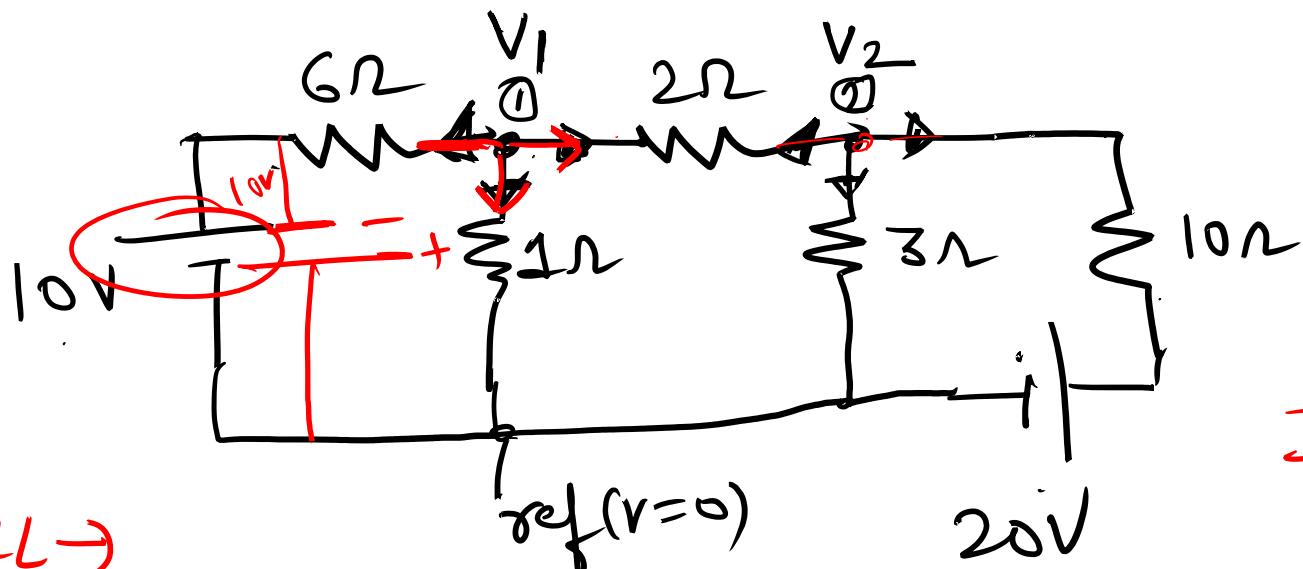

$$i = \frac{V}{R} = \frac{V_1 - V_2}{R}$$

\Rightarrow Nodal Analysis


KCL \rightarrow

At node 1

$$\frac{V_1 - 10}{6} + \frac{V_1 - 0}{1} + \frac{V_1 - V_2}{2} = 0$$

KCL at Node 2
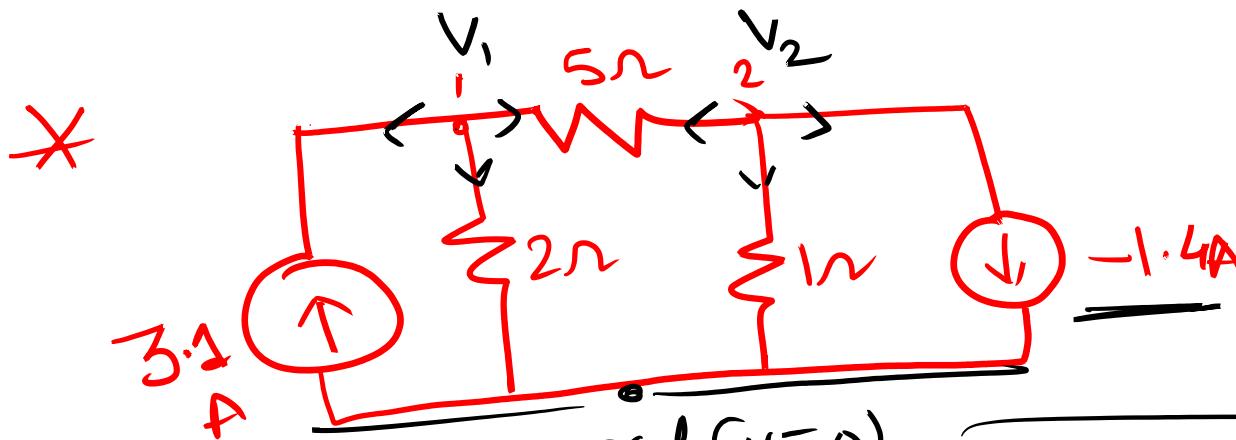
$$\frac{V_2 - V_1}{2} + \frac{V_2 - 0}{3} + \frac{V_2 - 20}{10} = 0$$



KCL \rightarrow
At node 1

ref ($v=0$)



$$\begin{cases} V_1 = 5 \text{ V} \\ V_2 = 2 \text{ V} \end{cases}$$

$$-3.1 + \frac{V_1 - 0}{2} + \frac{V_1 - V_2}{5} = 0$$

KCL at node 2

$$\frac{V_2 - V_1}{5} + \frac{V_2 - 0}{1} + (-\underline{\underline{1.4}}) = 0$$

* find $i_A; i_B; i_C$ using Nodal

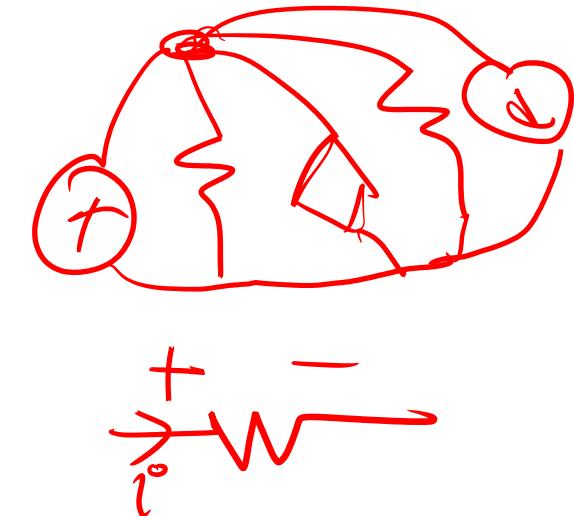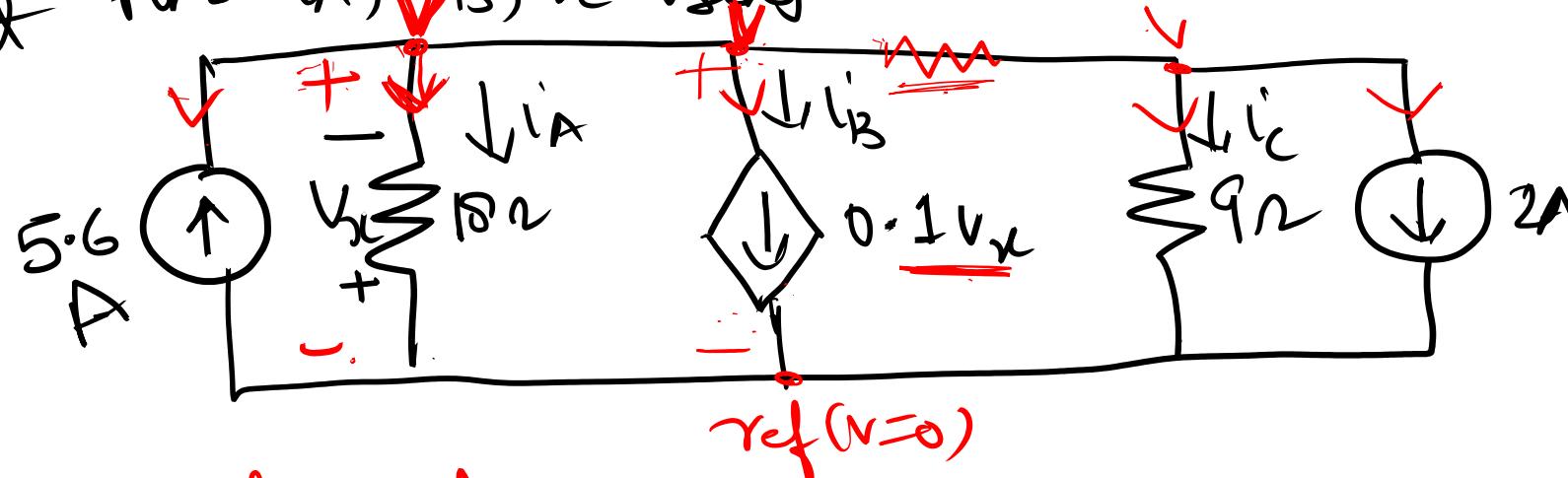


KCL eq for Node :

$$-5.6 + \frac{V_x}{18} + 0.1V_x + \frac{V_x}{9} + 2 = 0 \quad \textcircled{1}$$

$$V_x = -18i_A \quad \textcircled{2}$$

$V_x = -V$

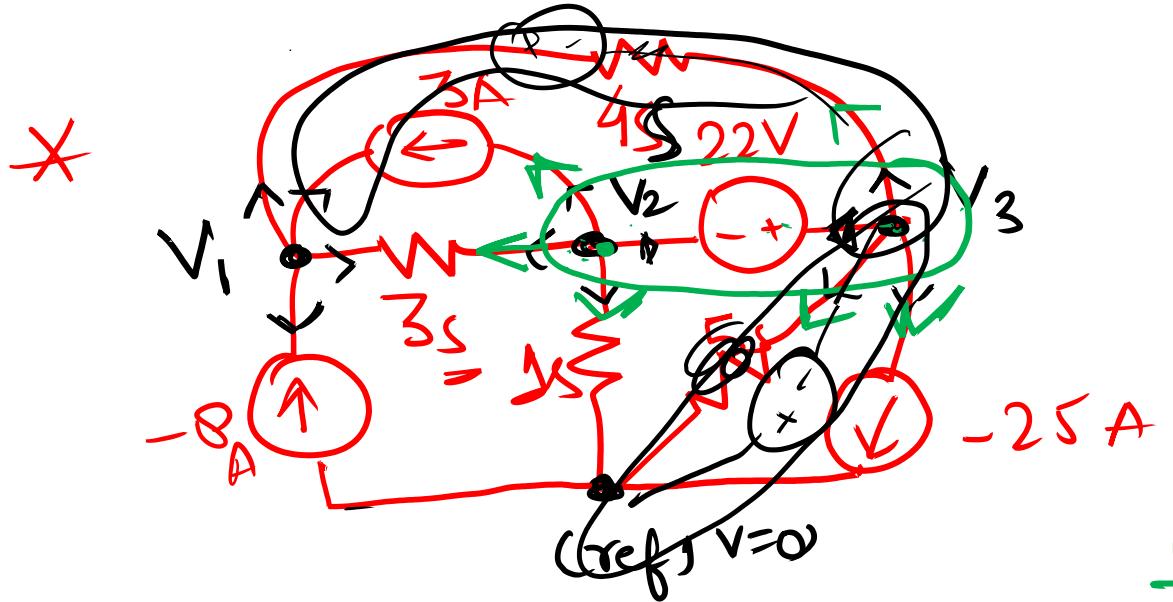

$\text{R}_f \frac{1}{R} = \text{S Conduct } \left(\frac{\text{A}^{-1}}{\text{s}} \right)$

$v_3 - v_2 = 22$

$v_1 - v_2 = 22$

$(v_1 - v_2) 2s$

KCL at Node 1

$$(v_1 - v_3)4 + (v_1 - v_2)3 - 3 - (-8) = 0 \quad \cancel{-8}$$

Super Node

KCL at Node 2

$$(v_2 - v_1)3 + 3 + (v_2 - 0)1 + ? = 0$$

KCL at Node 3

$$- + ? = 0$$

$$(v_2 - v_1)3 + 3 + v_2 \cdot 1 + (v_3 - v_1)4 + (v_3 - 0)5 + (-25) = 0$$

$\cancel{+ 25}$