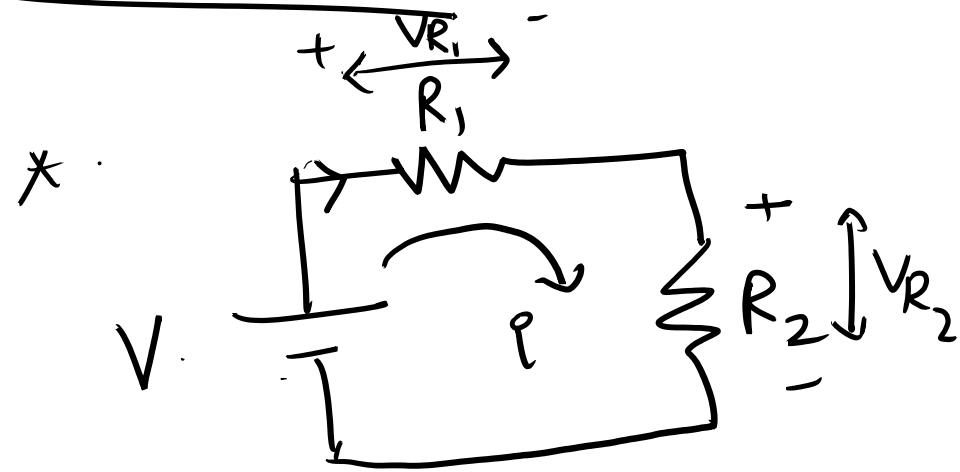


KVL ; KCL



Apply KVL;

$$-V + iR_1 + iR_2 = 0$$

$$i(R_1 + R_2) = V$$

$$i = \frac{V}{R_1 + R_2} \quad \textcircled{1}$$


$$V_{R_1} = IR_1 = i \cdot R_1 = \frac{R_1 V}{R_1 + R_2} \quad \textcircled{2}$$

$$V_{R_2} = IR_2 = iR_2 = \frac{R_2 V}{R_1 + R_2} \quad \textcircled{3}$$

Eq \textcircled{2} & \textcircled{3} \implies \underline{\text{Voltage Division}}

$$V_{R_1} = R_1 \frac{V}{(R_1 + R_2)}$$


$$V_{R_2} = R_2 \frac{V}{(R_1 + R_2)}$$

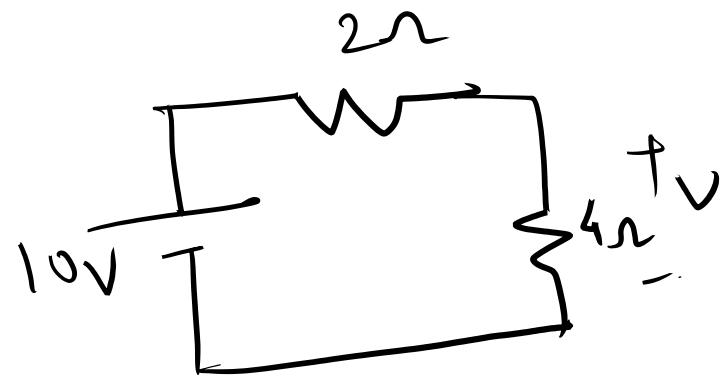

$$V = 4 \times \frac{10}{4+2} = \frac{40}{6} \text{ Volts}$$

Voltage Div. $\Rightarrow R \cdot \frac{V}{\text{Sum of } R}$

* Current Division

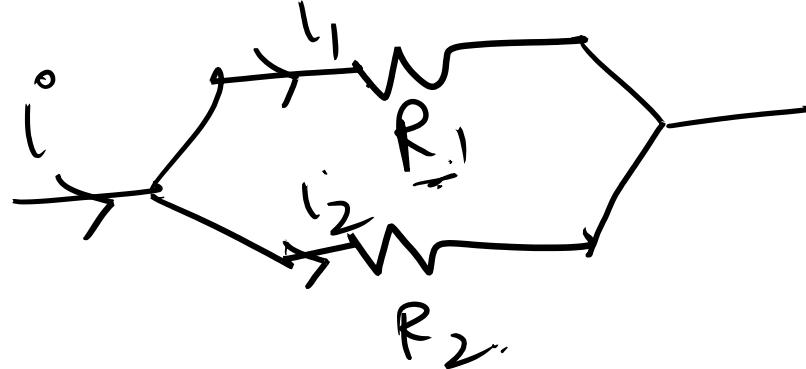

$$i_1 = \frac{i \cdot R_2}{R_1 + R_2}$$

$$i_2 = \frac{i \cdot R_1}{R_1 + R_2}$$

* Mesh Analysis

→ Identify Meshes & take some variables for mesh currents

→ Apply KVL in individual meshes.


Mesh ①

$$-10 + 2i_1 + 6(i_1 + i_2) = 0 \quad \textcircled{1}$$

Mesh ②

$$+4i_2 - 6 + 6(i_1 + i_2) = 0 \quad \textcircled{2}$$

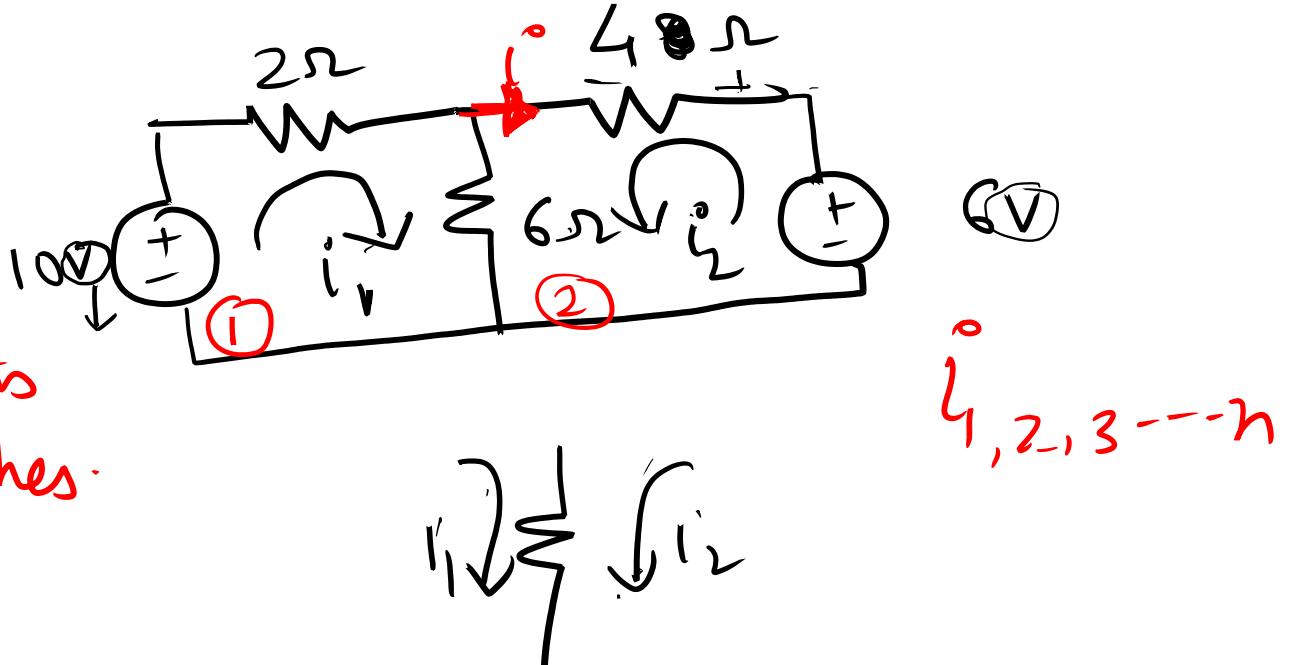
$$i_1 = \frac{16}{11} \text{ A} ; i_2 = -\frac{3}{11} \text{ A}$$



$$i_1, i_2 \underbrace{\qquad}_{f_{i_1}} \qquad \qquad \qquad i_2 \underbrace{\qquad}_{f_{i_2}}$$

$$\begin{aligned} i_1 &\underbrace{\qquad}_{f_{i_1}} \\ &= 6(i_2 - i_1) \\ 6(i_1 - i_2) &\qquad \end{aligned}$$

*

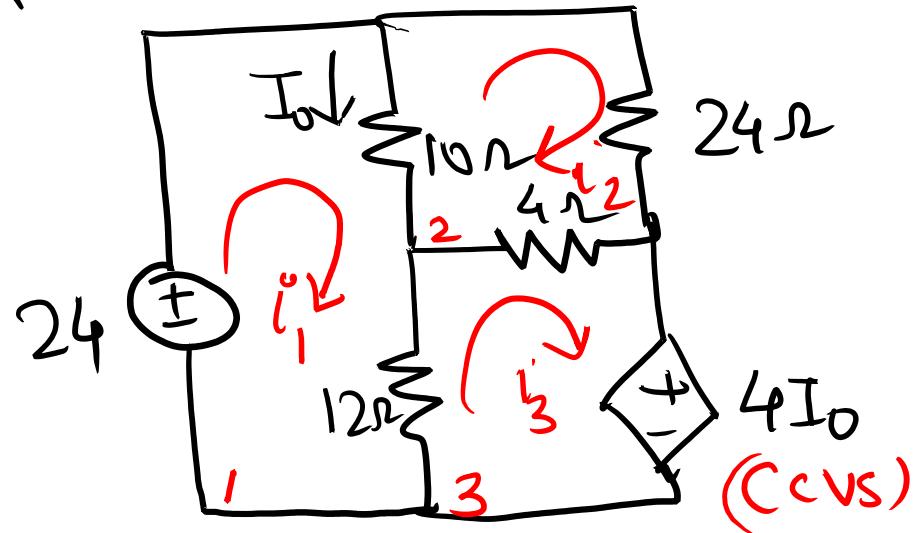

* Mesh 1

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0 \quad \text{--- (1)}$$


* Mesh 2

$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0 \quad \text{--- (2)}$$

* Mesh 3

$$4(i_3 - i_2) + 4I_0 + 12(i_3 - i_1) = 0 \quad \text{--- (3)}$$

$$I_0 = i_1 - i_2 \quad \text{--- (4)}$$

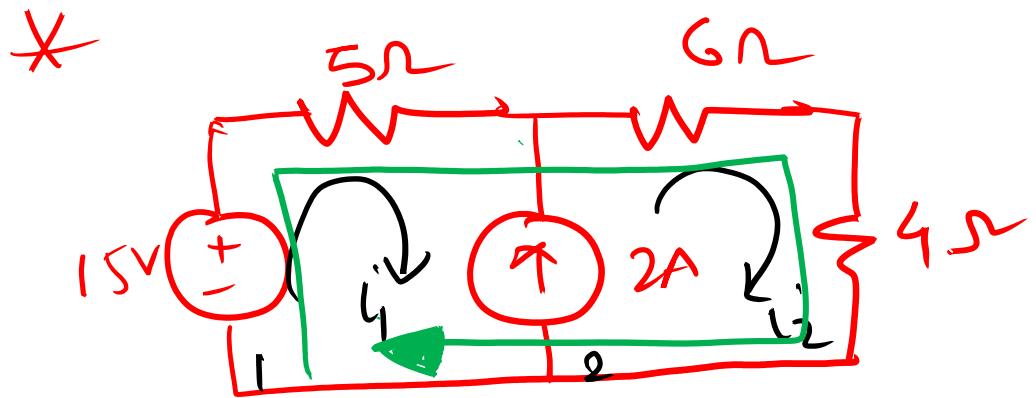


→ Super Mesh

$$-15 + 5i_1 + 6i_2 + 4i_2 = 0 \quad \text{---} ①$$

$$i_2 - i_1 = 2 \quad \text{---} ②$$


Mesh 1:


$$-15 + 5i_1 + ? = 0$$

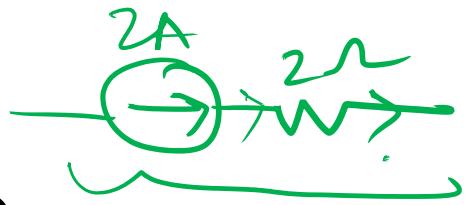

Mesh 2:

$$6i_2 + 4i_2 + ? = 0$$

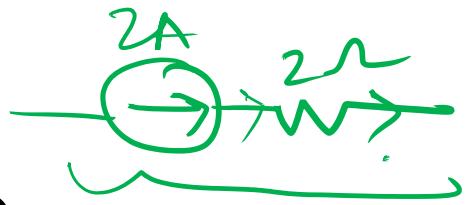

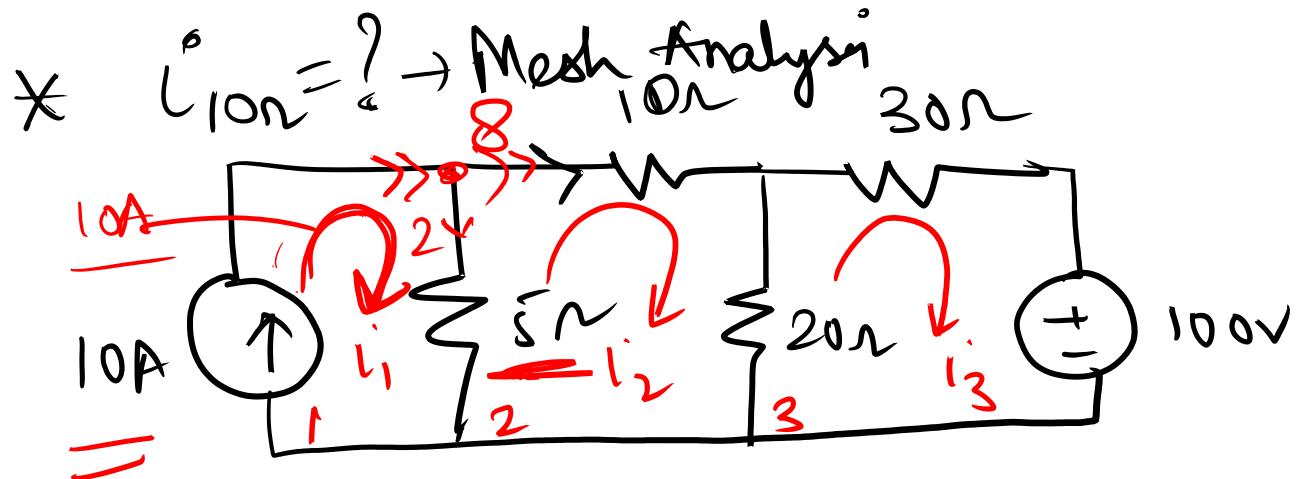

$$5(i_2 - i_1)$$

$$\underline{5(12 - 10) =}$$

20

Mesh 1: $\rightarrow i_1 = 10 \rightarrow 0$

Mesh 2: $10i_2 + 20(i_2 - i_3) + 5(i_2 - i_1) = 0$

2

Mesh 3:

$$\overline{30i_3 + 100 + 20(i_3 - i_2)} = 0$$

3

→ Mesh Analysis + Super Mesh

→ Nodal Analysis : (KCL)

① Identify nodes


② Mark the nodes
with unknown voltages

③ Take one node as a ref
with ($V=0$)


④ Take currents on all nodes

(outgoing current → +ive)

⑤ Finally write KCL eq. on each node

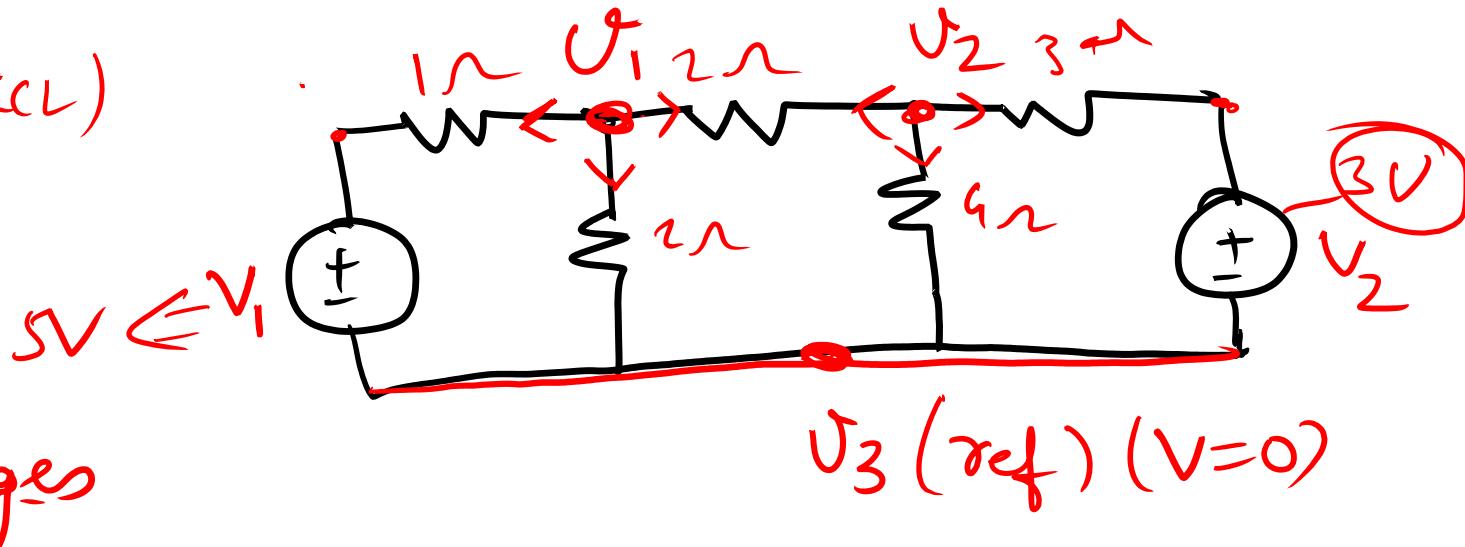

Q

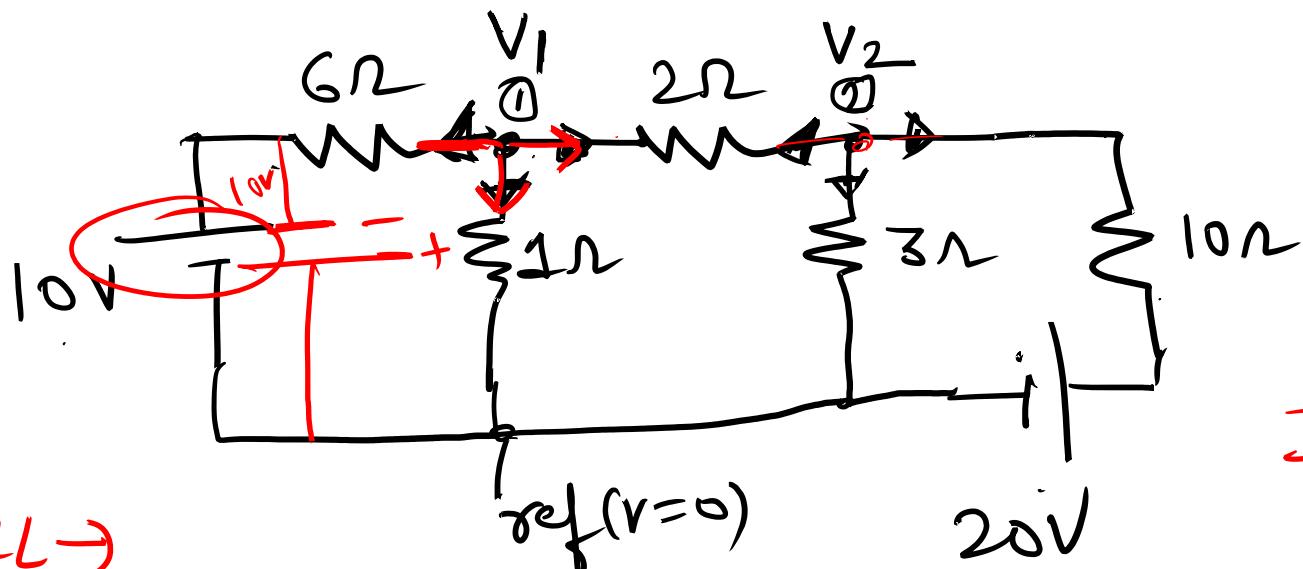

$$i = \frac{V}{R} = \frac{V_1 - V_2}{R}$$

⇒ Nodal Analysis


KCL →

At node 1

$$\frac{V_1 - 10}{6} + \frac{V_1 - 0}{1} + \frac{V_1 - V_2}{2} = 0$$

KCL at Node 2
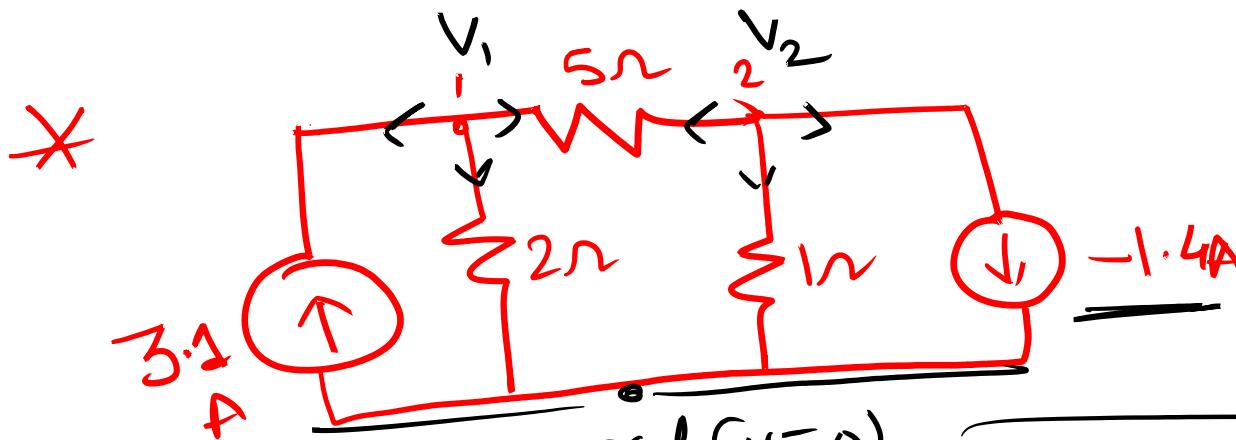
$$\frac{V_2 - V_1}{2} + \frac{V_2 - 0}{3} + \frac{V_2 - 20}{10} = 0$$



KCL \rightarrow
At node 1

$$\text{ref } (v=0)$$



$v_1 = 5 \text{ V}$
 $v_2 = 2 \text{ V}$

$$-3.1 + \frac{v_1 - 0}{2} + \frac{v_1 - v_2}{5} = 0$$

KCL at node 2

$$\frac{v_2 - v_1}{5} + \frac{v_2 - 0}{1} + (-\underline{\underline{1.4}}) = 0$$

* find $i_A; i_B; i_C$ using Nodal

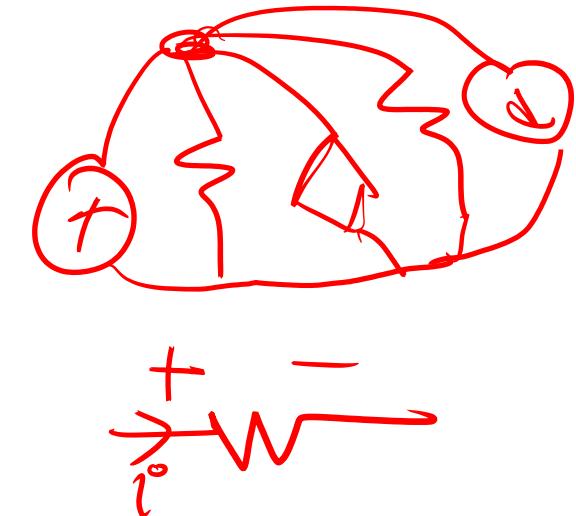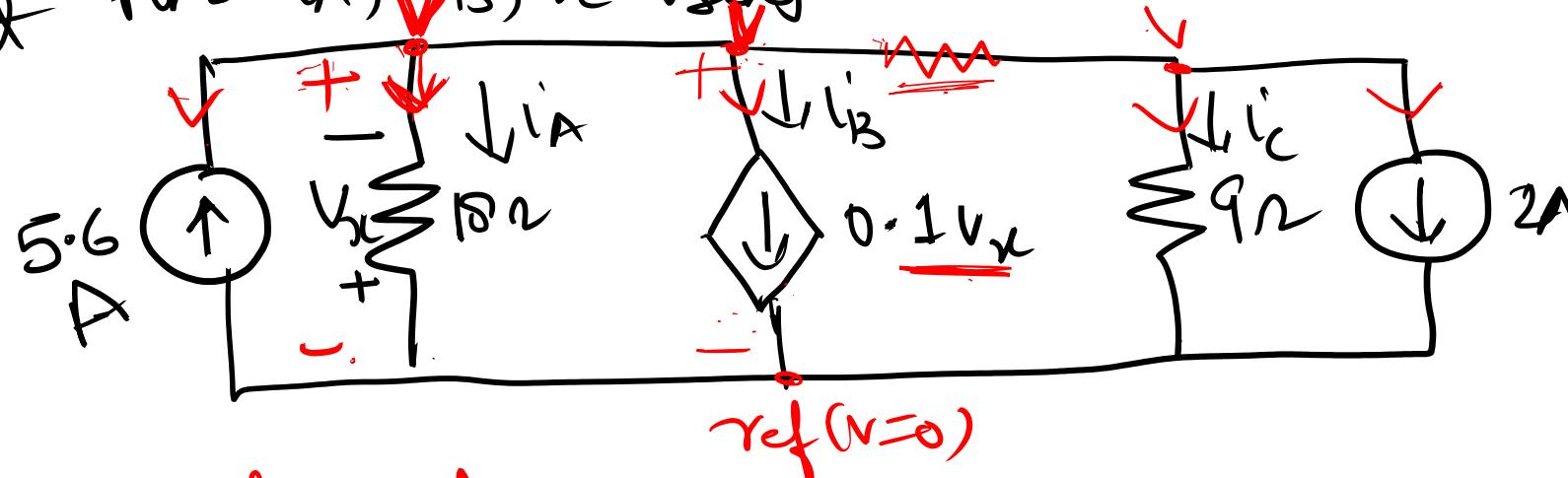


KCL eq for Node :


$$-5.6 + \frac{V_x}{18} + 0.1V_x + \frac{V_x}{9} + 2 = 0 \quad \textcircled{1}$$

$$V_x = -18i_A \quad \textcircled{2}$$

$V_x = -V$

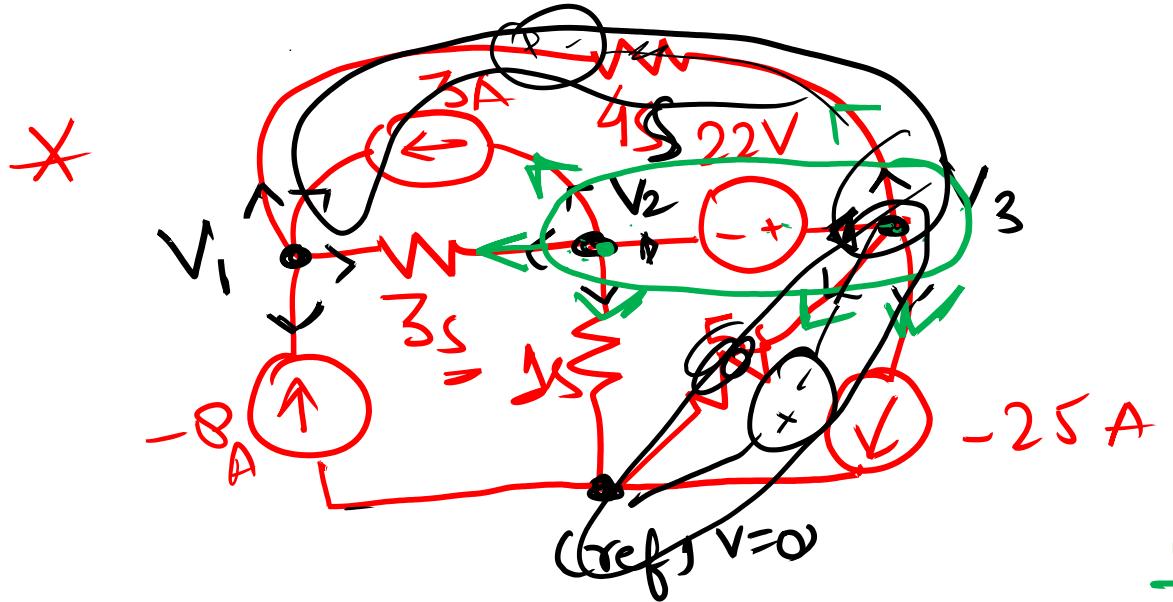

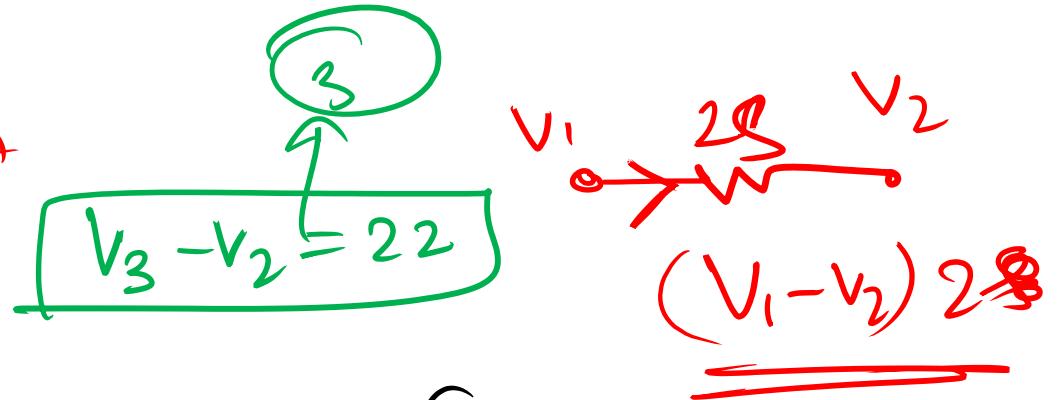$\text{R} \leftarrow \frac{1}{R} = \text{Conduct } \left(\frac{1}{s} \right)$



KCL at Node 1

$$(V_1 - V_3)4 + (V_1 - V_2)3 - 3 - (-8) = 0 \quad \cancel{-1}$$

KCL at Node 2

$$(V_2 - V_1)3 + 3 + (V_2 - 0)1 + ? = 0$$

KCL at Node 3

$$- + ? = 0$$


Super Node

$$\begin{aligned} & (V_2 - V_1)3 + 3 + V_2 \cdot 1 + (V_3 - V_1)4 \\ & + (V_3 - 0)5 + (-25) = 0 \end{aligned}$$

2

$$V_F = \frac{V}{I_S} \checkmark$$

$$V_2 = \frac{20}{5} \checkmark$$

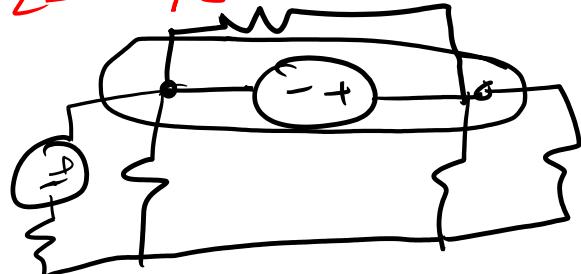

$$i = ? \Rightarrow \text{SuperNode}$$

(1) Identify Nodes

(2) Outgoing Currents


(3) Apply KCL at each node

- Consider Supernode as
a single node with the

node voltages as assumed in previous step
& Apply KCL at supernode

* find V, i using Nodal Analysis


SuperNode

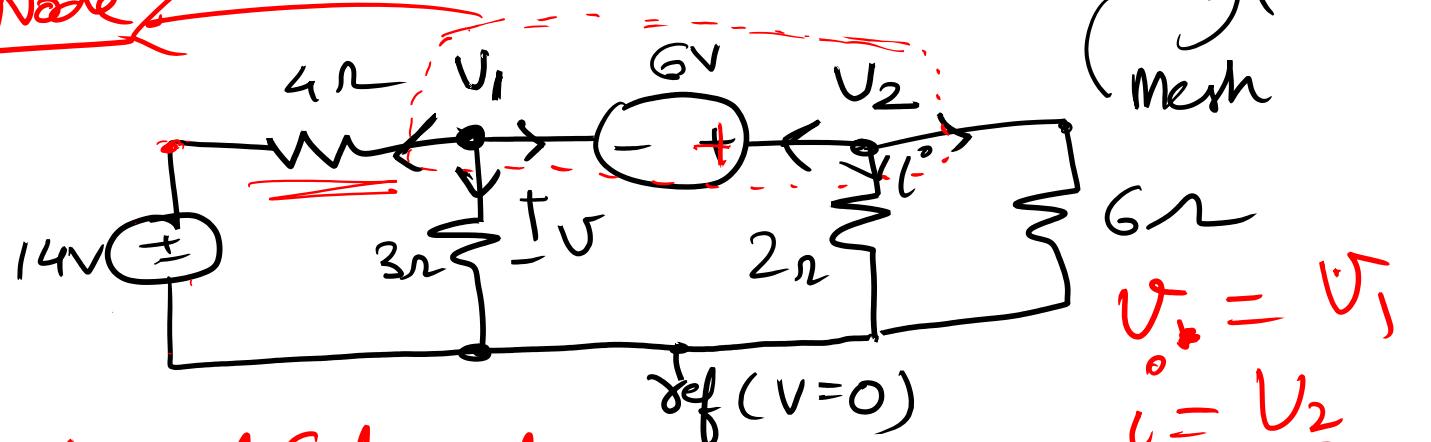

KCL at Supernode:

$$\frac{V_1 - 14}{4} + \frac{V_1}{3} + \frac{V_2}{6} + \frac{V_2}{2} = 0 \quad (i)$$

$$V_2 - V_1 = 6 \quad (ii)$$

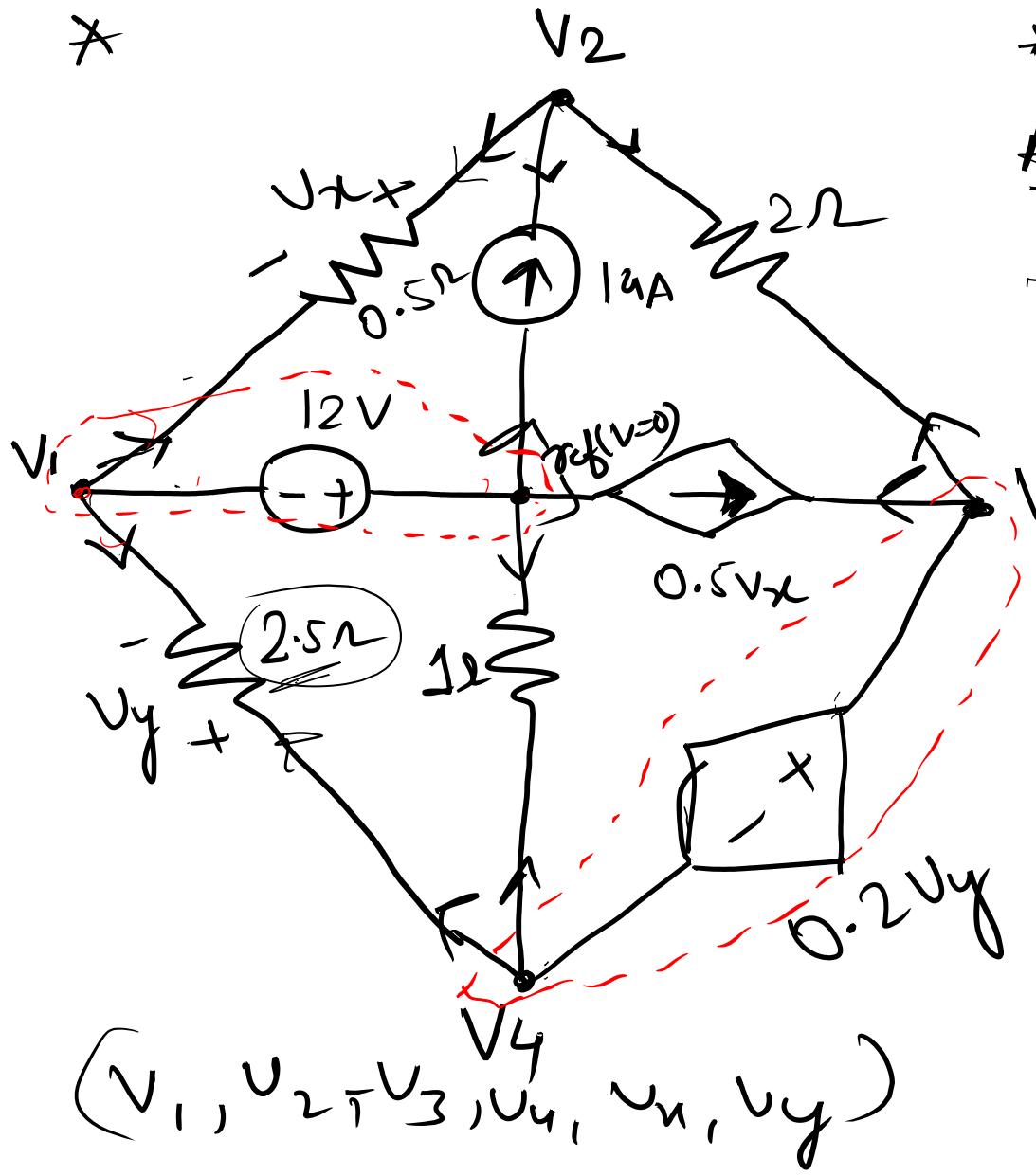

* $V_1 = -12V \quad \text{--- } ①$

At node 2:

$$\rightarrow \frac{V_2 - V_1}{0.5} - 14 + \frac{V_2 - V_3}{2} = 0 \quad \text{--- } ②$$

At super node 3-4:

$$\rightarrow \frac{V_3 - V_2}{2} - 0.5V_x + \frac{V_4 - V_3}{1} + \frac{V_4 - V_1}{2.5} = 0 \quad \text{--- } ③$$

$$V_3 - V_4 = 0.2V_y \quad \text{--- } ④$$

$$V_2 - V_1 = V_x \quad \text{--- } ⑤$$


~~$$(V_4 - V_1) = V_y \quad \text{--- } ⑥$$~~

$$\begin{aligned} 0 - V_1 &= 12 \\ V_1 &= -12 \end{aligned}$$

- KVL; KCL
- Mesh Analysis; Nodal Analysis
- (Super Mesh)

(Super Node) → Most powerful technique to solve any electrical circuit

Network Theorems

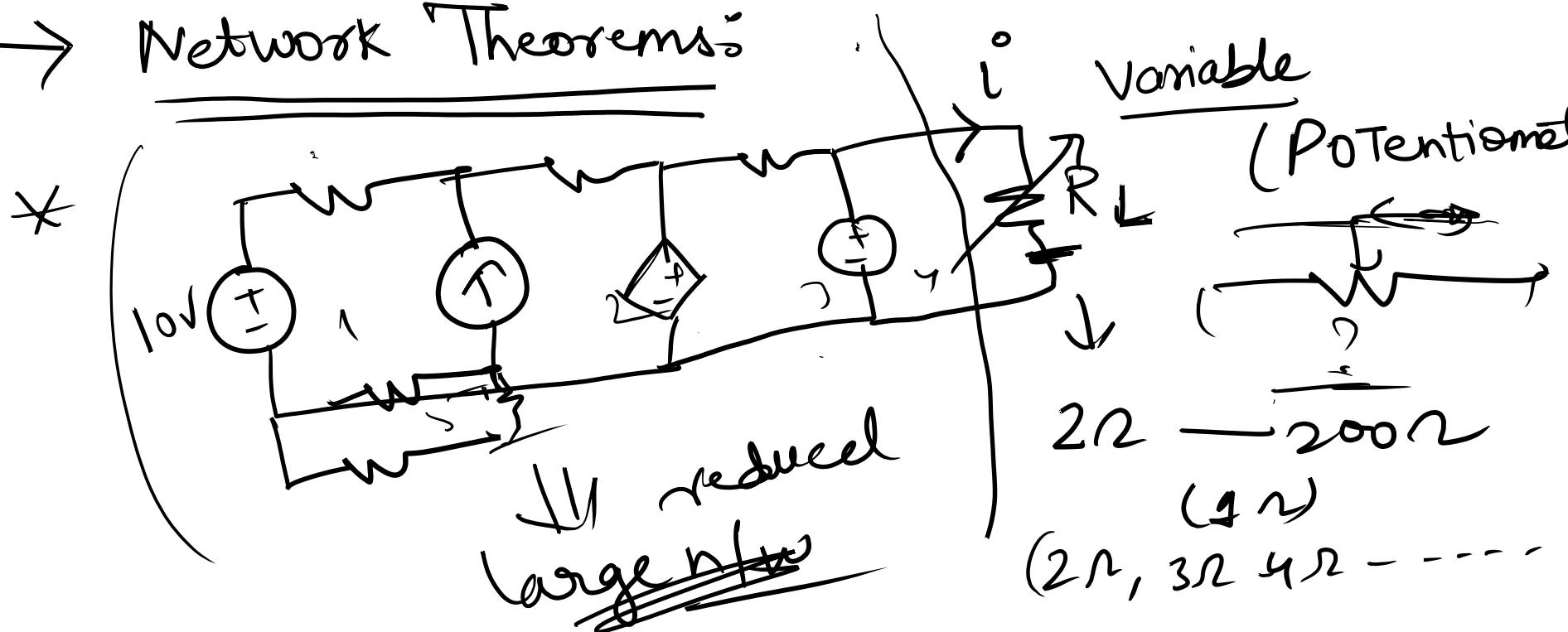

$$2R - 200R$$


$$(1R)$$

$$(2R, 3R, 4R, \dots, 200R) \rightarrow 5 \times 98$$


= 19 planes

$$i^o = (- - -)$$


= mesh

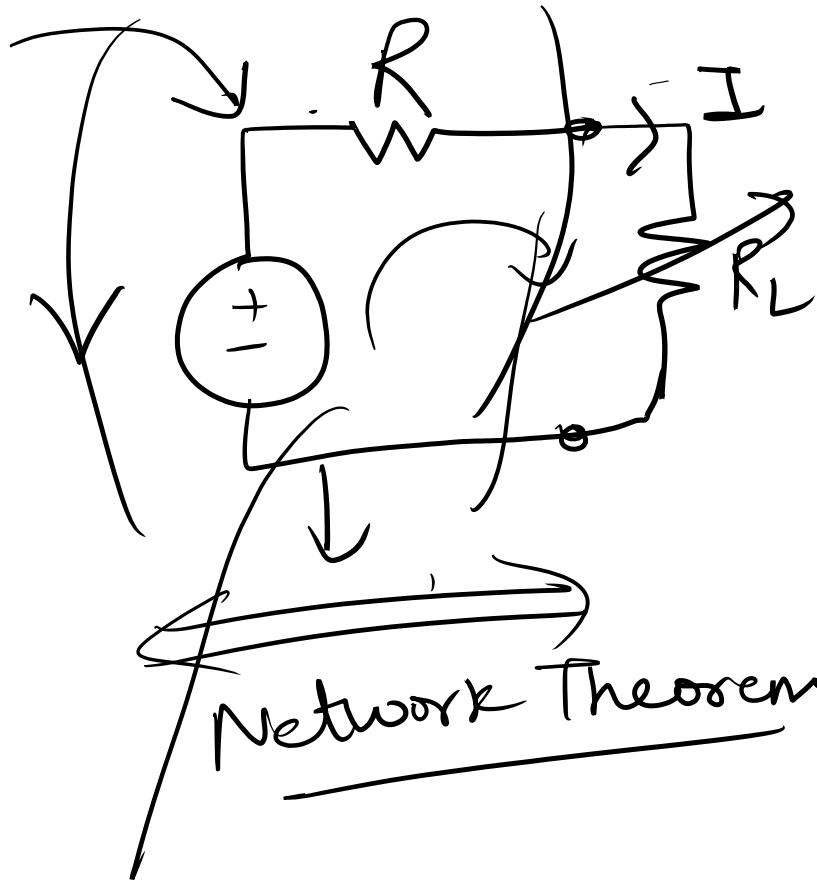

Thevenin's Theorem

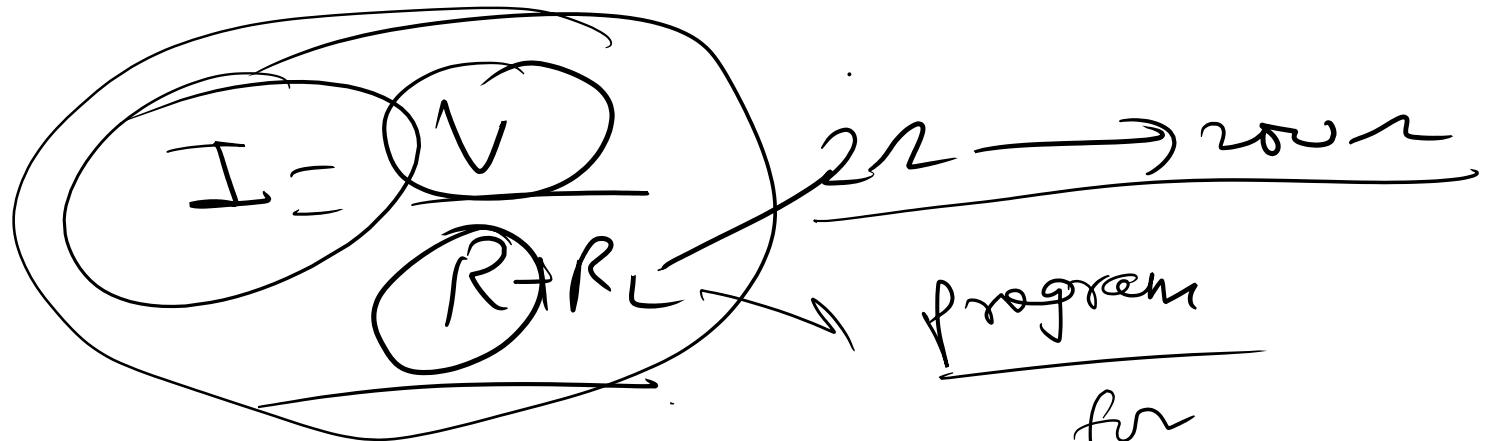


program
for
22 → 2021

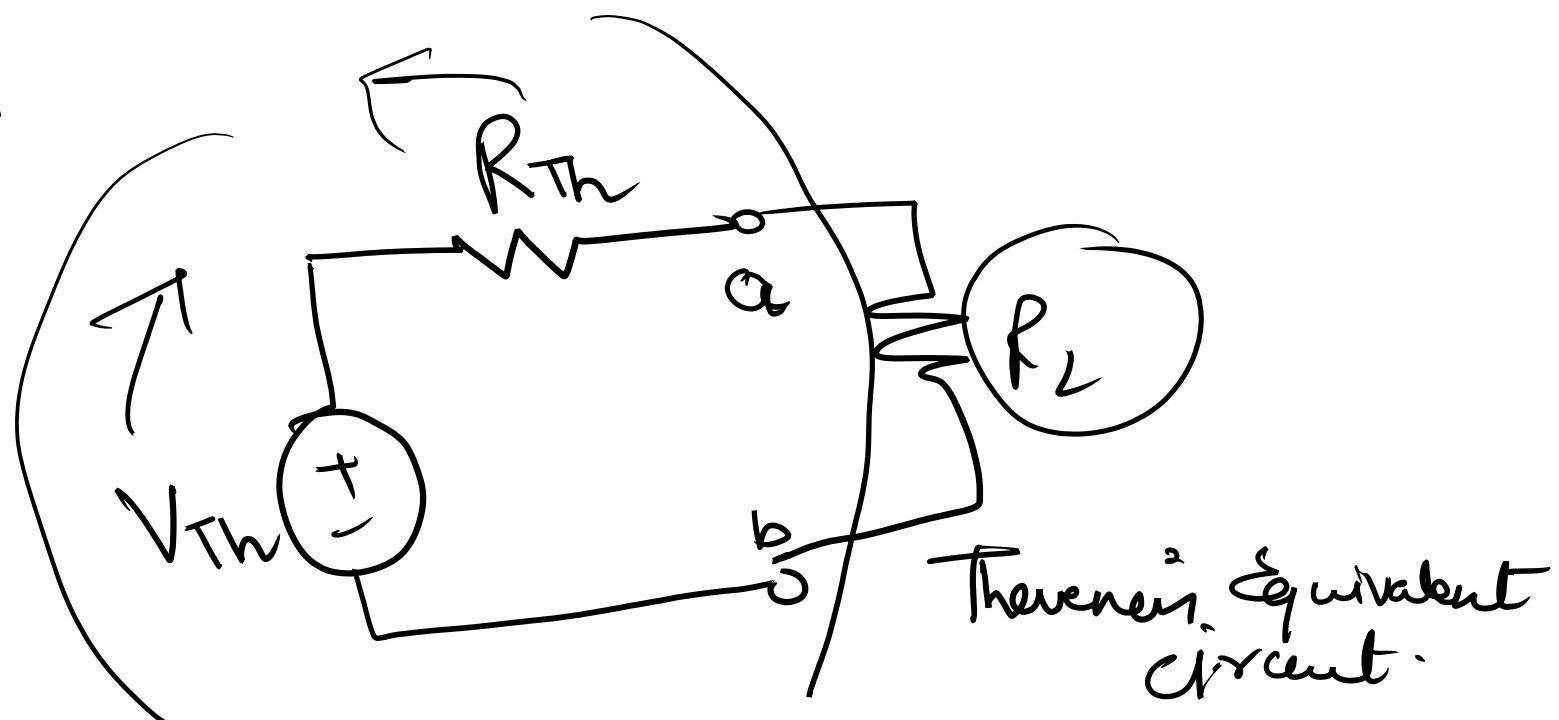

Thevenin's Equivalent
Circuit






Amplifiers
Ckt - Tuning

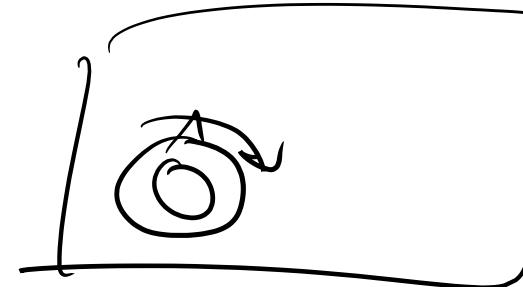


q_1, \dots MH 2

* Thevenin's Theorem

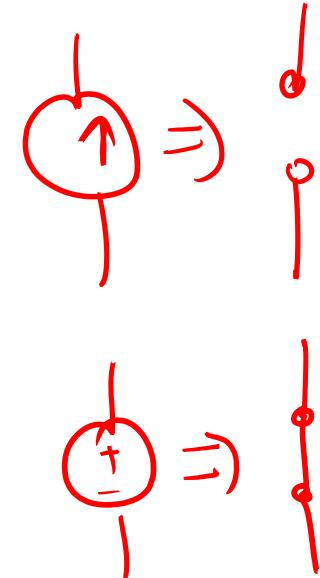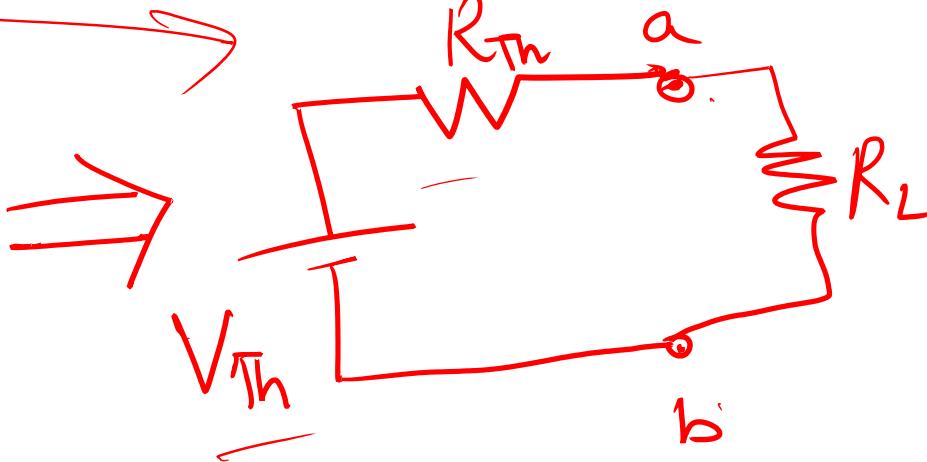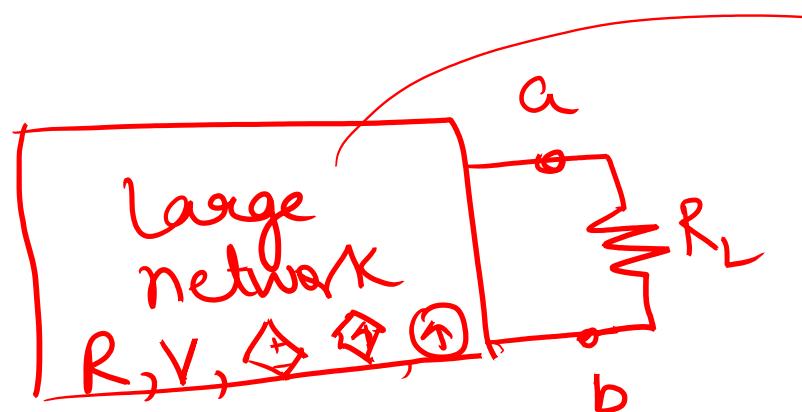



* Statement:

(i) V_{Th}

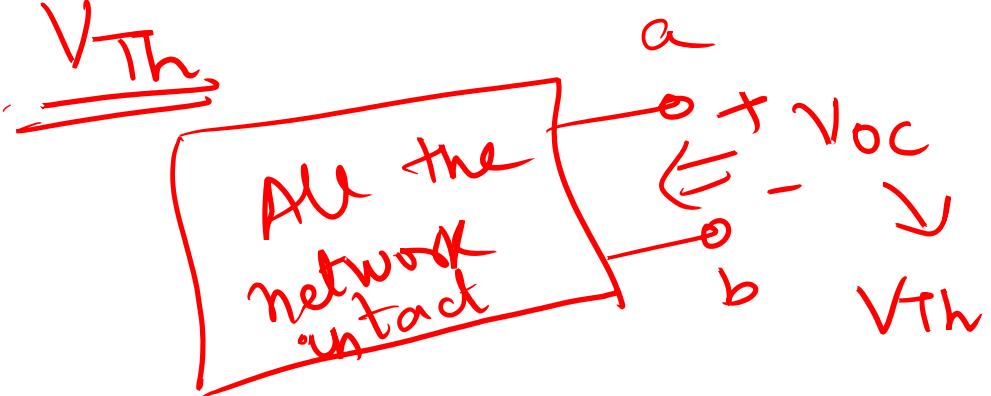


(ii) R_{Th}

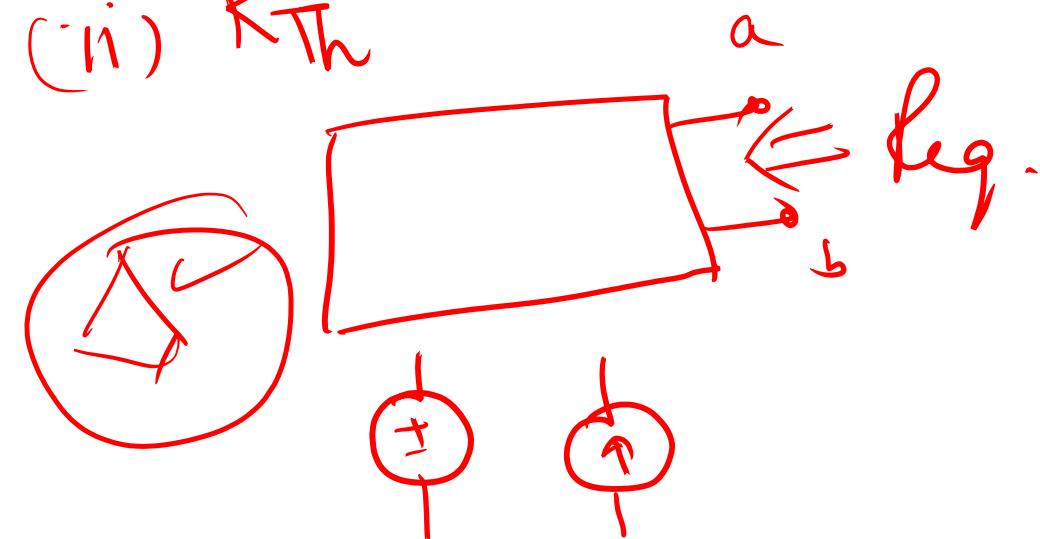

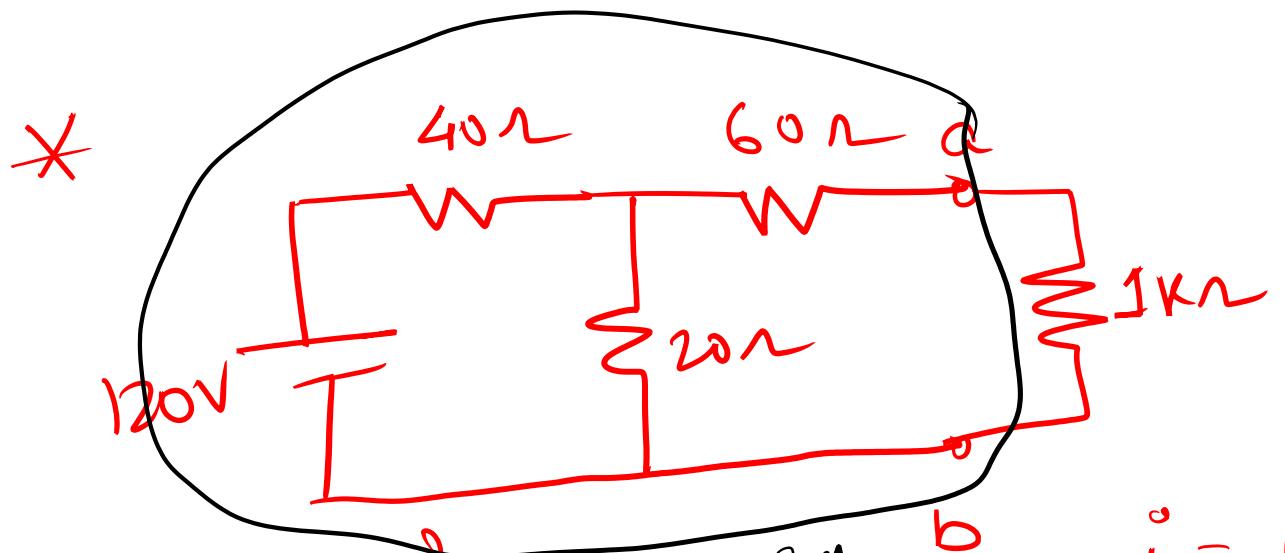


(i) $V_{Th} = 6$

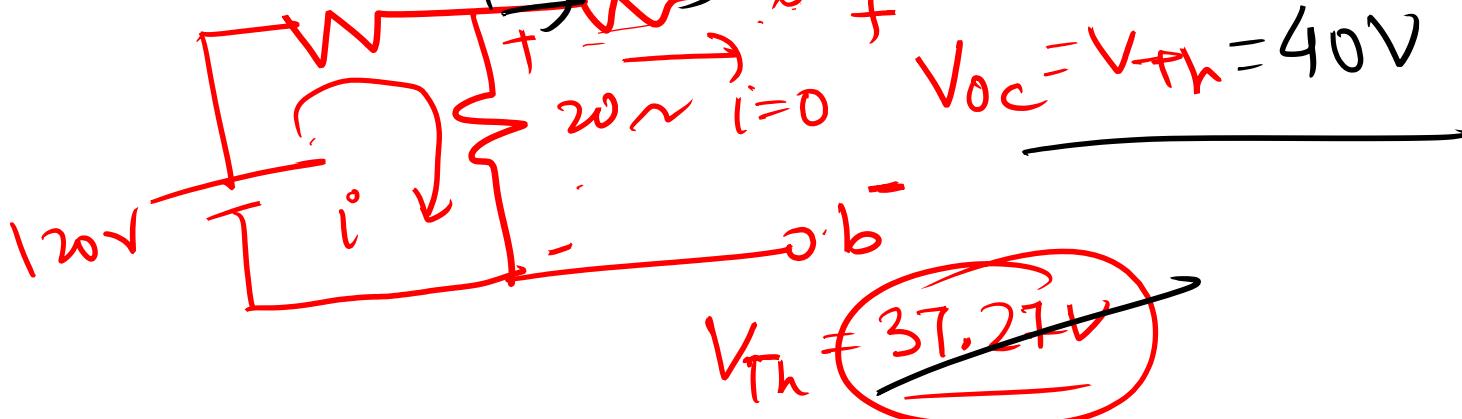

$$i = \frac{120}{60} = 2A$$

$$V_{oc} = V_{Th} = 40V$$

~~$V_{Th} = 37.27V$~~

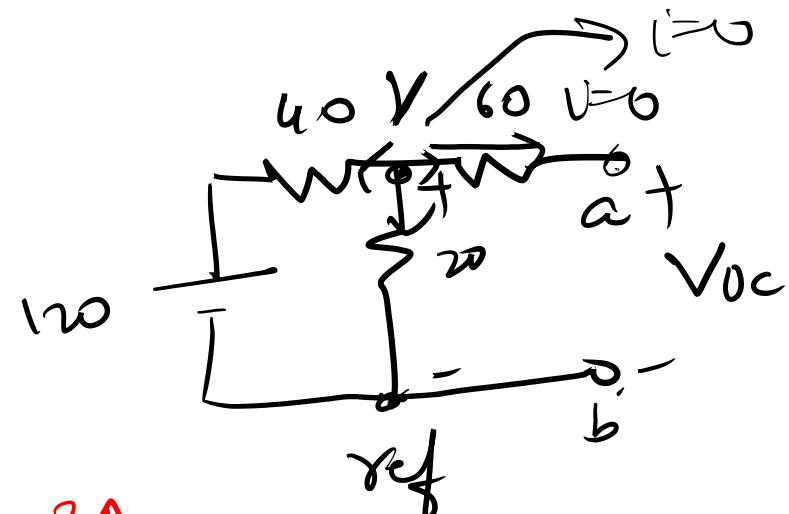

$$\frac{V - 120}{40} + \frac{V - 0}{20} = 0$$



$V \Rightarrow V_{oc}$

(2) R_{Th}




$(G_0 || 20) + 60$

$$R_{eq} = 73.3 \Omega$$

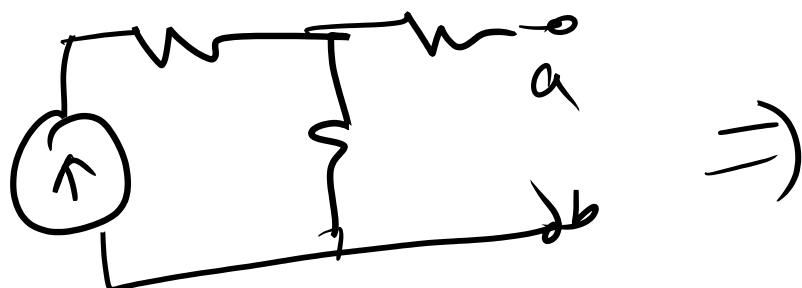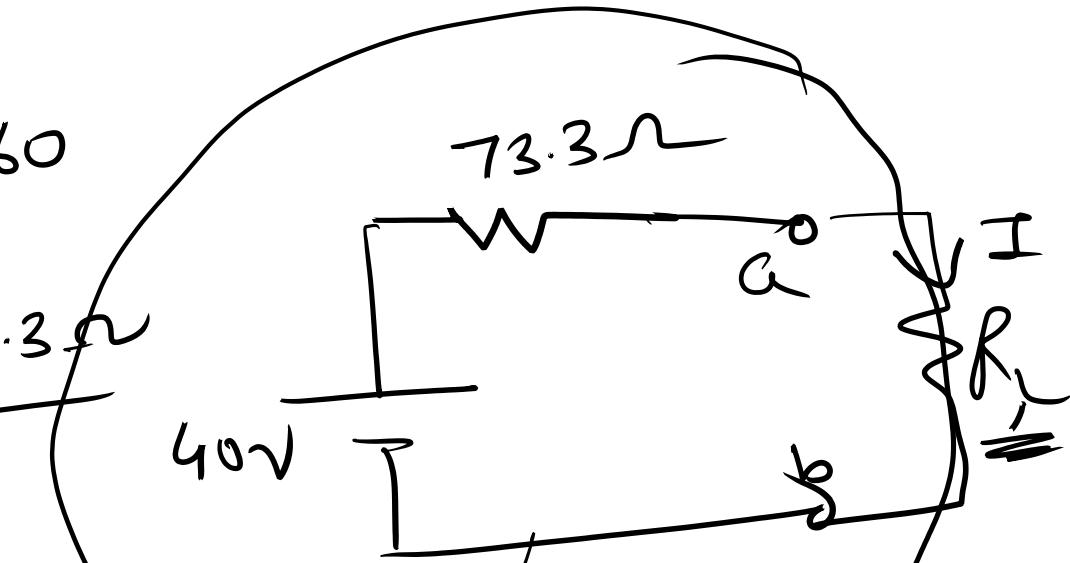


* Thevenize the given circuit across a-b

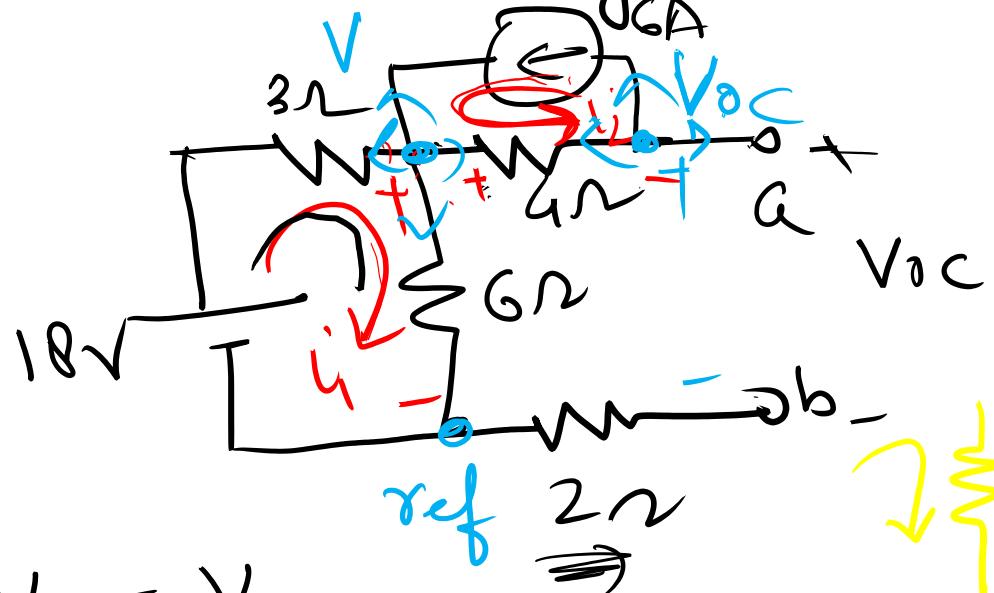

$$(i) V_{Th} = V_{oc}$$

$$-12 + 24 + V_{oc} = 0$$

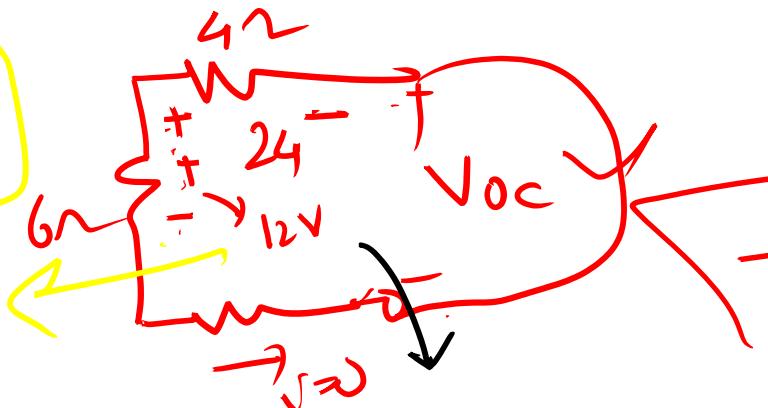

$$-12 + 24 + V_{oc} = 0$$

$$V_{oc} + 12 = 0$$

$$V_{6\Omega} \Rightarrow 6 \times 2 = 12V$$

$$V_{4\Omega} = 6 \times 4 = 24V$$

$$V_{oc} = -12V$$

$$\frac{V-18}{3} + \frac{V}{6} + \frac{V-V_{oc}}{4} - 6 = 0$$

$$i_2 = 6A$$



$$-18 + 3i_1 + 6i_2 = 0$$

$$9i_1 = 18$$

$$i_1 = 2A$$


$$\frac{V_{oc}-V}{4} + 6 = 0$$

$$\frac{V_{oc}-V}{4} = -6$$

$$V_{oc} - V = -24$$


$$V_{oc} = -12V$$

(ii) R_{Th}

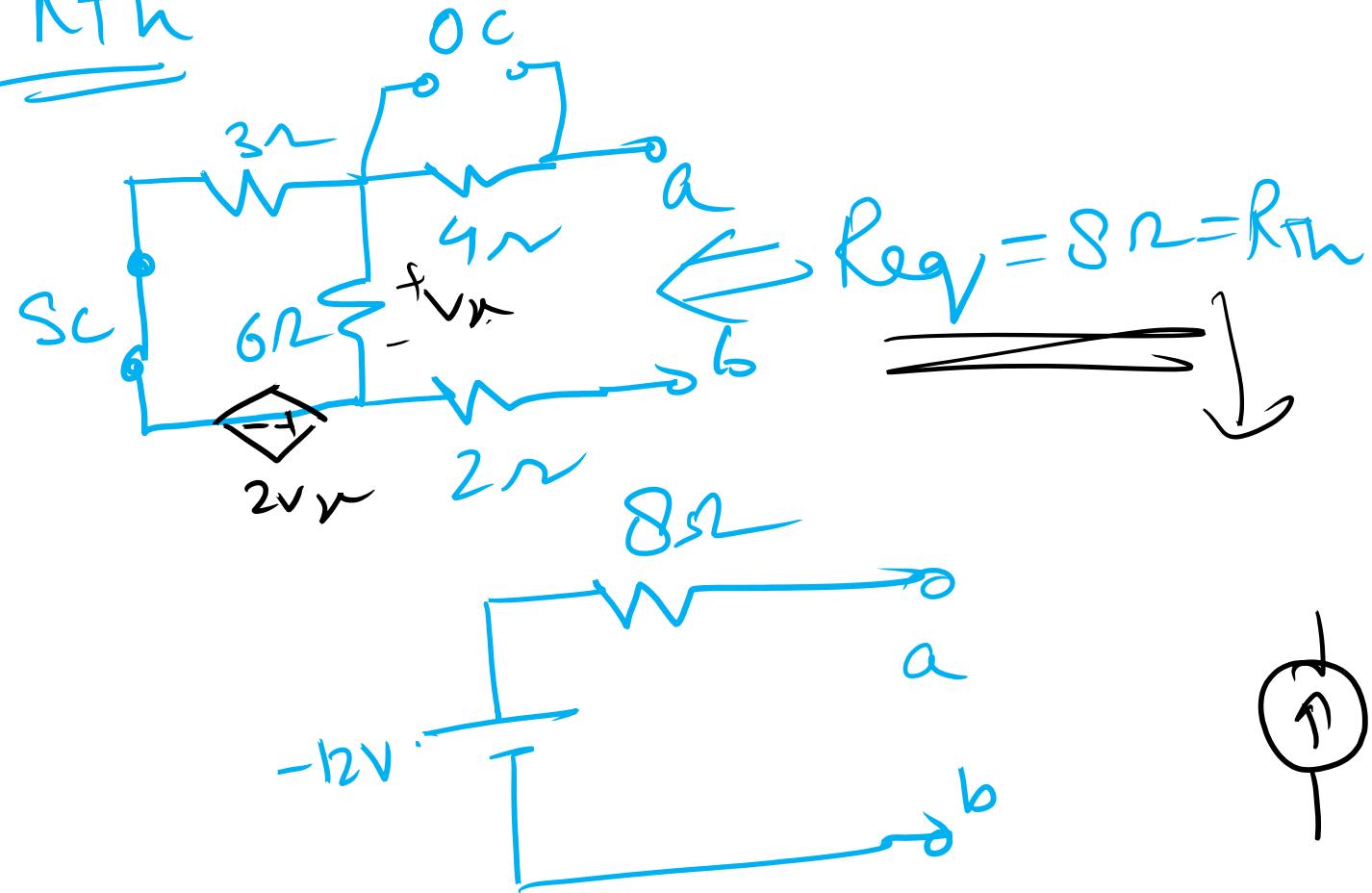

(i) $V_{Th} \Rightarrow V_{0C}$
 $(a-b)$

(ii) R_{Th}

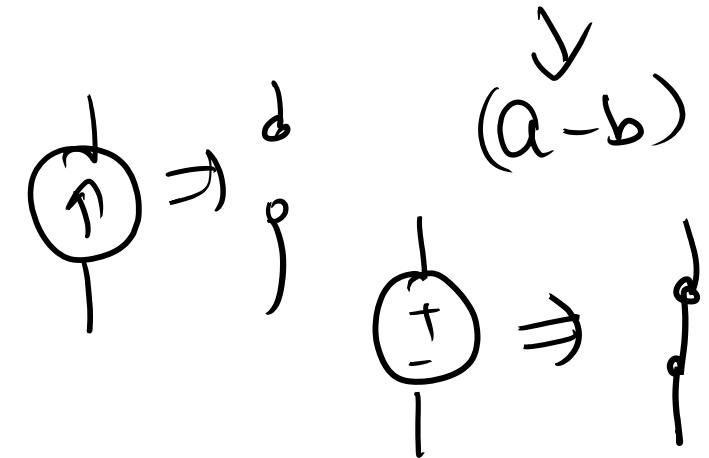

*

Thevenin Theorem

Independent sources
only

$$(1) V_{Th} \Rightarrow V_{oc}$$


(2) $R_{Th} \Rightarrow R_{eq}$ after
killing indep.
(Power sources)

Dependent + Independent
sources

$$(1) V_{Th} \Rightarrow V_{oc}(a-b)$$

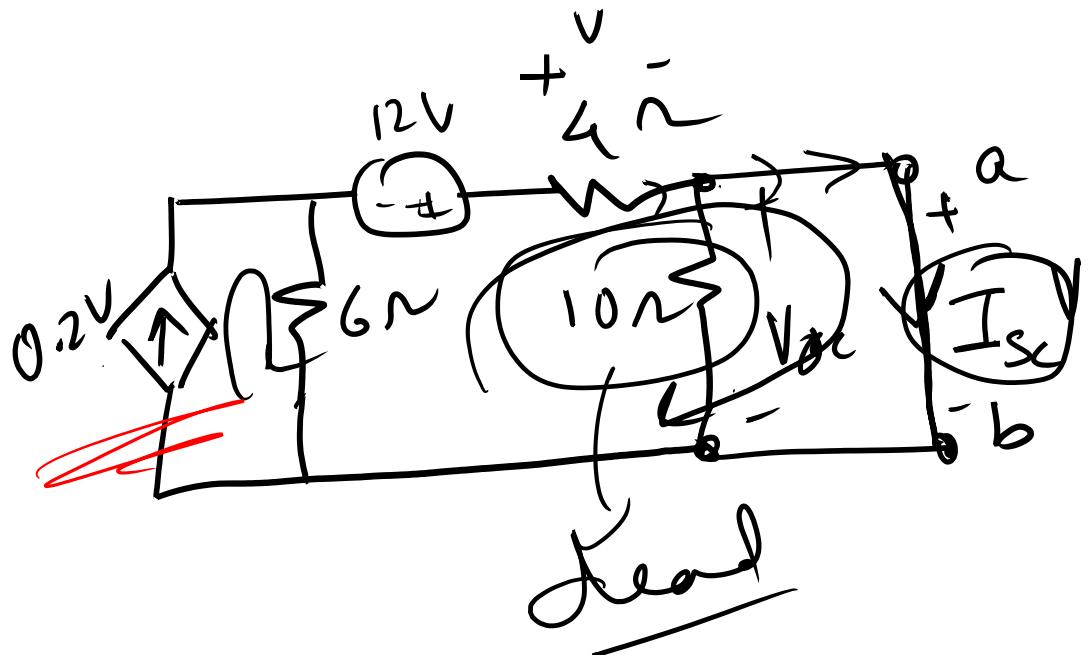(2) $I_{sc} \Rightarrow$ shorting
terminals


$$(3) R_{Th} = \frac{V_{oc}}{I_{sc}} - R$$



$$(1) V_{Th} = V_{oc}$$

$$(2) I_{sc} = a \text{ Amp}$$


$$(3) R_{Th} = \frac{V_{oc}}{a}$$

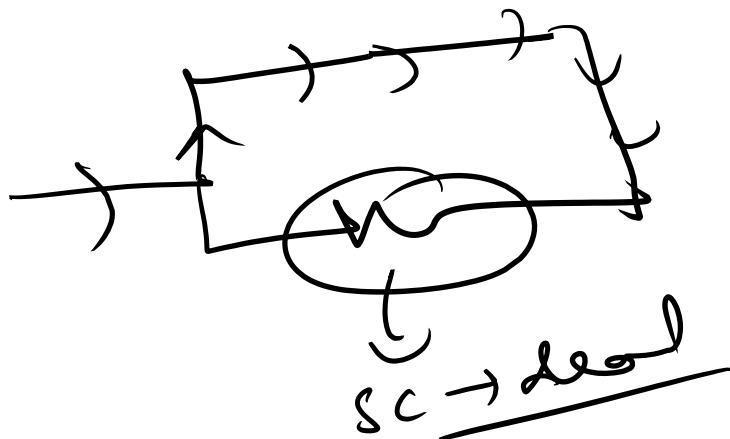

Thevenin Equivalent f (Dependent Sources)

- V_{Th}
- I_{Sc}
- $R_{Th} = \frac{V_{Th}}{I_{Sc}}$
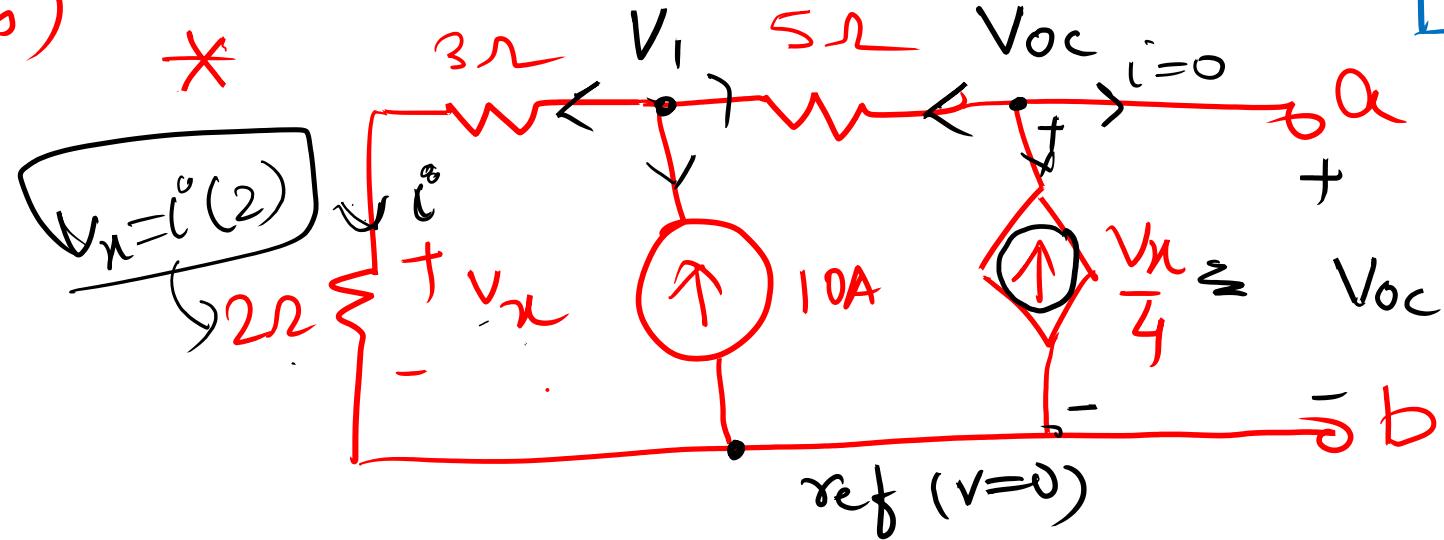
$$\textcircled{1} \quad V_{Th} (V_{oc})$$



$$\text{KCL at Node 1: } \frac{V_{1o}}{3+2} - 10 + \frac{V_1 - V_{oc}}{5} = 0 \quad \textcircled{1}$$


$$\text{Node 2: } \frac{V_{oc} - V_1}{5} - \frac{V_x}{4} = 0 \quad \textcircled{2}$$

$$V_x = \frac{2V_1}{5} \rightarrow \textcircled{3}$$



$$\frac{V_1 - i^o}{5} = 0$$

$$V_{oc} = 2(V_1)$$

$$V_{oc} = 150V$$

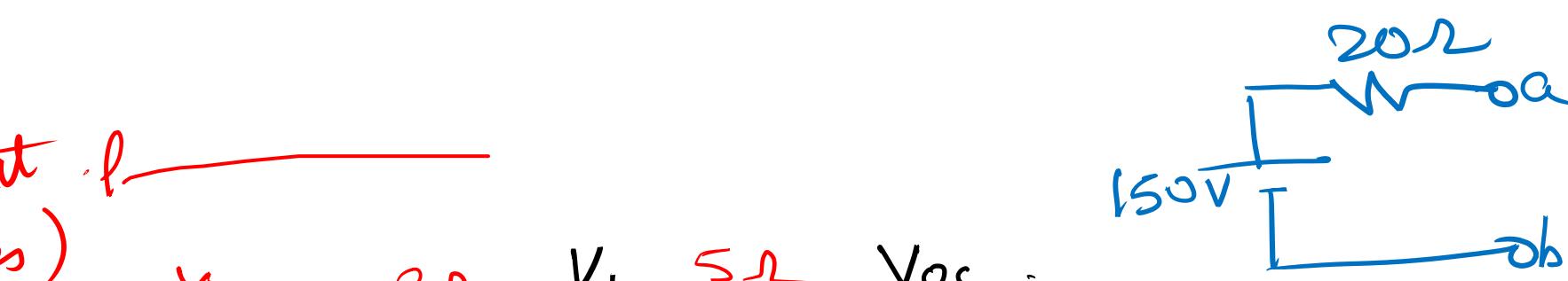

② I_{sc}

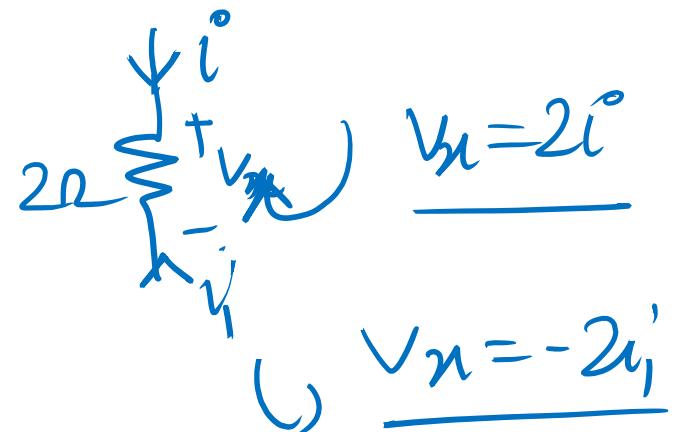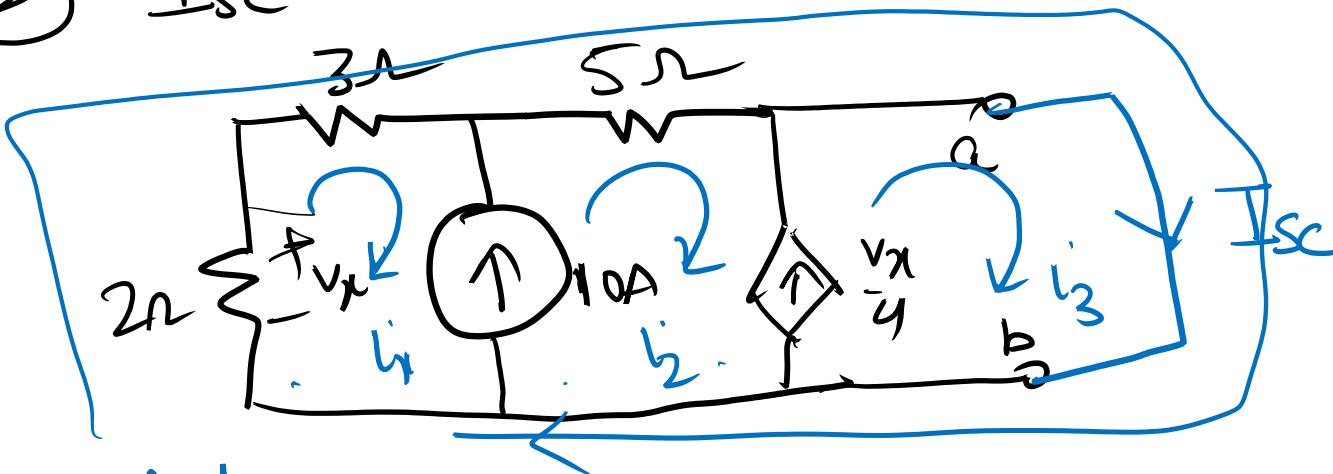

SuperMesh:

$$2i_1 + 3i_1 + 5i_2 = 0 \quad (1)$$

$$i_2 - i_1 = 10 \quad (2)$$

$$i_3 - i_2 = \frac{v_x}{4} \quad (3)$$

$$i_3 = 7.5 = I_{sc}$$


$$r_{Th} = \frac{V_{oc}}{I_{sc}}$$

$$= \frac{150}{7.5}$$

$$= \underline{\underline{20\Omega}}$$

$$v_x = -2i_1 \quad (4)$$


* Obtains Thvenin Eq :

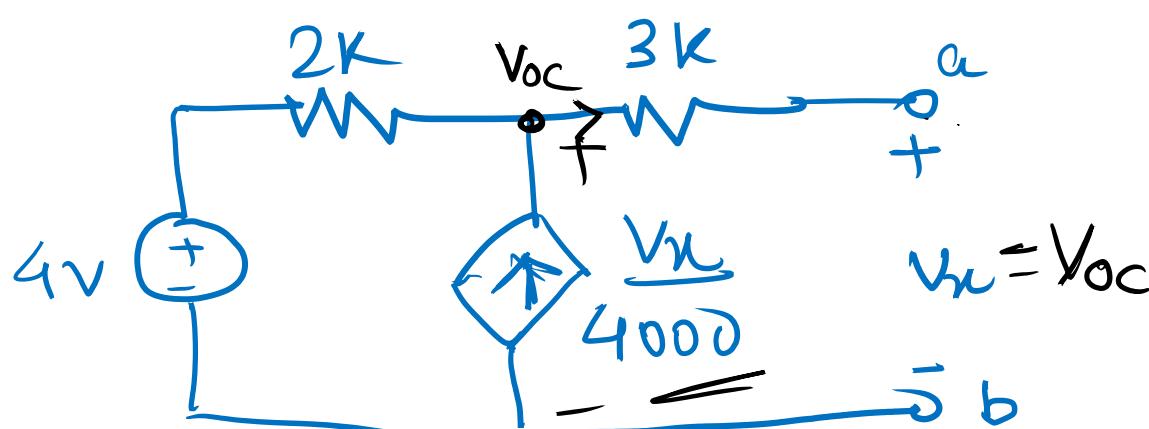

$$1K = \text{kiloohm} = 1 \times 10^3 \Omega$$

$$\frac{V_{OC}-4}{2000} - \frac{V_x}{4000} = 0$$



$$V_{OC} = V_x$$

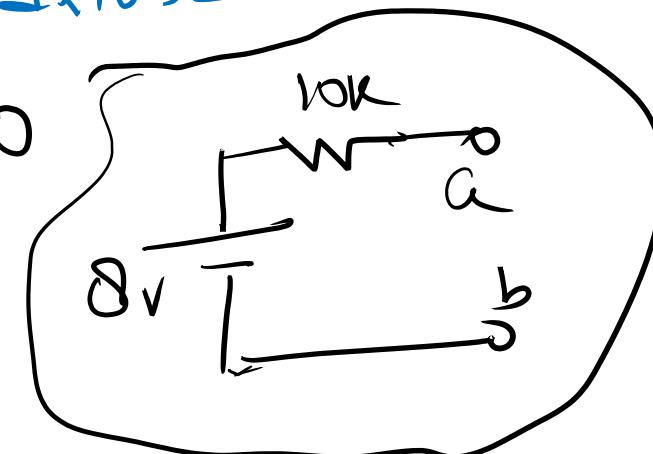


$$V_{OC} = 8V$$

$$I_{SC} = \frac{4}{5000} = 0.80mA$$
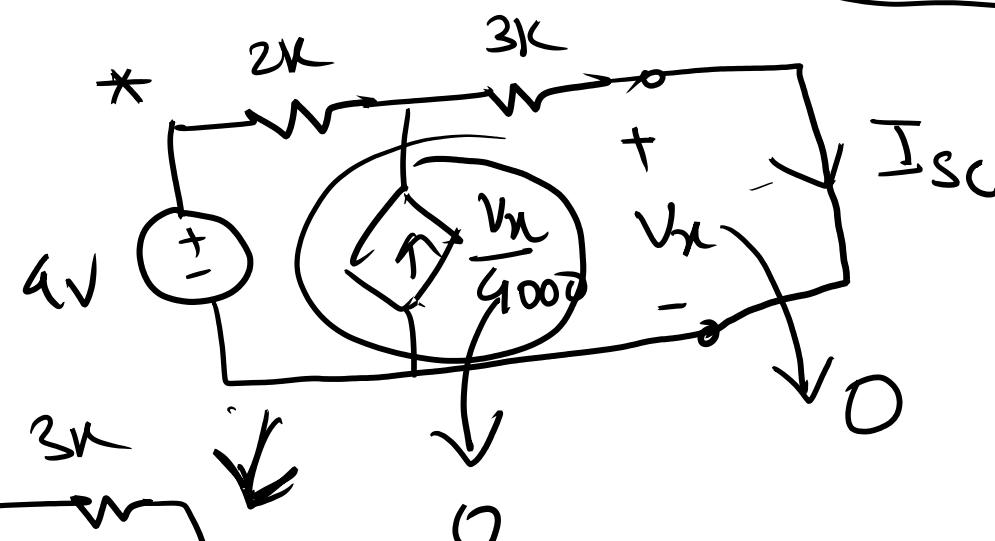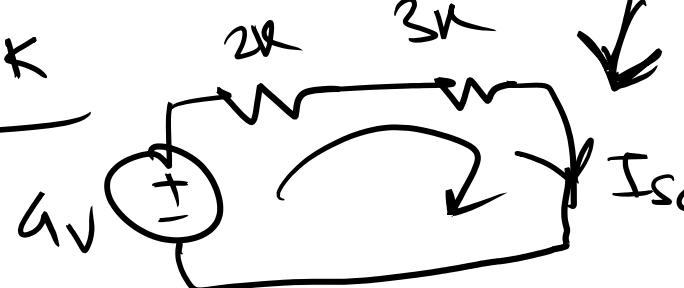
$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{80^{10}}{80 \times 10^{-3}} = 10K$$



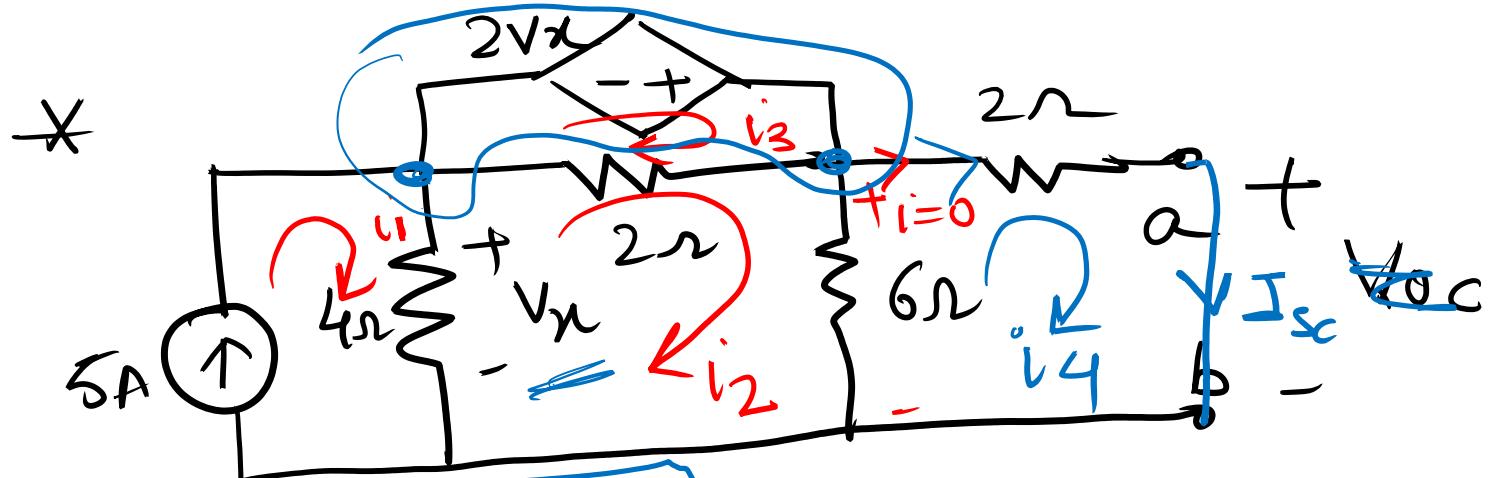

$$(1) V_{oc} (V_{Th}) = 20V$$

$$4(i_2 - i_1) + 2(i_2 - i_3) + 6i_2 = 0 \quad \textcircled{1}$$

$$-2V_x + 2(i_3 - i_2) = 0 \quad \textcircled{2}$$

$$i_1 = 5 \quad \textcircled{3}$$

$$V_x = 4(i_1 - i_2) \quad \textcircled{4}$$

$$(2) i_1 = 5 \quad \textcircled{1}$$

$$-2V_x + 2(i_3 - i_2) = 0 \quad \textcircled{2}$$

$$4(i_2 - i_1) + 2(i_2 - i_3) + 6(i_2 + i_4) = 0 \quad \textcircled{3}$$

$$6(i_4 - i_2) + 2i_4 = 0 \quad \textcircled{4}$$


$$V_x = 4(i_1 - i_2) \quad \textcircled{5}$$

$$i_4 = I_{sc} = 10A$$



$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{20}{10} = 2\Omega$$


* Steps for Thvenin

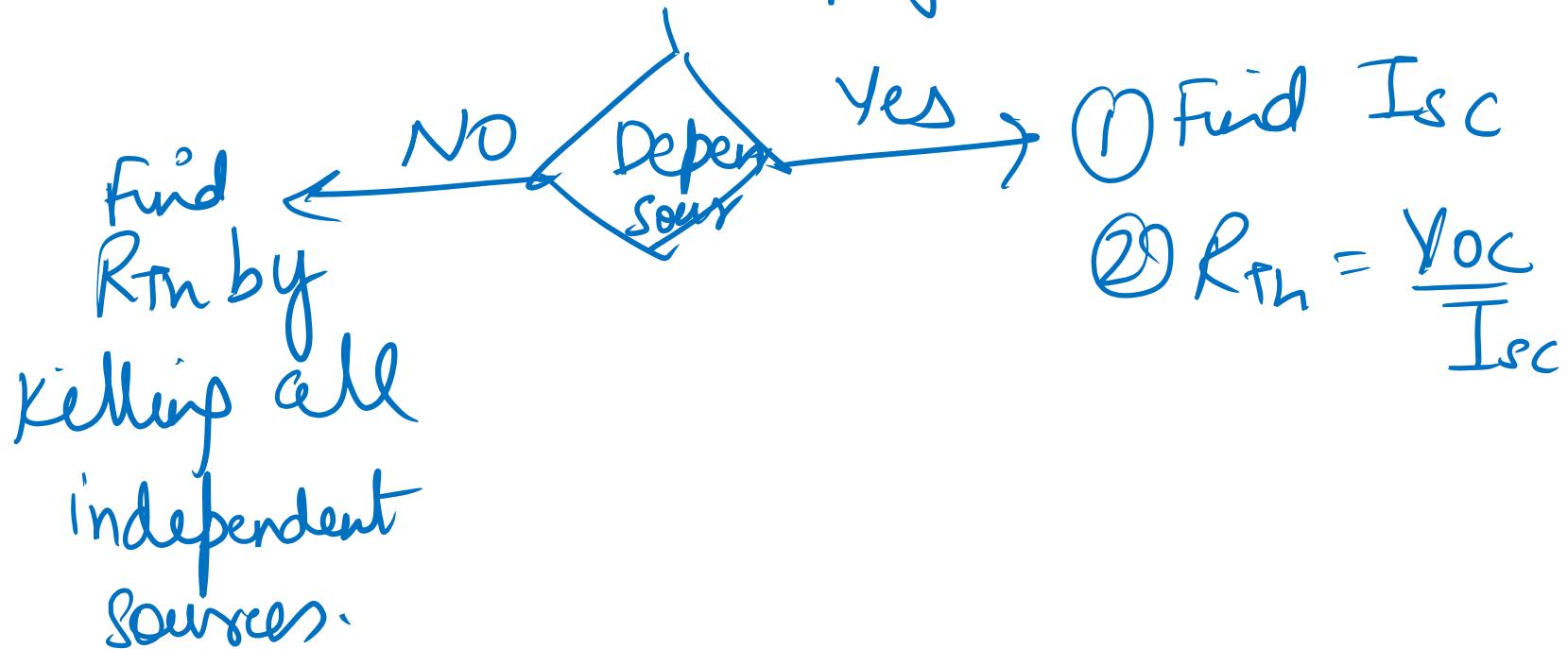- ① Identify a-b & remove any R_L
- ② Find V_{OC} at a-b keeping all intact




* NORTON's Theorem

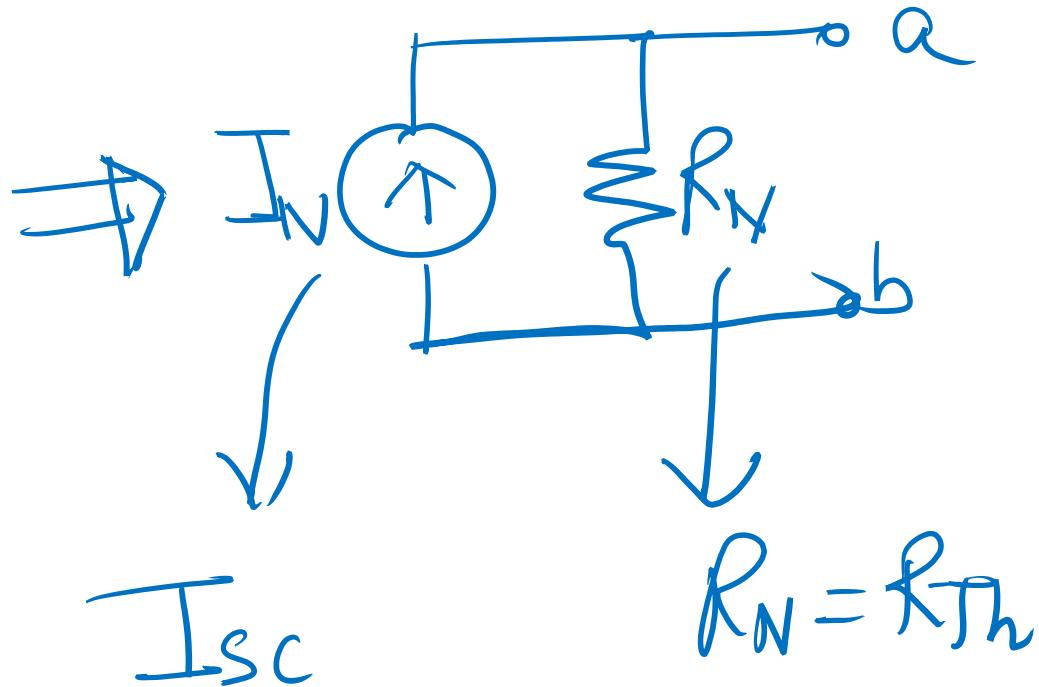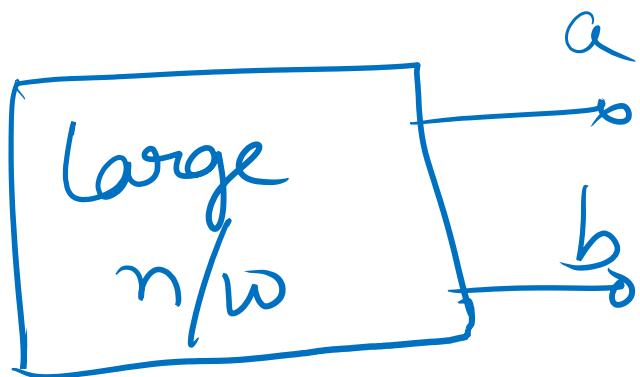

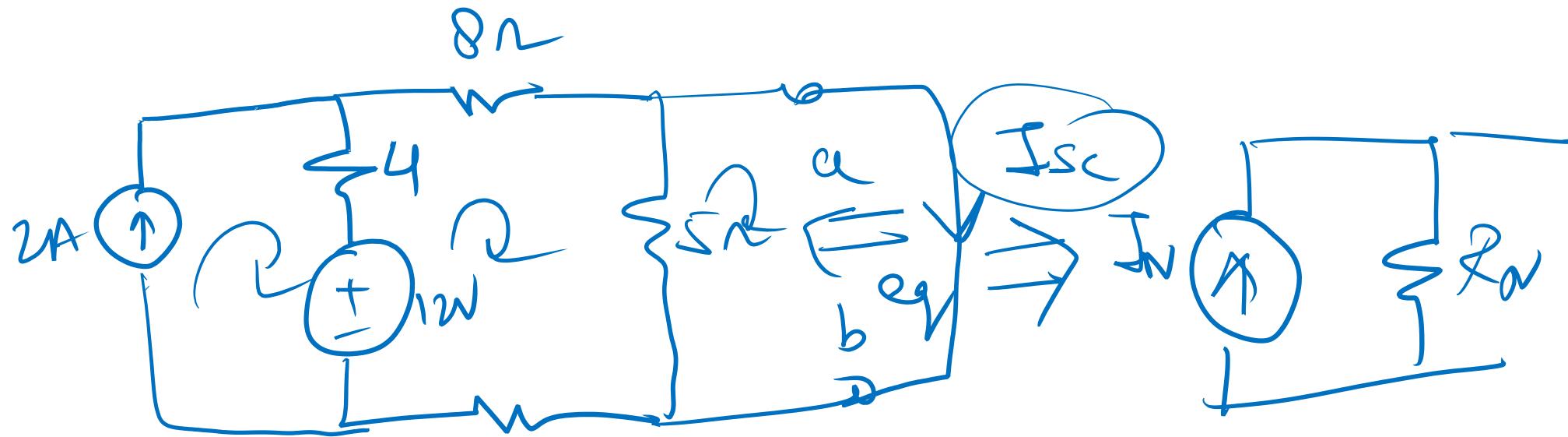

$$(2) R_N = R_{Th}$$


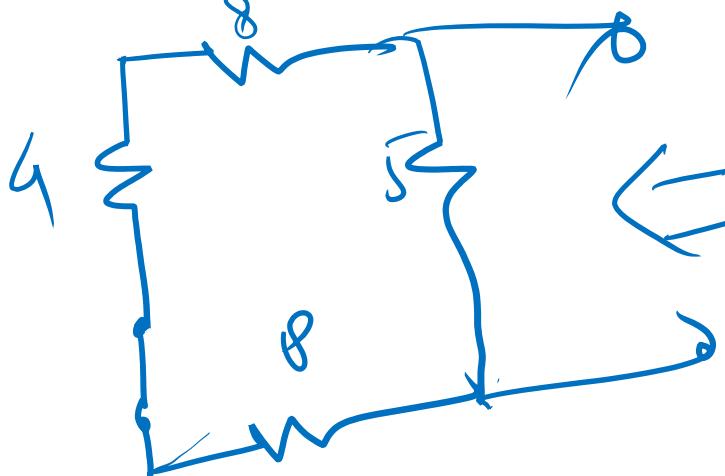


$$\leftarrow R_{eq} = 4\Omega = R_N$$

$$(1) I_N$$

$$\left\{ \begin{array}{l} \rightarrow V_{oc} \\ \rightarrow I_{sc} = I_N \\ \rightarrow R_N = \frac{V_{oc}}{I_{sc}} \end{array} \right.$$


\rightarrow Norton's Theorem

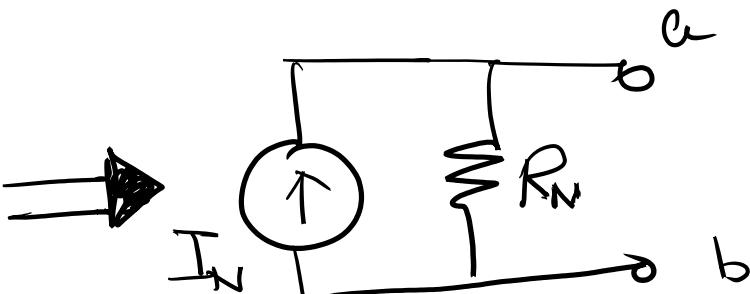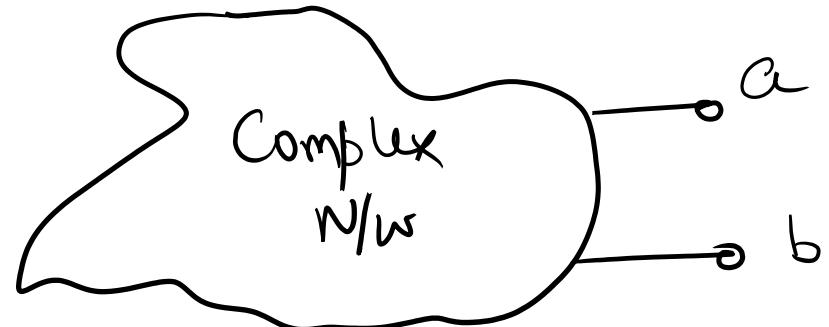

$$R_N = R_{Th}$$


$$I_N = I_{SC}$$

* Statement :

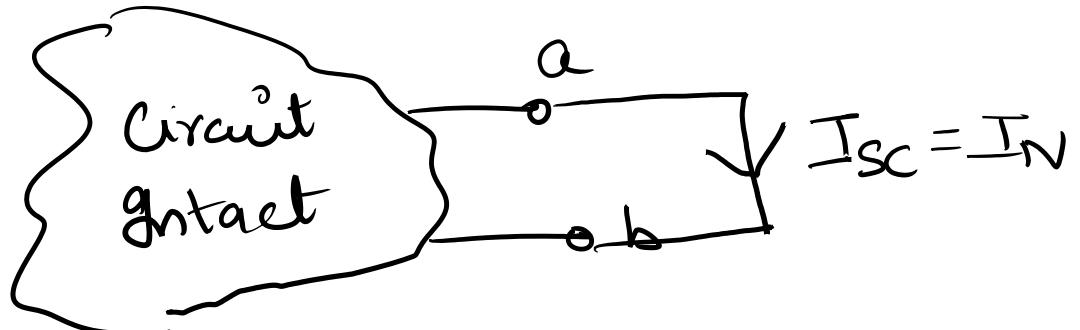


$$(i) I_N$$

$$I_{SC} = I_N$$

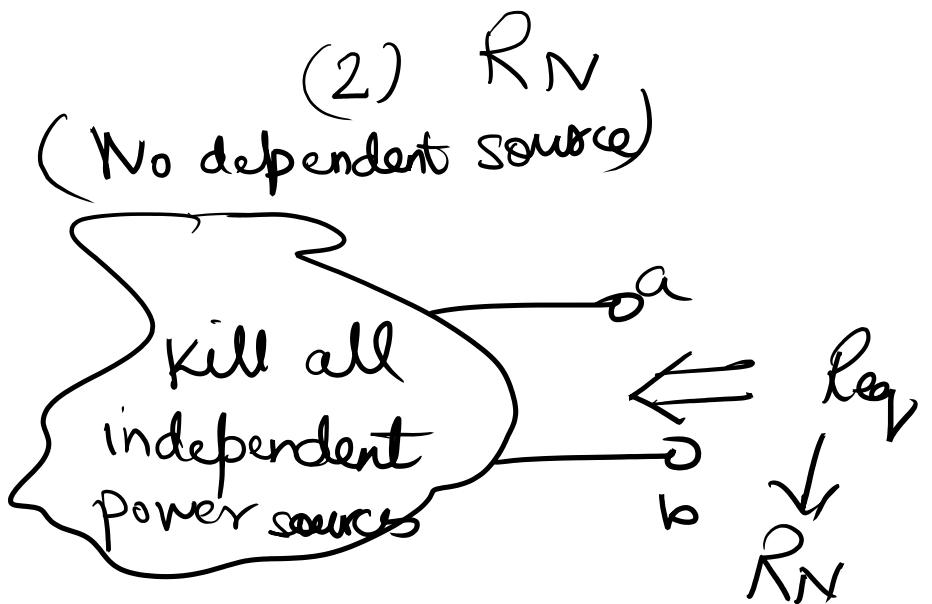

(Dependent sources)

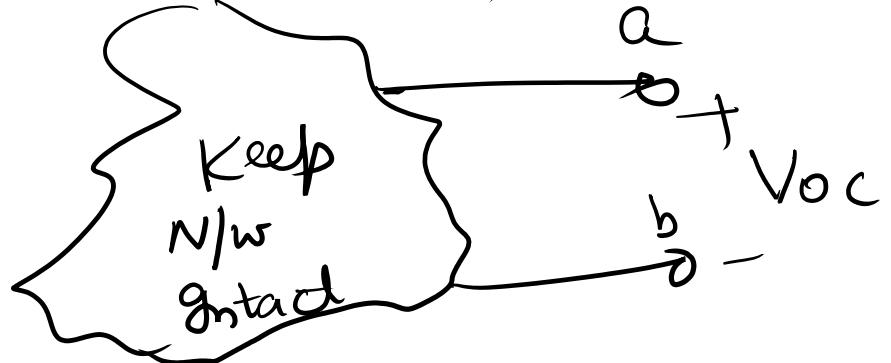


$$I_{sc} = I_N = ?$$

$$R_N = \frac{V_{oc}}{I_{sc}}$$

$$\begin{aligned} i_1 &= 2 \\ i_2 &= i_3 \end{aligned}$$

*

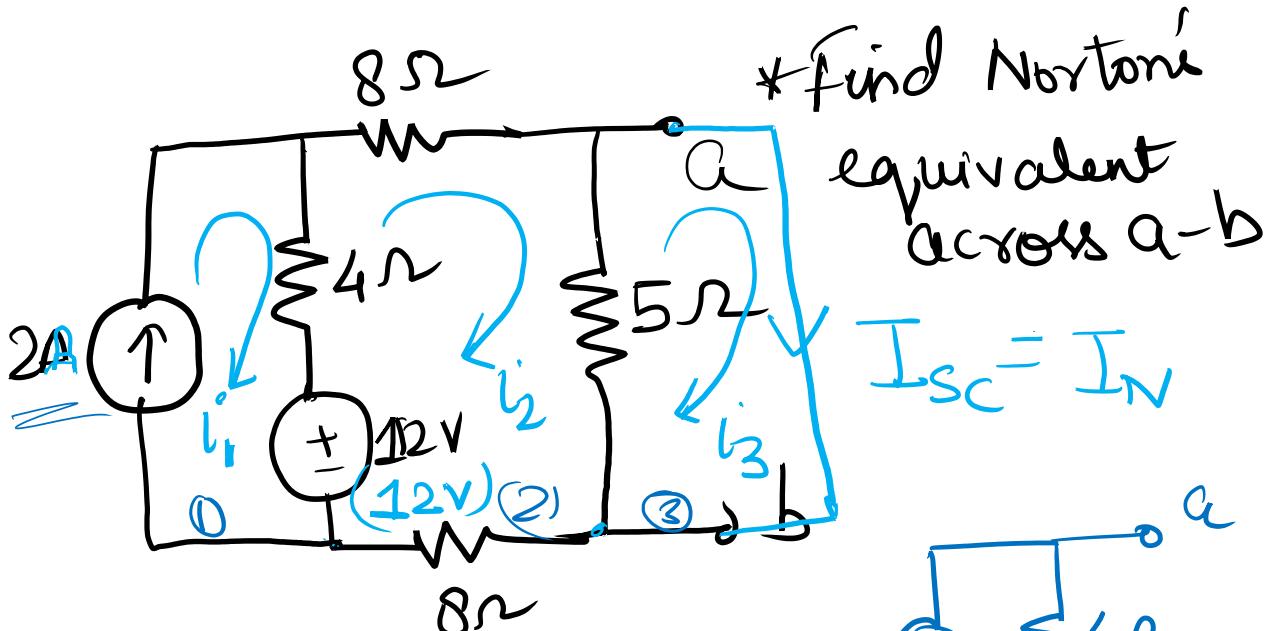

$$R_N = 4\Omega$$


$$I_N = \underline{5.33A_j} - \underline{\frac{1}{5}A}$$

$$4(i_2 - i_1) + 8i_2 + 5(i_2 - i_3) + 8i_2 - 12 = 0$$


$$5(i_3 - i_2) = 0 \quad \text{--- (2)}$$

$$i_1 = 2 \quad \text{--- (3)}$$



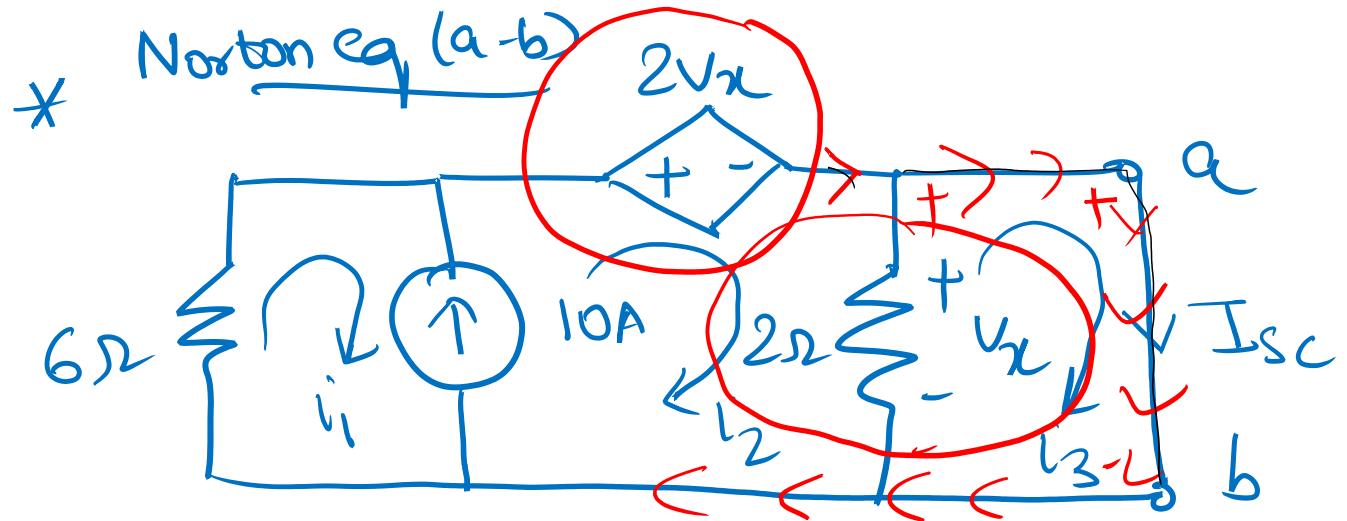


$$V_x = 0$$

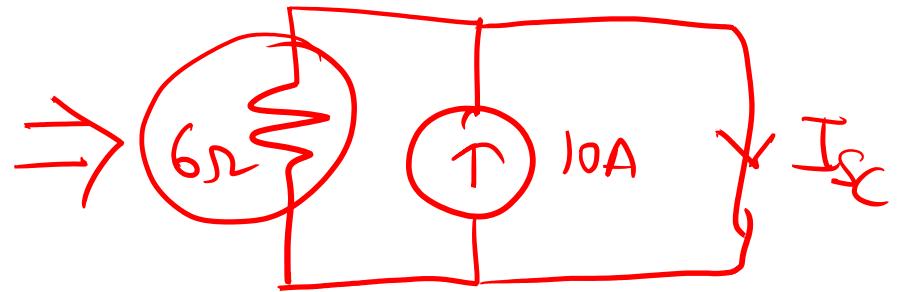


$$(1) I_N = I_{SC} = 10A$$


$$(2) V_{OC}$$

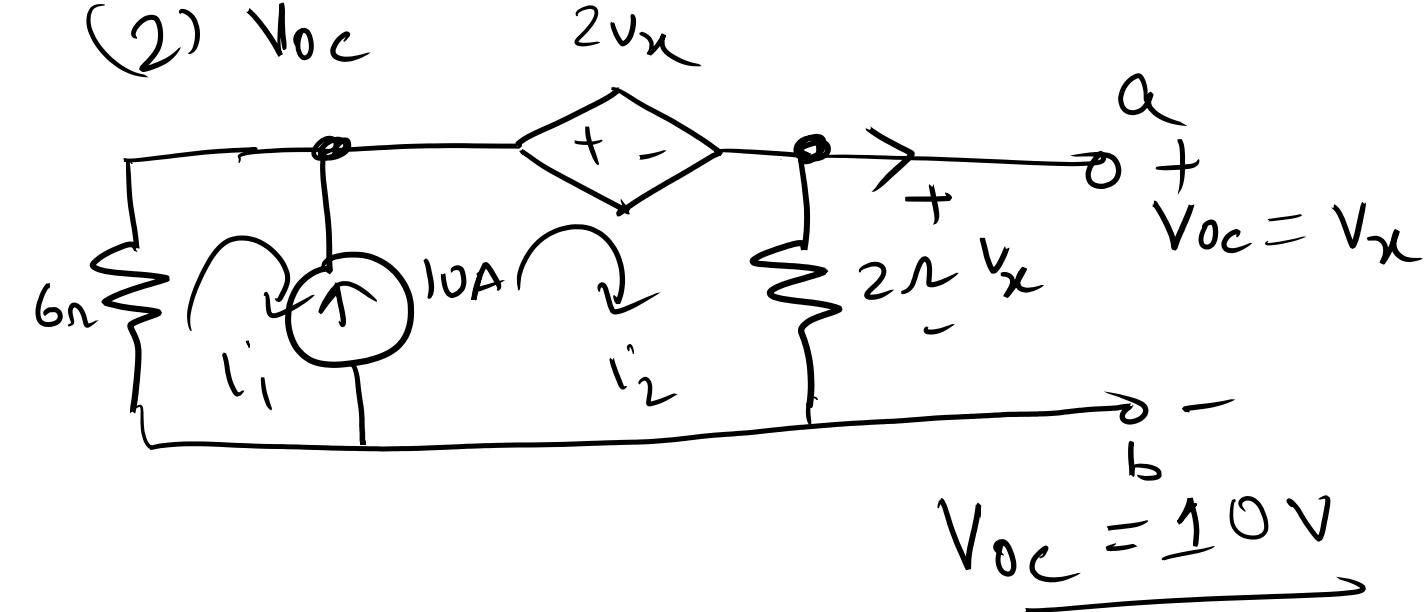


$$R_N = 1\Omega$$

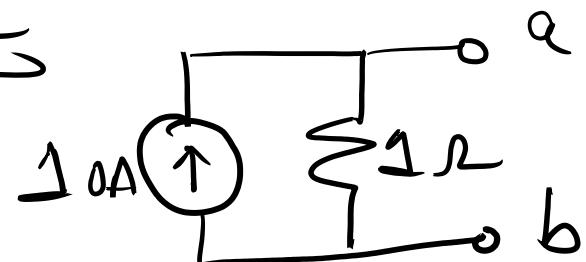

↓(Redraw)

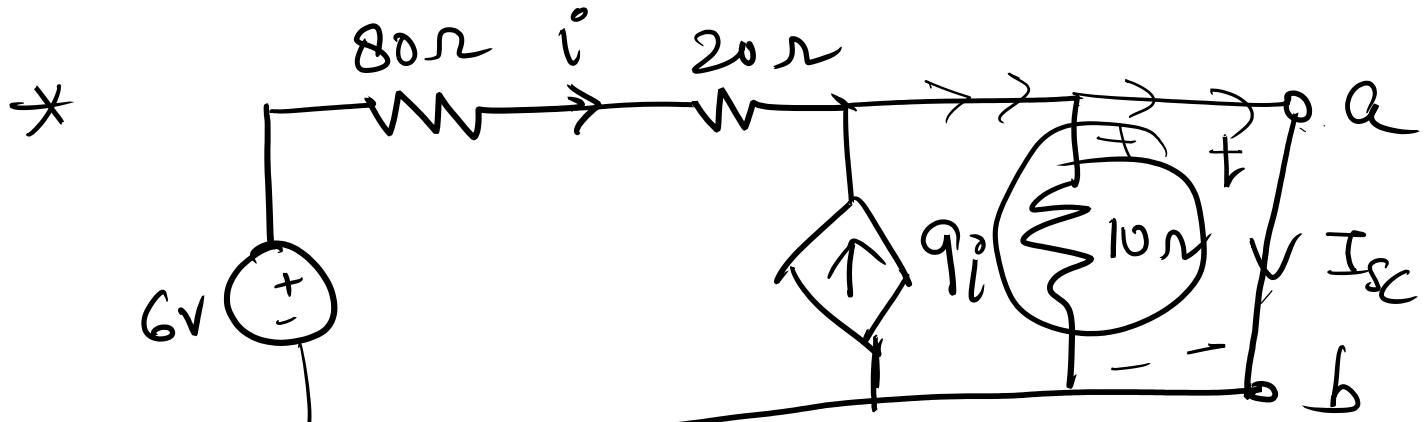

(1) I_{SC}

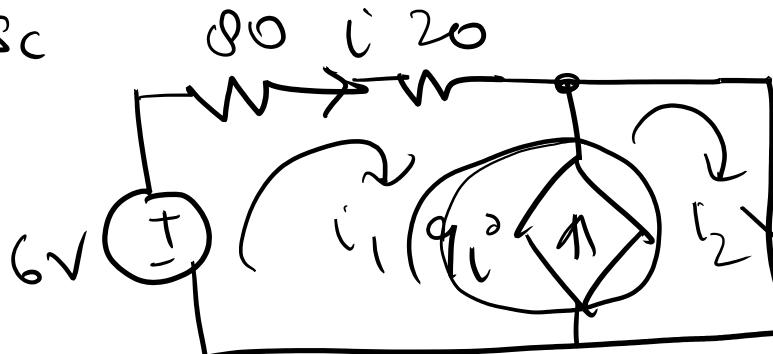


$$I_{SC} = 0.6 \text{ A}$$

$$-6 + 80i_1 + 20i_1 = 0$$

$$i_2 - i_1 = 9i_1$$

$$i = i_1$$

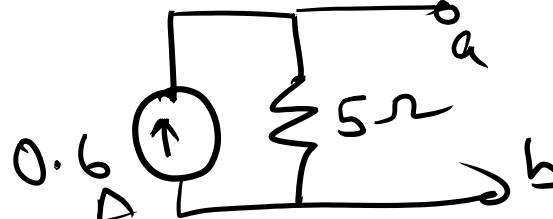


~~$I_{SC} = 0.48 \text{ A}$~~

~~$V_{OC} = 4.8 \text{ V}$~~

$$R_N =$$

~~$V_{OC} = 3 \text{ V}$~~

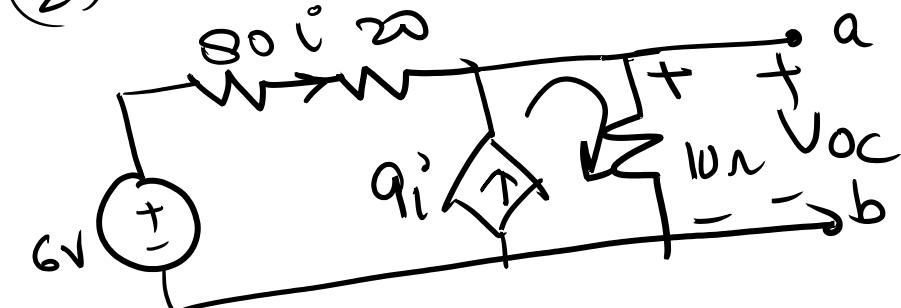

$$R_N = \frac{V_{OC}}{I_{SC}} = \frac{3}{0.6} = 5 \Omega$$