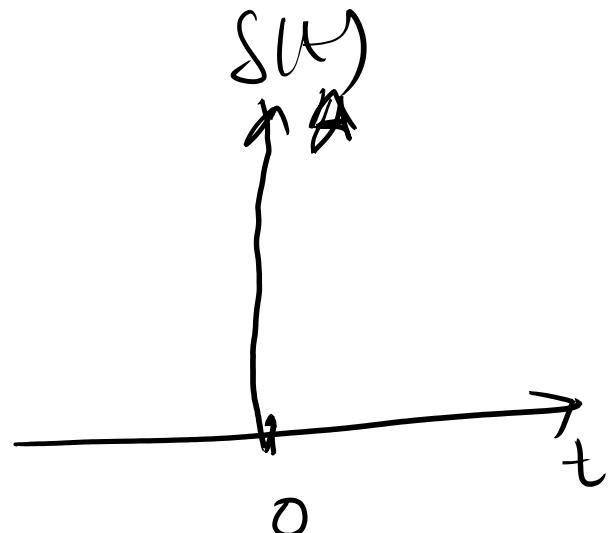


* Test Signals:


① Impulse function: (δ)

$$\delta(t) \begin{cases} A & t = 0 \\ 0 & \text{otherwise} \end{cases}$$



Unit Impulse function:
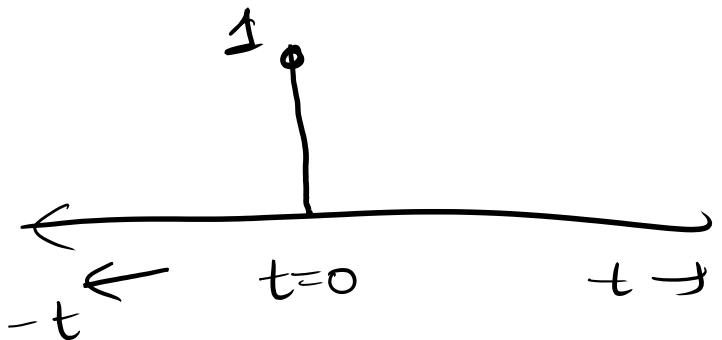
$$\delta(t) \begin{cases} 1 & t = 0 \\ 0 & \text{otherwise} \end{cases}$$



②

Step function : (u)

$$u(t) = \begin{cases} A & t > 0 \\ 0 & t < 0 \end{cases}$$


At $t=0$; Step function is undefined.

At $t=0 \rightarrow$ discontinuous

Unit Step function:

①
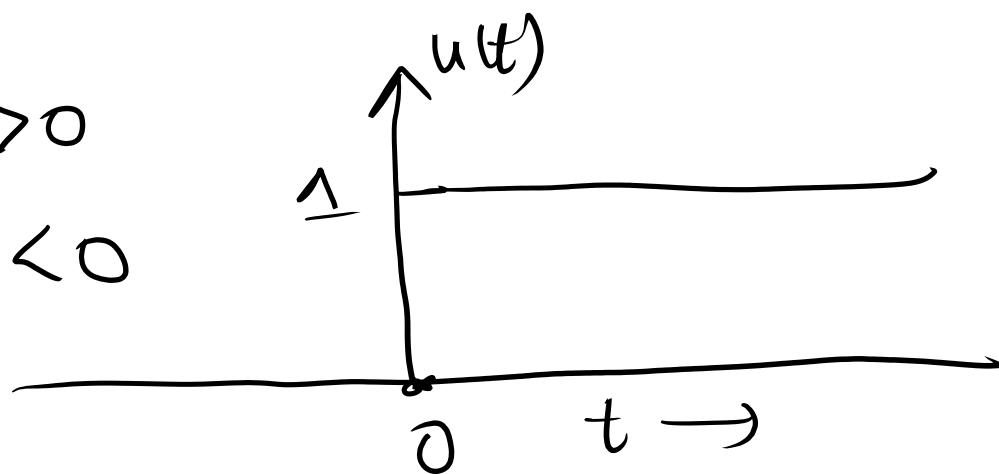
$$u(t) = \begin{cases} \frac{1}{0} & t > 0 \\ 0 & t < 0 \end{cases} \quad (A=1)$$





③ Ramp function ($r(t)$)

$$r(t) = \begin{cases} At & t \geq 0 \\ 0 & t < 0 \end{cases}$$


Unit ramp function:
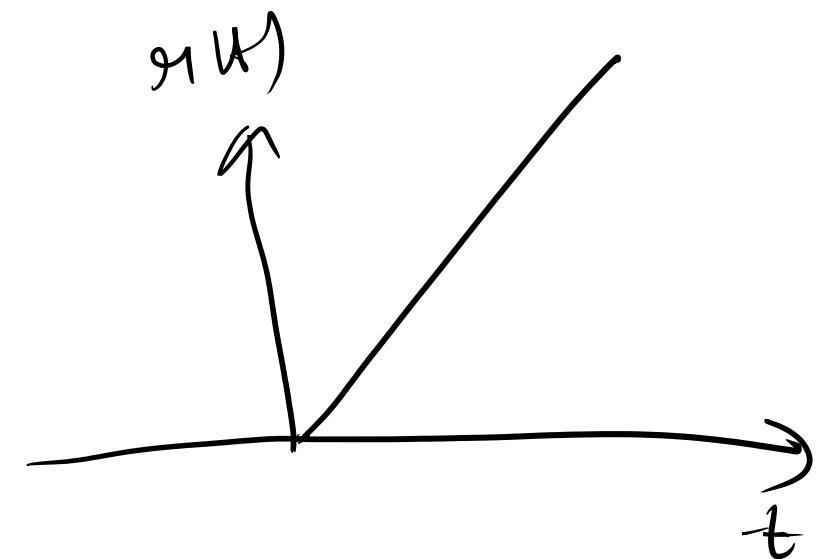
$$s(t) = \begin{cases} 1t & t \geq 0 \\ 0 & t < 0 \end{cases}$$



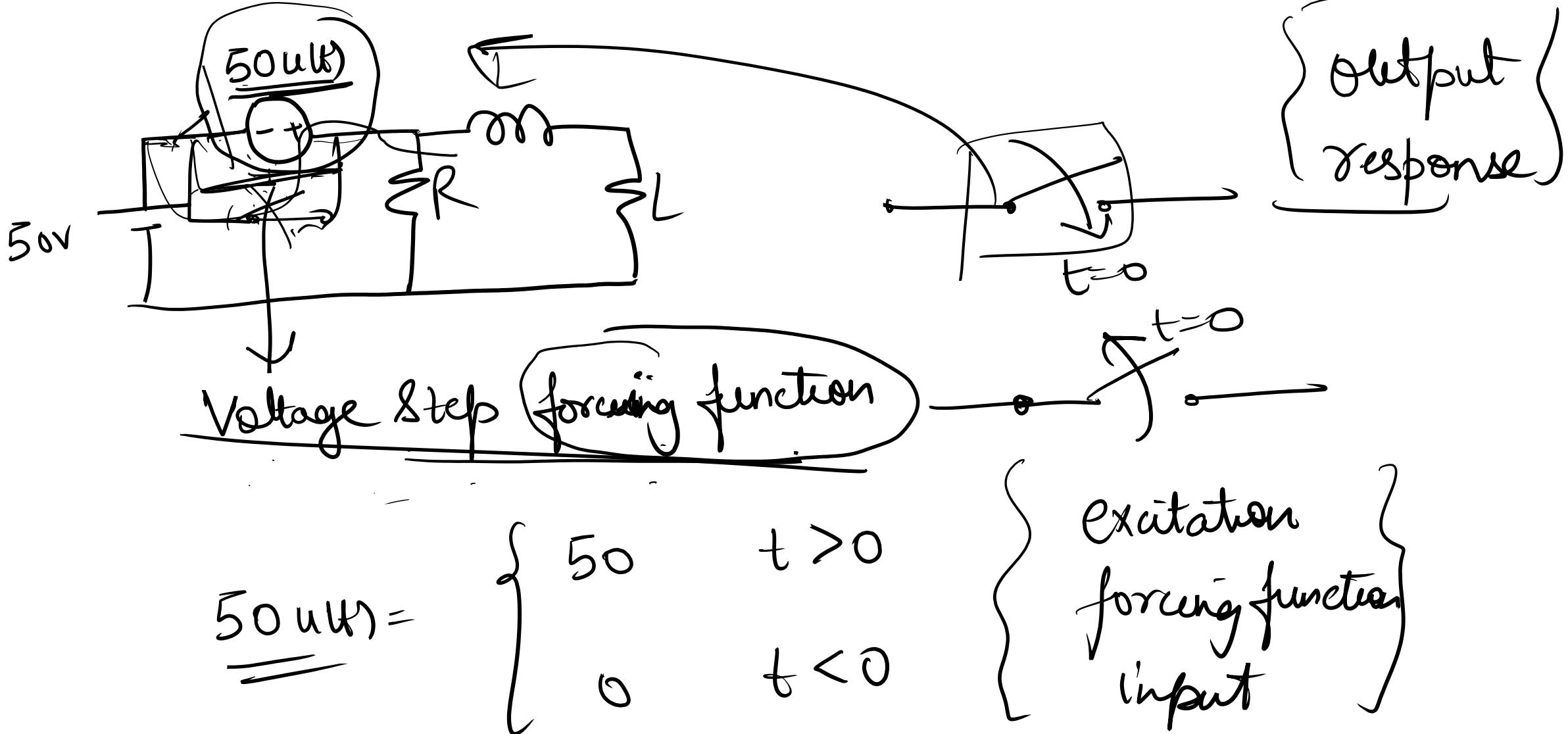

* Step response of RC circuit

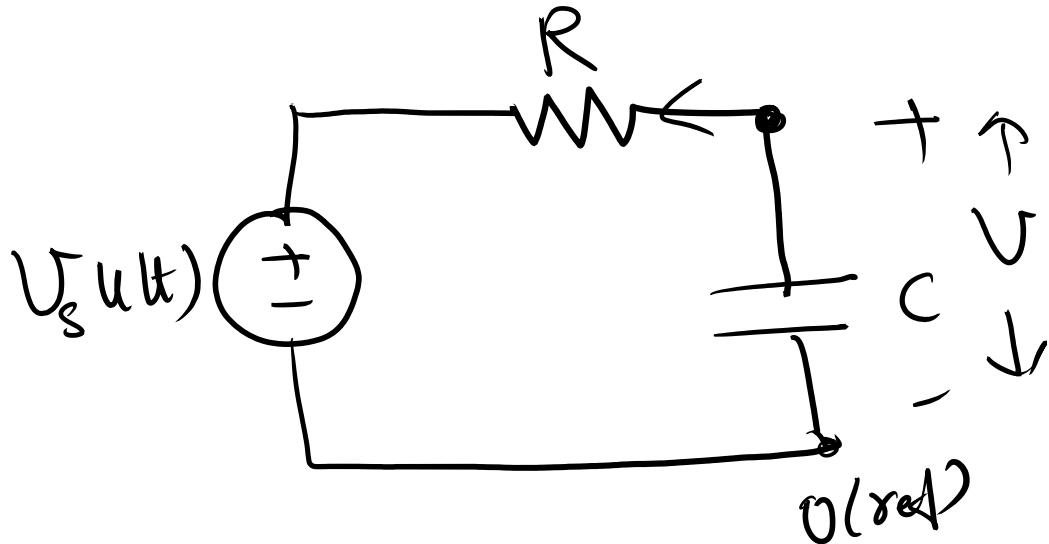

$$\frac{dV}{dt} = \frac{V_s - V}{RC}$$

$$t=0 \rightarrow V(0)$$

$$t=t \rightarrow V(t)$$

$$V_s(t) = \begin{cases} V_s & t>0 \\ 0 & t<0 \end{cases}$$

$$\frac{V - V_s(t)}{R} + \frac{Cd(V - 0)}{dt} = 0$$

$$\frac{V - V_s(t)}{R} + \frac{CdV}{dt} = 0 \quad \textcircled{1}$$

For $t>0$

$$-\frac{V}{R} - \frac{V_s}{R} + \frac{CdV}{dt} = 0 \quad \textcircled{2}$$

$$\frac{V}{R} + \frac{CdV}{dt} = \frac{V_s}{R}$$

$$\frac{V}{RC} + \frac{dV}{dt} = \frac{V_s}{RC}$$

* $V(t) = V_s + (V_0 - V_s)e^{-t/RC}$

let $\tau = RC$;

~~$V(t) = V_s + (V_0 - V_s)e^{-t/\tau}$~~

for source free circuits (RC)

~~$V_s = 0$~~


$V(t) = V_0 e^{-t/\tau}$

~~$V(t) = V(\infty) + (V(0) - V(\infty))e^{-t/\tau}$~~

initial

Steady state


*

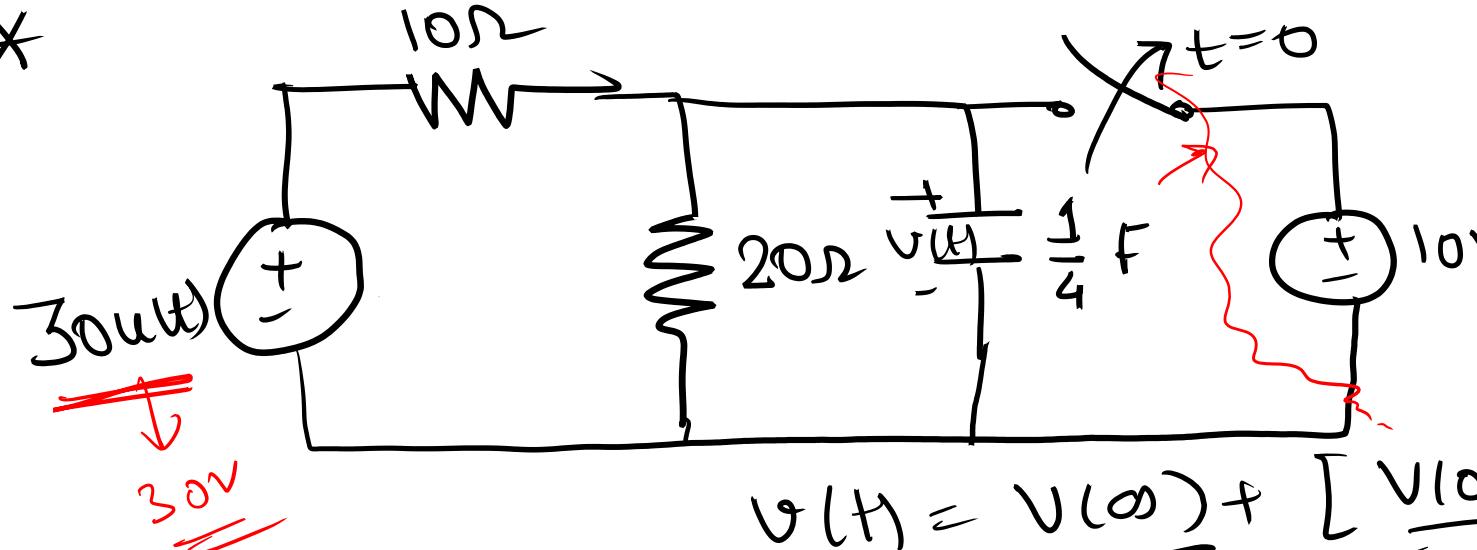

$v(t)$ for all time

$$v(t) = \underline{\underline{v(\infty)}} + \left[\underline{\underline{v(0)}} - \underline{\underline{v(\infty)}} \right] e^{-\frac{t}{\tau}}$$

$\tau = \text{Req. C.}$



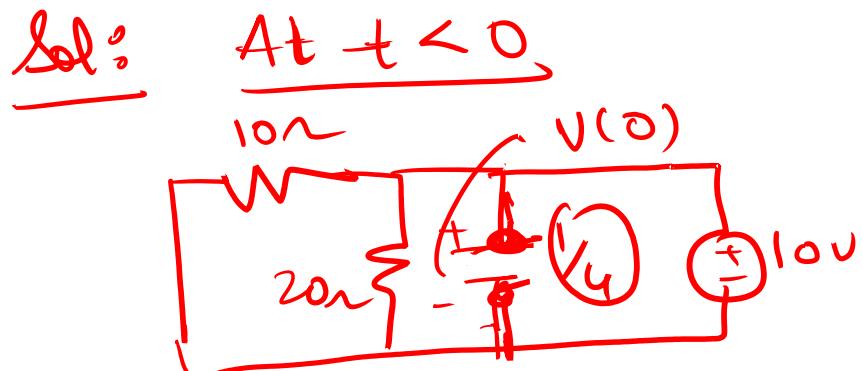


For $t > 0$

$\tau = \text{Req. C.}$

$$\tau = \frac{20}{3} \times \frac{1}{4} = \frac{5}{3} \text{ s}$$

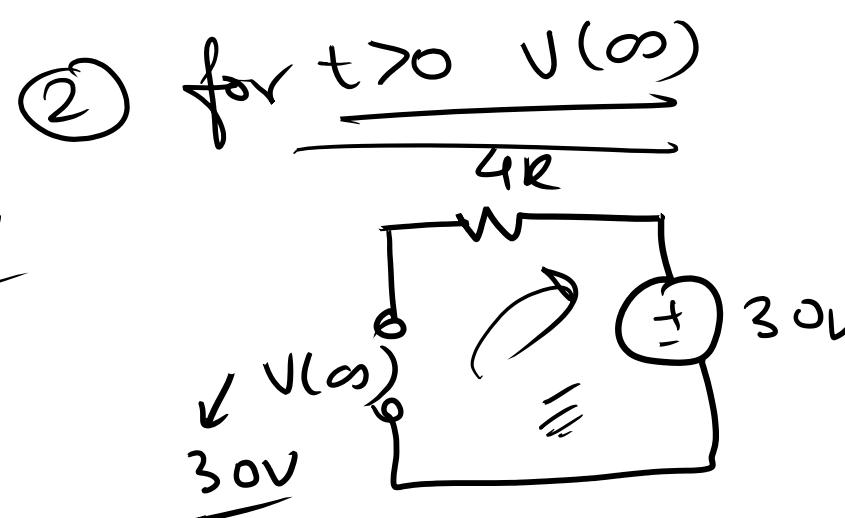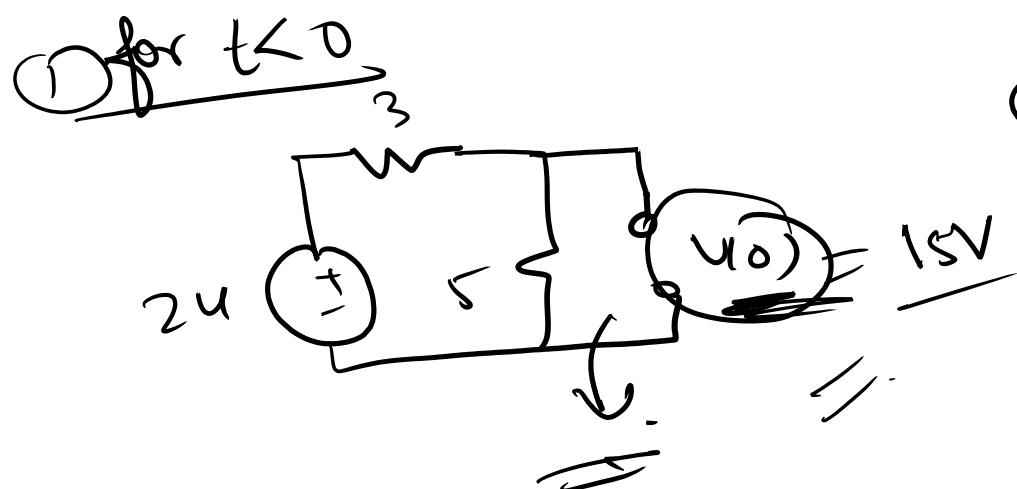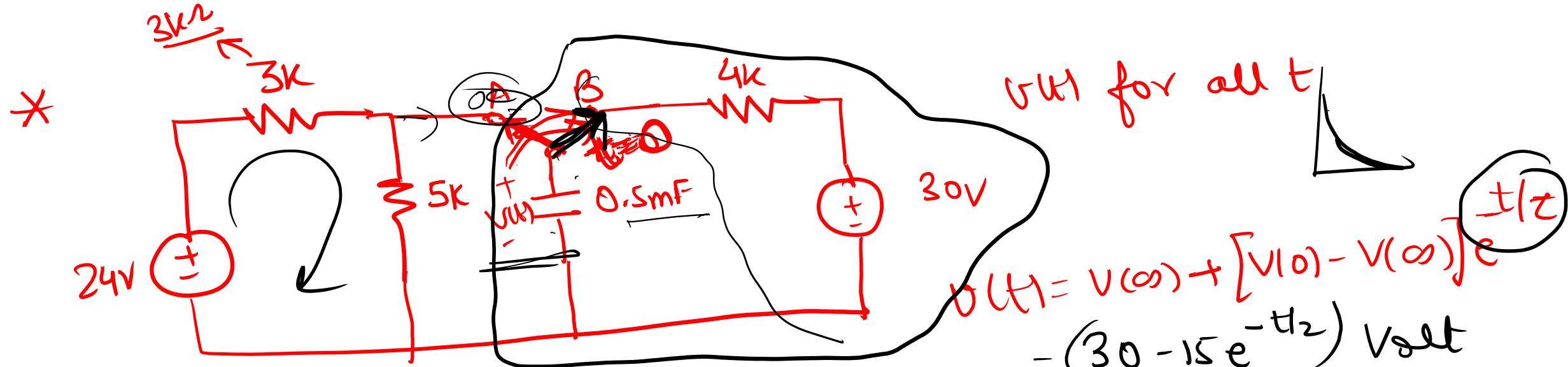
$$v(\infty) = \underline{\underline{20V}}$$



$$\text{Req} \Rightarrow 4\text{k}$$

$$= 4000 \times 0.5 \times 10^{-3}$$

*

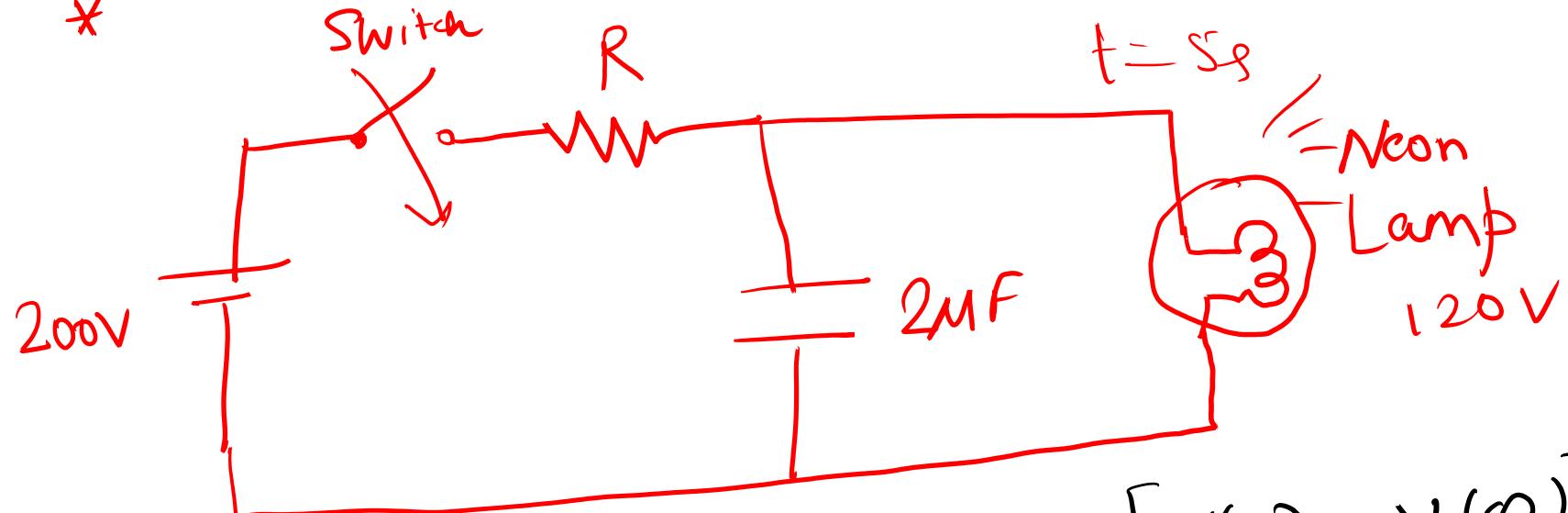


$$R = \frac{272 \text{ M}\Omega}{2.72/2.73 \text{ M}\Omega}$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$

$$120 = 200 + [0 - 200] e^{-t/\tau}$$

$$\tau = RC$$
$$= \frac{2 \times 10^6}{2 \times 10^6}$$

* Step Response of RL Circuit

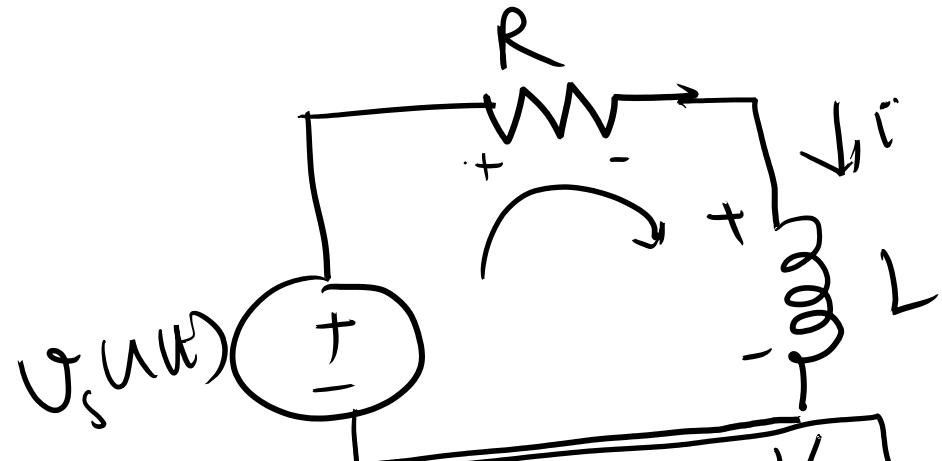

$$i(t) = \frac{V_s}{R} + \left(i(0) - \frac{V_s}{R} \right) e^{-t/\tau}$$

$$\int \frac{L di}{V_s - iR} = f(t)$$

$$-V_s u(t) + iR + \frac{L di}{dt} = 0$$

for $t > 0$; $u(t) = 1$

$$-V_s + iR + \frac{L di}{dt} = 0$$

$$iR + \frac{L di}{dt} = V_s \quad \text{--- (1)}$$

Homogeneous linear Differential Equation

$$i + \frac{L}{R} \frac{di}{dt} = \frac{V_s}{R}$$

$i = i(0)$

$$t=0$$

$$i(t) = \frac{V_s}{R} + \left(i(0) - \frac{V_s}{R} \right) e^{-t/\tau}$$


where $\tau = \frac{L}{R}$

$$i(t) = i_{ss} + \left(i(0) - i_{ss} \right) e^{-t/\tau}$$

where $i_{ss} = V_s / R$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau} \quad \text{Amp}$$

*

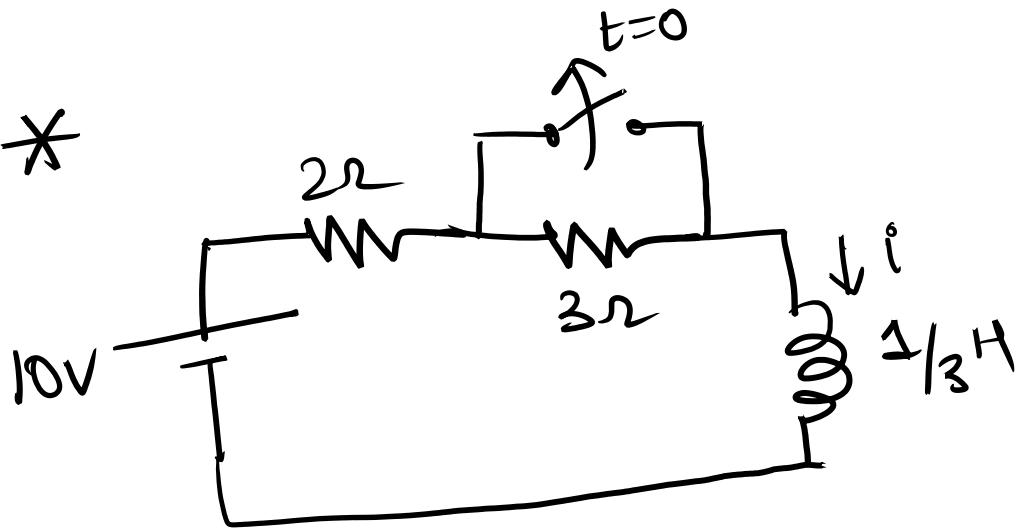

(i) $t < 0$

$$\dot{i}(0) = 5A$$

$$\boxed{\dot{i}(t) = \dot{i}(\infty) + [(\dot{i}(0) - \dot{i}(\infty)) e^{-\frac{t}{RC}}]}$$


$\dot{i}(t)$ for $t > 0$

$$\boxed{\dot{i}(t) = 2 + 3e^{-15t} \text{ (Amp)}} \quad \text{Ans}$$

(ii) $t > 0$

$$\dot{i}(\infty) = 2A$$

$$T = \frac{L}{R} = \frac{1}{15}s$$

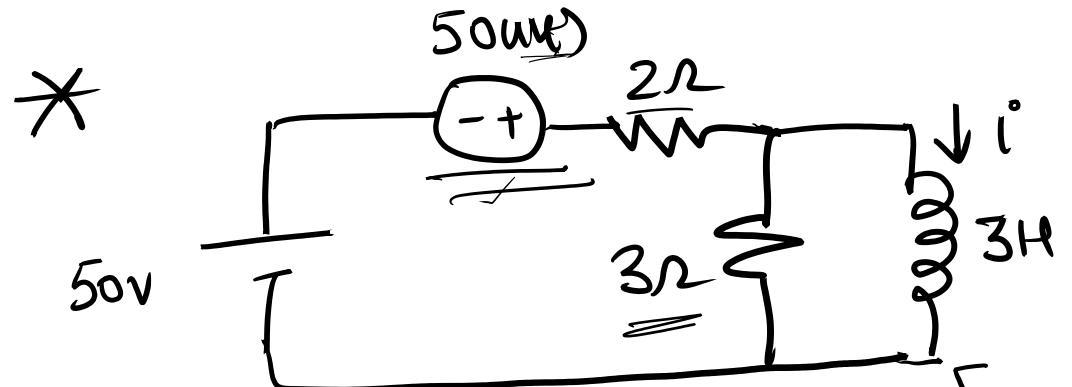

$i(t)$ for all t

$$i(t) = 20 - 10e^{-t/2.5} \text{ A}$$

(i) $t < 0$ $i(0) = X$ $i(t) = 50 + [25 - 50]e^{-t/2.5}$

$i(0) = 25 \text{ A}$

$\frac{25 + 50}{2} = 37.5 \text{ A}$

$\frac{25 - 50}{2} = -12.5 \text{ A}$

$i(t) = 50 - 25e^{-t/2.5} \text{ Amp}$


(ii) $t > 0$

$$i(0) = \underline{\underline{50 \text{ A}}}$$




$$-50 - 50 + 2i^{\circ} = 0$$

$i^{\circ} = 50 \text{ A}$

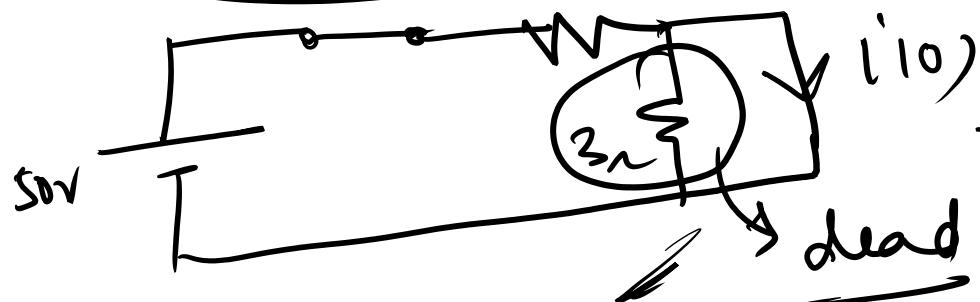

$$R_{eq} = \frac{6}{5} \Omega$$
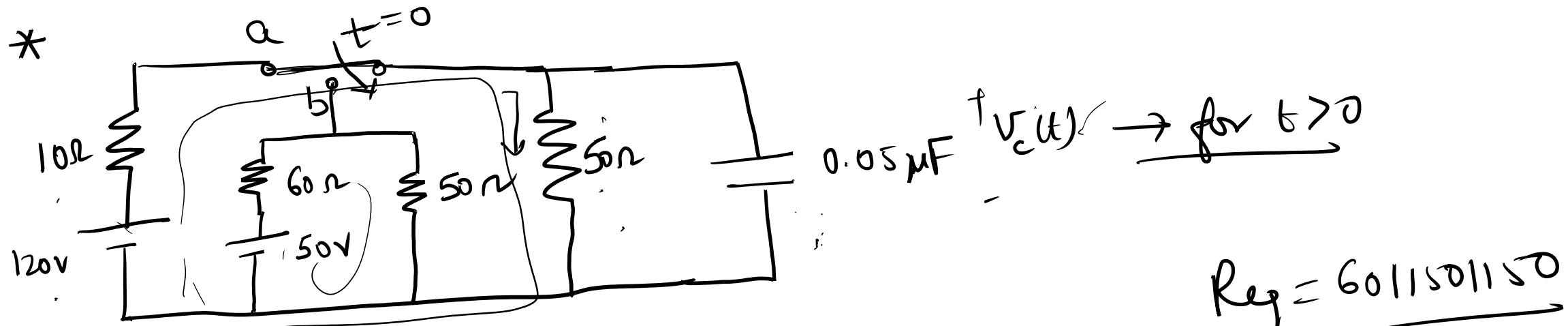
$$T = \frac{L}{R_{eq}} = \frac{3 \times 5}{6} = 2.5 \text{ s}$$



(i) $t < 0$

$$V_c(0) = 100V$$


(ii) $t > 0$

$$V_c(\infty) = 14.7V$$


$$\tau = R_{eq} \cdot C = 0.88ms$$

$$R_{eq} = \frac{60 \parallel 150 \parallel 150}{\frac{300}{17}} = \frac{300}{17}$$
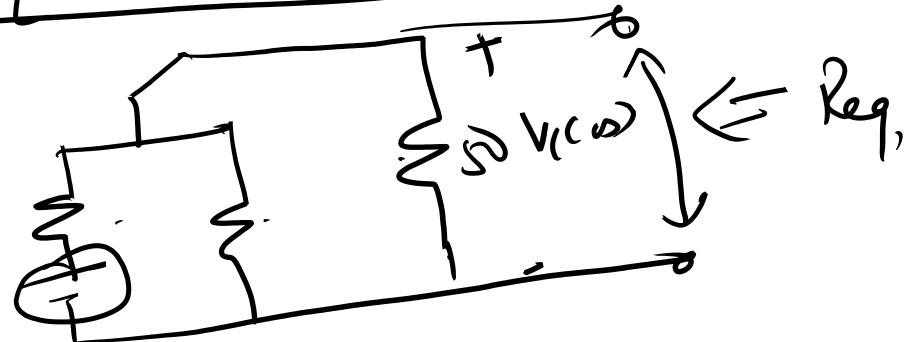
$$V_c(t) = V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-t/\tau}$$



for $t > 0$

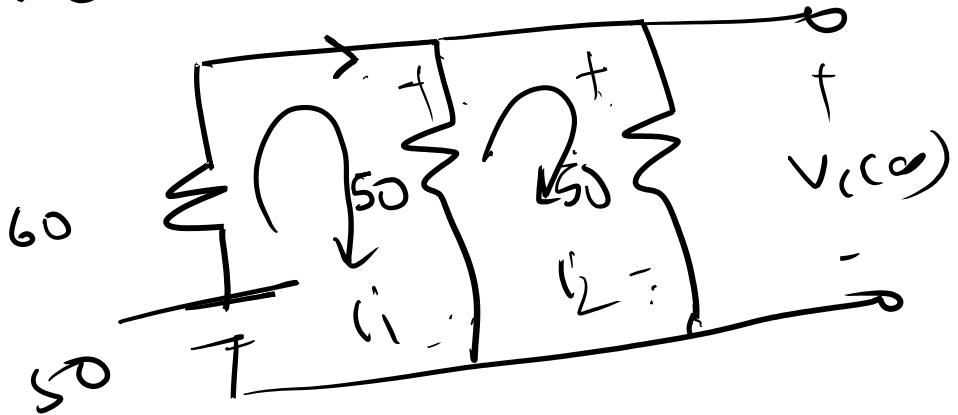

$$-50 + 60i_1 + 50(i_1 - i_2) = 0 = -50 + 110i_1 - 50i_2$$

$$50V_2 + 50(i_2 - i_1) = 0$$

$$100i_2 = 50i_1$$

$$i_2 = \frac{i_1}{2}$$

$$i_2 = \frac{25}{85} A.$$


$$V_L(\infty) = \frac{25}{85} \times 50 = 14.3 A$$

$$110i_1 - 50i_2 = 0$$

$$110i_1 - 50\left(\frac{i_1}{2}\right) = 50$$

$$110i_1 - 25i_1 = 50$$

$$i_1 = \frac{50}{85} A$$

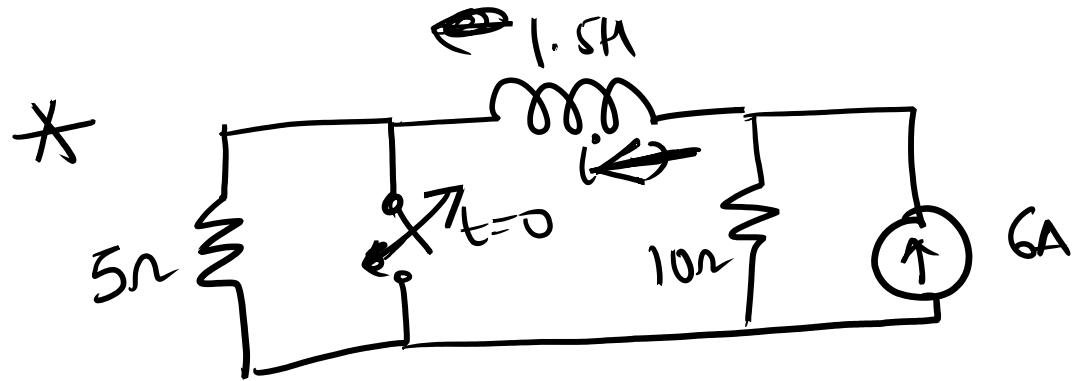

(i) for $t < 0$

$\& \overset{\circ}{i}(0^-) = 6A$ ✓

$\overset{\circ}{i}(0^-) = i(0) = i(0^+)$

$$i(t) = 4 + 2e^{-10t} \text{ Amp}$$

$$\overset{i(t) \text{ for } t > 0}{=} 4 + 2e^{-10t} \text{ (Amp)}$$


(ii) $t > 0$

$$\overset{\circ}{i}(\infty) = 4A$$

$$R_{eq} = 15\Omega$$

$$T = \frac{L}{R_{eq}} = \frac{15}{750} = \frac{1}{50} \text{ s}$$
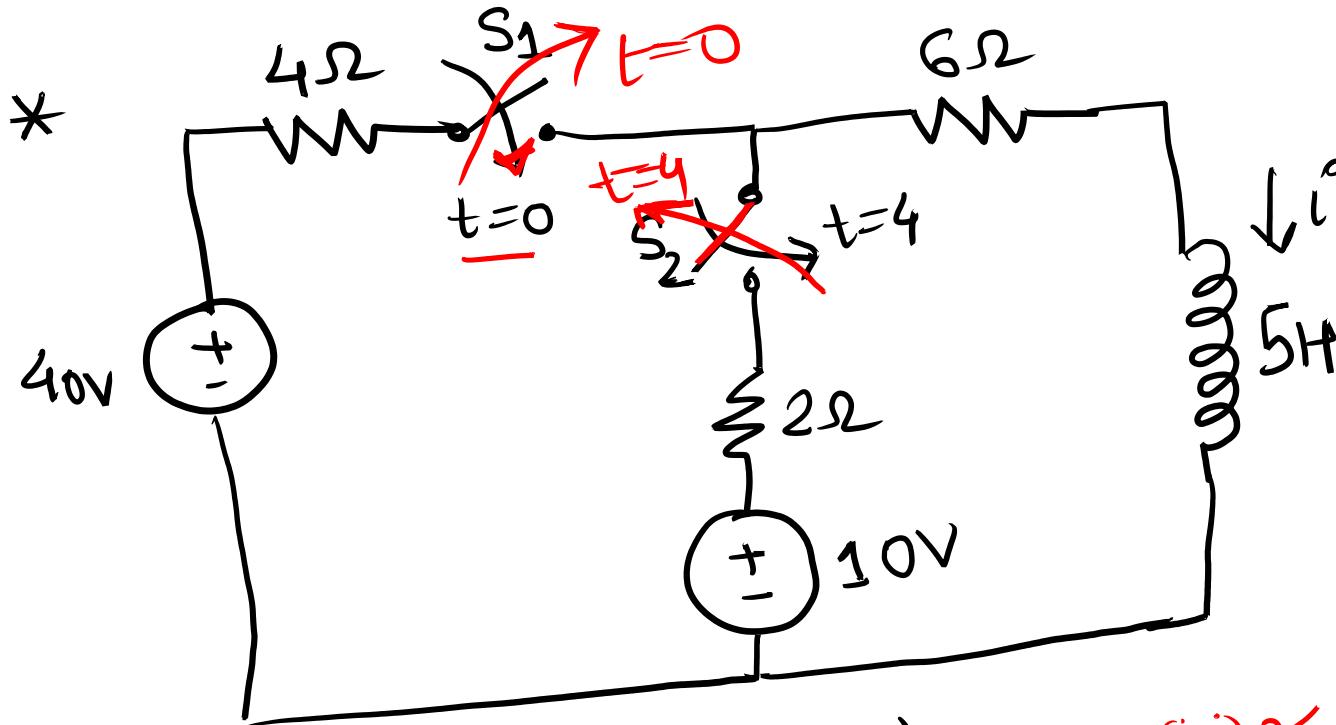
$$\& i(t) = \overset{\circ}{i}(\infty) + \left[\overset{\circ}{i}(0) - \overset{\circ}{i}(\infty) \right] e^{-t/T}$$




(i) for $t < 0$ ($S_1, S_2 \rightarrow \text{open}$)

$$i(0^-) = 0A = i(0^+) = i(0^+)$$


(i) $t < 0$

(ii) $0 < t < 4$

(iii) $t > 4$

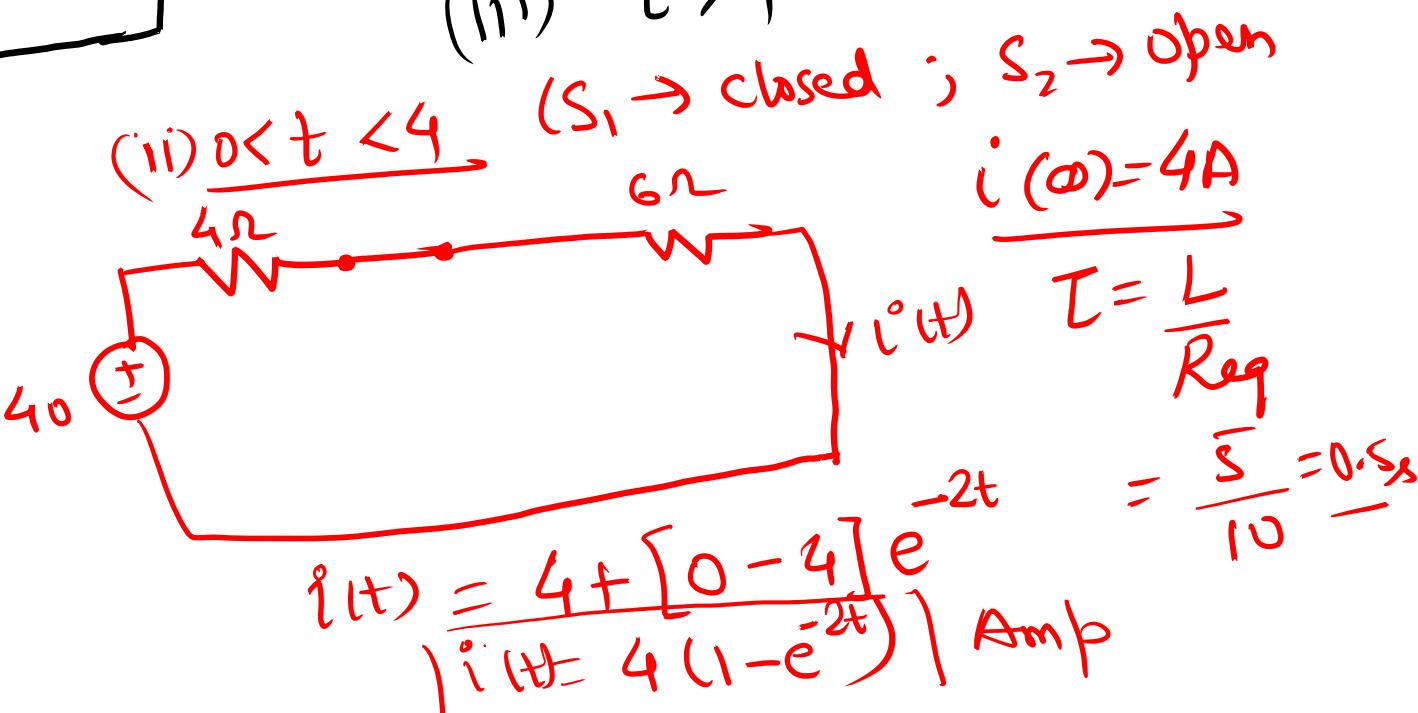

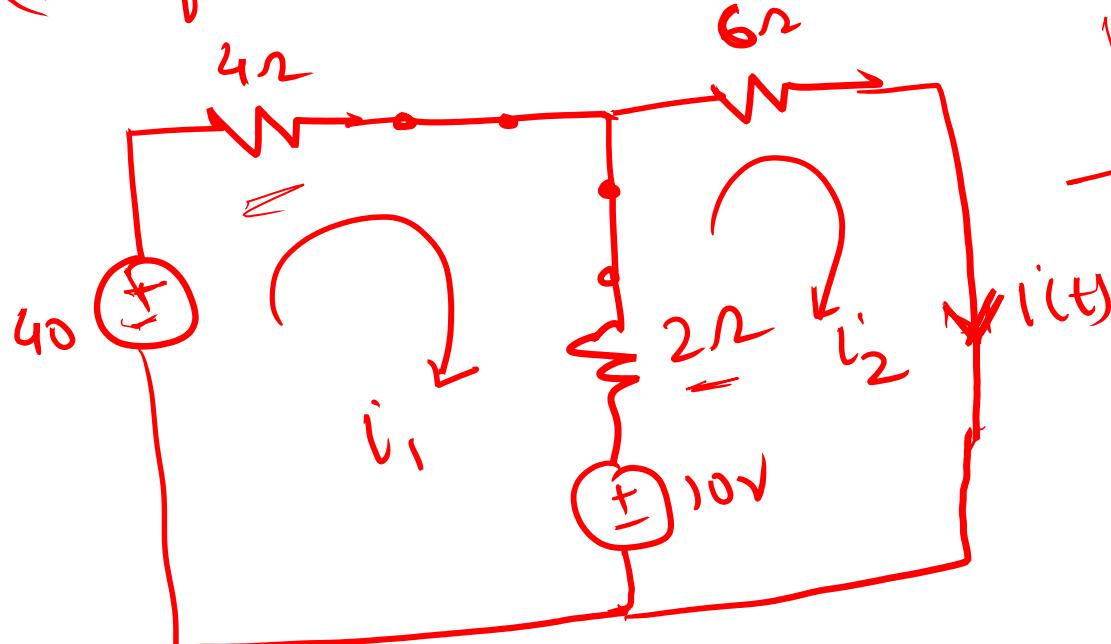(iii) for $t > 0$ ($S_1, S_2 \rightarrow \text{closed}$)



$$\underline{-40 + 4v_i + 2(i_1 - i_2)} = 0$$

$$+10$$

$$-10 + 2(i_2 + i) + 6v_2 = 0$$

$$\Rightarrow i_2 = i(\infty) = \underline{4.09 \text{ A}}$$


$$i(t) = i(\infty) + [i(4) - i(\infty)]e^{-\frac{t}{T}}$$

$$i(t) = 4(1 - e^{-\frac{t}{2}}) \quad \left\{ 0 < t < 4 \right\}$$

$$i(4) = 4(1 - e^{-2}) \text{ A}$$

$$= 4(1 - e^{-8}) \text{ A}$$
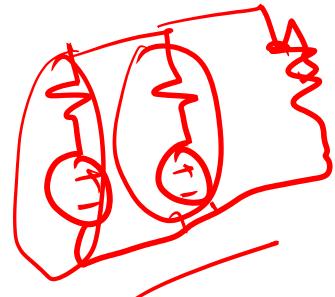
$$= \underline{\underline{4 \text{ A}}}$$



$$R_{eq} = (4||2) + 6 = 9.33 \Omega$$

$$T = \frac{L}{R_{eq}} = \frac{5}{7.33} \text{ s}$$