
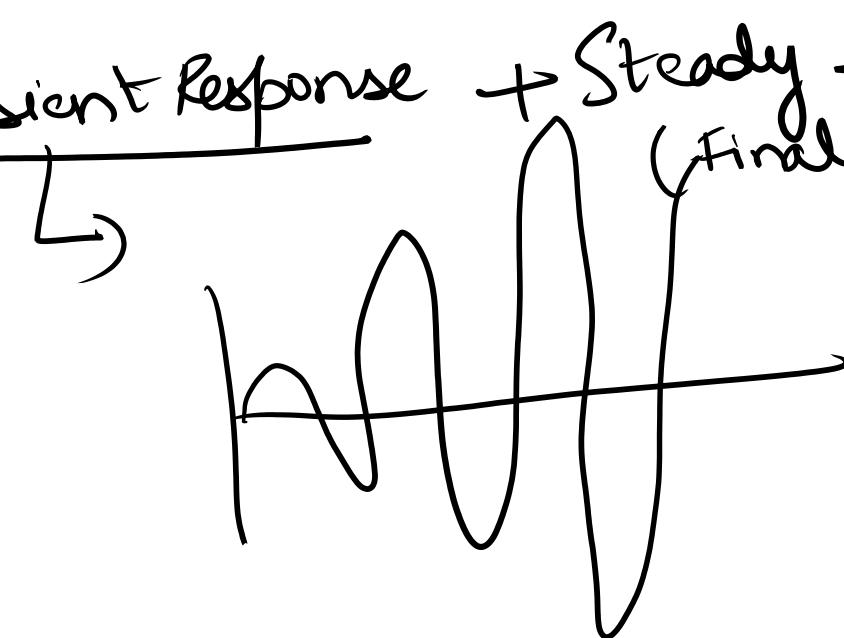
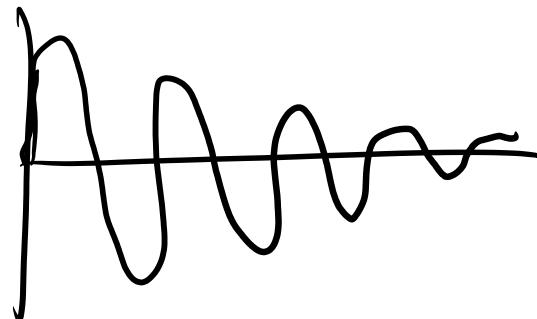


DC Transient Analysis

↳ 'Transitory' \Rightarrow Small period of time

- Excitation \Rightarrow Input
- Response \Rightarrow Output
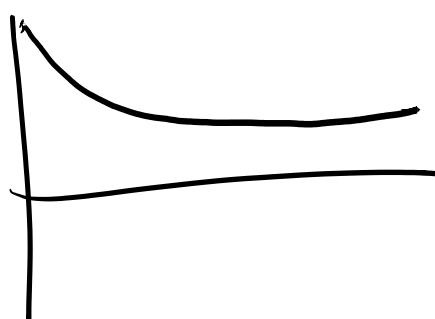
$$\text{Complete Response} = \underbrace{\text{Transient Response}}_{\text{Settling down}} + \text{Steady State} \quad (\text{Final})$$




* 1800's

electricity

magnetism

→ Oersted's

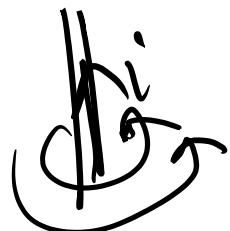→ Current carrying conductor produces magnetic field.



Faradays, Maxwell

⇒ Electromagnetism

L ⇒ Inductor
C ⇒ Capacitor

DC Transients → Transitory

$L \rightarrow$; $C \rightarrow$

- * Faraday & Henry → Changing magnetic field could induce a voltage in a neighbouring circuit

Induced voltage \propto time rate of change of current
which produced the magnetic field

$$V \propto \frac{di}{dt}$$

$$V = K \frac{di}{dt}$$

↳ 'L' → Inductor

$$V = L \frac{di}{dt}$$

Inductance:

Inductor (coil / Reactor)




Pure Inductance

$$L = N \frac{d\phi}{di} = N \phi \quad \textcircled{1}$$

ϕ = Magnetic flux
N = No. of turns

$$\checkmark \phi = \frac{\text{mmf}}{\text{Reluctance}} = \frac{Ni}{R}$$
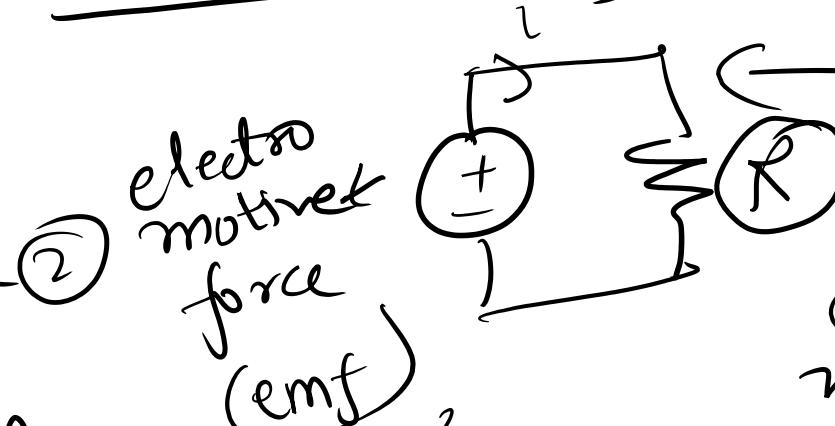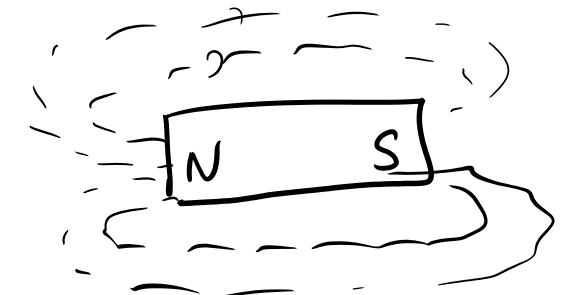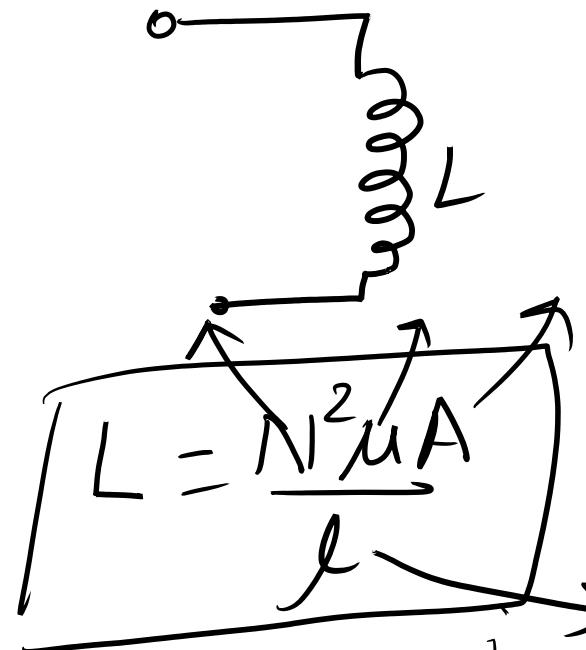
$$L = \frac{N^2 \phi}{i} = \frac{N^2 \mu A}{l}$$



Reluctance

(mmf) \rightarrow
magnetomotive
force


μ_0 = Permeability
 ϵ_0 = permittivity

$$V_L = L \frac{di}{dt}$$

No changing current;

$$\frac{di}{dt} = 0$$

$$\boxed{V_L = 0}$$

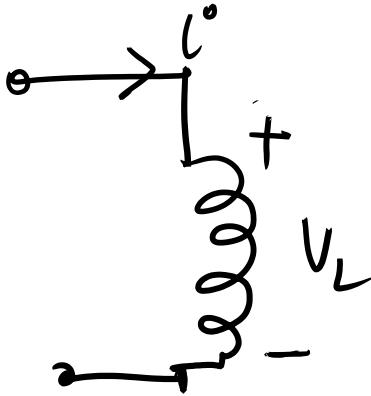

Unit of L

→ Henry (H)

In case of DC; $\frac{di}{dt} = 0$; $V_L = 0$;

inductor behaves as an ~~open~~ ^{short} circuit



* Capacitance:

$$q = CV$$

charge Capacitance

$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

$$i = C \frac{dv}{dt}$$

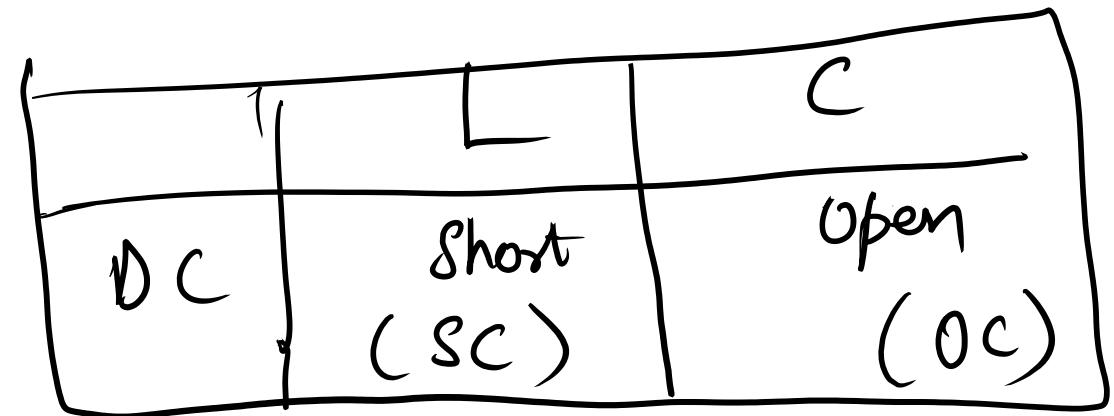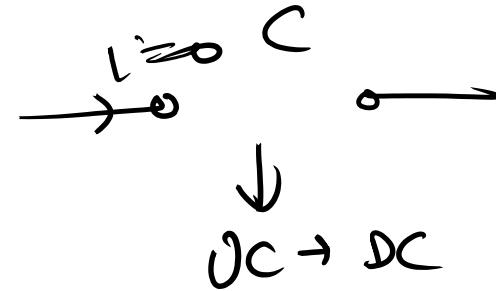

* if there is no changing potential;

$$\text{i.e. } \frac{dv}{dt} = 0 ; i = 0$$

$$\text{in DC; } \frac{dv}{dt} = 0$$

Capacitance will behave as
open circuit

$$i = C \frac{dv}{dt}$$

$$dt = 0 ; \frac{dv}{dt} = \infty ; i = \infty \times \underline{\text{not possible}}$$

→ Capacitor voltage cannot change instantaneously

* Capacitors



$$C = \frac{\epsilon A}{d}$$

$$i = C \frac{dv}{dt}$$

$$\frac{i}{C} dt = dv$$

$\star \boxed{U_C = \frac{1}{C} \int i dt + V_C(0)} \star$

* Energy stored in Inductance & Capacitance


$$W_L = ? \quad \frac{1}{2} L I^2$$

$$W_C = \frac{1}{2} C V^2$$


$L \rightarrow$ DC
(SC)

$C \rightarrow$ (OC)

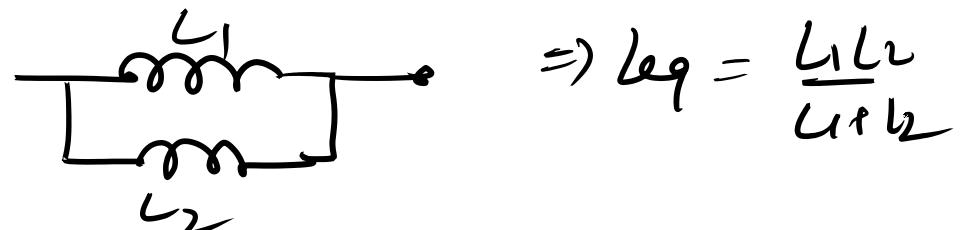
* ~~Inductors~~ Inductors in Series / Parallel



* Capacitors:

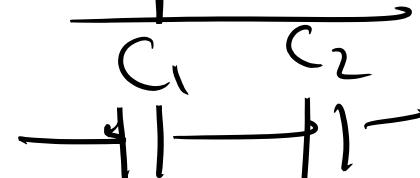

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

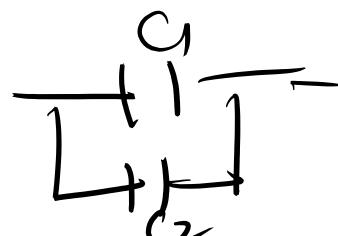

$$C_{eq} = C_1 + C_2$$


* Homogeneous Linear Differential Equations

↳ Variable Separation Method

* Response = $\frac{\text{Transient Response}}{\text{(Natural Response)}}$ + $\frac{\text{Steady State Response}}{\text{(Forced Response)}}$

* Source Free RL circuit

Assume inductor to be precharged.

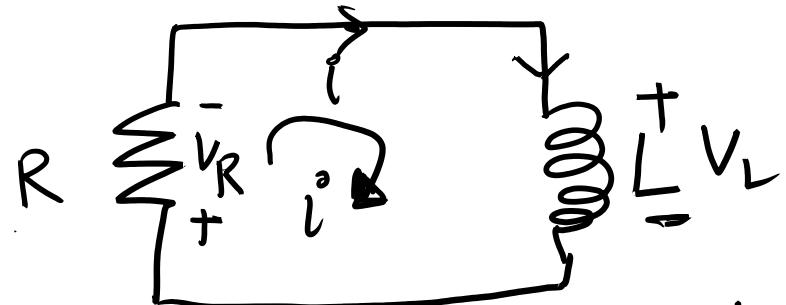

Apply KVL in the given circuit;

$$+V_R + V_L = 0 \quad \text{--- } ①$$

$$iR + L \frac{di}{dt} = 0 \quad \text{--- } ②$$

$$L \frac{di}{dt} = -iR$$

$$\frac{di}{i} = -\frac{R}{L} dt \quad \text{--- } ③$$

Eq 3
Integrating both sides
w.r.t. time

$$\text{At } t=0 \rightarrow I_0$$

$$\text{At } t=t \rightarrow i$$

$$\int \frac{di}{i} = -\frac{R}{L} \int dt$$

$$I_0 \quad i = I_0 e^{-\frac{Rt}{L}}$$

$$i = I_0 e^{-t/\tau}$$

Where $\tau = \frac{L}{R}$ Time constant

$$i = I_0 e^{-t/\tau}$$

$$\frac{i}{I_0} = e^{-t/\tau}$$

$$t=0; \frac{i}{I_0} = 1 \rightarrow 63\%$$


$$t=\tau; \frac{i}{I_0} = \frac{1}{e} = 0.37 \rightarrow 37\%$$

$$t=2\tau; \frac{i}{I_0} = \frac{1}{e^2} = 0.13 \rightarrow 13\%$$

$$t=3\tau; \frac{i}{I_0} = 0.049 \rightarrow 5\%$$

$$t=4\tau; \frac{i}{I_0} = 0.018 \rightarrow 2\%$$
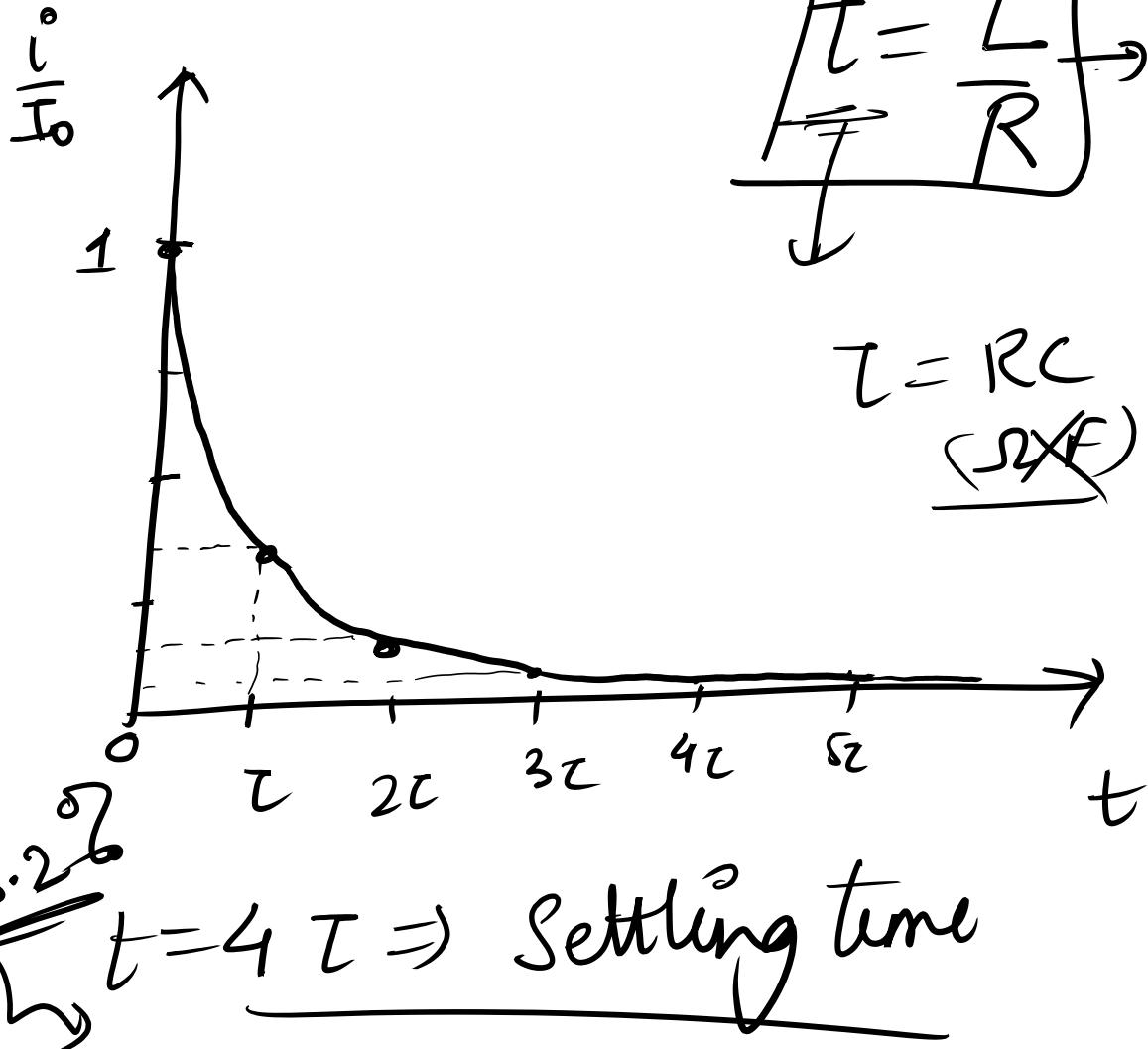
$$t=5\tau; \frac{i}{I_0} \approx 0.006 \rightarrow 1\%$$




$$\boxed{\tau = \frac{L}{R}} \rightarrow \underline{\underline{\text{seconds}}}$$

$$\tau = RC \quad (\text{s})$$

~~(SXF)~~

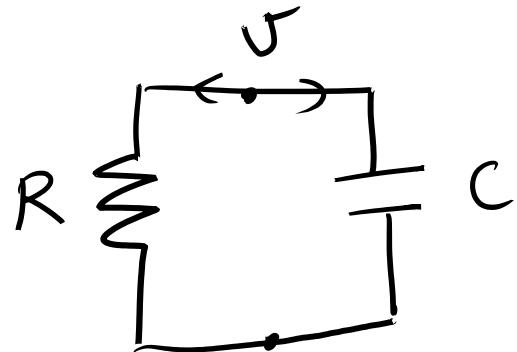* Source Free RC Circuit: (Assume that capacitor is precharged)



Applying KCL at node;

$$\frac{V-0}{R} + \frac{Cd(V-0)}{dt} = 0$$

$$\frac{V}{RC} + \frac{dV}{dt} = 0 \quad \text{--- } ①$$

for solving H.L.D.E; -

$$\frac{V}{RC} = -\frac{dV}{dt}$$

$$\int \frac{dV}{V} = - \int \frac{dt}{RC}$$

Integrating both sides w.r.t.

$$t=0 \rightarrow V_0$$

$$t=t \rightarrow V$$

$$V = V_0 e^{-t/RC}$$

$$V = V_0 e^{-t/\tau_{RC}}$$

τ = time constant for RC ckt = RC


$$V = V_0 e^{-t/\tau}$$

* Plot the response;


$$\Rightarrow \text{Settling time} = 4\tau$$

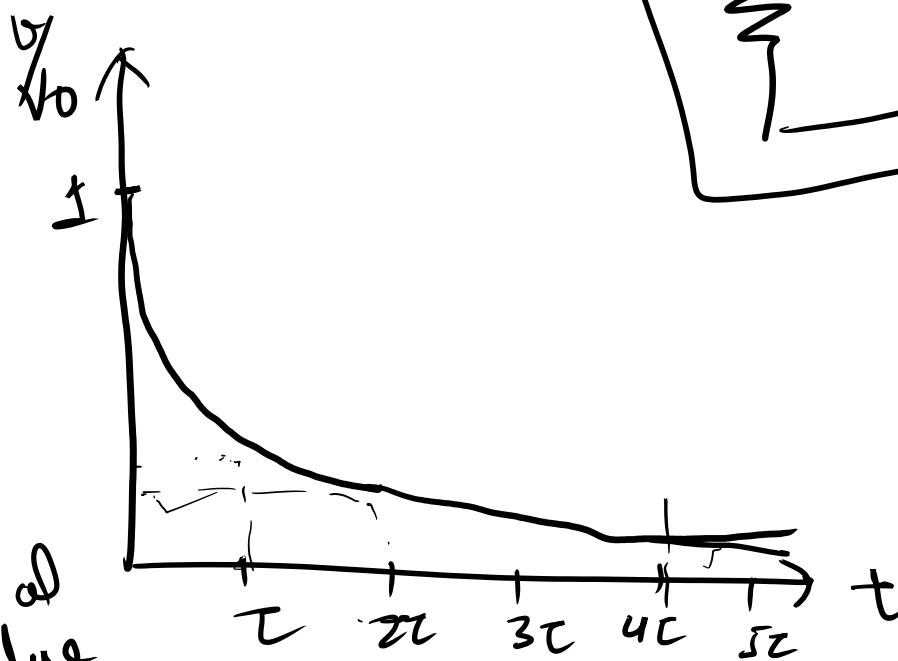(98.2%)

time at which the response has decayed to 98.2% of its initial value




• RL	$\frac{\tau}{L}$
• RC	RC

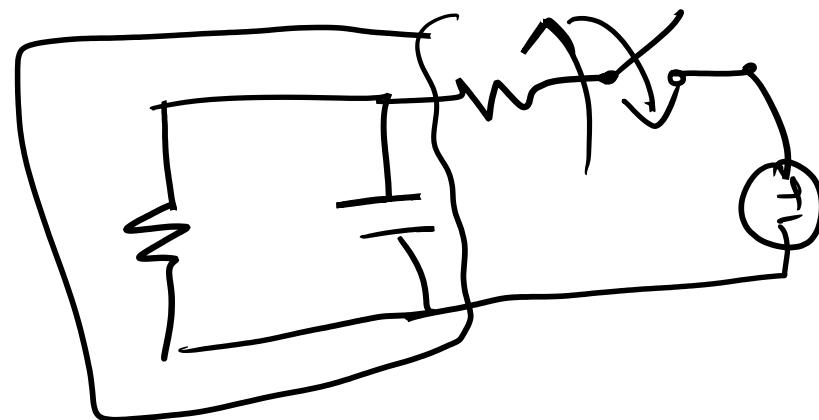


$$RL \Rightarrow i = I_0 e^{-t/\tau} \quad [\tau = L/R]$$
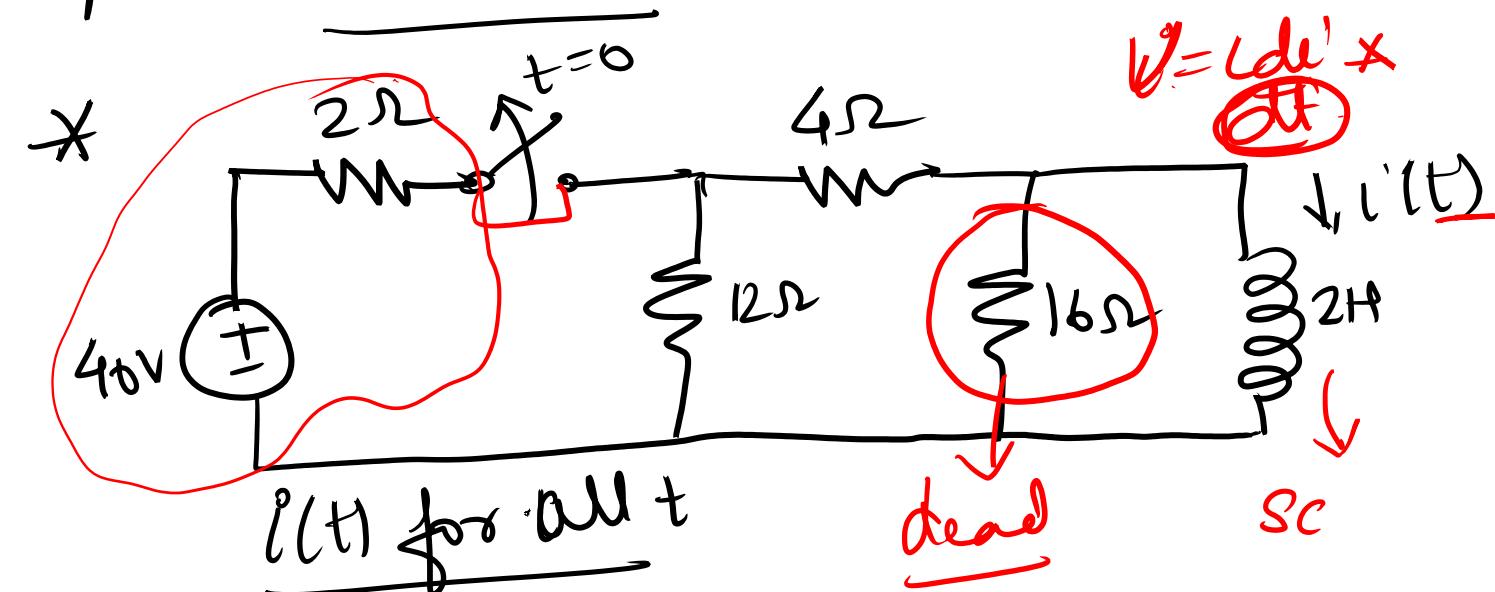
$$RC \Rightarrow V = V_0 e^{-t/\tau} \quad [\tau = RC]$$




$t = -\infty$ \leftarrow
 $t = 0^+$ \circlearrowleft
 $t = \infty$ \curvearrowright

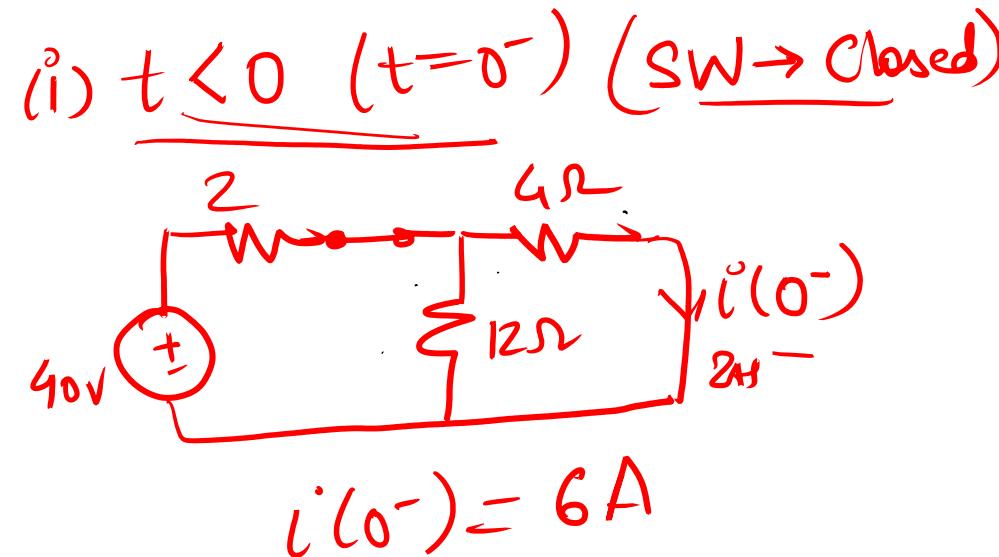
$$\tau = \frac{L}{R} = \underline{\underline{\tau}}_{\text{Req}}$$



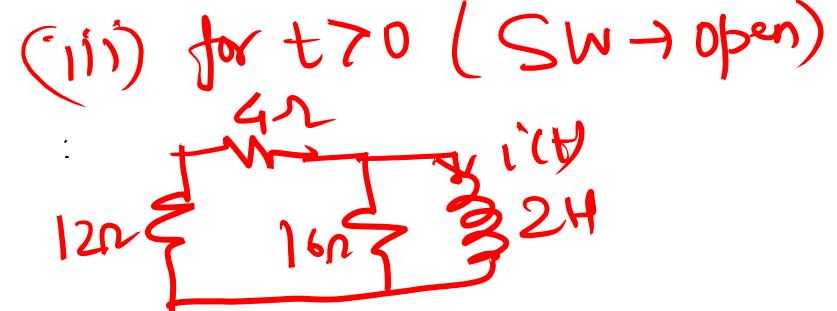(ii) Since inductor current
cannot change instantaneously

$$\underline{i(0^-)} = \underline{i(0)} = \underline{i(0^+)} = 6A$$




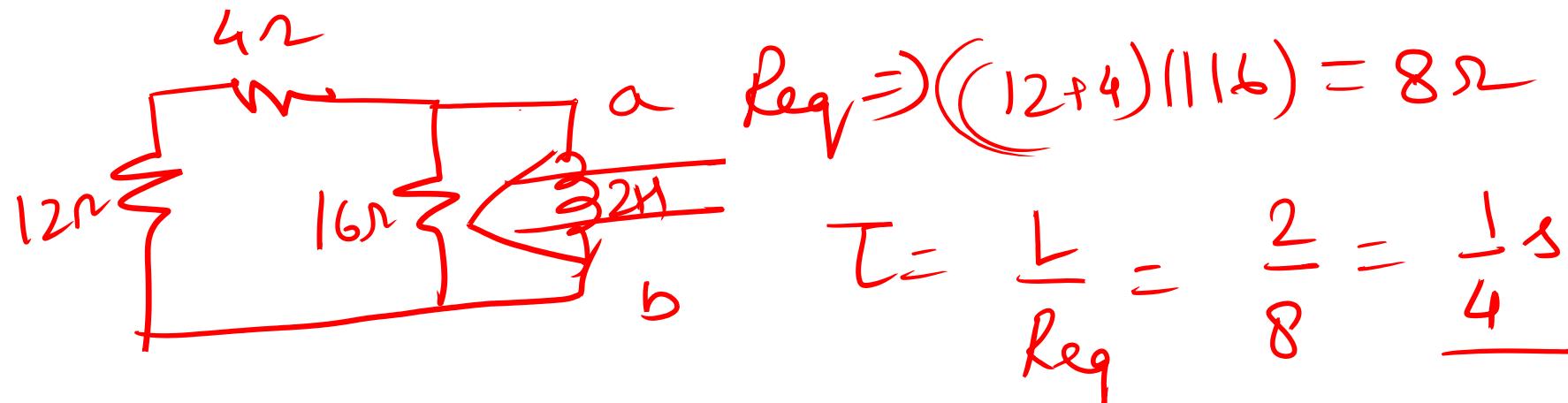

$$i = I_0 e^{-t/T}$$


$$i(t) = 6 e^{-t/(1/4)}$$

$$i(t) = 6 e^{-4t} \text{ (Amp)}$$

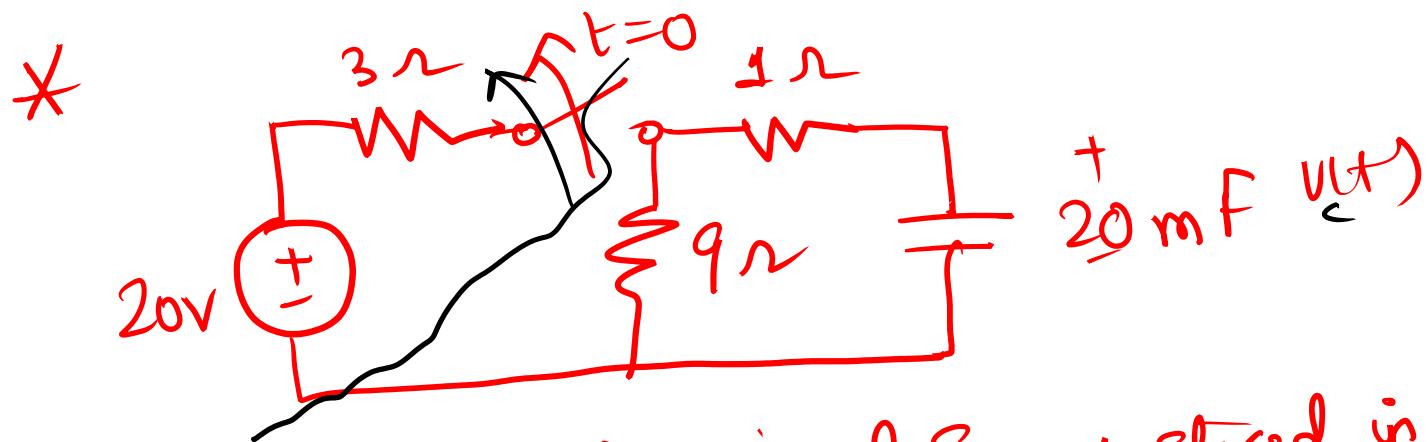

$\Rightarrow V_c(t)$ for $t > 0$ & initial Energy stored in capacitor

(i) $t < 0$ ($SW \rightarrow$ closed)

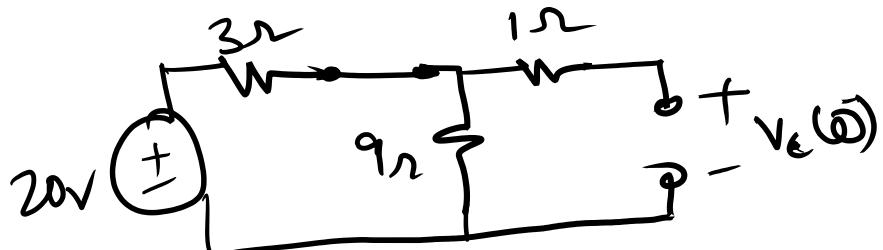

(ii) Since Cap. voltage cannot change

$$V_c(0^-) = V_c(0) = V_c(0^+) = \underline{\underline{15V}}$$

$$V_c(0^-) = \underline{\underline{15V}}$$

$$WE = \frac{1}{2} C V^2$$

$$= \frac{1}{2} \times 20 \times 10^{-3} \times (15)^2$$


instantaneously;

$$R_{eq} = 10\Omega$$

$$T = 10 \times 20 \times 10^{-3} S$$


$$= 0.2 s$$

$$V_c(t) = 15 e^{-t/0.2} V.$$

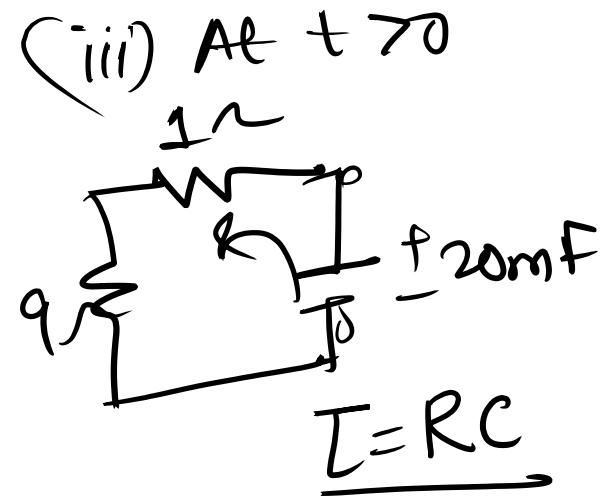


$$I = \underline{\underline{RC}}$$

$$T = R C$$

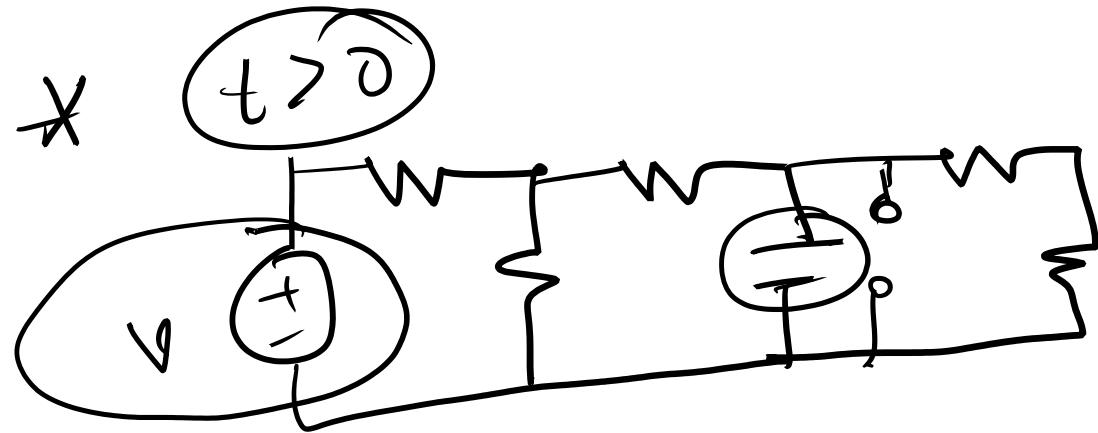

→ Sourced RL & RC circuit

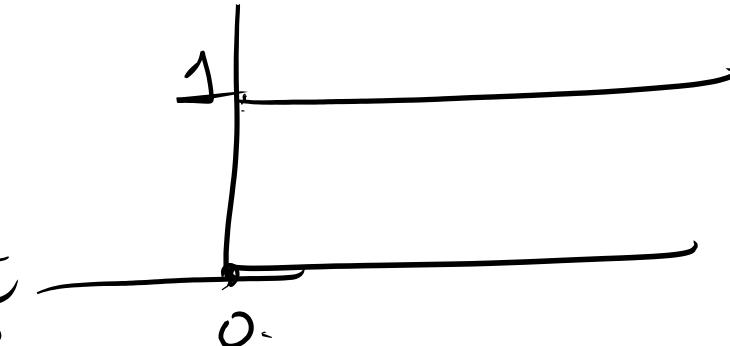

Test input

- 1. Ramp signal
- 2. Step signal
- 3. delta signal
- 4. Sinusoid

