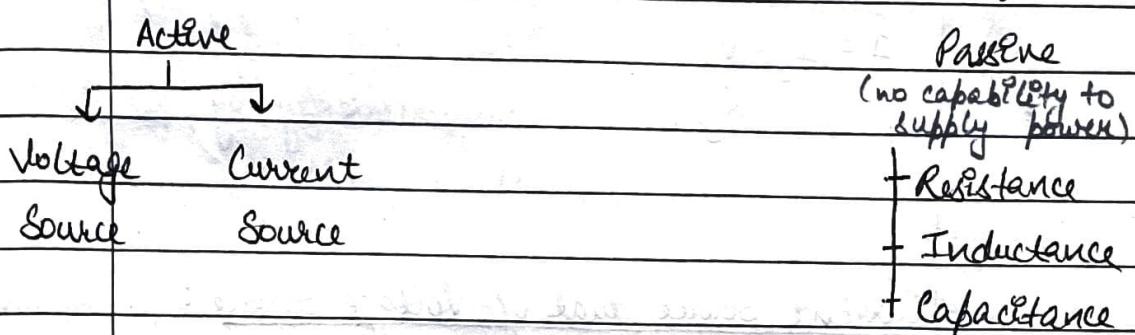


24/09/20 Ch. 1 - DC Circuits


Circuit Elements

- ① Resistance
- ② Inductance
- ③ Capacitance
- ④ Source



Circuit Elements




- Voltage Source :-

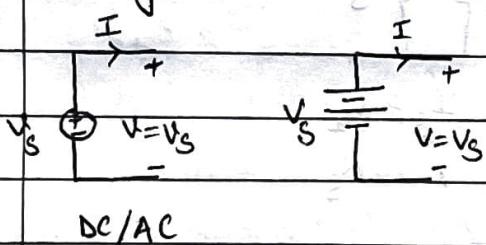

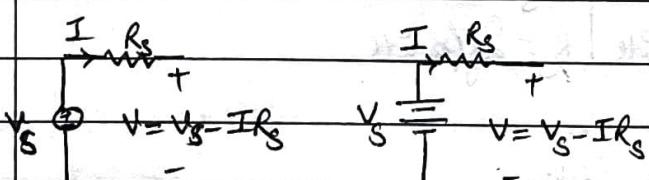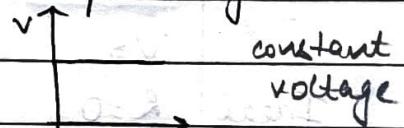Ideal VS \rightarrow it cont. to supply the same voltage irrespective of load.



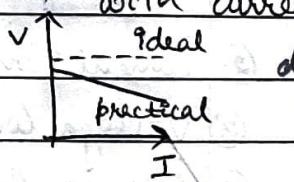
Practical VS \rightarrow it is not continuous and starts decreasing with current.



- ** In case of ideal voltage source $\Rightarrow R_s = 0$.

25/09/20

- Ideal Current Source :-

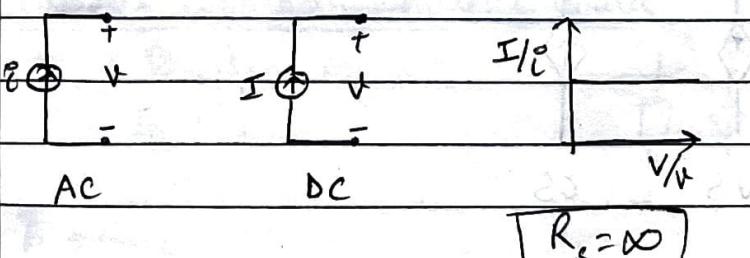


$[R_s \rightarrow$ internal resistance of current source]

Page No. _____

Date _____


• Practical Current Source :-

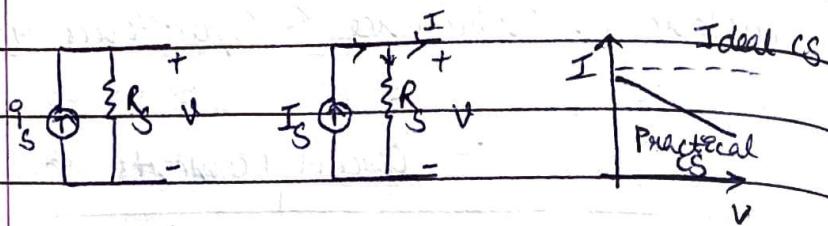

$$I = I_S - \frac{V}{R_S}$$

Current doesn't depend on voltage ideally but practically it decreases.

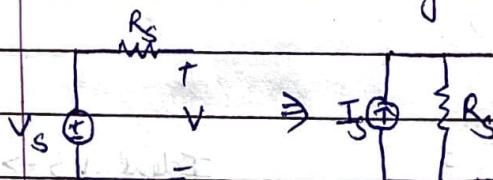• Current Source dual of Voltage Source :



$$V_S = R_S I_S$$

$$I_S = \frac{V_S}{R_S}$$

VS CS

Ideal $R_S = 0$ $R_S = \infty$

Practical $R_S = \text{Definite}$ $R_S = \text{Definite}$


• Dependent Source

① Voltage Controlled Voltage Source (Voltage supplied by VS is controlled by another voltage)

② Current Controlled Voltage Source

③ Voltage Controlled Current Source

④ Current Controlled Current Source

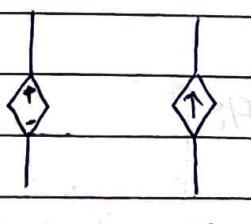

diamond-like shape
for dependent source

VS CS

① Voltage Controlled Voltage Source

$$V_{ab} = \alpha V_{xy}$$


$$\alpha = \frac{V_{ab}}{V_{xy}}$$

$$V_{xy}$$

$\alpha \rightarrow$ Voltage Ratio

e.g. Transformer

$$V_2 = \frac{N_2}{N_1} V_1$$

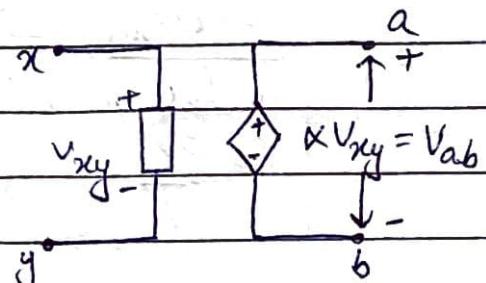

29/09/20


② Current Controlled Voltage Source

$$V_{ab} = r I_x$$

$$r = \frac{V_{ab}}{I_x}$$

$r \rightarrow$ Trans-resistance

e.g. Generator (AC & DC)

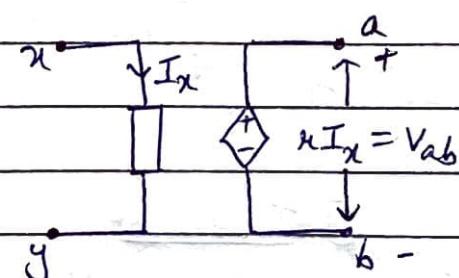


③ Voltage Controlled Current Source

$$I_a = g V_{xy}$$

$$g = \frac{I_a}{V_{xy}}$$

$g \rightarrow$ Trans-conductance

e.g. MOSFET

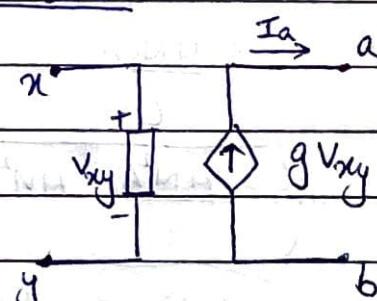


④ Current Controlled Current Source

$$I_a = \beta I_x$$

$$\beta = \frac{I_a}{I_x}$$

$\beta \rightarrow$ Current ratio

e.g. Transistor

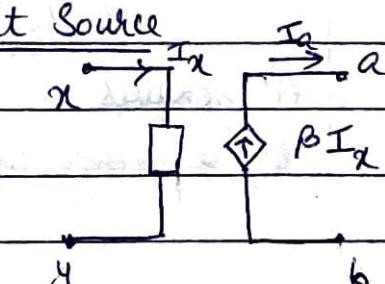

1/10/20

* Passive Circuit Elements

① Resistance (Ω)

It has the ability to obstruct the flow of current.

$$R = \frac{\rho l}{A}$$




Material resistivity (ρ)

Area (cross-sectional)

acc. to Ohm's Law $\Rightarrow V = IR$
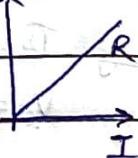
$$\rho = VI = I^2 R = \frac{V^2}{R} = G V^2$$



$G \rightarrow \pm$
(conductance) R

$$R_t = R_0 (1 + \alpha (T_t - T_0))$$

$\alpha \rightarrow +ve$ for conductor

$$W = \int_{-\infty}^t V(t) I(t) dt$$

-ve for insulator


semi-conductor

magnetic field intensity

② Inductors

$$Hl = Ni$$

$$L = \frac{A}{\rho} = \frac{N\phi}{I}$$

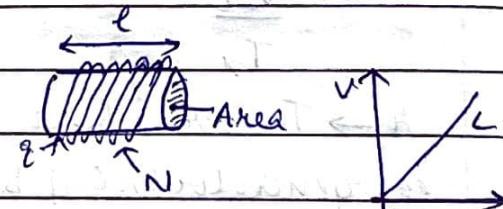

$$H = \frac{Ni}{l}$$

$$\phi = BA$$

$$= HBA$$

$$= \underline{H Ni A}$$

l

$$L = \frac{HN^2A}{l} = \underline{HN^2A}$$

$$V = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t V dt$$

$$W = \frac{1}{2} L i^2$$

$$= \frac{1}{L} \int_{t_0}^t V(t) + i(t_0)$$

It behaves as short-circuit in case of DC.
(store energy in the form of magnetic field)

③ Capacitance

$$C = \frac{A\epsilon}{d}$$

$$C = \frac{q}{V}$$

$$i = C \frac{dV}{dt}$$

$$dV = \int \frac{\epsilon dt}{C}$$

$$\Rightarrow V(t) = \frac{1}{C} \int_0^t \epsilon dt + \frac{1}{C} \int_0^t i dt$$

$$\Rightarrow V(t) = V(t_0) + \frac{1}{C} \int_{t_0}^t i dt$$

(if already charged)

It behaves as open-circuit in case of DC.

6/10/20

Kirchhoff's laws

① Kirchhoff's Current Law (KCL)

(at node or close boundary)
Algebraic sum of current on a junction is 0.


It is application of conservation of charge.

leaving \rightarrow outgoing \rightarrow +ve

entering \rightarrow incoming \rightarrow -ve

$$\sum_{n=1}^N i_n = 0$$

e.g.

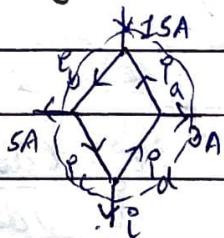

on a closed loop,

$$i_1 + i_2 + i_3 - i_4 = 0$$


$$i = \pm A$$

* Topology Terms (Circuit)

- (i) Branch - a simple circuit element representation.
- (ii) Node - interconnection of 2 or more circuit elements.
- (iii) Junction - interconnection of 3 or more circuit elements.
- (iv) Loop - closed path in circuit through which current passes.

(v) Mesh - independent loop (ℓ).

$$\ell = B - (n - 1)$$

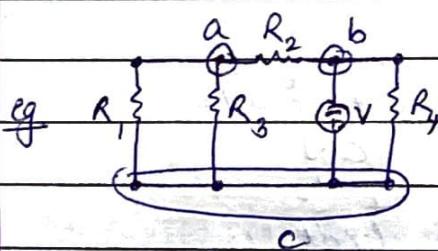


3 nodes (n)

3 junctions

6 branches

$$\ell = 6 - (3 - 1) = 3$$

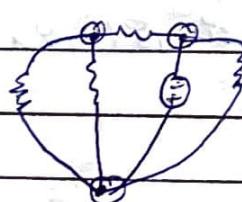

(loop)

Ques. Find v_2 .

$$e_1 = \pm e^{2t} \quad 2$$

$$v_3 = 2e^{-2t}$$

$$v_4 = 5e^{-2t}$$

$$v_2 = \frac{1}{L} \frac{dv_2}{dt}$$


$$-e_1 + e_2 - e_3 + 6e_4 - e_1 = 0$$

$$e_2 = -5e_1 + e_3 + e_4$$

$$\therefore e_2 = -4e^{-2t}$$

$$\text{So, } v_2 = \frac{1}{L} \times 2e^{-2t}$$

$$= 2e^{-2t}$$

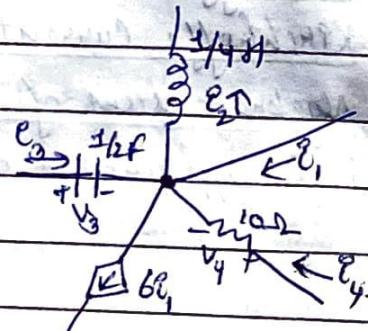

$$i_3 = \frac{CdV_3}{dt} = \pm \frac{2e^{-2t}}{2} C$$

$$= -2e^{-2t}$$

$$i_4 = \frac{V_4}{R_4} = 0.5e^{-2t}$$

10

(2) Kirchhoff's Voltage Law


It is based on conservation of energy, and applied in a closed path/loop. $\sum_{m=1}^M V_m = 0$

voltage rise $\rightarrow -ve$ $\ominus +$

voltage drop $\rightarrow +ve$ $+\ominus$


8/10/20

Series Equivalent of Resistance

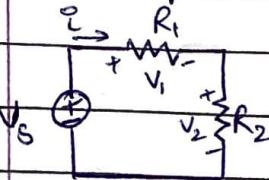
- 
 $V_1 = iR_1 ; V_2 = iR_2$
 $V_s = V_1 + V_2$
 $V_s = i(R_1 + R_2)$
 $i R_{eq} = V_s (R_1 + R_2)$
 $R_{eq} = R_1 + R_2$

- general, $i_k = \frac{V_s}{R_{eq}}$

Parallel Equivalent of Resistance

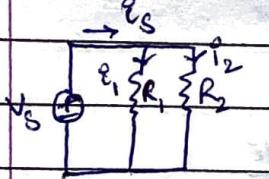- 
 $i_s = i_1 + i_2$
 $V_s = V_1 + V_2$
 $\frac{V_s}{R_{eq}} = \frac{V_s}{R_1} + \frac{V_s}{R_2}$
 $\frac{i_s}{R_{eq}} = \frac{i_1}{R_1} + \frac{i_2}{R_2}$


- general, $i_k = \frac{i_s \cdot R_{eq}}{R}$

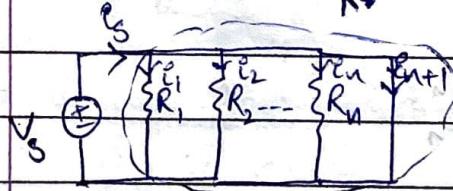- 
 $R_{eq} = 0 \rightarrow \text{Short circuit}$
 $i_{n+1} = i_s$
 $i_1 = i_2 = \dots = i_n = 0$

- Open circuit $\rightarrow R = \infty ; i = 0$


18x9 Ques.
278

find Req b/w a & b.

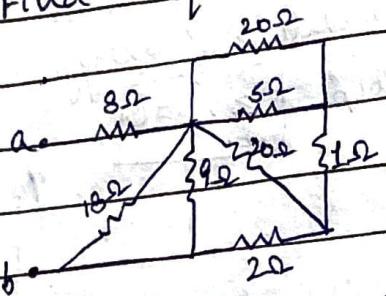

$$\begin{aligned}
 & \left[\left[(20||5) + 1 \right] || 20 \right] + 2 \left[\left[9 || 18 \right] \right] + 8 \\
 \Rightarrow & \left[\left[5 || 20 \right] + 2 \right] || 6 + 8 \\
 \Rightarrow & 3 + 8 \\
 = & 11 \Omega
 \end{aligned}$$

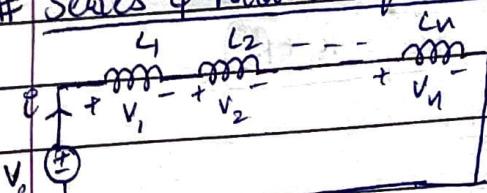Series & Parallel Equivalent of Inductance




$$V = \frac{L di}{dt}$$

$$V_s = V_1 + V_2 + \dots + V_n$$

$$V_s = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

$$L_{eq} \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt}$$

$$L_{eq} = \sum_{i=1}^n L_i$$

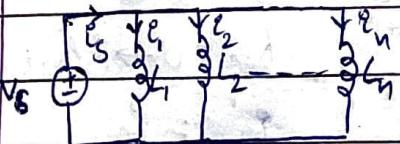


$$i_g = i_1 + i_2 + \dots + i_n$$

$$\frac{di_g}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} + \dots + \frac{di_n}{dt}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$


$$L_{eq} = L_1 + L_2 + \dots + L_n$$

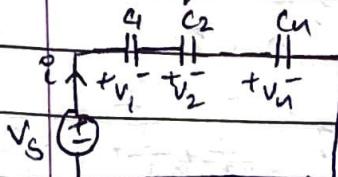Series & Parallel Equivalent of Capacitance

$$V_S = V_1 + V_2 + \dots + V_n$$

$$\frac{q}{C_{eq}} = \frac{q}{C_1} + \frac{q}{C_2} + \dots + \frac{q}{C_n}$$
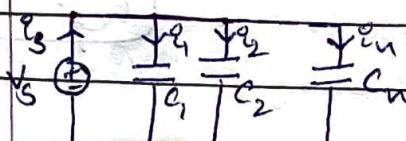
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$




$$Q_S = Q_1 + Q_2 + \dots + Q_n$$

$$C_{eq} \frac{dV_S}{dt} = C_1 \frac{dV_S}{dt} + C_2 \frac{dV_S}{dt} + \dots + C_n \frac{dV_S}{dt}$$

$$C_{eq} = \sum_{i=1}^n C_i$$


9/10/20

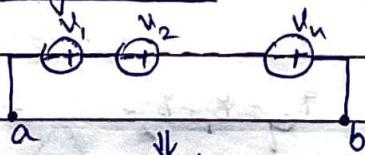Series - Parallel Connection of Source* Voltage Sources (Ideal)


$$V_{eq} = V_1 + V_2 + \dots + V_n$$

* * Restriction

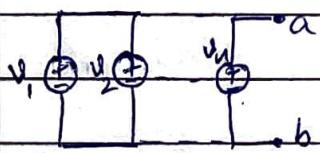all VS should have same voltage polarity & magnitude




$$V_{eq} = V_1 = V_2 = \dots = V_n$$

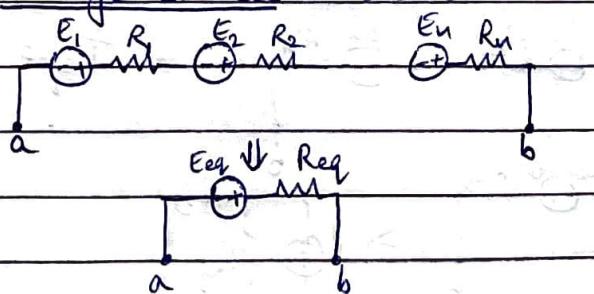
* Voltage Sources (Practical)

$$E_{eq} = E_1 + E_2 + \dots + E_n$$


$$R_{eq} = R_1 + R_2 + \dots + R_n$$

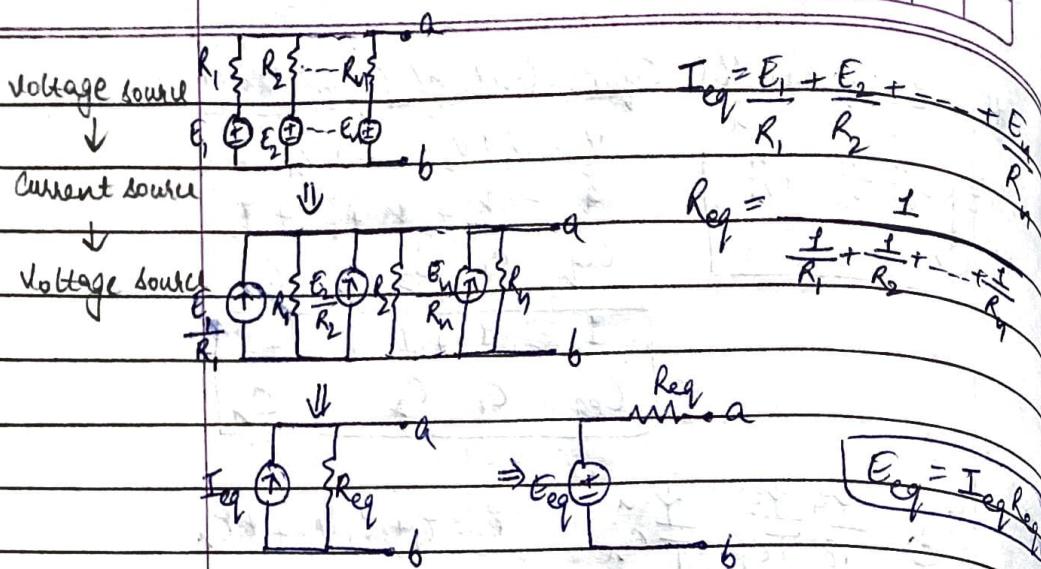


* Current Sources (Ideal)

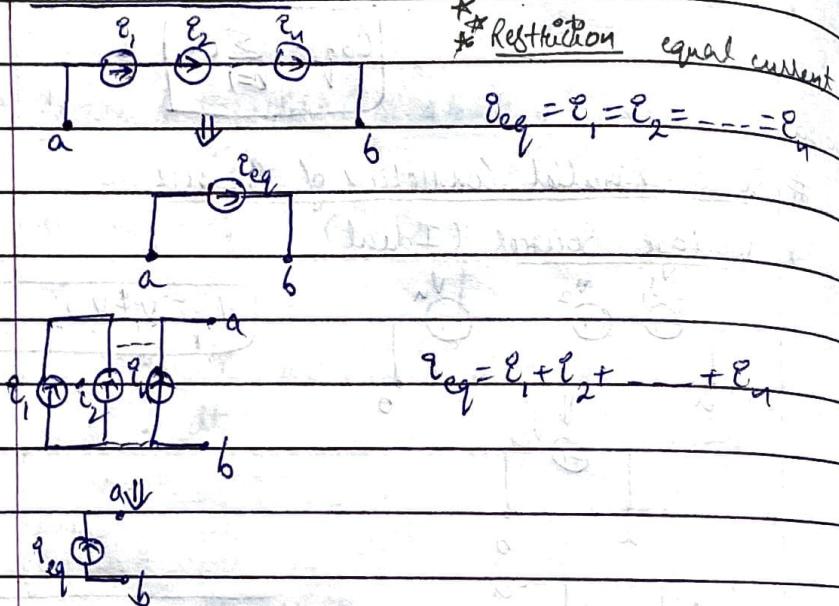

* Current Sources (Practical)

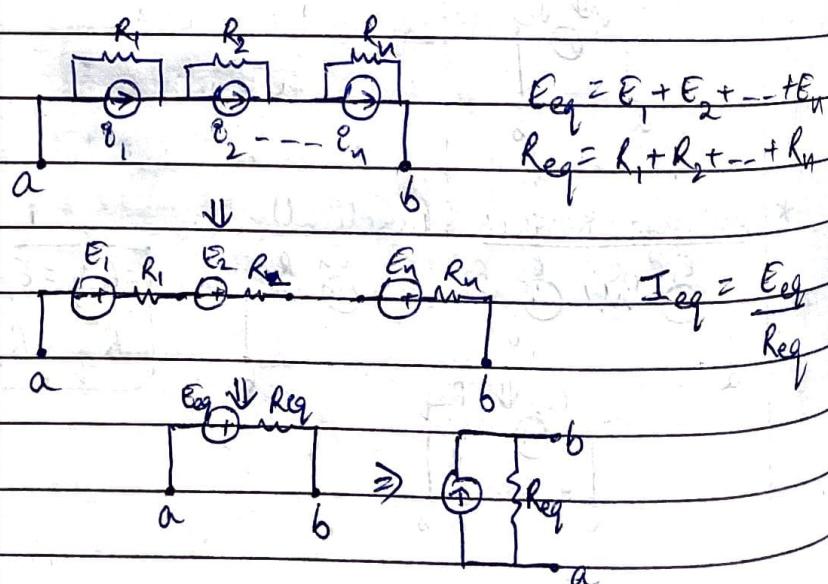

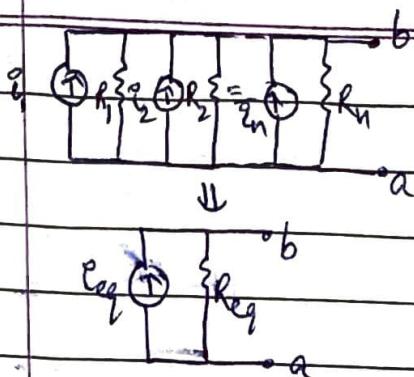

$$I_{eq} = I_1 + I_2 + \dots + I_n$$

$$R_{eq} = \frac{I}{I}$$




$$\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

13/10/20

Star-Delta Transformation

Star (Y)

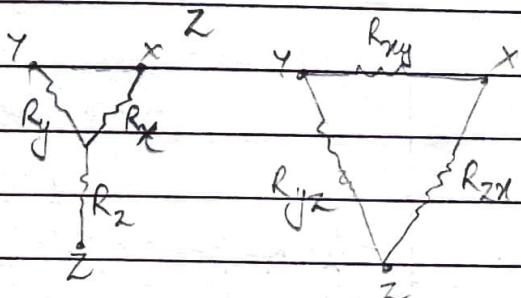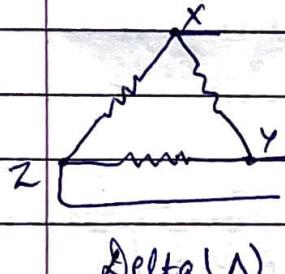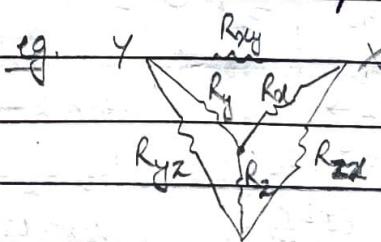Resistance between any pair of terminals is same in both arrangements.
(3rd terminal is open).



$$R_y + R_z = R_{yz} (R_{zx} + R_{xy}) \quad (1) \quad R_{xy}(\text{star}) = R_{xy}(\text{delta})$$

$$R_{xy} + R_{yz} + R_{zx} \quad R_{yz}(\text{star}) = R_{yz}(\text{delta})$$

$$R_x + R_z = R_{zx} (R_{xy} + R_{yz}) \quad (2) \quad R_{zx}(\text{star}) = R_{zx}(\text{delta})$$

$$R_{xy} + R_{yz} + R_{zx} \quad R_{xy}(\text{star}) = R_x + R_y$$

$$R_x = \frac{R_{xy} R_{zx}}{R_{xy} + R_{yz} + R_{zx}}$$

$$R_{xy}(\text{delta}) = R_{xy} \parallel (R_{yz} + R_{zx}) \\ = R_{xy} (R_{yz} + R_{zx}) / (R_{xy} + R_{yz} + R_{zx})$$

$$R_y = R_{xy} R_{yz}$$

$$R_{xy} + R_{yz} + R_{zx}$$

$$\therefore R_x + R_y = \frac{R_{xy} (R_{yz} + R_{zx})}{R_{xy} + R_{yz} + R_{zx}} \quad (3)$$

$$R_z = R_{zx} R_{yz}$$

$$R_{xy} + R_{yz} + R_{zx}$$

$$R_{xy} + R_{yz} + R_{zx}$$

Voltage Drop $\rightarrow +ve$
 Voltage Rise $\rightarrow -ve$

Page No.
 Date

$$R_{xy} = \frac{R_x R_y + R_y R_z + R_z R_x}{R_z}$$

$$R_{yz} = \frac{R_x R_y + R_y R_z + R_z R_x}{R_x}$$


$$R_{zx} = \frac{R_x R_y + R_y R_z + R_z R_x}{R_y}$$

15/10/20

KVL application

Mesh Analysis (mesh currents)

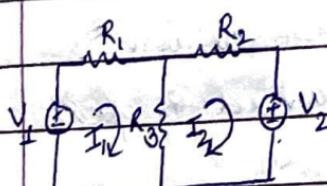Mesh is a loop that doesn't contain any other loop
 Inside Pt. (independent loop)



I_{R_2} I_1 I_2	Mesh 1 \rightarrow $I_{R_3} = I_1 - I_2$ $V_{R_3} = (I_1 - I_2)R_3$	Mesh 2 \rightarrow $I_{R_3} = I_2 - I_1$ $V_{R_3} = (I_2 - I_1)R_3$
-----------------------------	---	---

① Identify meshes

② Assign mesh currents (clockwise)

③ KVL equations for each mesh

Method for
only
independent
voltage
sources

$$\begin{aligned}
 & -V_A + R_1(I_1 - I_2) + R_3(I_1 - I_2) = 0 \\
 & \Rightarrow (R_1 + R_3)I_1 - R_3I_2 - R_3I_2 = V_A - ① \\
 & +V_B + R_3(I_2 - I_1) + R_2(I_2 - I_3) = 0 \\
 & \Rightarrow -R_3I_1 + (R_2 + R_3)I_2 - R_3I_3 = -V_B - ②
 \end{aligned}$$

$$\begin{bmatrix}
 R_1 + R_3 & -R_3 & -R_1 \\
 -R_3 & R_2 + R_3 & -R_2 \\
 -R_1 & -R_2 & R_1 + R_2 + R_3
 \end{bmatrix}
 \begin{bmatrix}
 I_1 \\
 I_2 \\
 I_3
 \end{bmatrix} = \begin{bmatrix}
 V_A \\
 -V_B \\
 0
 \end{bmatrix}$$

$$[R][I] = [V]$$

R_{ij}^{lo} \rightarrow mutual term; -ve of resistance b/w i^{th} & j^{th} mesh


R_{ii}^{lo} \rightarrow sum of resistances around i^{th} mesh

I_j \rightarrow j^{th} mesh current

v_j \rightarrow net voltage rise around the j^{th} mesh

16/10/20

Ques. ①

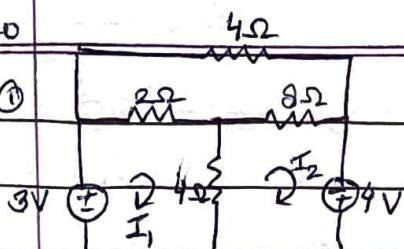

$$\left[\begin{array}{ccc|c} 2+4 & -4 & -2 & I_1 \\ -4 & 8+4 & -8 & I_2 \\ -2 & -8 & 2+8+4 & I_3 \end{array} \right] \quad \left[\begin{array}{c} 3 \\ 4 \\ 0 \end{array} \right]$$

$$I_1 = 2.678A, I_2 = 2.393A, I_3 = 1.75A$$

Ques. ② Find \varnothing_0 using mesh analysis.

$$\begin{aligned} -24 + 10(I_1 - I_3) + 12(I_1 - I_2) &= 0 \quad \textcircled{1} & \varnothing_0 \downarrow \begin{matrix} 10\Omega & 2\Omega & 24V \\ 2\Omega & 4\Omega & \\ \end{matrix} \\ 12(I_2 - I_1) + 4(I_2 - I_3) + 4\varnothing_0 &= 0 \quad \textcircled{2} & 24V \quad \begin{matrix} \varnothing_0 \\ I_1 \end{matrix} \quad \begin{matrix} I_2 \\ I_3 \end{matrix} \\ 24I_3 + 4(I_3 - I_2) + 10(I_3 - I_1) &= 0 \quad \textcircled{3} & \begin{matrix} 24\Omega \\ 4\Omega \end{matrix} \quad \begin{matrix} I_1 \\ I_2 \end{matrix} \quad \begin{matrix} \varnothing_0 \\ I_3 \end{matrix} \end{aligned}$$

$$\varnothing_0 = I_1 - I_3 \quad \textcircled{4}$$

$$I_1 = -3.2143A, I_2 = -9.642A, I_3 = -5A$$

$$\varnothing_0 = 1.7857A$$

* Circuit with Current Source

① → CS is in outer loop

② → CS is in branch b/w two meshes (Super mesh analysis)

$$\begin{aligned} \textcircled{1} \quad \left[\begin{array}{ccc|c} 2\Omega & I_3 & 2\Omega & \\ I_1 & 4\Omega & I_2 & \\ \hline I_1 & I_2 & & \end{array} \right] \quad -3 + 2(I_1 - I_3) + 4(I_1 - I_2) &= 0 \quad \textcircled{1} \\ 3V \quad \textcircled{2} \quad \left[\begin{array}{ccc|c} & I_3 & & \\ I_1 & 4\Omega & I_2 & \\ \hline I_1 & I_2 & & \end{array} \right] \quad 4I_3 + 8(I_3 - I_2) + 2(I_3 - I_1) &= 0 \quad \textcircled{2} \\ \textcircled{3} \quad \left[\begin{array}{ccc|c} & I_3 & & \\ I_1 & 4\Omega & I_2 & \\ \hline I_1 & I_2 & & \end{array} \right] \quad 4(I_2 - I_1) + 8(I_2 - I_3) &= 0 \quad \textcircled{3} \end{aligned}$$

$$\therefore I_2 = 4A$$

Solve using ①, ② and $I_2 = 4A$.

$$\Rightarrow -3 + 2I_1 - 2I_3 + 4I_2 - 6 = 0$$

$$\Rightarrow 4I_3 + 8I_3 - 32 + 2I_3 - 2I_1 = 0$$

$$\Rightarrow 19 = 6I_1 - 2I_3$$


$$\Rightarrow (32 = 14I_3 - 2I_1) \times 3$$

$$96 = -6I_1 + 42I_3$$

$$115 = 40I_3$$

$$I_1 = 4.125A$$

$$I_3 = 2.875A$$

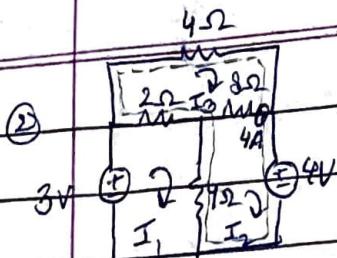

$$-3 + 2(I_1 - I_2) + 4(I_1 - I_2) = 0 \quad \text{---(1)}$$

Combine mesh 2 & mesh 3 to form
super mesh.


$$4I_2 + 4 + 4(I_2 - I_1) + 2(I_2 - I_1) = 0 \quad \text{---(2)}$$

$$\frac{I_2}{2} - I_3 = 4 \quad \text{---(3) (constraint)}$$

$$I_1 = 2.91A ; I_2 = 3.75A ; I_3 = -0.25A$$

20/10/20

Ques. ①

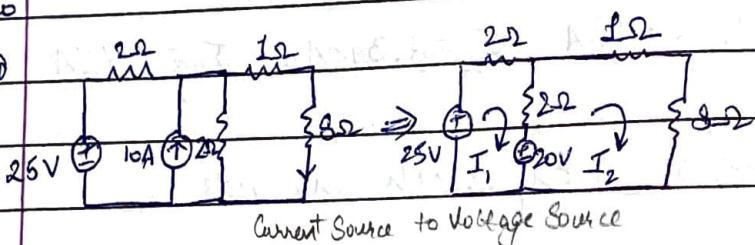

Current Source to Voltage Source

$$-25 + 2I_1 + 2(I_1 - I_2) + 20 = 0 \quad \text{---(1)}$$

$$I_2 + 8I_2 - 20 + 2(I_2 - I_1) = 0 \quad \text{---(2)}$$

$$4I_1 - 2I_2 = 5$$

$$(2I_1 + 11I_2 = 20) \times 2$$


$$-4I_1 + 22I_2 = 40$$

$$20I_2 = 45$$

$$I_2 = 2.25A$$

$$I_1 = 2.875A$$

Ques. ②

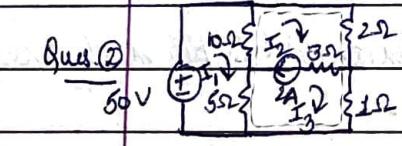

Determine the current

through 5Ω using mesh analysis.


$$\text{mesh 2} \quad \text{mesh 3} \quad \Rightarrow -50 + 10(I_1 - I_2) + 5(I_1 - I_2) = 0 \quad \text{---(1)}$$

$$(\text{super mesh}) \quad \Rightarrow 2I_2 + I_3 + 5(I_3 - I_1) + 10(I_2 - I_1) = 0 \quad \text{---(2)}$$

$$\Rightarrow I_2 - I_3 = 2 \quad \text{---(3)}$$

$$I_1 = 20A ; I_2 = 17.33A ; I_3 = 15.33A$$

$$I_{5\Omega} = I_1 - I_3 = 4.67A$$

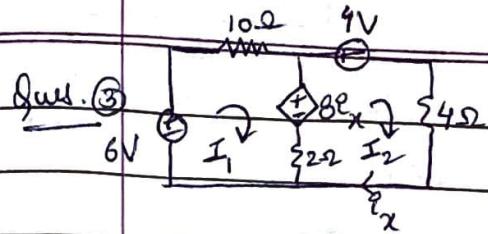

Determine I_x using mesh analysis

$$\Rightarrow -6 + 10I_1 + 8I_x + 2(I_1 - I_2) = 0 \quad \text{--- (1)}$$

$$\Rightarrow +4 + 4I_2 + 2(I_2 - I_1) - 8I_x = 0 \quad \text{--- (2)}$$

$$I_x = I_2$$

$$\Rightarrow -6 + 12I_1 + 6I_x = 0 \Rightarrow 2I_1 + I_x = 1$$

$$\Rightarrow +4 - 2I_1 - 2I_x = 0 \Rightarrow -2I_1 - 2I_x = 4$$

$$-I_x = -3$$

$$I_x = 3A$$

$$I_1 = -1A$$


Ques. ④ Find i_1, i_2, i_3 using mesh analysis.

$$i_1 = 15A$$

$$i_2 = 17A$$

$$i_3 = 11A$$

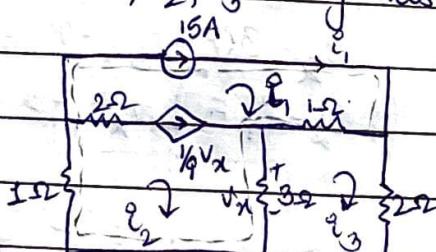we have a current source
∴ super.
mesh can
be applied
in
mesh ① &
mesh ②



Mesh ③ →

$$\Rightarrow +2i_3 + 3(i_3 - i_2) + (i_3 - i_1) = 0 \quad \text{--- (1)}$$

$$\Rightarrow 6i_3 - 3i_2 - i_1 = 0$$

$$\Rightarrow 6i_3 - 3i_2 = 15$$

$$i_2 - i_1 = \frac{1}{9}V_x \quad \text{--- (2)}$$

$$\Rightarrow 2i_3 - i_2 = 5$$

$$V_x = 3(i_2 - i_3) \quad \text{--- (3)}$$

$$\Rightarrow 3i_2 - 3i_3 = 9i_2 - 9i_3$$

$$\Rightarrow 9i_1 - 3i_3 = 6i_2$$

$$\Rightarrow 3i_1 = 2i_2 + i_3$$

$$\Rightarrow 45 = 2i_2 + i_3$$

$$45 = 2i_2 + i_3$$

$$10 = -i_2 + 4i_3$$

$$55 = 5i_3$$

$$i_3 = 11A$$

$$i_2 = 17A$$

* when we have a current source in the branch, we don't know the voltage across it. ∴ we use super mesh by combining individual meshes.


Page No. _____

Date _____

22/10/20

22

Ques. ⑥

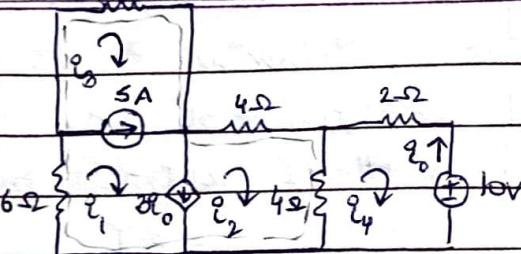

Mesh 4 →

$$2i_4 + 10 + 4(i_1 - i_2) = 0$$

$$\Rightarrow 6i_4 - 4i_2 = -10$$

$$\Rightarrow 3i_4 - 2i_2 = -5 \quad \text{--- (6)}$$

Mesh 1, 2, 3 →

$$2i_3 + 4i_2 + 4(i_2 - i_4) + 6i_1 = 0 \quad \text{--- (7)}$$


$$i_1 - i_3 = 5 \quad \text{--- (8)}$$

$$i_1 - i_2 = 3i_0 \quad \text{--- (9)}$$

$$i_0 = -i_4 \quad \text{--- (10)}$$

$$i_1 = -8.75A; i_2 = 13.75A; i_3 = 13.75A; i_4 = 7.5A$$

Ques. ⑦

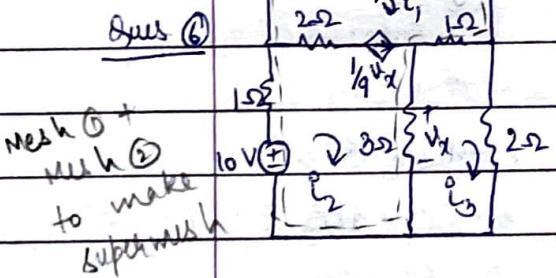

$$V_x = 3(i_2 - i_3) \quad \text{--- (1)}$$

$$i_2 - i_1 = \frac{1}{9} V_x \quad \text{--- (2)}$$

$$2i_3 + 3(i_3 - i_2) + i_3 - i_1 = 0 \quad \text{--- (3)}$$

$$5i_3 + 1(i_1 - i_3) + 3(i_2 - i_3) - 10 + i_2 = 0 \quad \text{--- (4)}$$

$$9i_2 - 9i_1 = 3i_2 - 3i_3$$

$$6i_3 - 3i_2 - i_1 = 0 \quad \text{--- (5)}$$

$$6i_2 = 9i_1 - 3i_3$$

$$6i_1 - 2i_2 + 2i_3 = 10 \quad \text{--- (6)}$$

$$2i_2 = 3i_1 - i_3 \quad \text{--- (7)}$$

$$6i_1 - 2i_2 + 2i_3 = 10$$

$$6i_1 - 2i_2 + 2i_3 = 10$$

$$-6i_1 - 18i_2 + 36i_3 = 0$$

$$6i_1 - 4i_2 - 2i_3 = 0$$

$$-20i_2 + 38i_3 = 0$$

$$2i_2 + 4i_3 = 10$$

$$20i_2 + 40i_3 = 100$$

$$i_1 = 1.32A \quad 78i_3 = 110$$

$$i_2 = 1.49A$$

$$i_3 = 1.4A$$

$$i_1 = 0.97A$$

$$i_2 = 2.2A$$


$$i_3 = 1.9A$$

23/10/20



Nodal Analysis

- focused approach
- KCL at diff. nodes
- * Steps in nodal analysis

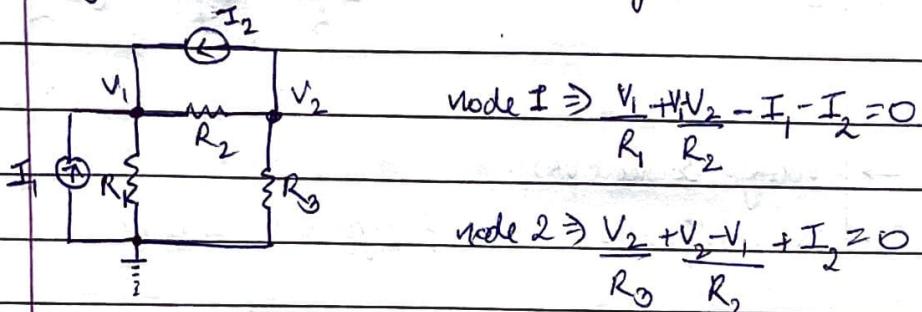
- ① Identify the nodes & select one as a reference.
- ② assign voltage to each node w.r.t. ref.
- ③ apply KCL at all nodes except ref. node.



→ Only CS (current source)

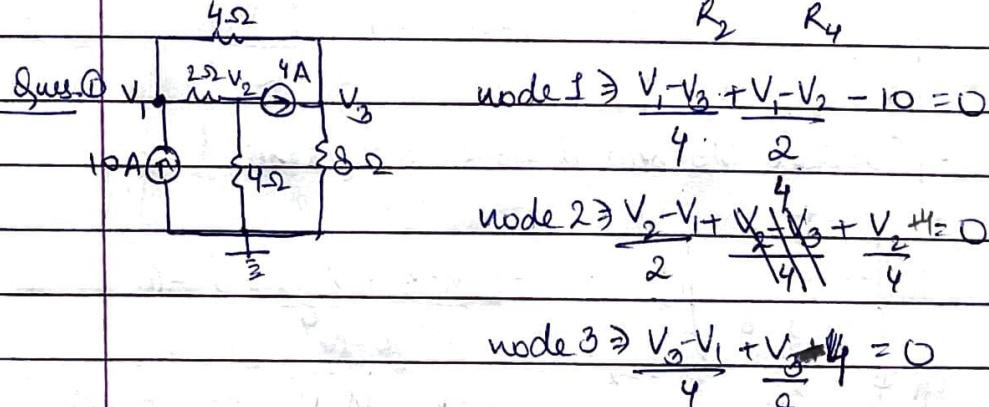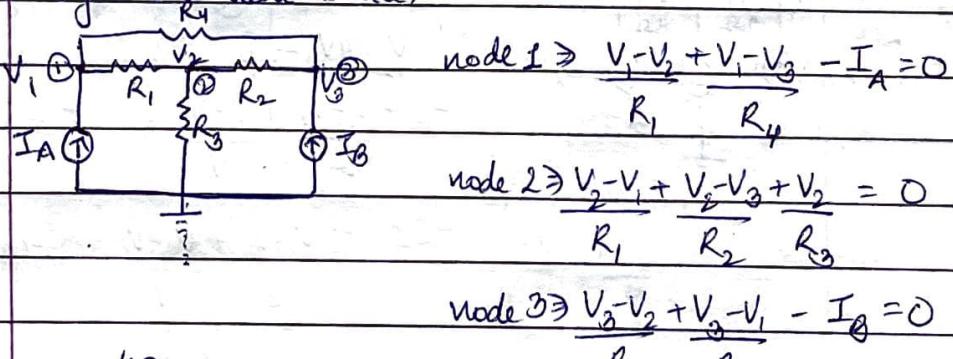
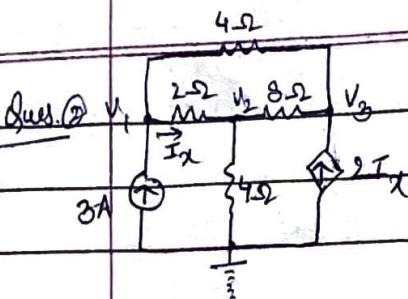
$$V_1 = 40V ; V_2 = 21.33V ; V_3 = 37.33V$$



$$E_x = \frac{V_1 - V_2}{2}$$

$$\text{node 1} \Rightarrow \frac{V_1 - V_3}{4} + \frac{V_1 - V_2}{2} - 3 = 0$$

$$V_1 = -168V$$

$$\text{node 2} \Rightarrow \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{8} + \frac{V_2}{4} = 0$$

$$V_2 = -132V$$

$$V_3 = -202V$$


$$\text{node 3} \Rightarrow \frac{V_3 - V_2}{8} + \frac{V_3 - V_1}{4} - 2 \left(\frac{V_1 - V_2}{2} \right) = 0$$

26/10/20

→ Voltage Source (VS)

- Ideal VS b/w a node & reference

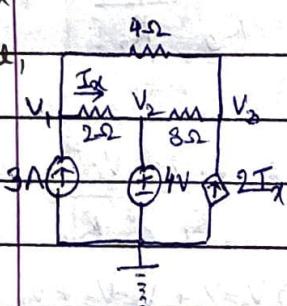node at which
 V_5 is there
with ref. node,
no need KCL
apply



$$V_2 - 0 = 4V$$

$$V_2 = 4V \quad \text{--- (1)}$$


$$-3 + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = 0 \quad \text{--- (2)}$$

$$-2I_x + \frac{V_3 - V_2}{8} + \frac{V_3 - V_1}{4} = 0 \quad \text{--- (3)}$$

$$\text{also, } I_x = \frac{V_1 - V_2}{2}$$

- Practical VS b/w a node & reference

KCL at all
the 3 nodes

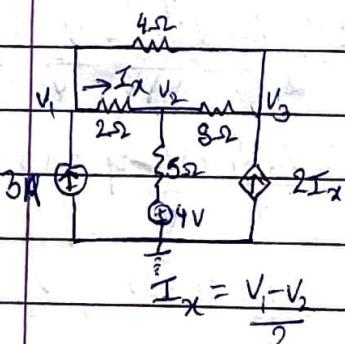


$$-3 + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = 0 \quad \text{--- (1)}$$

$$\frac{V_3 - V_2}{8} + \frac{V_3 - V_1}{4} - 2I_x = 0 \quad \text{--- (2)}$$

$$\frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{8} + \frac{V_2 - 4 - 0}{5} = 0 \quad \text{--- (3)}$$

- Practical VS b/w two reference nodes

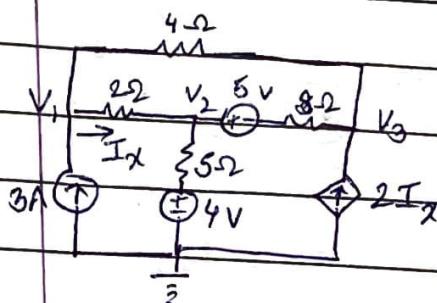


$$\frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} - 3 = 0 \quad \text{---(1)}$$

$$\frac{V_2 - V_1}{2} + \frac{V_2 - 4}{5} + \frac{V_2 - 5 - V_3}{8} = 0 \quad \text{---(2)}$$

$$\frac{V_3 - V_1}{4} - 2I_x + \frac{V_3 - V_2}{8} + 5 = 0 \quad \text{---(3)}$$

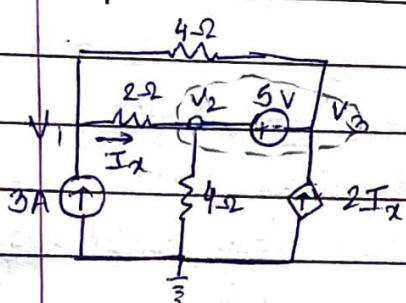- Ideal VS b/w two non-reference nodes.
(super node)



$$\frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} - 3 = 0 \quad \text{---(1)}$$

Combine node 2 & 3 to make super node and apply KCL at super node.


Constraint:

$$V_2 - V_3 = 5 \quad \text{---(3)}$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{4} + \frac{V_3 - V_1}{4} - 2I_x = 0 \quad \text{---(2)}$$

$$I_x = \frac{V_1 - V_2}{2}$$

Ques. ⑥

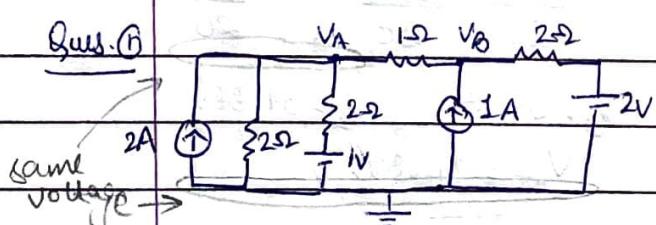

Find V_A & V_B using nodal analysis.

$$\frac{V_A - 1}{2} + \frac{V_A - V_B}{1} - 2 + \frac{V_A}{2} = 0 \quad \text{---(1)}$$


$$\frac{V_B - V_A}{1} - 1 + \frac{V_B - 2}{2} = 0 \quad \text{---(2)}$$

$$V_B = 3.25V$$

$$V_A = 2.875V$$

29/10/20

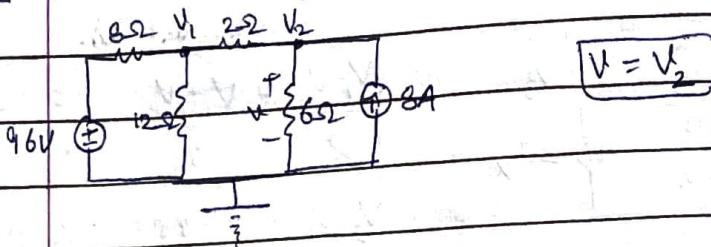Ques. ①) Determine voltage V in the network using nodal analysis.




$$\frac{V_1 - 96 - 0}{8} + \frac{V_1}{12} + \frac{V_1 - V_2}{2} = 0 \quad \text{---(1)}$$

$$\frac{V_2 - V_1}{2} - \frac{8 + V_2}{6} = 0 \quad \text{---(2)}$$

$$\frac{V_2 = V = 52.6 \text{ V}}{V_1 = 54 \text{ V}}$$

Ques. ②

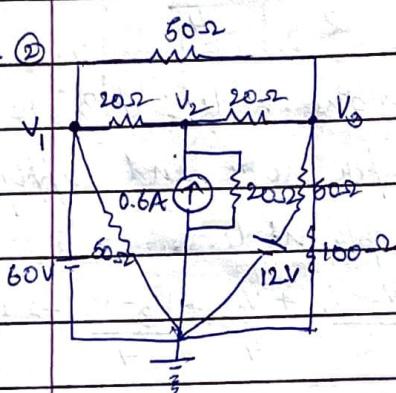

Find voltage across 100Ω resistor using nodal analysis.


$$\underline{V_1 = 60V}$$

$$\underline{\frac{V_3 - V_1}{60} + \frac{V_2 - V_1}{20} + \frac{V_3}{100} + \frac{V_3 - 12}{50} = 0.1}$$

$$\frac{V_2 - V_1}{20} + \frac{V_2 - V_3}{20} - 0.6 + \frac{V_2}{20} = 0 \quad \text{(2)}$$

$$V_1 = 31.68 \text{ V} \quad V_2 = 34.66 \text{ V}$$

$$V_{100} = 31.68 \text{ V}$$

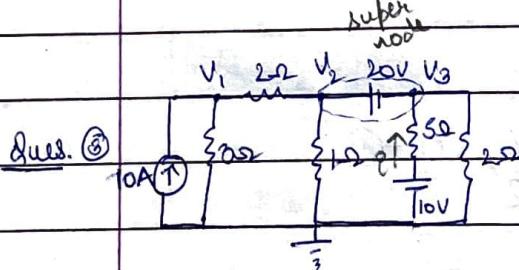

Find the current through
5Ω resistor using nodal analysis

$$\frac{-10 + \underline{V_1} + \underline{V_1 - V_2}}{3 - 2} = 0 - \textcircled{1}$$

$$\cancel{V_2 - V_1 + V_2 - 20 + V_3 + V_4 = 0}$$


$$\frac{V_2}{2} + \frac{V_3}{3} \neq 1$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_3 - 10}{5} + \frac{V_3}{2} = 0 \quad (2)$$

$$V_2 - V_3 = 20 - \textcircled{3}$$

$$V_1 = 18.04V \quad V_2 = 11.6V \quad V_3 = -8.4V$$

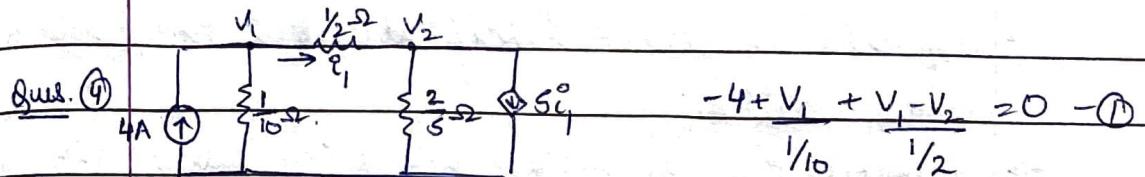
$$I_{6A} = \frac{V_3 - 10}{5} = \frac{-8.4 - 10}{5} = -3.68A \text{ (upward direction)}$$



$$\frac{V_2 - V_1}{1/2} + \frac{V_2}{5} = 0 \quad \text{---(2)}$$

$$I_1 = \frac{V_1 - V_2}{1/2}$$
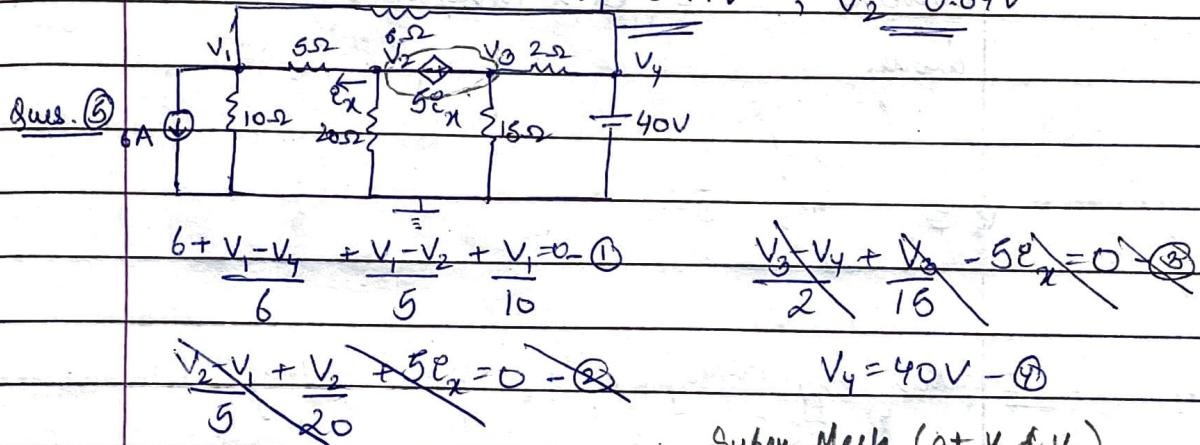
$$V_1 = 0.44V \quad ; \quad V_2 = 0.64V$$



Super Mesh (at V_2 & V_3)

$$V_3 - V_2 = 5e_x \quad \text{---(2)}$$

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} + \frac{V_3 - V_4}{2} + \frac{V_3}{15} = 0 \quad \text{---(3)}$$




$$e_x = \frac{V_2 - V_1}{5}$$

$$V_1 = 10V ; V_2 = 20V ; V_3 = 30V$$

30/10/20

Superposition Theorem

- applicable to linear circuits (directly proportional relationship, e.g. $V = IR$)
 - applicable to circuits having at least 2 independent sources
- It states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of voltages across (or currents through) that element due to each independent source acting alone.

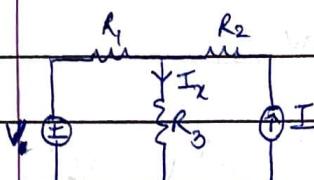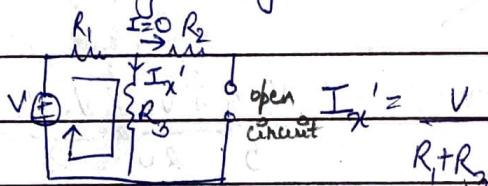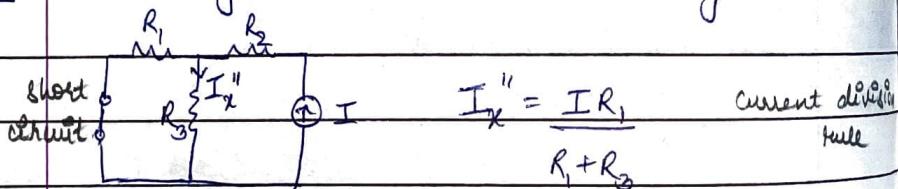
Case I When only voltage source V is actingCase II When only current source I is acting

$$I_x = I_x' + I_x''$$

1/10/20

 5Ω 10Ω


Ques. ①

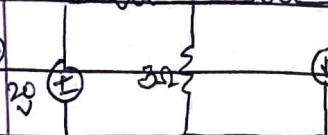

④ 5A


Find the current in 3Ω resistance using superposition theorem.

Case 1: only 20V is acting

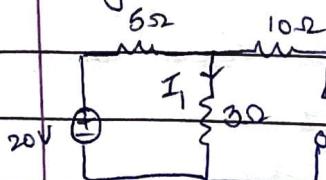

$$I_1 = \frac{20}{5+3} = \frac{20}{8} = 2.5 \text{ A}$$


Case 2: when only 5A is acting

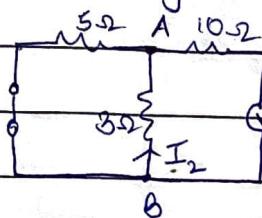


$$I_2 = \frac{5 \times 5}{5+3} = \frac{25}{8} = 3.125 \text{ A}$$

$$I_{\text{net}} = 3.125 - 2.5 = 0.625 \text{ A } (B \rightarrow A)$$

Ques. ② Find voltage across 2Ω resistor using superposition theorem.

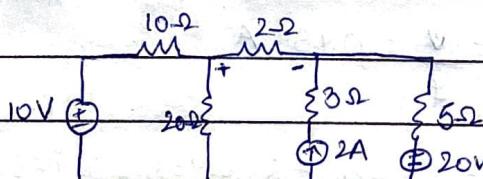

Case 1: only 10V is acting

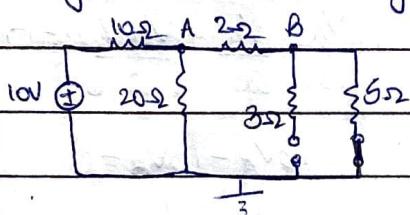

$$V_A = 10$$

$$V_B - 10 + V_B = 0$$

$$\frac{+V_B}{2} = 5$$

$$V_B = 50$$

$$\frac{V_A - 10}{10 \times 2} + \frac{V_A}{2} + \frac{V_A - V_B}{2 \times 10} = 0 \quad \text{--- (1)}$$

$$\Rightarrow 2V_A - 20 + V_A + 10V_A - 10V_B = 0 \quad I'_{2\Omega} = \frac{V_A - V_B}{2} = \frac{10 - 50}{2} = \frac{-40}{2} = -20$$

$$\Rightarrow 13V_A - 10V_B = 20$$

$$V_B = 50$$

$$I'_{2\Omega} = 1.43 \text{ A}$$

$$\frac{V_B - V_A}{2} + \frac{V_B}{5} = 0 \quad \text{---(2)}$$

$$\Rightarrow \frac{7V_B - 6V_A}{10} = 0$$

$$\Rightarrow 7V_B = 6V_A$$

$$\Rightarrow V_A = 1.4V_B$$

$$13 \times 1.4V_B - 10V_B = 20$$

$$(18.2 - 10)V_B = 20$$

$$V_B = 2.44A$$

$$V_A = 3.416A$$

$$I'_{22} =$$

Nodal
Analysis

$$\frac{V - 10}{10} + \frac{V}{20} + \frac{V}{\frac{7}{2}} = 0 \quad \text{---(1)}$$


$$0.293V = 1$$

$$V = 3.416V$$

$$I'_{AB} = \frac{V}{\frac{7}{2}} = 0.487A$$

$$V_{AB}' = 2 \times I'_{AB} = 2 \times 0.487 = 0.974V$$

Case 2: only 2A is acting

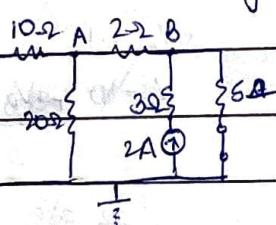

$$V_A + \frac{V_A}{2} + \frac{V_A - V_B}{6} = 0 \quad \text{---(1)}$$

$$10V_A - 10V_B = 0$$

$$\Rightarrow 1.8V_A = V_B$$

$$I'' = 0.432A$$

$$\text{current } \frac{V_B - V_A}{2} + \frac{V_B}{5} + \frac{V_B}{2} - 2 = 0 \quad \text{---(2)}$$


$$V'_{BA} = 2 \times I'' = 1.464V$$

$$\frac{V_B - V_A}{2} + \frac{V_B}{5} = 2$$

~~$$\Rightarrow 2V_B - 2V_A + 5V_B = 20$$~~

~~$$\Rightarrow 7V_B - 5V_A = 20$$~~

case 0: only 20V gs acting

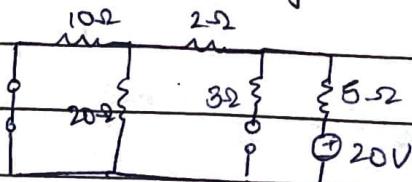

$$I_{20V} = \frac{20}{20+4} = \frac{20}{24} = \frac{20}{4} \times 3 = 1.463A$$


$$V_{BA}'' = 2 \times 1.463 \\ = 2.926V$$

$$V_{2\Omega} = -0.9 + 6 + 1.464 + 2.926 \\ = 3.414V \quad (B \rightarrow +ve; A \rightarrow -ve)$$

5/11/20

- Superposition Theorem in presence of Dependent Source
- Dependent sources are kept as it is.
- No. of cases = No. of independent sources


Ques. ⑥

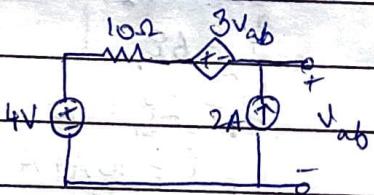

Find V_{AB} using superposition theorem.

Case 1: Only 4V source is acting

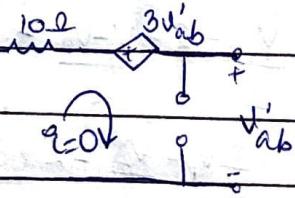because of
open circuit
 $I=0$
Voltage
also changes
across ab




KVL \Rightarrow

$$-4 + 10 \times I + 3V'_{AB} + V'_{AB} = 0$$

$$4V'_{AB} = 4$$

$$V'_{AB} = 1V$$

Case 2: Only 2A source is acting

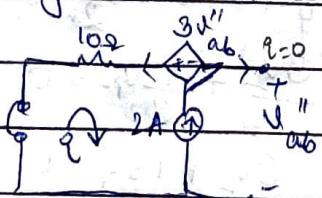

KCL \Rightarrow

$$\frac{V''_{AB}}{10} - (-3V''_{AB}) - 2 = 0$$

$$V''_{AB} = 5V$$

OR KVL \Rightarrow

$$10i + 3V_{ab}'' + V_{ab}''' = 0$$


$$i = -2A$$

$$V_{ab}''' = 5V$$

According to superposition theorem,

$$V_{ab} = V_{ab}' + V_{ab}''' = 6V$$


Ques ④

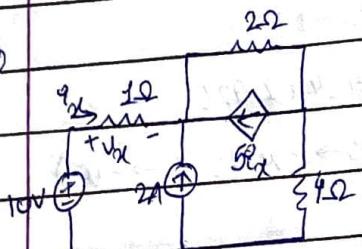

Find V_x using

superposition theorem

Case 1: only 10V is acting

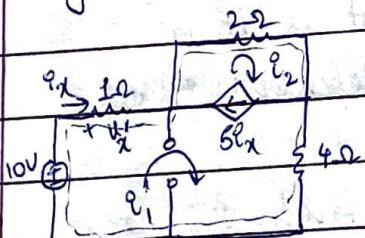

$$i_2 - i_1 = 5e_x \quad \text{---(1)}$$

$$-10 + i_1 + 2e_x + 4i_2 = 0 \quad \text{---(2)}$$

$$5e_x + 2i_2 = 10$$


$$e_x = 6e_x$$

$$5e_x + 12e_x = 10$$

$$e_x = 10/17 A$$

$$\therefore V_x' = \frac{10}{17} = 0.588V$$

Case 2:

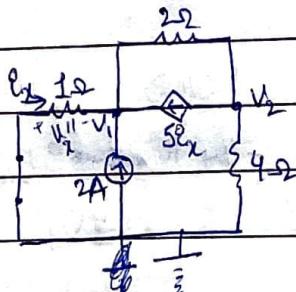

$$\frac{V_1}{1} - 2 + V - V_2 - 5e_x = 0 \quad \text{---(1)}$$

$$\frac{3V_1}{2} - \frac{V_2}{2} - 2 + 5V_1 = 0$$

$$\frac{V_2}{2} + 2 - \frac{15}{2} V_1 = 0$$

$$e_x = -V_1$$

$$\frac{V_2}{4} + 5e_x + \frac{V_2 - V_1}{2x2} = 0 \quad \text{---(2)}$$

$$\frac{3V_2}{4} + \frac{4}{2x2} V_1 = 0$$

$$3V_2 + 18V_1 = 0$$

$$V_2 = -6V_1$$

$$-\frac{3V_1}{10} + \frac{4}{10}V_1 + 2 = 0$$

$$2 = \frac{23}{10}V_1$$

$$V_1 = 20$$


$$V_x'' = -0.706A$$

$$\text{Net } V_x = 0.588 - 0.706$$

$$V_x = \underline{-0.118V}$$

Thevenin's Theorem

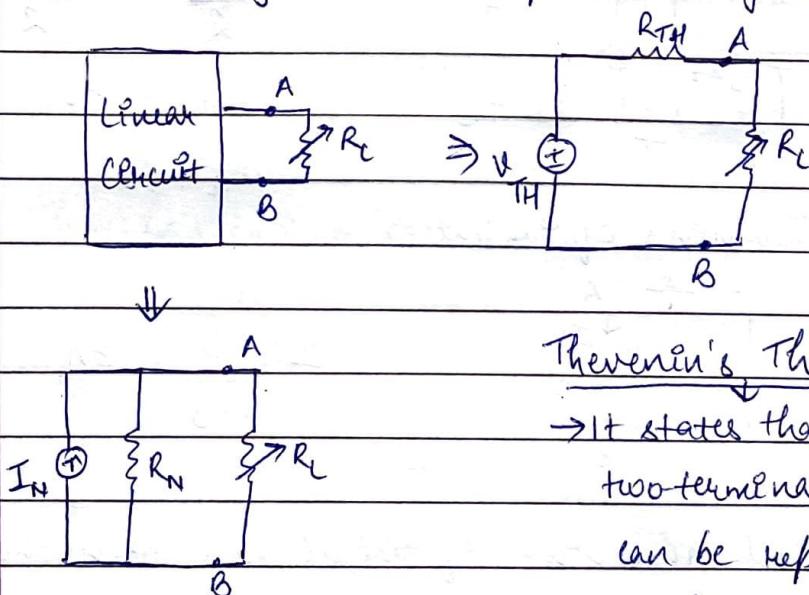- applicable when R_L is variable.
- calculate R_L for maximum power transfer to load.



Thevenin's Theorem

→ It states that a linear two-terminal linear circuit can be represented by an equivalent circuit

Norton's Theorem ($R_N = R_{TH}$)

consisting of voltage source (V_{TH}) and a resistor (R_{TH}) in series.


V_{TH} : open circuit terminal voltage

R_{TH} : equivalent resistance looking into the terminals while load is disconnected & independent sources are inactive.


$VS \rightarrow$ short circuit ; $CS \rightarrow$ open circuit

6/11/20

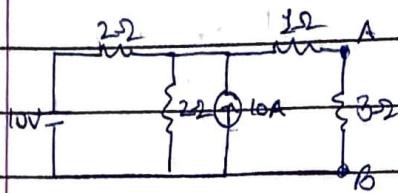Ques.① find the current through 3Ω resistor using Thévenin's Theorem




for $R_{TH} \Rightarrow$

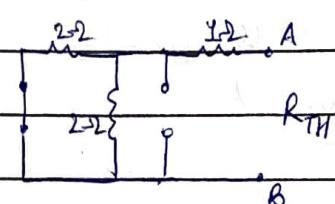

$$R_{TH} = (2+2) + 1 = 5\Omega$$

$$R_{TH} = 2\Omega$$


for $V_{TH} \Rightarrow$

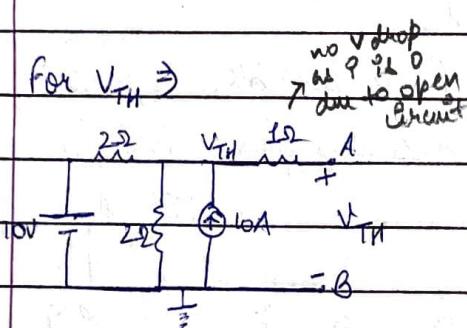

$$\frac{V_{TH}}{2} - 10 + \frac{V_{TH} - 10}{2} = 0$$


$$V_{TH} = 15V$$

Thévenin's Equivalent \Rightarrow

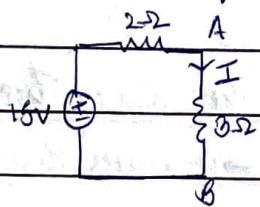


$$I = \frac{15}{2+3} = 3A$$

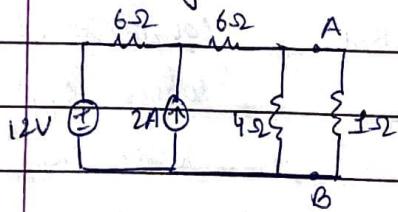Ques.② find Thévenin's Equivalent and then the current I through 1Ω .




For $R_{TH} \Rightarrow$

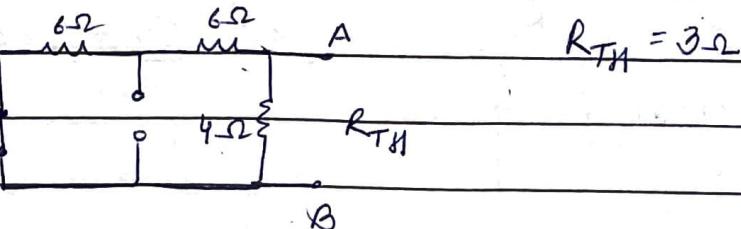

$$R_{TH} = 3\Omega$$

For $V_{TH} \Rightarrow$

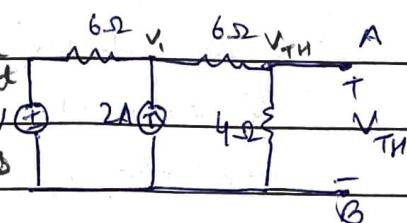V_{TH} is
not a node
because current
through 6Ω
& 4\Omega resistors
is same



$$\frac{V_1 - 12}{6} + \frac{V_1 - V_{TH}}{6} - 2 = 0 \quad \textcircled{1}$$

$$2V_1 - V_{TH} = 24$$

$$\frac{V_{TH} - V_1}{6} + \frac{V_{TH}}{4} = 0 \quad \textcircled{2}$$

$$\frac{-2 + V_1 - 12}{6} + \frac{V_1}{6+4} = 0 \quad \text{OR}$$

$$10V_{TH} - 4V_1 = 0$$

$$V_1 = 15V$$


$$V_1 = \frac{5}{2}V_{TH}$$

$$V_{TH} = 4 \times \frac{15}{10} = 6V$$

~~$$\frac{2 \times 5}{2}V_{TH} - V_{TH} = 24$$~~


$$V_{TH} = 6V$$


Thevenin's Equivalent \Rightarrow

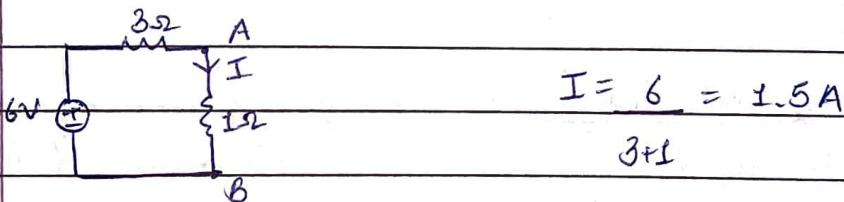


$$I = \frac{6}{3+1} = 1.5A$$

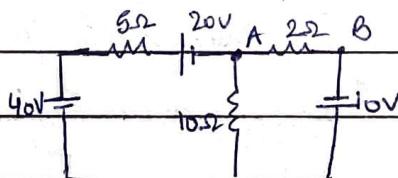Ques.② Calculate the current through 2Ω resistor using Thevenin's Theorem.



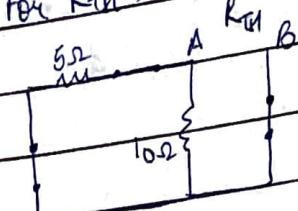For $R_{TH} \Rightarrow$ 

$$R_{TH} = \frac{50}{15} = 3.33\Omega$$

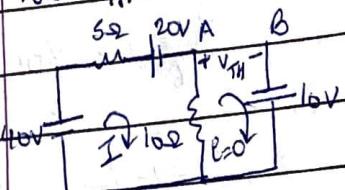For $V_{TH} \Rightarrow$ 

$$V_{TH} - 10 - 10I = 0 \quad \text{---(1)}$$


$$V_{TH} = 10 + 10I$$

$$-40 + 5I + 20 + 10I = 0 \quad \text{---(2)}$$

$$15I = 20$$

$$I = \frac{4}{3}$$

$$V_{TH} = 10 + \frac{40}{3} = \frac{70}{3} = 23.33V$$

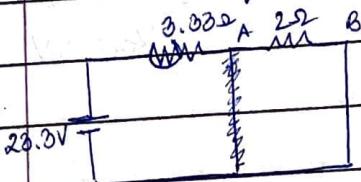Thevenin's Equivalent \Rightarrow 

$$I = \frac{23.33}{2+2} = 4.33A$$

$$2+2.33$$



10/11/20 # Norton's Theorem

It states that a linear two-terminal circuit can be represented by an equivalent circuit consisting of a current source (I_N) and a resistor (R_N) in parallel.

$I_N \rightarrow$ short circuit current through the terminals.


$R_N \rightarrow$ same as R_{TH} .

Steps

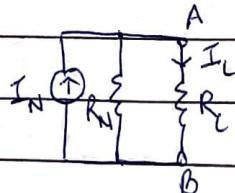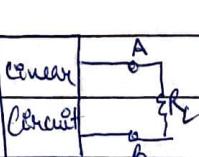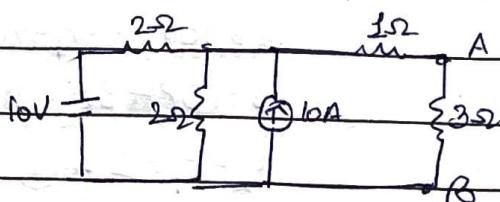(1) Calculate I_N or I_s (2) Calculate R_N or R_{TH} 


$$I_L = \frac{I_N \times R_N}{R_N + R_L}$$

Ques. ① Find the current through 3Ω resistor using Norton's Theorem.



$$R_N = R_{TH} = 2\Omega$$

for I_{SC} \Rightarrow

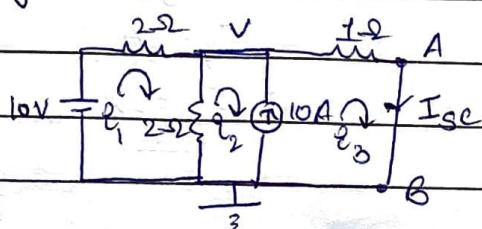

$$-10 + 2e_1 + 2(e_1 - e_2) = 0 \quad \text{--- (1)}$$

$$4e_1 - 2e_2 = 10$$

$$2e_1 - e_2 = 5$$

$$e_3 - e_2 = 10 \quad \text{--- (2)}$$

$$e_2 = e_1 \quad \text{--- (3)}$$


$$e_1 = e_2 = 5A$$

$$e_3 = 15$$


$$I_{SC} = \frac{4.5}{1} = 4.5A$$

$$\therefore I_L = \frac{4.5 \times 2}{2+3} = 3A$$

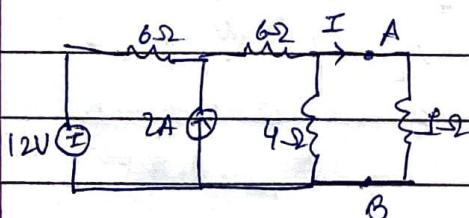Ques. ② Find the current through 1Ω resistor using Norton's Theorem.



$$R_N = R_{TH} = 3\Omega$$

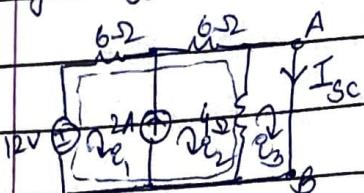for I_{SC} \Rightarrow 

$$-12 + 6\varnothing_1 + 6\varnothing_2 + 4(\varnothing_2 - \varnothing_3) = 0 - 0$$


$$12 = 10\varnothing_2 + 6\varnothing_1 - 4\varnothing_3$$

$$6 = 3\varnothing_1 + 5\varnothing_2 - 2\varnothing_3$$

$$\varnothing_2 - \varnothing_1 = 2 - \textcircled{2}$$

$$4(\varnothing_3 - \varnothing_2) = 0 - \textcircled{3}$$

$$\varnothing_3 = \varnothing_2$$

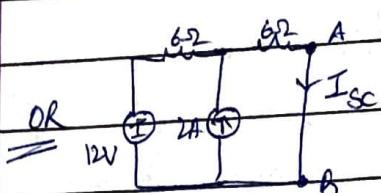

$$4 \times 0 = 0$$

$$4+0$$

\therefore short circuit in parallel with another resistance

$$6 = 3(\varnothing_3 - 2) + 5\varnothing_2 - 2\varnothing_1$$

$$6 = 6\varnothing_2 - 6$$

$$\varnothing_3 = 2A$$

$$\therefore I_{SC} = 2A$$

$$\frac{V-12}{6} + \frac{V}{6} - 2 = 0$$

$$V = 12V$$


$$I_{SC} = \frac{V}{6} = 2A$$

$$\therefore I_L = \frac{2 \times 3}{3+1} = 1.5A$$


→ Dependent Sources in Norton's Theorem

$$R_{TH} = R_N = \frac{V_{oc}}{I_{sc}}$$

Ques. ② Obtain Thevenin's & Norton's Equivalent of the circuit.

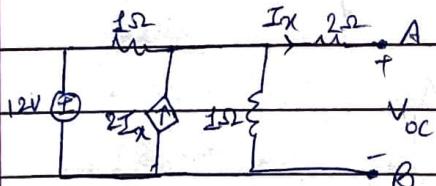for $V_{oc} \Rightarrow$

$$I_x = 0$$

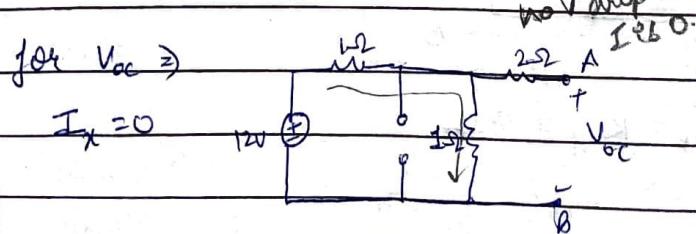


$$V_{oc} = \frac{12}{2} \times 6V$$

series

$$I+1=2.5V$$

for $I_{SC} \Rightarrow$

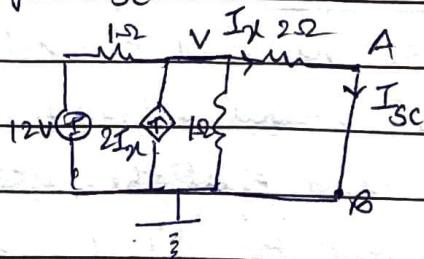


$$I_{SC} = I_x = \frac{V}{2}$$

$$\frac{V-12}{1} - 2I_x + \frac{V}{1} + \frac{V}{2} = 0$$

$$V = 8V$$

$$I_x = 4A = I_{SC}$$

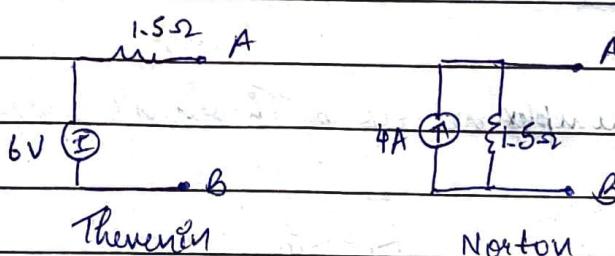
$$R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{6}{4} = 1.5\Omega$$




Thvenin

Norton

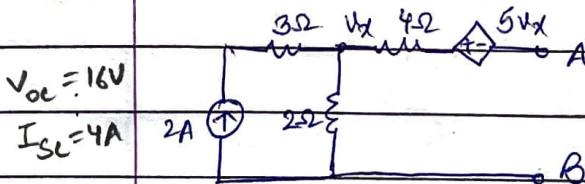Ques. ④ Draw Thvenin's & Norton's Equivalent.



for $V_{OC} \Rightarrow$

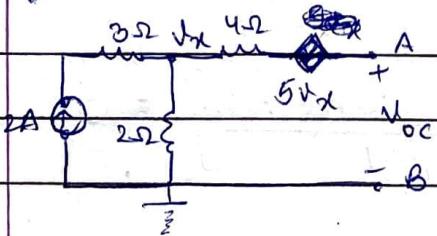


$$\frac{V_x}{2} - 2 + \frac{V_x}{4} = 0$$

$$\frac{3V_x}{4} = 2$$


12/11/20

Maximum Power Transfer Theorem

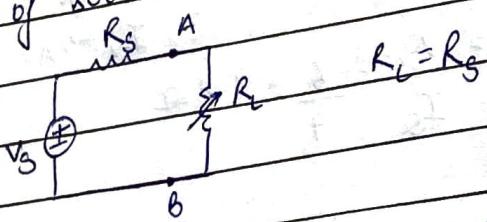It states that to obtain maximum external power from a source with finite internal resistance, the resistance of the load must equal the resistance of source as viewed from its output terminals.



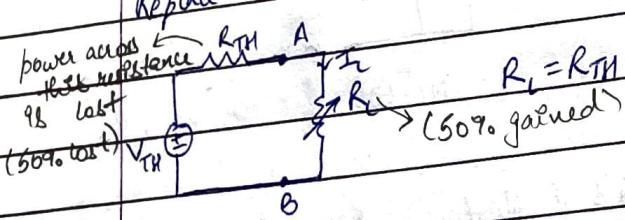Replace the complex network by Thevenin's Equivalent.



$$\text{Proof: } P = I^2 R = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L$$

$$\frac{dP}{dR_L} = 0$$

$$\frac{dR_L}{dR_L}$$

$$\Rightarrow V_{TH}^2 \frac{d}{dR_L} \left(\frac{R_L}{(R_{TH} + R_L)^2} \right)$$

$$\Rightarrow V_{TH}^2 \left[\frac{(R_{TH} + R_L)^2 - R_L \cdot 2(R_{TH} + R_L) \cdot 1}{(R_{TH} + R_L)^4} \right] = 0$$

$$\Rightarrow R_{TH} + R_L = 2R_L$$

$$\Rightarrow R_{TH} = R_L$$

$$\frac{d^2P}{dR_L^2} < 0$$

$$\frac{dR_L^2}{dR_L}$$

$$\frac{d^2P}{dR_L^2} = -\frac{V_{TH}^2}{(R_{TH} + R_L)^3}$$

$$P_{max} = I_c^2 R_{TH}$$

$$= \frac{V_{TH}^2}{(R_{TH} + R_{TH})^2} R_{TH}$$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}}$$


$$\eta = \frac{\text{Output}}{\text{Input}} = \frac{P_{max}}{P_{max} + P_{loss}}$$

$$P_{loss} = I_c^2 \cdot R_{TH}$$


$$= \frac{V^2_{TH}}{4R_{TH}}$$

$$\therefore \eta = 0.5 \text{ or } 50\%.$$

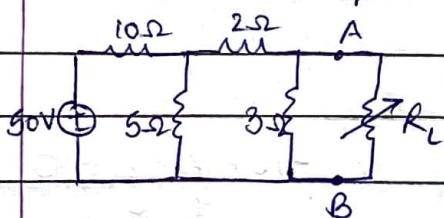Ques. ① Find the max. power that can be transferred to R_L .




for R_{TH}

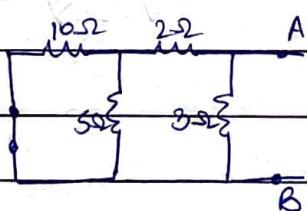

$$R_{TH} = 1.92\Omega$$

for V_{TH}

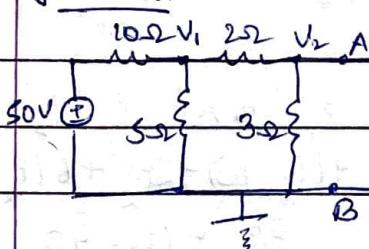

$$\frac{V_1 - 50}{10} + \frac{V_2 - 5}{5\Omega} + \frac{V_1 - V_2}{3\Omega} = 0 \quad \text{--- (1)}$$

$$\frac{8V_1 - 5V_2}{10} = 5$$

$$\frac{8V_1 - 5V_2}{10} = 50$$

$$\frac{V_2 - V_1}{2\Omega} + \frac{V_2}{3\Omega} = 0$$

$$\frac{5V_2}{6} - \frac{3V_1}{6} = 0$$

$$5V_2 = 3V_1$$


$$V_1 = 10V$$

$$V_2 = 6V$$

$$\therefore V_{TH} = V_2 = 6V$$


Thévenin's Equivalent \Rightarrow

$$R_{TH} = 1.92 \Omega$$

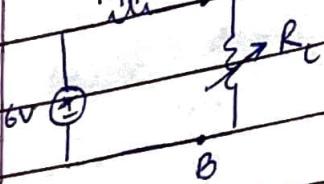


$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{6^2}{4 \times 1.92} = 4.6875 \text{ W}$$

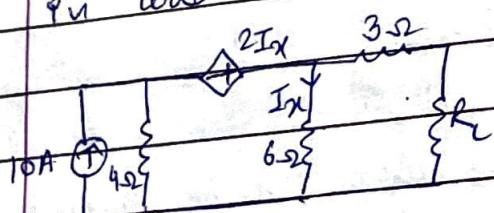Ques. ② calculate the max. power that may be dissipated in load resistance R_L .



for $V_{oc} \Rightarrow$

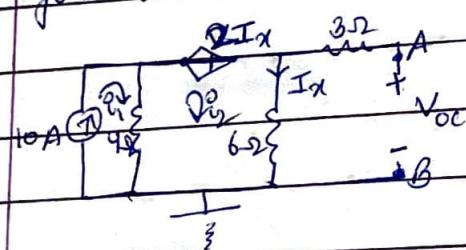

$$-10 + \frac{V}{4} + \frac{V}{6} = 0$$

$$\begin{aligned} 10 &= \frac{10V}{24} \\ V &= 24V \end{aligned}$$

$$\varrho_1 = 10A, I_x = \varrho_2$$


$$4(\varrho_2 - \varrho_1) - 2I_x + 6I_x = 0$$

$$8I_x = 4 \times 10$$

$$I_x = 5A$$

$$\therefore V_{oc} = 6 \times 5 = 30V$$

for $I_{sc} \Rightarrow$

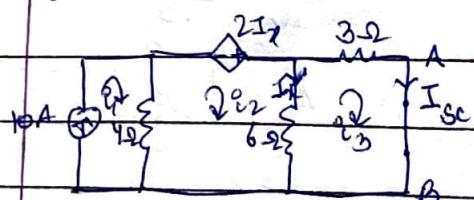

$$\varrho_1 = 10A, I_x = \varrho_2$$

$$4(\varrho_2 - 10) - 2(\varrho_2) + 6(\varrho_2 - \varrho_3) = 0$$


$$8\varrho_2 - 6\varrho_3 = 40$$

$$3\varrho_3 + 6(\varrho_3 - \varrho_2) = 0 - 40$$

$$9\varrho_3 = 6\varrho_2$$

$$\frac{3}{2}\varrho_3 = \varrho_2$$

CS dual of VS \rightarrow

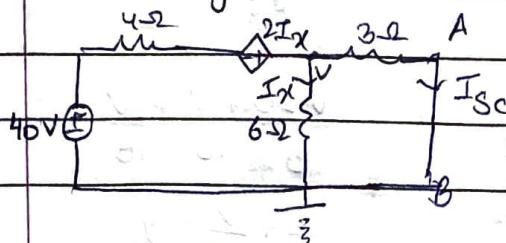

$$V - 2I_x \cdot 4\Omega + V + \frac{V \cdot 2}{3\Omega} = 0$$

$$I_x = \frac{V}{6}$$

$$\frac{V}{4} - \frac{V}{12} + \frac{V}{2} = 10$$

$$V = 15V$$

$$\therefore I_{sc} = \frac{V}{R} = \frac{V}{6} = 5A$$


$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{30}{5} = 6\Omega$$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(30)^2}{4 \times 6} = \underline{\underline{37.5W}}$$

17/11/20


Reciprocity Theorem

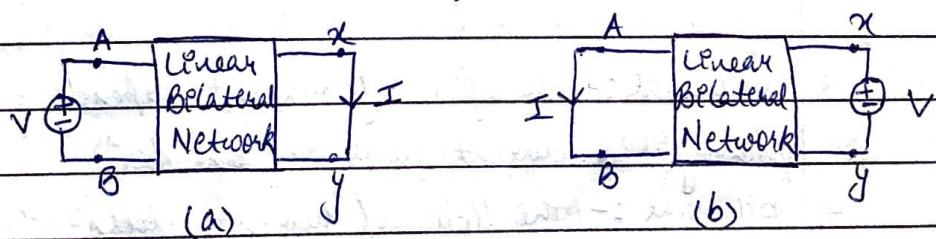It states that in a linear bilateral, active single source network, the ratio of excitation and response remains same when excitation and response positions are interchanged.




Trans-resistance $\rightarrow \frac{V}{I} = \frac{V}{I} \rightarrow$ Network is reciprocal

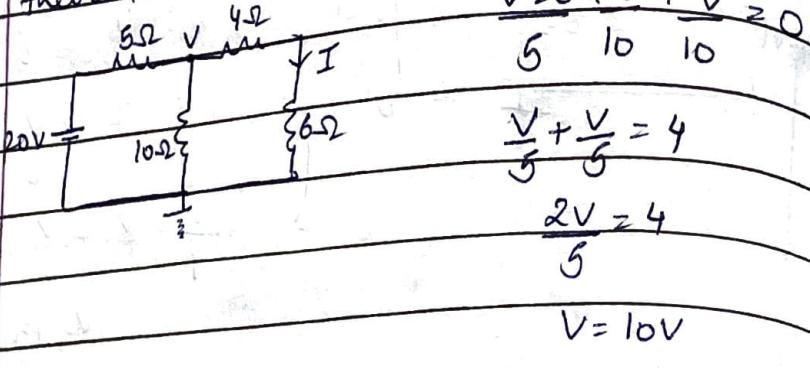Ques.① calculate current I and verify reciprocity
theorem.




$$\therefore I = \frac{V}{10} = 1A$$

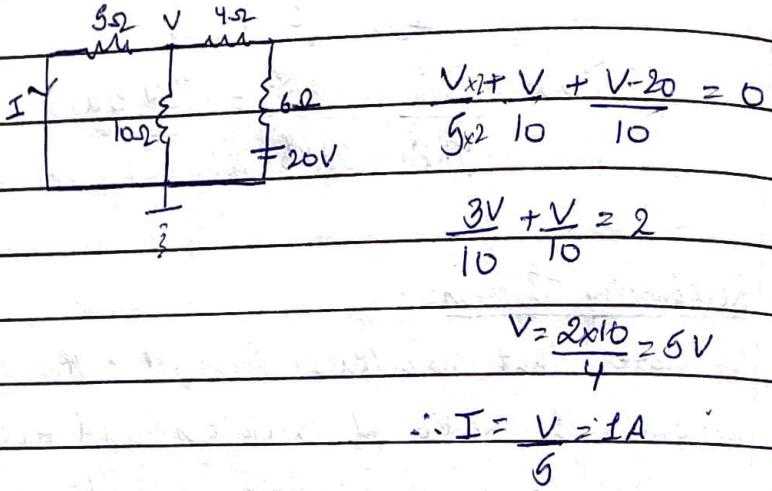

So, this network is reciprocal.

- * Unilateral :- the flow of current depends on the polarity (i.e. current flows in one direction).
- * Bilateral :- the flow of current doesn't depend on the terminal (i.e. current can flow in both directions).

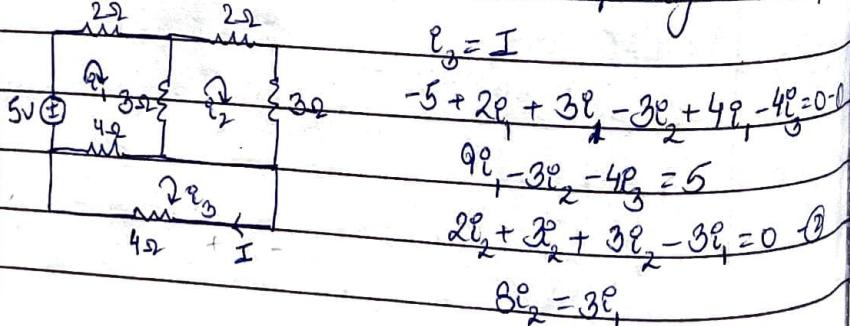Ques.② find current I and validate the reciprocity theorem



$$4e_2 + 4e_3 - 4e_1 = 0 \quad \textcircled{3}$$

$$8e_1 = 4e_1$$


$$2e_1 = e_1$$

$$e_2 = \frac{3e_1}{8} = \frac{3 \times 2e_3}{84} = \frac{3e_3}{4}$$

$$9 \times 2e_3 - 3 \times \frac{3e_3}{4} - 4e_3 = 5$$

$$\frac{14e_3}{4} - \frac{9e_3}{4} = 5$$

$$e_3 = 0.4255A = I$$

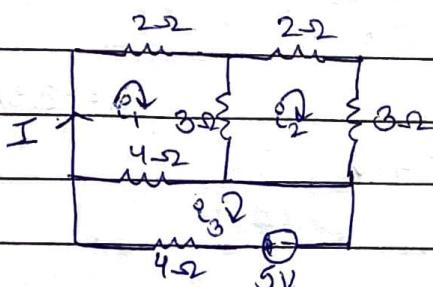

$$I = e_1$$

$$2e_1 + 3e_2 - 3e_3 + 4e_1 - 4e_3 = 0 \quad \textcircled{1}$$

$$9e_1 - 3e_2 - 4e_3 = 0$$

$$5e_2 + 3e_3 - 3e_1 = 0 \quad \textcircled{2}$$

$$3e_2 = 3e_1$$

$$5 + 4e_3 = 0$$

$$9e_1 - \frac{9}{8}e_1 + 5 = 0$$

$$e_3 = -1.25A$$


$$e_1 = 0.4255A = I$$

$$e_2 = \frac{3}{8}e_1$$

\therefore this network is reciprocal

Ques ③ find voltage V and verify reciprocity theorem.

$$e_1 = 10A$$

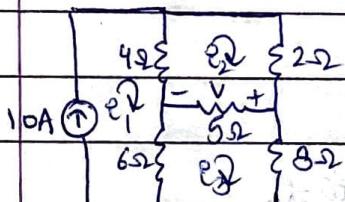

$$V = (e_2 - e_3) 5$$

$$4e_2 - 40 + 2e_2 + 5e_2 - 5e_3 = 0 \quad \textcircled{1}$$

$$11e_2 + 5e_3 = 40$$

$$8e_3 + 6e_2 - 6e_1 + 5e_2 + 5e_3 = 0 \quad \textcircled{2}$$

$$e_2 = 6.46A$$

$$19e_3 + 5e_2 = 60$$

$$e_3 = 4.67A$$


~~$$26P + 5P = 200$$~~

$$\therefore V = 6.45V$$

~~$$16e_2 = 140$$~~

~~$$e_2 = 8.75A$$~~

~~$$e_2 = 8.75A$$~~

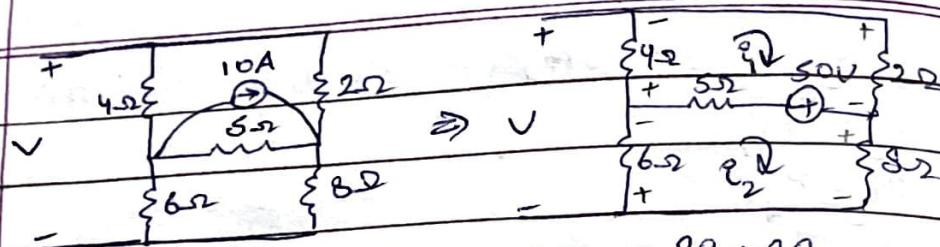

$$V = -4e_1 - 6e_2 = 2e_1 + 8e_2$$

$$4e_1 + 2e_1 + 50 + 5e_1 - 5e_2 = 0 \quad \text{---} (1)$$

$$5e_2 - 11e_1 = 50$$

$$e_2 = \frac{50 + 11e_1}{5}$$

$$19\left(\frac{10 + 11e_1}{5}\right) - 5e_1 = 50$$

$$140 = 5e_1 - \frac{19 \times 11e_1}{5}$$

$$e_2 = 1.64A$$

$$e_1 = -3.8A$$

$$V = 5.44V$$

19/11/20

Negative Resistance in Transistor (this is possible)

$$V_{oc} = V_{TH}$$

$$I_{sc} = I_N$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}} \rightarrow -ve$$

$$I_{sc}$$


Load resistance \rightarrow delivering power to circuit


$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$\downarrow \\ -ve \text{ value}$$

Millman's Theorem

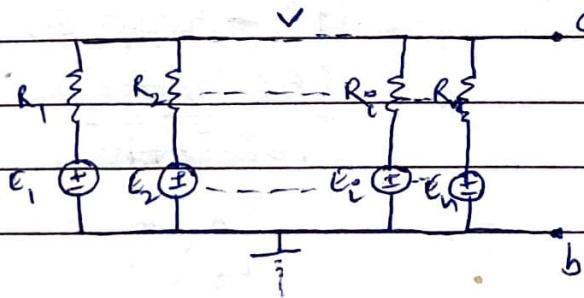- application of KCL / nodal method.
- source transformation.



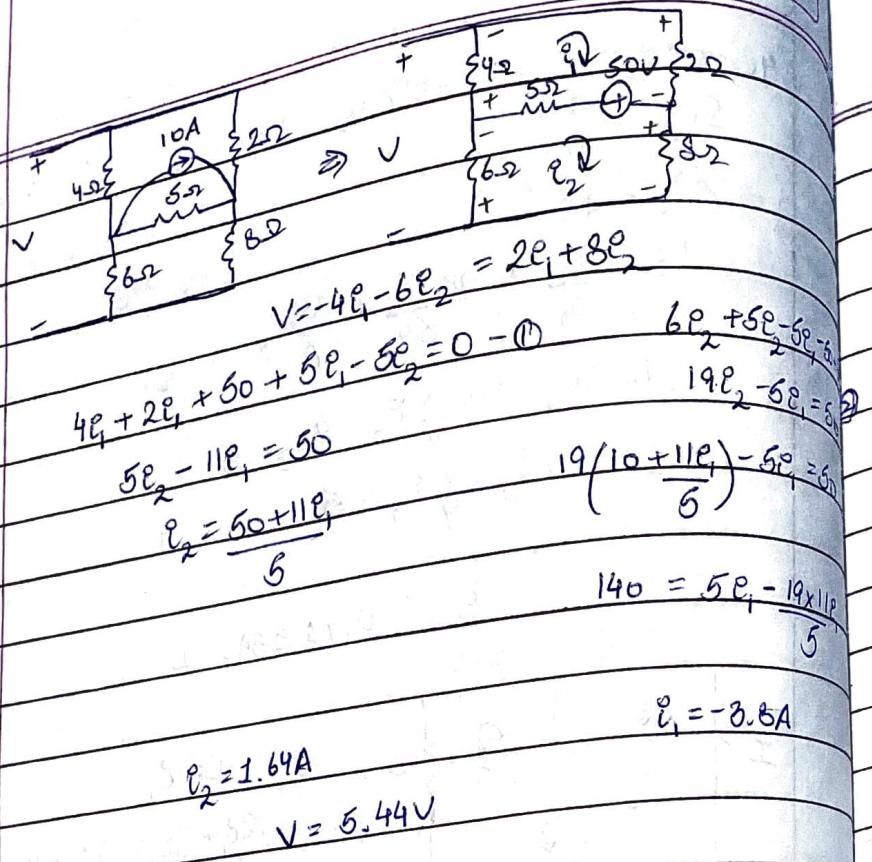

11/11/20
Negative Resistance in Thevenin (this is possible)

$$V_{OC} = V_{TH}$$

$$I_{SC} = I_N$$

$$R_{TH} = \frac{V_{OC}}{I_{SC}} \rightarrow -ve$$


Load resistance \rightarrow delivering power to circuit

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

\downarrow
-ve value

Millman's Theorem

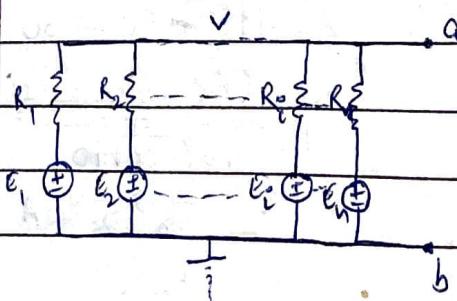- application of KCL / nodal method.
- source transformation.



$$\frac{V - E_1}{R_1} + \frac{V - E_2}{R_2} + \dots + \frac{V - E_i}{R_i} + \frac{V - E_n}{R_n} = 0 \quad (\text{nodal analysis})$$


$$V = \frac{E_1}{R_1} + \frac{E_2}{R_2} + \dots + \frac{E_i}{R_i} + \dots + \frac{E_n}{R_n}$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_i} + \dots + \frac{1}{R_n}$$


$V_m = V \rightarrow \text{Millman Voltage}$

$$\frac{1}{R_m} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

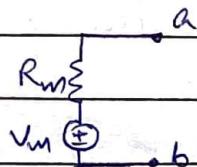$R_m \rightarrow \text{Millman Resistance}$



\rightarrow Current Sources

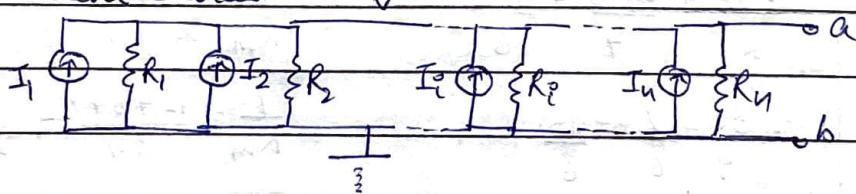


$$\frac{V}{R_1} - I_1 + \frac{V}{R_2} - I_2 + \dots + \frac{V}{R_i} - I_i + \dots + \frac{V}{R_n} - I_n = 0$$

$$V \left[\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right] = I_1 + I_2 + \dots + I_i + \dots + I_n$$

$$V = \frac{I_1 + I_2 + \dots + I_i + \dots + I_n}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_i} + \dots + \frac{1}{R_n}}$$

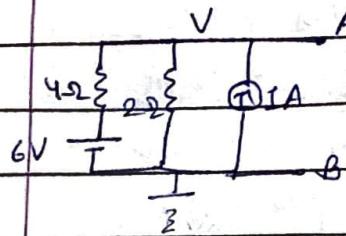Ques-6) Find Millman's eq. b/w terminals AB.



$$\frac{V-6}{4} + \frac{V}{2} - 1 = 0$$

$$\frac{V}{4} + \frac{Vx2}{2x2} - 1 + 3\frac{1}{2}$$

$$\frac{3V}{4} = \frac{5}{2}$$


$$V_m = \frac{5}{2} \times 4 = 10 = 3.33$$

$$I = \frac{1}{4} + \frac{1x2}{2x2} = 3$$

$$R_m = \frac{4}{3} = 1.33\Omega$$

$$R_m = \frac{4}{3} = 1.33\Omega$$

(2)

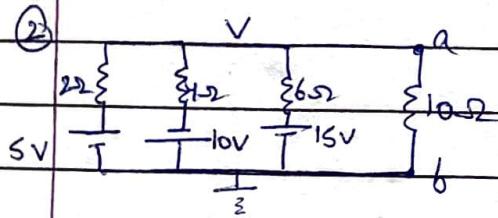

Find current through
10Ω resistor.

$$\frac{V-5}{2} + \frac{V+10}{4} + \frac{V-15}{6} = 0$$

$$I = \frac{1}{2} + \frac{1}{4} + \frac{1}{6}$$

$$\frac{3V}{4} + \frac{V}{6} = \frac{15}{2}$$

$$R_m = \frac{12+6+4}{24} = \frac{22}{24}$$

$$\frac{22V}{24} = 15$$

$$R_m = 1.09\Omega$$



$$V_m = 2.73V$$

$$R_m = 1.09\Omega$$

$$V_m = 2.73V$$

$$I_{10\Omega} = \frac{2.73}{10+1.09} = 0.246A$$

$$10+1.09$$

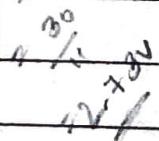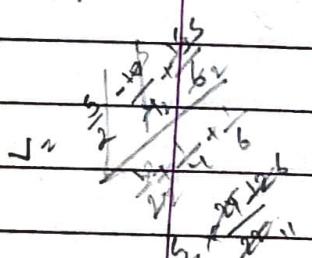

11/20 Ch. 2 - Steady State Analysis of DC Circuits

Transient Analysis


- Energy storage component

① Inductor

② Capacitor

- Switching operations

* Resistance

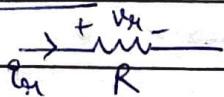

$$v_R = i_R R$$


Transient & Steady State

time dependent solution

↓

time independent

* Capacitor

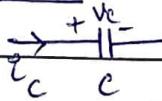

$$v_C = \frac{1}{C} \int i_C dt$$

It opposes instantaneous change in voltage.

$$v_C(0^-) = v_C(0^+)$$


when switching is done at $t=0 \Rightarrow$

$0^- \rightarrow$ before closing / opening

$0^+ \rightarrow$ after closing / opening

Under steady state, capacitor behaves as open circuit.

* Inductor

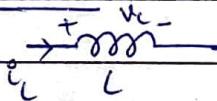

$$v_L = L \frac{di_L}{dt}$$

It opposes the instantaneous change in current.

$$v_L(0^-) = v_L(0^+)$$

Under steady state, inductor behaves as short circuit.

$RL / RC \rightarrow 1^{st}$ order differential eqⁿ

$RCL / LC \rightarrow 2^{nd}$ order differential eqⁿ

$y = \text{transient} + \text{steady state}$
(natural) (forced)

Source free \rightarrow discharging
with source \rightarrow charging

Page No. _____
Date _____

Source Free RC Circuit

as R & C
are ~~not~~
series

$$V_c(0) = V_0$$

$$I_R = I_C$$

$$V_c + V_R = 0$$

$$V_c + \mathcal{E}_R R = 0$$

$$I_C = \frac{C dV_c}{dt} = I_R$$

$$V_c + C R dV_c = 0$$

$$\frac{dV_c}{dt} = -\frac{V_c}{RC}$$

$$\int \frac{dV_c}{V_c} = \int -\frac{1}{RC} dt$$

$$\ln V_c = -\frac{t}{RC} + k$$

$$\text{at } t=0 \Rightarrow V_c(0) = V_0$$

$$\ln V_0 = k$$

$$\ln V_c = -\frac{t}{RC} + \ln V_0$$

$$\ln V_c - \ln V_0 = -\frac{t}{RC}$$

$$\frac{\ln V_c}{V_0} = -\frac{t}{RC}$$


$$\frac{V_c}{V_0} = e^{-t/RC}$$

$$V_c = V_0 e^{-t/RC}$$

[where $\tau = RC$]

↓
time constant
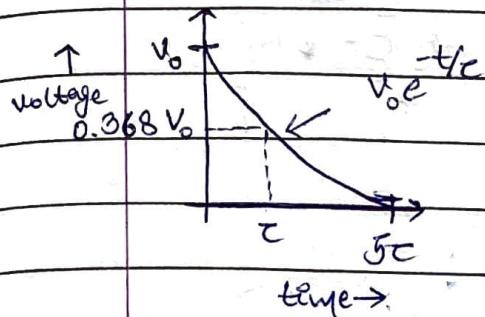
$$i_c = \frac{C dV_c}{dt} = -\frac{V_o e^{-t/\tau}}{R}$$



$$V_c(t) = V_o e^{-t/\tau}$$

$$i_c(t) = -\frac{V_o e^{-t/\tau}}{R}$$


$$\frac{V_c(t)}{V_o} = e^{-t/\tau}$$

24/11/20

Rate of decay of voltage $\rightarrow \frac{d}{dt} \left(\frac{V_c(t)}{V_o} \right) = -\frac{1}{\tau} e^{-t/\tau}$

Initial rate of decay, $t=0$
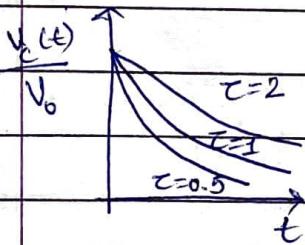
$$\frac{d}{dt} \left(\frac{V_c(t)}{V_o} \right) = -\frac{1}{\tau} \quad \text{Smaller value of } \tau \rightarrow \text{fast decay}$$




$$W = \frac{1}{2} C V_o^2$$

initial energy stored in the capacitor

Source Free RL Circuit

$$i(0) = I_0$$

$$\omega(0) = \frac{L}{R} I_0^2$$

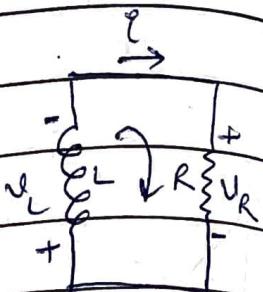

$$V_L + V_R = 0$$

$$\frac{L di}{dt} + iR = 0$$

$$\frac{L di}{dt} = -iR$$

$$\frac{di}{dt} = -\frac{R}{L} i$$

$$\int i \frac{di}{dt} = \int -\frac{R}{L} dt$$

$$\ln i = -\frac{R}{L} t + A$$

$$\text{at } t=0 \Rightarrow i(0) = I_0$$

$$\ln I_0 = A$$

$$\ln i - \ln I_0 = -\frac{Rt}{L}$$


$$\frac{\ln i}{I_0} = -\frac{Rt}{L}$$

$$\frac{i}{I_0} = e^{-\frac{Rt}{L}}$$

$$I_0$$

$$i = I_0 e^{-\frac{Rt}{L}}$$

[where $\tau = L/R$]

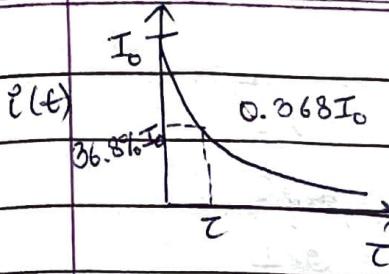

$$e = e^{-Rt/T}$$

$$\frac{d}{dt} \left(\frac{i}{I_0} \right) = -\frac{R}{L} e^{-Rt/L}$$

$$= \frac{-t}{2} e^{-t/2}$$

$$\frac{t}{2} = -1$$

$$V_R(t) = iR = I_0 R e^{-t/T}$$

$$V_C(t) = \frac{L \frac{dI}{dt}}{\frac{1}{C}} = -L I_0 \frac{e^{-t/C}}{C} = -R I_0 e^{-t/C}$$

* NOTE: Reg \rightarrow across terminals of L/C.


$$\tau = \text{Req. C}$$

RC circuit

$$\tau = \underline{1}$$


\downarrow Req
RL circuit

Ques. ①

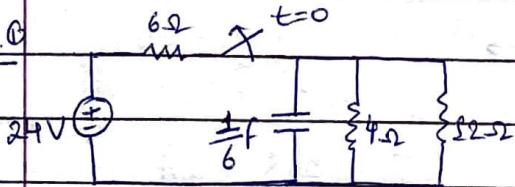

For capacitor, find $v(t)$,

$$\frac{q(t)}{\omega_0(0)}$$

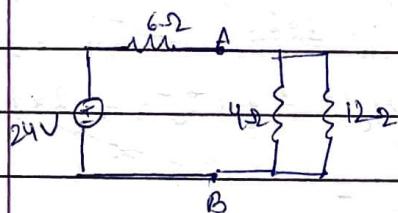

$$\therefore V_{AB} = \underline{24 \times 3} = 8V$$


3+6

$$V_1 = 8V$$

$$\omega_c(\omega) = \frac{1}{2} C V_0^2$$

$$= \frac{1}{2} \times \frac{1}{6} \times 64$$

$$= 5.33 \text{ J}$$

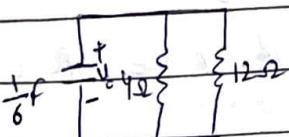After switching \rightarrow 

$$V_c(t) = V_0 e^{-t/\tau}$$


$$\tau = R_{eq} C$$

$$= 3 \times \frac{1}{6}$$

$$= 0.5 \text{ sec}$$

$$V_c(t) = 8 e^{-2t} \text{ V}$$


$$q_c(t) = -\frac{V_0}{R_{eq}} e^{-t/\tau} = -\frac{8}{3} e^{-2t} \text{ A}$$

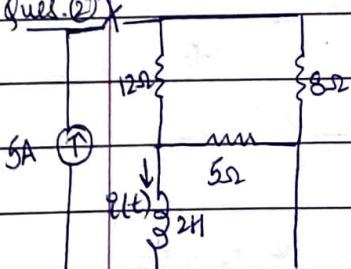ques. ② $t=0$ find $v(t)$ for $t > 0$.

$$v(t) = I_0 e^{-t/\tau}$$

Before switching \rightarrow

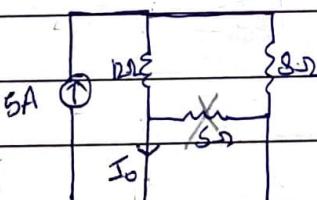no current through 5Ω
at time $t=0$
short
current always flows
(least resistance path)




$$I_0 = 5 \times 8 = 2 \text{ A}$$

$$12+8$$

$$w_c(0) = \frac{1}{2} L I_0^2 = \frac{1}{2} \times 2 \times 4$$

$$= 4 \text{ J}$$

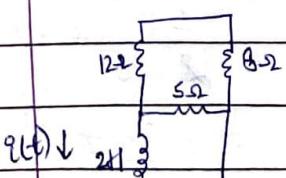After switching \rightarrow 

$$\tau = L = \frac{2}{R_{eq}} = \frac{2}{20+5} = \frac{2}{25} = \frac{1}{12.5} \text{ sec}$$

$$q(t) = 2 e^{-\frac{t}{\tau}} \text{ A}$$


$$v(t) = -I_{0e}^{-t/\tau} = -8 e^{-2t} \text{ V}$$

26/11/20

Step Response of RC Circuit

Initial voltage (v)

$$v(0^-) = v(0^+) = V_0$$

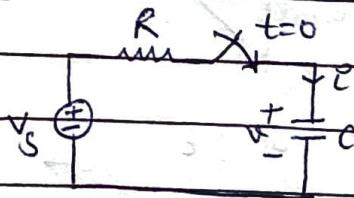

at $t=0$ switch is closed

$$t > 0$$

$$-V_s + iR + v = 0 \quad \therefore R = \frac{CdV}{dt}$$

$$-V_s + RC \frac{dv}{dt} + v = 0$$

$$v - V_s = -RC \frac{dv}{dt}$$

$$\int \frac{dv}{v - V_s} = \frac{-1}{RC} \int dt$$

$$\ln(v - V_s) = \frac{-1}{RC} t + A$$

$$\text{at } t=0, v(0^-) = v(0^+) = V_0$$

$$\ln(V_0 - V_s) = A$$

$$\ln(v - V_s) = \frac{-t}{RC} + \ln(V_0 - V_s)$$

$$\ln\left(\frac{v - V_s}{V_0 - V_s}\right) = \frac{-t}{RC}$$

$$v - V_s = e^{-t/RC}$$


$$V_0 - V_s$$

$$v - V_s = (V_0 - V_s) e^{-t/RC}$$

$$v = V_s + (V_0 - V_s) e^{-t/RC}$$

(Steady) forced state response \leftarrow $v(t) = V_s + (V_0 - V_s) e^{-t/\tau}$ Natural response
 response (transient) where $\tau \rightarrow \text{time constant} = RC$
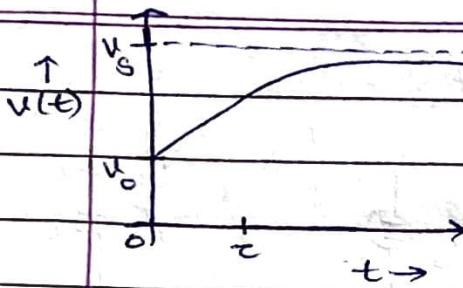
$$v(t) = \begin{cases} V_0, & t \leq 0 \\ V_s + (V_0 - V_s) e^{-t/\tau}, & t \geq 0 \end{cases}$$



$$V_s = V(\infty), \quad V_0 = V(0)$$

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

If capacitor is initially uncharged,
 $V(0) = 0$

$$V(t) = V_s (1 - e^{-t/\tau})$$


$$i = \frac{CdV}{dt}$$

$$i = -C V_s e^{-t/\tau} \downarrow \tau$$

charged

uncharged $\rightarrow i = \frac{V_s e^{-t/\tau}}{R}$
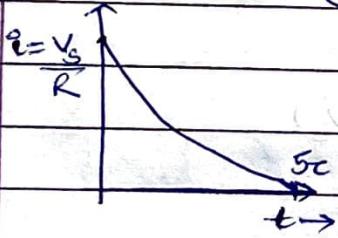
$$i = -\left(\frac{V_0 - V_s}{R}\right) e^{-t/\tau}$$



Step Response of RL Circuit


Initial inductor current

$$i(0^+) = i(0^+) = I_0$$

$t > 0$

$$-V_s + Ri + L \frac{di}{dt} = 0$$

$$\text{at } t=0, i(0) = I_0$$

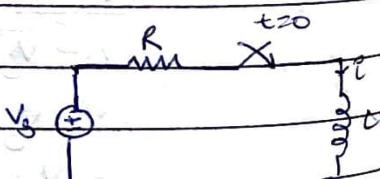


$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$

$$[\tau = L/R]$$

$i(\infty) = \frac{V_s}{R}$ = steady state value of current
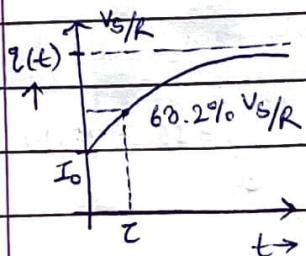
$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$



$$i(t) = \begin{cases} I_0, & t \leq 0 \\ \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}, & t \geq 0 \end{cases}$$

If inductor is initially uncharged,


$$I_0 = 0$$

$$i(t) = \begin{cases} 0, & t \leq 0 \\ \frac{V_s}{R} (1 - e^{-t/\tau}), & t \geq 0 \end{cases}$$

$$v_L(t) = \frac{L di}{dt}$$

$$v_L(t) = \frac{L V_s}{R \tau} e^{-t/\tau}$$

$$v_L(t) = V_s e^{-t/\tau}$$

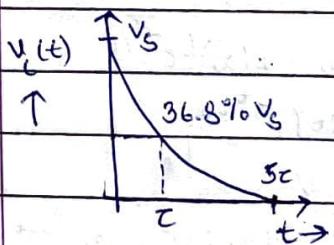


* NOTE: $RC \rightarrow \tau = R_{TH} C$

$$RL \rightarrow \tau = \frac{L}{R_{TH}}$$

$R_{TH} \rightarrow$ equivalent resistance seen from capacitor / inductor

27/11/10

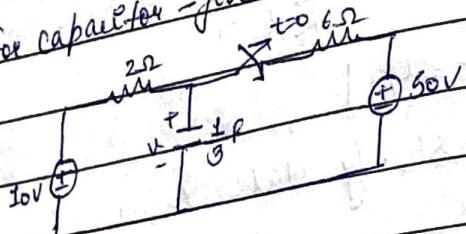Ques. Q) For capacitor - find $v(t)$, $i_c(t)$, and $w_c(0)$.




Before switching →

$$w_c(0) = \frac{1}{2} CV_0^2$$

$$V(0^-) = V(0^+) = 10V$$

$$w_c(0) = \frac{1}{2} \times \frac{1}{3} \times 10 \times 10 = \frac{100}{6} = \frac{50}{3} = 16.67 \text{ Joules}$$

After switching →

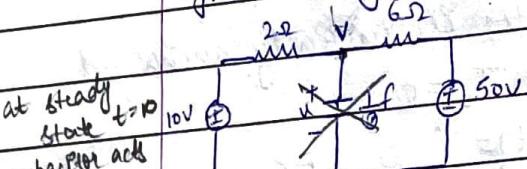

at steady state
t=10
capacitor acts
as open circuit

$$\frac{V-10}{2} + \frac{V-50}{6} = 0$$

$$\frac{2V}{3} = 5 + \frac{25}{3} = \frac{40}{3}$$

$$V = 20V$$

$$\therefore V(\infty) = 20V$$

$$R_{eq} = \frac{6 \times 2}{6+2} = 1.5\Omega \quad \tau = C R_{eq} = \frac{1}{3} \times \frac{8}{2} = 0.51$$

$$So, V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$


$$= 20 + [10 - 20] e^{-t/0.5}$$

$$= 20 - 10e^{-2t} V$$

$$i_c(t) = C \frac{dV}{dt} = \frac{1}{3} [-10e^{-2t} \cdot (-2)] = \frac{20}{3} e^{-2t}$$


$$i_c(t) = 6.67 e^{-2t} A$$

Ques. ② Find current $i(t)$

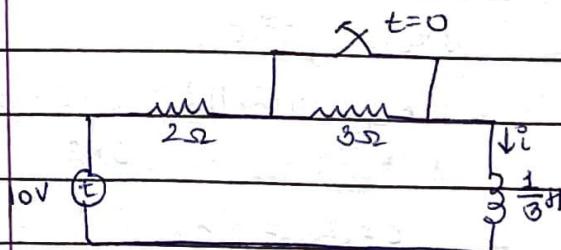

Before switching →

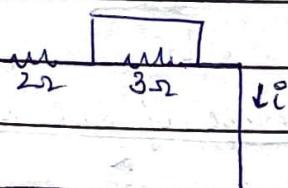
inductor
behaves as
short
circuit
except
at $t=0$
as
it has
long
time



$$\therefore i = \frac{10}{2} = 5A = i(0^-) = i(0^+)$$

After switching →

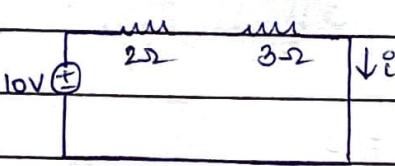inductor
behaves as
short
circuit
except
at $t=0$
as
it has
long
time



$$i(\infty) = \frac{10}{5} = 2A$$

$$R_{eq} = 2 + 3 = 5\Omega$$

$$C = L = \frac{1}{2} = \frac{1}{5}$$


$$R_{eq} = 3 \times 5 = 15$$

$$i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/C}$$

$$i(t) = 2 + [5 - 2] e^{-15t}$$


$$= 2 + 3e^{-15t} A$$

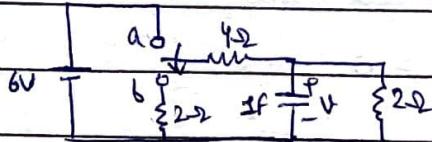Ques. ③ In the network shown in fig., the switch is moved from a to b at $t=0$. Find $v(t)$.



Before switching →

capacitor
acts
as
open
circuit

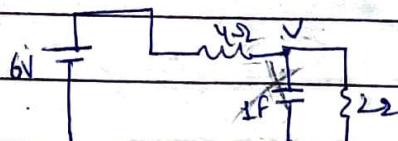

$$V - 6 + \frac{V}{2} = 0$$

$$\frac{3V}{4} = \frac{6}{2}$$

$$V = 2V \quad \therefore V(0^+) = V(0^-) = 2V$$

After switching \rightarrow

$$\frac{4\Omega}{m}$$

source free
RC circuit


$$V(t) = V_0 e^{-t/\tau}$$

$$R_{eq} = (4+2) \parallel 2 = \frac{6 \times 2}{6+2} = 1.5 \Omega$$

$$\tau = L R_{eq} = 1.5 s$$

$$V(t) = 2e^{-t/1.5} V$$

1/12/20

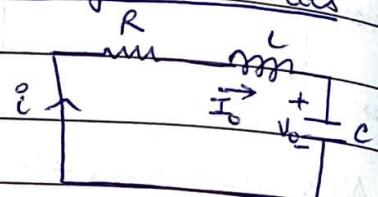Natural / Source free response of RLC seriesat $t=0^-$,inductor current - I_0 capacitor voltage - V_0 

$$RI + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i dt = 0$$

at $t=0^+$,

$$i = I_0, \quad V_c = V_0$$

$$RI_0 + L \frac{di}{dt} + V_0 = 0$$

$$\left. \frac{di}{dt} \right|_{t=0} = -\frac{1}{L} (RI_0 + V_0)$$

$$RI + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i dt = 0$$

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i = 0$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

characteristic
equation

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

Standard form →

$$s^2 + 2\zeta s + \omega_n^2 = 0$$

$$\text{or } s^2 + 2\zeta \omega_n s + \omega_n^2 = 0$$

$\omega_n \leftarrow \omega_n \rightarrow \text{natural frequency}$

$\zeta \leftarrow \frac{\zeta}{\omega_n} \rightarrow \text{damping ratio}$

$$\zeta = \frac{\zeta}{\omega_n}$$

$$s_1 = -\frac{R}{2L} + \sqrt{\frac{(R)^2}{(2L)} - \frac{4}{4LC}} = -\frac{R}{2L} + \sqrt{\frac{(R)^2 - \frac{4}{LC}}{LC}}$$

$$s_2 = -\frac{R}{2L} - \sqrt{\frac{(R)^2 - \frac{4}{LC}}{LC}}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_n^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_n^2}$$

$$\omega_n = \frac{1}{\sqrt{LC}}, \quad \alpha = \frac{R}{2L}, \quad \zeta = \frac{R}{2\sqrt{LC}}$$

Case (1) Overdamped

$$\alpha > \omega_n \text{ or } \zeta > 1$$

Case (2) Critically damped

$$\alpha = \omega_n \text{ or } \zeta = 1$$

Case (3) Under damped

$$\alpha < \omega_n \text{ or } \zeta < 1$$

* Overdamped

$$\alpha > \omega_n \text{ or } \zeta > 1$$

s_1 & s_2 are real but negative

$$i(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

* Critically damped

$$\alpha = \omega_n \text{ or } \zeta = 1$$

s_1 & s_2 are equal and negative

$$\frac{d^2\theta}{dt^2} + 2\zeta \frac{d\theta}{dt} + \omega_n^2 \theta = 0$$

$$\omega_n = \zeta \quad \frac{d^2\theta}{dt^2} + 2\zeta \frac{d\theta}{dt} + \zeta^2 \theta = 0$$

$$\Rightarrow \frac{d^2\theta}{dt^2} + \zeta \frac{d\theta}{dt} + \zeta \frac{d\theta}{dt} + \zeta^2 \theta = 0$$

$$\Rightarrow \frac{d}{dt} \left[\frac{d\theta}{dt} + \zeta \theta \right] + \zeta \left[\frac{d\theta}{dt} + \zeta \theta \right] = 0$$

$$\Rightarrow \left[\frac{d\theta}{dt} + \zeta \theta \right] \left[\frac{d}{dt} + \zeta \right] = 0$$

↓
j

$$\Rightarrow \frac{df}{dt} + \zeta f = 0$$

$$f = k_1 e^{-\zeta t}$$

$$\frac{d\theta}{dt} + \zeta \theta = f = k_1 e^{-\zeta t}$$

premultiplied by $e^{\zeta t}$

$$e^{\zeta t} \frac{d\theta}{dt} + \zeta e^{\zeta t} \theta = k_1$$

$$\int \frac{d}{dt} (k_1 e^{\zeta t}) = k_1$$

$$\int d(k_1 e^{\zeta t}) = \int k_1 dt$$

$$k_1 e^{\zeta t} = k_1 t + k_2$$

$$\theta(t) = (k_1 t + k_2) e^{-\zeta t}$$

* Underdamped

$$\zeta < \omega_n \text{ or } \xi < 1$$

s_1 & s_2 are complex and conjugate

$$\theta(t) = e^{-\zeta t} [(k_1 + k_2) \cos \omega_d t + j(k_1 - k_2) \sin \omega_d t]$$

$$\omega_d = \sqrt{\omega_n^2 - \zeta^2} = \omega_n \sqrt{1 - \xi^2}$$

- inductor oppose the change in instantaneous current.
- capacitor oppose the instantaneous change in voltage.

Page No.	
Date	


3/12/20

Step Response of RLC Series

$$-V_S + V_R + V_L + V_C = 0$$

$$V_R + V_L + V_C = V_S$$
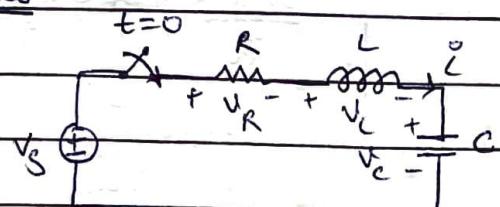
$$iR + L \frac{di}{dt} + \frac{1}{C} \int i dt = V_S - \textcircled{1}$$




$$\text{differentiating } \frac{R di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$

$$\rightarrow \text{variable } \frac{RC di}{dt} + LC \frac{d^2 i}{dt^2} + \frac{i}{C} = 0 \quad \therefore i = \frac{C dV_C}{dt}$$

value of i in $\textcircled{1}$ -

$$V_C \rightarrow \text{variable } \frac{RC dV_C}{dt} + LC \frac{d^2 V_C}{dt^2} + V_C = V_S$$

* Parallel RLC

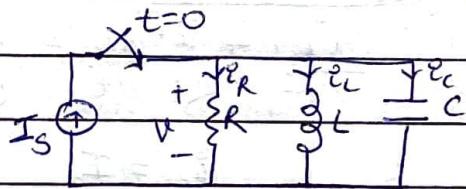

$$i_R + i_L + i_C = I_S$$

$$\text{differentiating } \frac{V}{R} + \frac{1}{L} \int V dt + \frac{C dV}{dt} = I_S - \textcircled{1}$$

$$\rightarrow \text{variable } \frac{1}{R} \frac{dV}{dt} + \frac{V}{L} + \frac{C d^2 V}{dt^2} = 0 \quad \therefore V = \frac{L dI_C}{dt}$$

value of V in $\textcircled{1}$ -

$$V = \frac{L}{R} \frac{d^2 i_C}{dt^2} + \frac{1}{C} \frac{d^2 i_C}{dt^2} + i_C = I_S$$

$$a_2 \frac{d^2 x(t)}{dt^2} + a_1 \frac{dx(t)}{dt} + a_0 x(t) = b_0 f(t)$$

$$\frac{d^2 x(t)}{dt^2} + \frac{a_1}{a_2} \frac{dx(t)}{dt} + \frac{a_0}{a_2} x(t) = \frac{b_0}{a_2} f(t)$$

$$\frac{d^2x(t)}{dt^2} + 2\zeta\omega_n \frac{dx(t)}{dt} + \omega_n^2 x(t) = k_{eff}(t)$$

$$\omega_n = \sqrt{\frac{a_0}{a_2}}, \quad 2\zeta\omega_n = \frac{a_1}{a_2}$$

natural frequency

$$\zeta = \frac{a_1}{2\sqrt{a_0 a_2}}$$

$$k_g = \frac{b_0}{a_2} \rightarrow DC \text{ gain}$$

$$\text{characteristic equation} \quad s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$$

Total Response = Steady State Response
+ Transient Response

$$x(t) = x_{ss} + x_t(t)$$

→ for Parallel RLC

$$\frac{d^2i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} = \frac{I_s}{LC} \quad \begin{matrix} \alpha = 1 \\ 2RC \end{matrix}$$

$$i_{ss} = I_s \quad (\text{steady state})$$

• Overshaded

$$\zeta > 1 \text{ or } \alpha > \omega_n$$

$$i(t) = I_s + k_1 e^{st} + k_2 e^{s_2 t}$$

• Critically damped


$$\zeta = 1 \text{ or } \alpha = \omega_n$$

$$i(t) = I_s + (k_1 t + k_2) e^{-\alpha t}$$

• Underdamped

$$\zeta < 1 \text{ or } \alpha < \omega_n$$
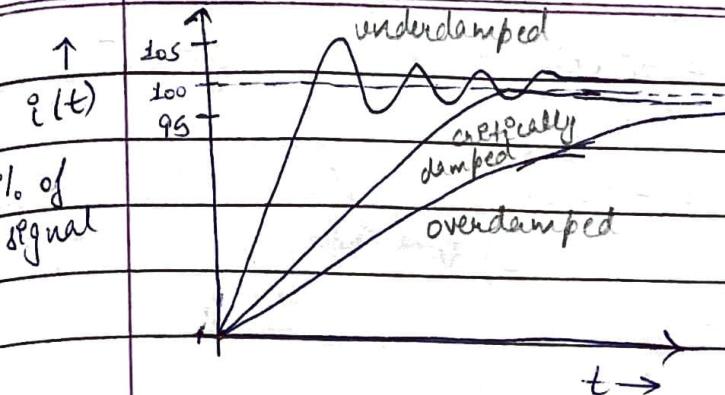
$$i(t) = I_s + e^{-\alpha t} [k_1 + k_2] \cos \omega_d t + j(k_1 - k_2) \sin \omega_d t$$




4/12/20

Ques. (i) For the circuit find -

$$\text{i) } i(0^+) \text{ and } v(0^+)$$

$$\text{ii) } \frac{di}{dt}(0^+) \text{ and } \frac{dv}{dt}(0^+)$$
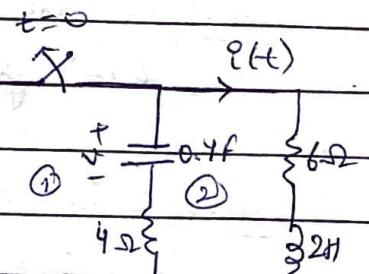
$$\text{iii) } i(\infty) \text{ and } v(\infty)$$



Sol. Before switching operation -

at $t = 0^-$ \rightarrow short circuit

\rightarrow open circuit

$$v(0^-) = 12V$$

$$i(0^-) = \frac{12}{6} = 2A$$

$$\therefore v(0^+) = v(0^-) = 12V$$

$$i(0^+) = i(0^-) = 2A$$

After switch is open -

KVL in loop (2)

$$\Rightarrow 6i(0^+) + v_L(0^+) + 4i(0^+) - v_C(0^+) = 0$$


$$\Rightarrow -10i(0^+) + v_C(0^+) = L \frac{di}{dt}(0^+)$$

$$\Rightarrow -10 \times 2 + 12 = 2 \frac{di}{dt}(0^+)$$

$$\Rightarrow \frac{di}{dt}(0^+) = -4A/\text{sec}$$

$$\frac{CdV_0(0^+)}{dt} = -i(0)$$
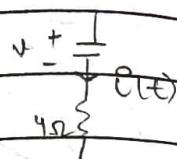
$$\frac{dV(0^+)}{dt} = -5 \text{ V/sec}$$




capacitor &
inductor gets
discharged

$$i(\infty) = 0$$

$$v(\infty) = 0$$

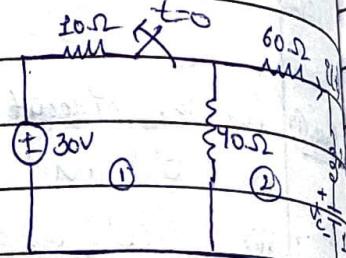Ques. 2 For the given circuit find
 $i(t)$ for $t > 0$.



Sol. Before switching -

C → open

L → short

no current
flows in ②
at C is
open
switch

$$i(0^-) = i(0^+) = 0$$

$$V_c(0^-) = V_c(0^+) = 40 \times \frac{30}{10+40} = 24 \text{ V}$$

After switching -

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$



$$\chi = \frac{R}{2L} = \frac{100}{2 \times 25} = 2 \text{ Ohms}$$

$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2.5 \times 10^{-3}}} = \frac{1}{\sqrt{2.5 \times 10^{-4}}} = \frac{1}{5 \times 10^2} = 20 \text{ rad/sec}$$

$$\chi = \omega_n$$

∴ critically damped

$$i(t) = (k_1 t + k_2) e^{-\chi t}$$

$$\text{at } t=0, i(0^+) = i(0^-) = 0$$

$$0 = (0 + k_2) e^{0 \times 0} = k_2$$

$$k_2 = 0$$

$$\frac{di}{dt} = e^{-kt} k_1 + (k_1 t + k_2) (-k) e^{-kt}$$

KVL -

$$\Rightarrow 100 \ell(0^+) + V_L(0^+) + V_C(0^+) = 0$$

$$\Rightarrow 100 \ell(0^+) + V_C(0^+) = -L \frac{di(0^+)}{dt}$$

$$\Rightarrow 100 \times 0 + 24 = -2.5 \frac{di(0^+)}{dt}$$

$$\Rightarrow \frac{di(0^+)}{dt} = -9.6 \text{ A/sec}$$

at $t = 0^+$

$$-9.6 = 0 + k_1$$

$$k_1 = -9.6$$


$$\text{So, } i(t) = \underline{-9.6t e^{-20t}}$$

8/12/20

AC Circuits


✓ $I_m \rightarrow$ peak / maximum value✓ $I \rightarrow$ root mean square value✓ $I_{av} \rightarrow$ average value✓ $i \rightarrow$ instantaneous value★ Phasors

$$i = I_m \sin \omega t$$

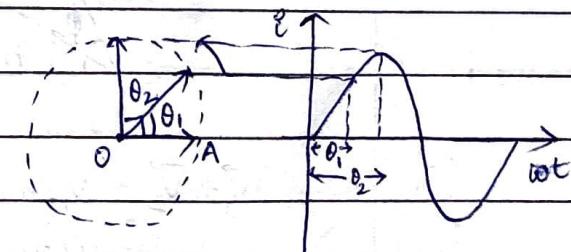 $\omega \rightarrow$ angular speed

* Reference

$$v = V_m \sin(\omega t + \phi)$$

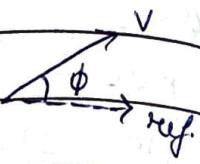

NOTE:

j-operator

$$j = \sqrt{-1}$$

$$j = \theta = \sqrt{-1}$$

as it is representation of instantaneous current

$\therefore j'$ is vreal.

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$\begin{aligned} & \text{Real} \\ & V_{m\text{real}} = V_m \cos(\omega t + \phi) \end{aligned}$$

$$v = V_m \sin(\omega t + \phi)$$

$$= \text{Im} [V_m e^{j(\omega t + \phi)}]$$

$$= \text{Im} [\sqrt{2} V_m e^{j\omega t} e^{j\phi}]$$

$$+ j V_m \sin(\omega t + \phi)$$

$$V_{m\text{real}} = V = \frac{V_m}{\sqrt{2}}$$

$$\vec{V} = V \angle \phi \quad \begin{matrix} V_{\text{real}} \\ V_{\text{imag/reactive}} \end{matrix}$$

$$\vec{V} = V \cos \phi + j V \sin \phi$$


$$|V| = \sqrt{V_{\text{real}}^2 + V_{\text{reactive}}^2}$$

$$\phi = \tan^{-1} \frac{V_{\text{reactive}}}{V_{\text{real}}}$$

$$V_{\text{real}}$$

$$V_1 = V_{m1} \sin(\omega t + \phi_1) \Rightarrow \vec{V}_1 = V_1 \angle \phi_1$$
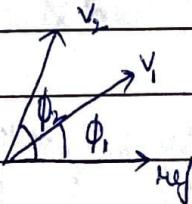
$$V_2 = V_{m2} \sin(\omega t + \phi_2) \Rightarrow \vec{V}_2 = V_2 \angle \phi_2$$



$$\text{Addition } \vec{V}_1 + \vec{V}_2 = V_1 \angle \phi_1 + V_2 \angle \phi_2$$

$$= V_1 \cos \phi_1 + j V_1 \sin \phi_1 + V_2 \cos \phi_2 + j V_2 \sin \phi_2$$

$$= (V_1 \cos \phi_1 + V_2 \cos \phi_2) + j (V_1 \sin \phi_1 + V_2 \sin \phi_2)$$

$$\vec{V} = \vec{V}_1 + \vec{V}_2 = V \cos \phi + j V \sin \phi$$

$$a+jb = r \angle \theta$$

$$r = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1} b/a$$

Page No. _____

Date _____

$$\left[\begin{array}{l} v(t) = \sqrt{2} V \sin(\omega t + \phi) \\ \text{or } v(t) = \sqrt{2} V \cos(\omega t + \phi) \end{array} \right]$$

Subtraction $\vec{V}_1 - \vec{V}_2 = V_1 \angle \phi_1 - V_2 \angle \phi_2$
 $= (V_1 \cos \phi_1 - V_2 \cos \phi_2) + j(V_1 \sin \phi_1 - V_2 \sin \phi_2)$

Multiplication $\vec{V}_1 \times \vec{V}_2 = V_1 V_2 \angle (\phi_1 + \phi_2)$

Division $\frac{\vec{V}_1}{\vec{V}_2} = \frac{V_1}{V_2} \angle (\phi_1 - \phi_2)$

10/12/20

Time derivative & integral of a Phasor \rightarrow

$$v(t) = V_m \sin(\omega t + \phi)$$


$$v(t) = \text{Im} [\sqrt{2} V e^{j\omega t} e^{j\phi}]$$

$$\frac{dv(t)}{dt} = \text{Im} [\sqrt{2} V j\omega e^{j\omega t} e^{j\phi}]$$

$$\frac{d\vec{V}}{dt} = j\omega V e^{j\phi} = j\omega \vec{V}$$

$$\int v(t) dt = \text{Im} [\sqrt{2} V \frac{e^{j\omega t}}{j\omega} e^{j\phi}]$$
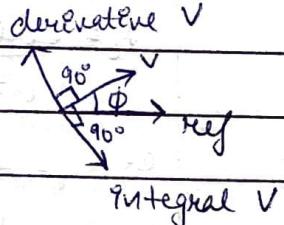
$$\begin{aligned} \int \vec{V} dt &= \frac{V}{j\omega} e^{j\phi} = \frac{\vec{V}}{j\omega} \\ &= -\frac{j^2}{j\omega} \vec{V} = -\frac{\omega}{j\omega} \vec{V} \end{aligned}$$



e.g. $\vec{V}_1 = 3 \angle 15^\circ$ $\vec{V}_2 = 2.5 \angle 45^\circ$

cosine as reference

$$\vec{V} = \vec{V}_1 + \vec{V}_2$$

$$= 3 \angle 15^\circ + 2.5 \angle 45^\circ$$

$$= 3 \cos 15^\circ + j 3 \sin 15^\circ + 2.5 \cos 45^\circ + j 2.5 \sin 45^\circ$$

$$= (3 \cos 15^\circ + 2.5 \cos 45^\circ) + j(3 \sin 15^\circ + 2.5 \sin 45^\circ)$$

$$\vec{V} = 4.66 + j 2.54$$

$$= 5.31 \angle 28.6^\circ$$

Instantaneous $v(t) = 5.31\sqrt{2} \cos(\omega t + 28.6^\circ)$
form

* Circuit Parameters

(1) Resistance, R


$$v_R(t) = e_R(t)R$$

$$v_R = e_R R$$


$$e_R = \frac{v_R}{R}$$

$$= \frac{V_m \sin \omega t}{R}$$

$$\vec{V}_R = \vec{I}_R R$$

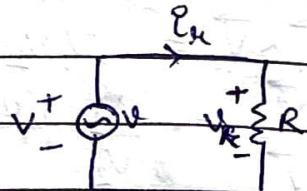


$$v = V_m \sin \omega t$$

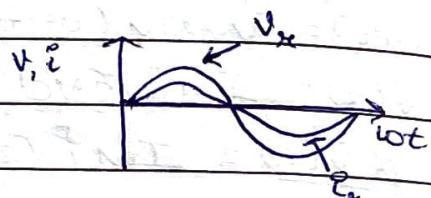

$$\vec{I}_R \quad \vec{V}_R \quad \text{no phase difference}$$

(2) Inductance, L

$$v_L = L \frac{de_L}{dt}$$

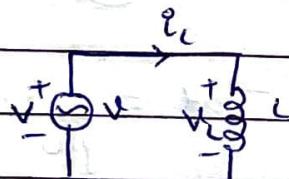


$$\text{or } e_L = \pm \frac{1}{L} \int v_L dt$$

$$v = V_m \sin \omega t$$

$$= \pm \frac{1}{L} \int V_m \sin \omega t dt$$

$$= \frac{V_m}{\omega L} (-\cos \omega t)$$


Current
lags by
 90°

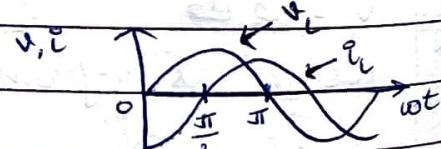

$$e_L = \frac{(V_m)}{\omega L} \sin \omega t (\omega t - 90^\circ)$$


$$(\omega L) \rightarrow X_L$$
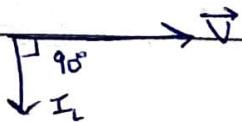
$$\vec{I}_L = \frac{\vec{V}}{\omega L} \angle -90^\circ = \frac{\vec{V} \cdot -j}{\omega L} = \frac{\vec{V}}{j \omega L} = \frac{\vec{V}}{j X_L}$$



(3) Capacitance, C

$$V_C = \frac{1}{C} \int i_C dt$$

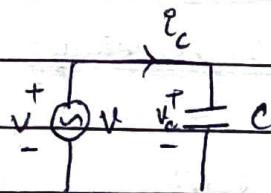

$$v = V_m \sin \omega t$$


$$i_C = C \frac{dV_C}{dt}$$

$$\vec{V} = V \angle 0^\circ$$

$$= C \frac{dV_m \sin \omega t}{dt}$$

$$= CV_m \cos \omega t \cdot \omega$$
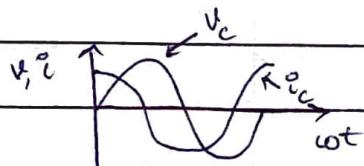
$$= V_m \omega C \sin(\omega t + 90^\circ)$$



$$i_C = \frac{V_m}{\pm j\omega C} \sin(\omega t + 90^\circ)$$

$$I_C = \frac{\vec{V}}{\pm j\omega C} = \frac{\vec{V}_j}{\pm j\omega C} = \vec{V}_j \angle 90^\circ$$


$$\vec{I}_C = \frac{\vec{V}}{j\omega C} = \frac{\vec{V}}{-jX_C}$$

11/12/20

* Series RL Circuit

$$V = V_R + V_L$$
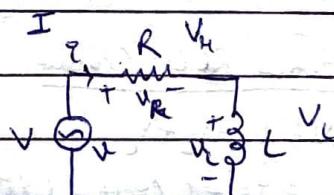
$$V = \mathcal{E}R + \frac{d\mathcal{E}}{dt}$$




$$\text{Phasor relation} \rightarrow \vec{V} = \vec{V}_R + \vec{V}_L$$

$$= \vec{I}R + \vec{I}jX_L$$

$$IX_L = V_L \quad \vec{V} = \vec{I}(R + jX_L)$$

phasor diagram

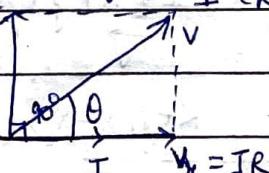

$$I = \frac{\vec{V}}{R + jX_L} = \frac{\vec{V}}{Z} = \vec{V} \angle \theta$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$\theta = \tan^{-1} \left(\frac{V_L}{V_R} \right) = \tan^{-1} \left(\frac{X_L}{R} \right)$$




* Series RC Circuit

$$V = V_R + V_C$$

$$= \underline{R}I + \frac{1}{C} \int \underline{dQ} dt$$
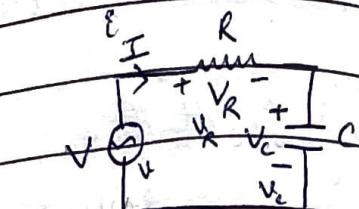
$$\text{Phasor Relation} \rightarrow \vec{V} = \vec{V}_R + \vec{V}_C$$




$$\begin{aligned} \vec{V} &= \vec{IR} + \vec{I}jX_C \\ \vec{I} &= \vec{I}(R - jX_C) \end{aligned}$$

$$Z = R - jX_C$$

$$|Z| = \sqrt{R^2 + X_C^2}$$


$$\theta = \tan^{-1}\left(\frac{X_C}{R}\right)$$

Phasor Diagram

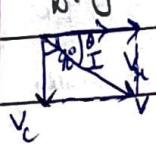

$$\theta = \tan^{-1}\left(\frac{V_C}{V_R}\right)$$

Impedance triangle

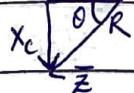


$$I = \frac{\vec{V}}{Z} = \frac{\vec{V}}{|Z|} \angle \theta$$

* Series RLC Circuit

$$V = V_R + V_L + V_C$$
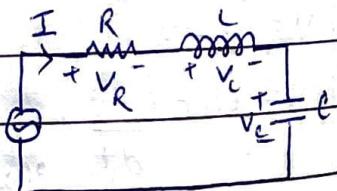
$$= \underline{R}I + \frac{1}{L} \int \underline{dQ} dt + \frac{1}{C} \frac{\underline{dQ}}{dt}$$



$$\text{Phasor Relation} \rightarrow \vec{V} = \vec{V}_R + \vec{V}_L + \vec{V}_C$$

$$= \vec{IR} + \vec{I}jX_L + \vec{I}(-jX_C)$$


$$\vec{I} = \vec{I}[R + j(X_L - X_C)]$$

$$I = \frac{\vec{V}}{Z} = \frac{\vec{V}}{|Z|} \angle \theta$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\theta = \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$

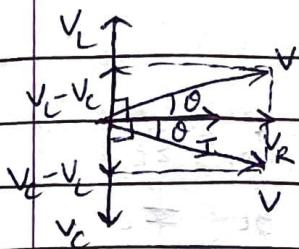$\theta \rightarrow +ve \rightarrow$ Inductive
 $\theta \rightarrow -ve \rightarrow$ Capacitive



$$V_L = I X_L$$

$$V_C = I X_C$$

purely resistive

① if $X_L = X_C \Rightarrow Z = R \rightarrow$
current lagging by θ $V_L > V_C \rightarrow$ inductive

current leading by θ ② if $X_C > X_L \Rightarrow V_C > V_L \rightarrow$ capacitive

* Parallel RLC Circuit

$$\vec{E} = \vec{E}_R + \vec{E}_L + \vec{E}_C$$

$$\vec{I} = \vec{I}_R + \vec{I}_L + \vec{I}_C$$

$$= \frac{\vec{V}}{R} + \frac{\vec{V}}{jX_L} + \frac{\vec{V}}{jX_C}$$

$$= \vec{V} \left[\frac{1}{R} + \frac{1}{jX_L} - \frac{1}{jX_C} \right]$$


$$= \vec{V} \left[\frac{1}{R} - \frac{j}{X_L} + \frac{j}{X_C} \right]$$

$$\boxed{\vec{I} = \vec{V} [G - jB_L + jB_C]}$$


$$\vec{I} = \vec{V} Y \quad \text{conductance}$$

$$\text{where, } \boxed{Y = G + j(B_C - B_L)}$$

admittance

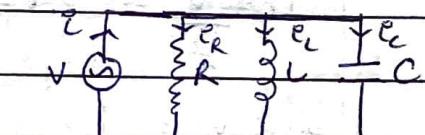

phasor diagram

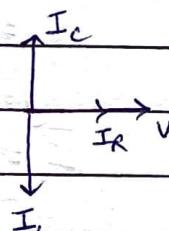

$$Y = \frac{1}{Z}$$

Productive susceptance


capacitive susceptance

15/12/20

* Practical Parallel Circuit

$$I = I_1 + I_2$$

$$V = V_{R_1} + V_L = V_{R_2} + V_C$$

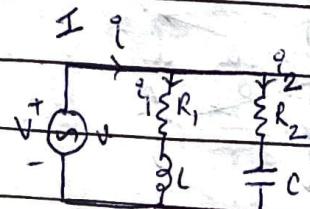

$$\vec{V} = \vec{V}_{R_1} + \vec{V}_L = I_1 \vec{Z}_1$$

$$= I_1 (R_1 + jX_L)$$

$$\vec{V} = \vec{V}_{R_2} + \vec{V}_C = I_2 \vec{Z}_2$$

$$= I_2 (R_2 - jX_C)$$

$$\vec{I}_1 = \frac{\vec{V}_0}{\vec{Z}_1} = \frac{V_0}{R_1 + jX_L} = I_1 \angle \theta_1$$

$$\vec{I}_2 = \frac{\vec{V}_0}{\vec{Z}_2} = \frac{V_0}{R_2 - jX_C} = I_2 \angle \theta_2$$

$$\vec{I} = \vec{I}_1 + \vec{I}_2$$

$$= I_1 \angle \theta_1 + I_2 \angle \theta_2$$


$$= I_1 \cos \theta_1 + j I_1 \sin \theta_1 + I_2 \cos \theta_2 + j I_2 \sin \theta_2$$

$$\vec{I} = (I_1 \cos \theta_1 + I_2 \cos \theta_2) + j (-I_1 \sin \theta_1 + I_2 \sin \theta_2)$$

$$|I| = \sqrt{(I_1 \cos \theta_1 + I_2 \cos \theta_2)^2 + (-I_1 \sin \theta_1 + I_2 \sin \theta_2)^2}$$

$$\theta = \tan^{-1} \frac{(-I_1 \sin \theta_1 + I_2 \sin \theta_2)}{(I_1 \cos \theta_1 + I_2 \cos \theta_2)}$$
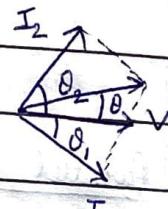
$$(I_1 \cos \theta_1 + I_2 \cos \theta_2)$$



* Power Components & Power factor

$$P = VI$$

$$V = V_m \sin \omega t \quad I = I_m \sin(\omega t - \theta)$$

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t - \theta)$$

$$= \frac{V_m I_m}{2} (2 \sin \omega t \sin(\omega t - \theta))$$

2

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} [\cos(\omega t - \omega t + \theta) - \cos(\omega t + \omega t - \theta)]$$

 $\sqrt{2} \quad \sqrt{2}$


$$= VI [\cos \theta - \cos(2\omega t - \theta)]$$

$$P_{av} = \frac{1}{T} \int_0^T P = \frac{1}{T} \int_0^T VI [\cos\theta - \cos(2\omega t - \theta)] dt$$

$$P = VI \cos\theta \rightarrow \text{active power (watts)}$$

$$S = VI$$
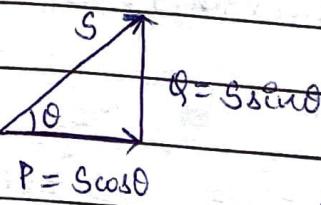
$$Q = VI \sin\theta \rightarrow \text{reactive power (VAR)}$$



Complex AC power

$$\vec{S} = S \angle \theta$$

$$= P + jQ$$

$$= VI^* \rightarrow \text{conjugate}$$

$$= V(I\angle\theta)^*$$

$$= VI \angle \theta$$

$$= \underbrace{VI \cos\theta}_P + j \underbrace{VI \sin\theta}_Q$$

use $\theta \rightarrow$ power factor
always +ve [0, 1]

lag RL circuit

lead RC circuit

Ques. (1) Let a series circuit consume 700 W at power factor of 0.707 lead with applied voltage $141.18 \text{V} (314t + 30)$. Find the circuit elements. Find current, voltage across each element in phasor and in instantaneous form. Calculate reactive power (VAR).

$$V(t) = 141.18 \text{V} (314t + 30)$$

$$P = 700 \text{ W} \quad pf = 0.707 \text{ lead}$$

$$\cos\theta = 0.707 = \frac{1}{\sqrt{2}}$$

$$\therefore \theta = 45^\circ$$

$$P = VI \cos \theta$$

$$V_{m1} = 141.1$$

$$\Rightarrow P_0 = 99.84 I \times 0.707$$

$$V = V_m / \sqrt{2} = 99.84 V$$

$$I = 9.92 A$$

$$Z = V = \underline{99.84} = 10.06 \Omega$$

$$I = 9.92$$

Leading current
 ∵ Capacitor is present
 So, required
 RC branch.

$$R = Z \cos \theta = 10.06 \times 0.707 = 7.11 \Omega$$



$$X_c = Z \sin \theta = 10.06 \times \sin 45^\circ = 7.11 \Omega$$

$$X_c = \perp$$

$$2\pi f C$$

$$C = \perp = \perp = 4.44 \times 10^{-4} F$$

$$2\pi f X_c = 3.14 \times 7.11$$

$$V_R = I R = 9.92 \times 7.11 = 70.53 V$$

$$V_c = I X_c = 9.92 \times 7.11 = 70.53 V$$

Phasor form

$$\vec{V} = 99.84 \angle 30^\circ$$

$$\vec{I} = 9.92 \angle (30 + 45^\circ) = 9.92 \angle 75^\circ$$

$$\vec{Z} = 10.06 \angle -45^\circ$$

$$\vec{V}_R = 70.53 \angle 75^\circ$$

$$\vec{V}_c = -j IX_c = -70.53 \angle 75^\circ - 90^\circ = 70.53 \angle -15^\circ$$

Instantaneous values

$$i = \sqrt{2} \times 9.92 \sin(314t + 75^\circ)$$

$$V_R = \sqrt{2} \times 70.53 \sin(314t + 75^\circ)$$

$$V_c = \sqrt{2} \times 70.53 \sin(314t - 15^\circ)$$

$$Q = VI \sin \theta$$

$$= 99.84 \times 9.92 \times \sin 45^\circ$$

$$Q = 700.32 \text{ VAR}$$

* Resonance in Series Circuit

$$I = \frac{V}{R + j(X_L - X_C)}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$X_L = \omega L = 2\pi f L$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

LC combination acts as short circuit.

max. current

resistive circuit

least impedance

$$X_L = X_C$$

$$\therefore Z = R$$


$$\theta = \tan^{-1} \frac{X_L - X_C}{R} = 0^\circ$$

$$\text{pf} = \cos \theta = \cos 0^\circ = 1$$

Circuit behaves as resistive circuit.

$$X_L = X_C$$


$$IX_L = IX_C$$

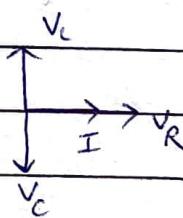

$$V_L = V_C$$

$$\therefore V = V_R$$

Ques-① A coil 'X' takes 2A at pf of 0.8 lagging with an applied potential difference of 10V. Second coil 'Y' takes 2A with a pf of 0.7 lagging and applied potential of 5V. What voltage will be required to produce a total current of 2A with coils X and Y in series. Find out the pf. of the combination.

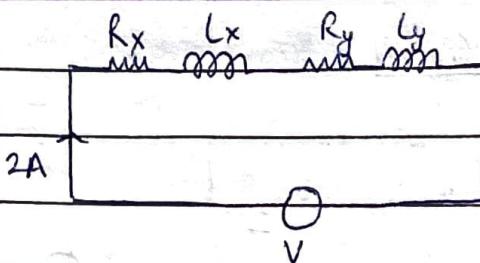Sol.

$$V_x = 10V$$

$$I_x = 2A$$

$$\text{pf}_x = 0.8 \text{ lag}$$

$$Z_x = \frac{V_x}{I_x} = \frac{10}{2} = 5\Omega$$

$$\cos\theta = \frac{R}{Z}$$

$$R_x = 5 \times 0.8 = 4\Omega$$

$$Z_x = \sqrt{R_x^2 + X_x^2}$$

$$X_x^2 = Z_x^2 - R_x^2$$

$$X_x = \sqrt{25 - 16} = 3\Omega$$

for series combination of 2 coils \Rightarrow

$$Z = \sqrt{(R_x + R_y)^2 + (X_x + X_y)^2}$$

$$= 7.48\Omega$$


as it is an

$$V = IZ = 2 \times 7.48 = 14.96V$$

inductive

$$\text{circuit (ff)} \quad \text{cos}\theta = \frac{R_x + R_y}{Z} = \frac{5 + 5}{7.48} = 0.768 \text{ lagging}$$

- (2) Find the capacitance which must be connected in series with a 100W, 110V lamp in order that the lamp may draw its normal current when the combination is connected to 230V, 50Hz supply.

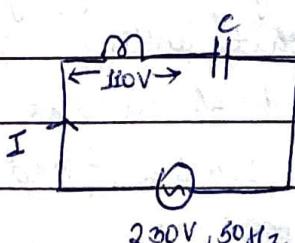Sol.

230V, 50Hz

Lamp \rightarrow resistive load

$$P = VI$$

$$I = \frac{100}{200} = 0.909A$$

~~200~~

$$C = 14.323 \text{ nF}$$

$$V^2 = V_R^2 + V_C^2$$

$$V_L = \sqrt{12100 + 52900} = 202V$$

$$X_C = \frac{V_L}{I} = \frac{202}{0.909} = 222.22\Omega$$

$$C = \frac{1}{2\pi f X_C} = 14.323 \text{ nF}$$

$$2\pi f X_C$$


13/12/20

* Quality factor (Q -factor)

$Q_1 \rightarrow$ least selective

$Q_2 \rightarrow$ medium selectivity

$Q_3 \rightarrow$ highest selectivity

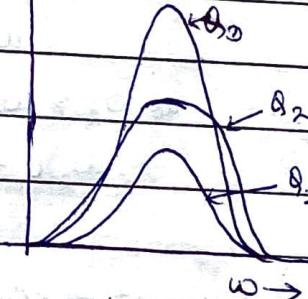

Q -factor relates the max. energy stored to energy dissipated per cycle of oscillation.

$$\text{Voltage magnification } Q = \frac{V_L}{V_R} = \frac{V_L}{V} = \frac{IX_L}{IR} = \frac{X_L}{R} = \frac{\omega_0 C}{R}$$

$$Q = \frac{V_C}{V_R} = \frac{V_C}{V} = \frac{IX_C}{IR} = \frac{X_C}{R} = \frac{1}{\omega_0 CR}$$

$$\text{Or } Q = \frac{1}{2} \cdot \frac{L I_0^2}{I^2 R} = \frac{\pi^2 L (\sqrt{2} I)^2}{I^2 R} = \frac{2\pi f L}{R} = \frac{\omega_0 L}{R}$$

Half Power Frequencies (ω_1, ω_2)

at ω_0 ,

$$I_{\max} = \frac{V_m}{R}$$


at ω_1, ω_2 ,

$$I = \frac{V_m}{\sqrt{2}R} = \frac{I_{\max}}{\sqrt{2}}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{2}R$$

$$\therefore (X_L - X_C)^2 = R^2$$
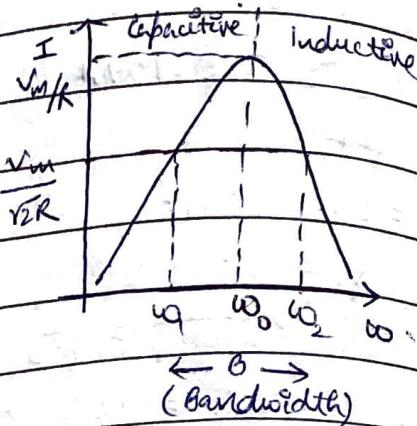
$$X_L - X_C = \pm R \Rightarrow \omega L - \frac{1}{\omega C} = \pm R$$



at $\omega_1 < \omega_0 \Rightarrow$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R$$

at $\omega_2 > \omega_0 \Rightarrow$

$$\omega_2 L - \frac{1}{\omega_2 C} = +R$$

$$LC\omega_1^2 + RC\omega_1 - 1 = 0$$

$$\omega_1^2 + \frac{R}{L}\omega_1 - \frac{1}{LC} = 0$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}}$$

2

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$B = \omega_2 - \omega_1 = \frac{R}{L}$$

$$\omega_1, \omega_2 = \pm \frac{1}{LC} = \omega_0^2$$

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$Q = \frac{\omega_0 L}{R} = \frac{\omega_0}{B}$$

$$\omega_1, \omega_2 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \mp \frac{w}{2Q}$$

when $Q \geq 10 \rightarrow$ High Q circuit

$$\text{then, } \omega_1 \approx \omega_0 - \frac{\omega_0}{2Q} \approx \omega_0 - \frac{B}{2} \quad \begin{matrix} \text{symmetric} \\ \text{about } \omega_0 \end{matrix}$$

$$\omega_2 \approx \omega_0 + \frac{\omega_0}{2Q} \approx \omega_0 + B$$

22/12/20

* Resonance in RLC Parallel Circuit

$$\vec{I}_m = \vec{I}_R + \vec{I}_L + \vec{I}_C$$

$$\vec{I}_R = \frac{V}{R}$$

$$\vec{I}_L = \frac{V}{jX_L}$$


$$\vec{I}_C = \frac{V}{-jX_C}$$

$$\vec{I}_m = \frac{V}{R} + \frac{V}{jX_L} - \frac{V}{jX_C}$$

$$\vec{I}_m = \vec{V} [G_1 + j(B_L - B_C)] = \vec{V} Y$$

$$B_C = \omega C$$

$$B_L = \frac{1}{\omega L}$$

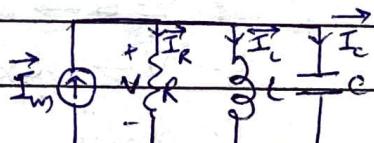

at resonance, $\omega f = 1$.

Circuit behaves as purely resistive.

Reactive component of admittance (Y) = 0

$$B_C - B_L = 0$$

$$B_C = B_L$$

at resonance, $\omega_0 C = \frac{1}{L}$

$$\omega_0 L$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$\omega < \omega_0 \Rightarrow B_L > B_C$ (Inductive)

$\omega = \omega_0 \Rightarrow B_C = B_L$ (Resistive)

$\omega > \omega_0 \Rightarrow B_C > B_L$ (Capacitive)

at resonance,

$$V = V_{\max} = I_m R$$

- $B_L = B_C$
- $Y = G \rightarrow \text{minimum}$
- $V \rightarrow \text{maximum}$
- Supply current passes through R
- $I_C = I_L$ (but not zero)
- parallel LC combination acts like open circuit
- $\vec{I}_m = \vec{I}_R, |\vec{I}_L| = |\vec{I}_C| \neq 0$
- $Q = \text{Current through } L/C$
Current through resistance
 $= \frac{I_L}{I_R} \text{ or } \frac{I_C}{I_R}$

$$Q = \frac{Y/X_L}{X/R} = \frac{R}{X_L} = \frac{R}{\omega_0 L}$$

$$\text{or } Q = \frac{Y/X_C}{X/R} = \frac{R}{X_C} = R\omega_0 C$$

Half Power Frequency


$$\sqrt{V} = \frac{V_{max}}{\sqrt{2}}$$

$$\Delta = IY \quad I = VY$$

$$Y = \frac{1}{R} + j(\omega C - \frac{1}{\omega L}) = \frac{\sqrt{2}}{R}$$

$$\omega_1 = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$
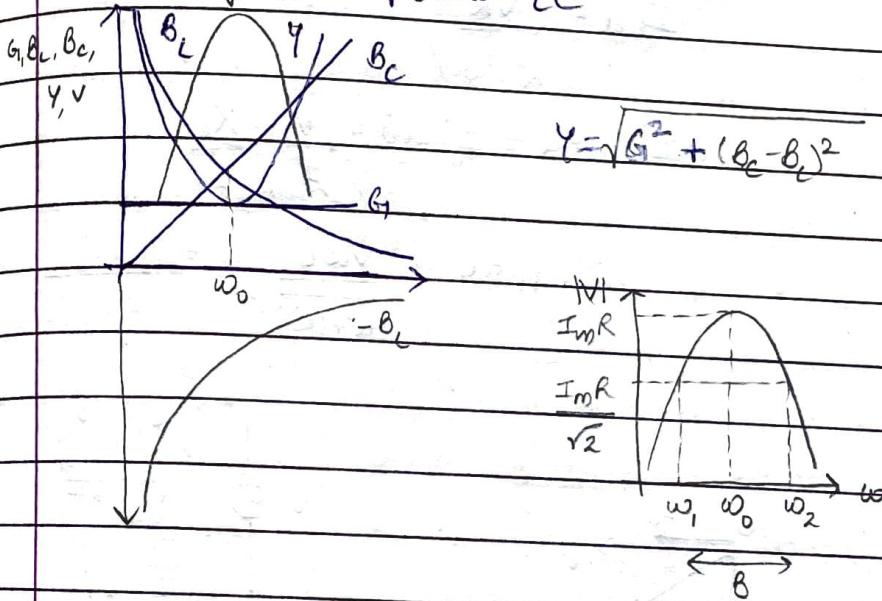
$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$



$$\beta = \omega_2 - \omega_1 = \pm \frac{\omega_0}{RC}$$

$$\omega_1, \omega_2 = \omega_0 \sqrt{1 + \left(\frac{1}{2\beta}\right)^2} \mp \frac{\omega_0}{2\beta}$$


24/12/20

* Power Factor Correction

Compensator is connected in parallel to load.

$$\vec{I} = \vec{I}_L + \vec{I}_C$$
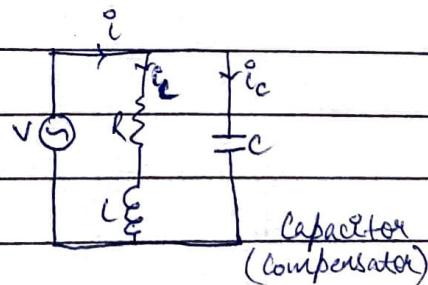
$$\vec{I}_L = \frac{\vec{V}}{R + j\omega L} = \frac{\vec{V}}{R + jX_L}$$




I_C

$$\vec{I}_C = \vec{V} = \frac{\vec{V}}{Z} \angle \theta$$

$Z \angle \theta$

$$Z = \sqrt{R^2 + (\omega C)^2}$$

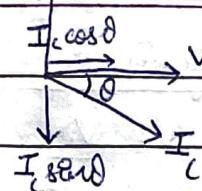

$$\theta = \tan^{-1} \left(\frac{\omega C}{R} \right)$$

$$\vec{V} = V \angle \theta$$




$$I_{\text{real}} = I_C \cos \theta = \frac{V}{Z} \cdot \frac{R}{Z}$$

$$= \frac{V}{\sqrt{R^2 + (\omega C)^2}} \cdot \frac{R}{\sqrt{R^2 + (\omega C)^2}}$$

$$I_{\text{real}} = \frac{VR}{R^2 + (\omega C)^2}$$


$$I_{\text{reactive}} = I_C \sin \theta = \frac{V}{Z} \cdot \frac{X_C}{Z}$$
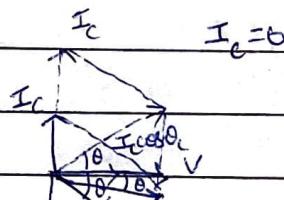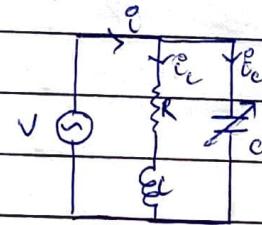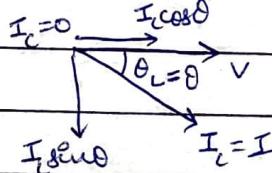
$$I_{\text{reactive}} = \frac{V \omega L}{\sqrt{R^2 + (\omega C)^2}} = \frac{V \omega L}{R^2 + (\omega C)^2}$$



$I \rightarrow$ total current $\rightarrow 0$ with V

$I_C \rightarrow 0$ with V

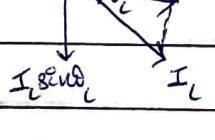

$\bullet I_C < I_C \sin \theta_L, \theta < \theta_L \rightarrow \text{lagging}$

$\bullet I_C = I_C \sin \theta_L, \theta = 0^\circ, I = I_C \cos \theta_L, p_f \rightarrow 1$

$\bullet I_C > I_C \sin \theta_L, p_f \rightarrow \text{leading}$


* Resonance in Tank Circuit

- unity pf
- supply frequency is varied

$$I_C = I_s \sin \theta_C$$

$$I_s = \frac{V}{X_C} = V \omega C$$
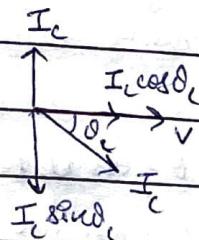
$$I_s \sin \theta_C = \frac{V \omega L}{R^2 + (\omega L)^2}$$



at resonance,

$$\frac{V \omega_s C}{I_s} = \frac{V \omega_s L}{R^2 + (\omega_s L)^2}$$

$$R^2 + (\omega_s L)^2 = L$$

C

$$\omega_s = \sqrt{\frac{1 - R^2}{LC}}$$

If R is very small \rightarrow approaches to 0.

$$\omega_s = \frac{1}{\sqrt{LC}}$$

Supply current,

$$I = I_s \cos \theta_C$$

$$= \frac{VR}{R^2 + (\omega_s L)^2}$$

$$= \frac{VR}{LC}$$

$$= \frac{V}{Z}$$

for tank circuit only

$$= \frac{V}{L/R_C}$$

$Z = \frac{L}{RC} \rightarrow$ dynamic impedance

Q-factor,

ratio of reactive to real factor of current $Q = \frac{I_C}{I} = \frac{I_C}{I_s \cos \theta_C} = \frac{\omega_s L}{R}$

as $I_C = I_s \sin \theta_C$

Ques. A single phase load of 5kW operates at a pf of 0.6 lagging. It is proposed to improve pf to 0.95 lagging by connecting a capacitor across the load. Calculate capacitor kVA rating.


Sol.

$$\theta = \cos^{-1} 0.95$$

$$\theta_c = \cos^{-1} 0.6$$

$$VI_L \cos \theta_c = VI \cos \theta = 5 \text{ kW}$$
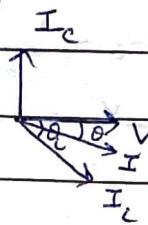
$$VI_L = \frac{5}{0.6} = 8.33 \text{ kVA}$$



$$pf = 0.6$$

$$\text{Reactive power} = VI_L \sin \theta$$

$$= 8.33 \sin(\cos^{-1} 0.6)$$

$$= 6.667 \text{ kVAR}$$

$$\text{New Reactive power demand} = VI \sin \theta$$

$$VI \cos \theta = 5$$

$$pf = 0.95$$

$$VI = \frac{5}{0.95} = 5.263 \text{ kVA}$$

$$\text{New Reactive power} = 5.263 \sin(\cos^{-1} 0.95)$$

$$= 1.6434 \text{ kVAR}$$

$$\text{Capacitor rating} = \text{Old reactive power demand} - \text{New reactive power demand}$$

$$= 6.667 - 1.6434$$

$$= \underline{\underline{5.0236 \text{ kVAR}}}$$

5/1/2021

#

Three-Phase System

- a 3-phase system is considered as three separate single phase systems displaced from each other by 120° .



$$V_R = V_m \sin(\omega t)$$

$$V_Y = V_m \sin(\omega t - 120^\circ)$$

$$V_B = V_m \sin(\omega t - 240^\circ) = V_m \sin(\omega t + 120^\circ)$$

* Interconnection of 3-phases

Neutral

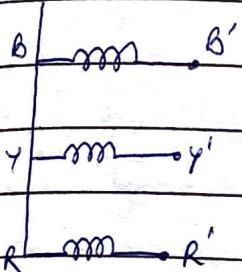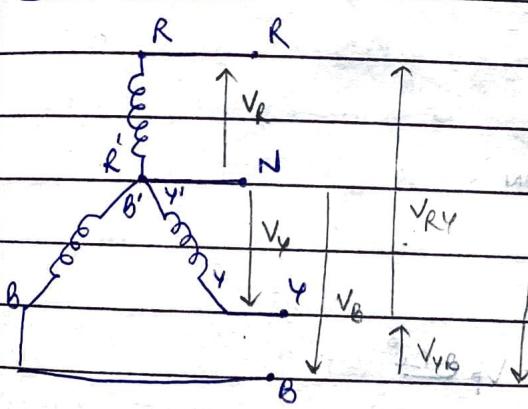Star Connection (Y-connection)

Phase voltage →

voltage b/w
neutral & coils



Line Voltage →

voltage b/w
two coils

$$I_L = I_P$$

↙ ↘

Line current Phase current

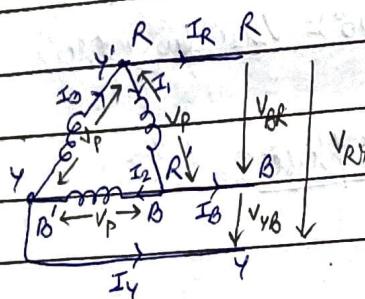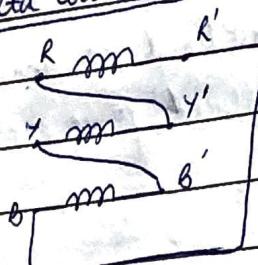Delta Connection

$$V_P = V_L$$

↓ →
 phase line
 voltage voltage

Star Connection

$$V_{RY} = V_R - V_Y$$

$$\text{or } V_{RN} - V_{YN}$$

$$\vec{V}_R = V_p \angle 0^\circ$$

$$\vec{V}_Y = V_p \angle 120^\circ$$

$$V_{RY} = V_p \angle 0^\circ - V_p \angle -120^\circ$$


$$= V_p [\cos 0^\circ + j \sin 0^\circ - (\cos (-120^\circ) + j \sin (-120^\circ))]$$

$$= V_p [1 + 0 - (-\frac{1}{2} - j\frac{\sqrt{3}}{2})]$$

$$= V_p [3/2 + \frac{\sqrt{3}}{2}j]$$

$$= \sqrt{3} V_p \angle 30^\circ$$

Line voltage
leads phase
voltage by
30°

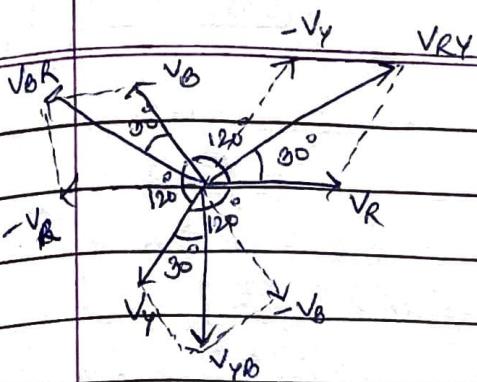

$$V_{YB} = \vec{V}_Y - \vec{V}_B = \sqrt{3} V_p (-90^\circ)$$

$$V_{BR} = \vec{V}_B - \vec{V}_R = \sqrt{3} V_p (-210^\circ) \text{ or } \sqrt{3} V_p (150^\circ)$$

4/1/22

* Delta Connection



$$\vec{I}_1 = \vec{I}_2 + \vec{I}_3$$

$$\vec{I}_2 = \vec{I}_1 - \vec{I}_3$$

$$\vec{I}_3 = \vec{I}_1 + \vec{I}_2$$

$$\vec{I}_1 = \vec{I}_2 - \vec{I}_3$$

$$\vec{I}_3 = \vec{I}_1 - \vec{I}_2$$

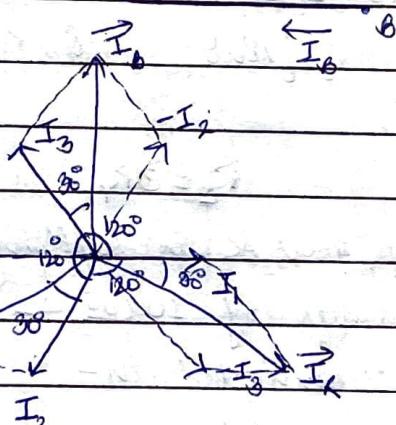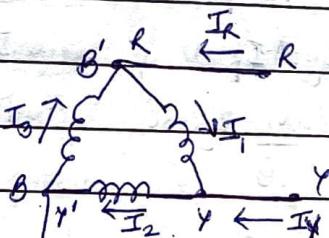

line
phase current
lags behind

phase current
by 30°

$$\vec{I}_1 = I_p \angle 0^\circ$$

$$\vec{I}_2 = I_p \angle -120^\circ$$

$$\vec{I}_3 = I_p \angle -240^\circ$$

$$\vec{I}_0 = \vec{I}_1 - \vec{I}_3$$

$$= I_p \angle 0^\circ - I_p \angle -240^\circ$$

$$= I_p [\cos 0 + j \sin 0^\circ - (\cos(-240^\circ) + j \sin(-240^\circ))]$$

$$= I_p [1 + 0 - (-\frac{1}{2} + 0.866j)]$$

$$= \sqrt{3} I_p \angle 30^\circ$$

$$\vec{I}_0 = \sqrt{3} I_p \angle 90^\circ$$

$$\vec{I}_4 = \sqrt{3} I_p \angle 150^\circ = \sqrt{3} I_p \angle 210^\circ$$

* Power in 3-phase

Single phase \rightarrow

$$P = VI \cos \theta$$

$$Q = VI \sin \theta$$

Three-phase \rightarrow

$$P = 3V_p I_p \cos \theta$$

$$Q = 3V_p I_p \sin \theta \rightarrow \text{phase voltage}$$

angle b/w
and phase current.

Star

$$V_L = \sqrt{3} V_p$$

$$I_L = I_p$$

$$P = 3 \cdot \frac{V_L \cdot I_L \cos \theta}{\sqrt{3}}$$

$$= \sqrt{3} V_L I_L \cos \theta$$

$$Q = \sqrt{3} V_L I_L \sin \theta$$

Delta

$$V_L = V_p$$

$$I_L = \sqrt{3} I_p$$

$$P = 3 \cdot \frac{V_L \cdot I_L \cos \theta}{\sqrt{3}}$$

$$= \sqrt{3} V_L I_L \cos \theta$$

$$Q = \sqrt{3} V_L I_L \sin \theta$$

$$P_\Delta = 3P_Y$$

e.g. a 3- ϕ , 400V AC is supplying a load formed by 3 impedances of $10(30^\circ) \Omega$. find power when load is connected in-


a) star b) delta

STAR

$$P = 3V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$V_L = 400V$$
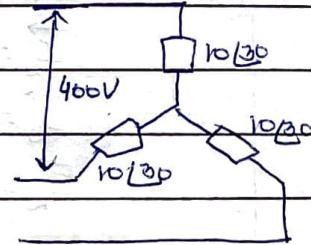
$$V_p = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230V$$



$$I_p = \frac{V_p}{Z} = \frac{230}{10(30)} = 23 \angle -30^\circ$$

$$P_Y = 3 \times 230 \times 23 \times \cos(-30^\circ)$$

DELTA

$$V_L = V_p$$


$$I_p = \frac{V_p}{Z} = \frac{400}{\sqrt{3}} \angle -14^\circ$$

$$P = 3 \times 400 \times 40 \cos(-30^\circ)$$

$$\therefore P_\Delta = 3P_Y$$

Power Measurement

- 3 phase system
- (i) 3 wattmeter \rightarrow balanced & unbalanced
 - (ii) 2 wattmeter \rightarrow balanced & unbalanced
 - (iii) 1 wattmeter \rightarrow balanced

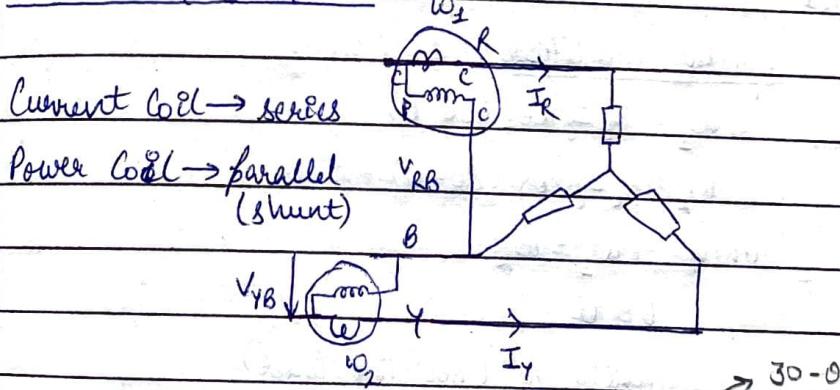* Two Wattmeter Method

$$W_1 = I_R V_{RB} \cos(\text{angle b/w } I_R \text{ & } V_{RB})$$

$$W_2 = I_Y V_{YB} \cos(\text{angle b/w } I_Y \text{ & } V_{YB})$$

$30+0$


$$W_1 = I_R V_{RB} \cos(30-0)$$

$$W_2 = I_Y V_{YB} \cos(30+0)$$

$$\begin{cases} I_R = I_Y = I_p = I \\ V_{RB} = V_{YB} = V_C \end{cases}$$

$$W_1 = V_C I_C \cos(30-0)$$

$$W_2 = V_C I_C \cos(30+0)$$

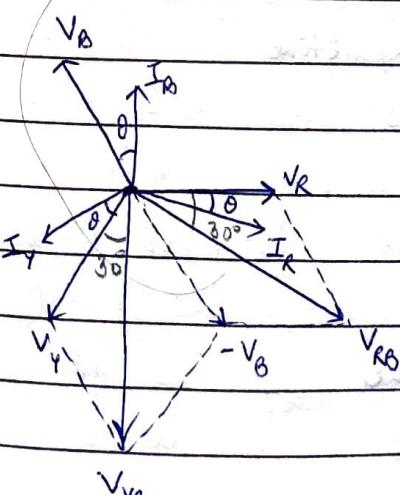

$$\begin{aligned}\omega_1 + \omega_2 &= V_L I_L [120\cos(30^\circ - \theta) + j120\sin(30^\circ - \theta)] \\ &= \frac{\sqrt{3}}{2} V_L I_L \cos(\theta)\end{aligned}$$

$$(\omega_1 + \omega_2 = \frac{\sqrt{3}}{2} V_L I_L \cos \theta)$$

$$(\omega_2 - \omega_1 = \frac{\sqrt{3}}{2} V_L I_L \sin \theta)$$

$$\tan \theta = \frac{\omega_2 - \omega_1}{\sqrt{3} \cdot \omega_1 + \omega_2}$$

$$\theta = \tan^{-1} \left[\sqrt{3} \frac{(\omega_2 - \omega_1)}{(\omega_1 + \omega_2)} \right]$$

$$\cos \theta = \text{pf} = \cos \left[\tan^{-1} \left[\sqrt{3} \frac{(\omega_2 - \omega_1)}{(\omega_1 + \omega_2)} \right] \right]$$

3/3/22

Special Conditions

$$\omega_1 = V_L I_L \cos(30^\circ - \theta)$$

$$\omega_2 = V_L I_L \cos(30^\circ + \theta)$$

① when $\omega_1 = \omega_2$

$$\theta = 0^\circ$$

∴ unity pf (Resistive load)

② when one wattmeter will read zero

$$\theta = 60^\circ$$

$\omega_2 = 0 \rightarrow$ inductive

$\omega_2 = 0 \rightarrow$ capacitive

pf is 0.5

③ when $\theta = 90^\circ$

zero pf

$$\omega_2 = -\omega_1$$

$$\therefore \omega_1 + \omega_2 = 0$$

(4) when a wattmeter will read -ve.

$$60^\circ < \theta < 90^\circ$$

$$0 < \cos \theta < 0.5$$

Ques. ① Three inductive coils each with a resistance of 15Ω and an inductance of $0.03H$ are connected in (i) star (ii) delta, to 3-phase, $400V$; $50Hz$ supply. Calculate -

(a) phase current and line current

(b) total power absorbed

Sol. (i) STAR

$$V_p = V_L = \frac{400}{\sqrt{3}} = 230.94V$$

$$I_p = \frac{V_p}{Z_p}$$


$$Z_p = \sqrt{R_p^2 + X_p^2} = 17.72\Omega$$

$$\therefore [X_p = 2\pi f L] \quad \cos \theta = \frac{R_p}{Z_p} = 0.846$$

$$I_p = 13.03A$$

$$I_L = I_p = 13.03A$$
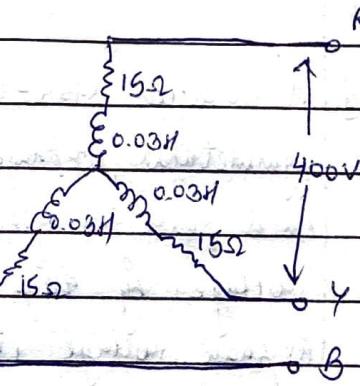
$$P = 3V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta = 637.22 W$$



(ii) DELTA

$$Z_p = 17.72\Omega$$

$$\cos \theta = 0.846$$

$$V_p = V_L = 400V$$

$$I_p = \frac{V_p}{Z_p} = \frac{400}{17.72} = 22.57A$$

$$I_i = \sqrt{3} I_p = 39.1A$$

$$P = 22913.1W$$

- (2) Two wattmeters connected to measure the power input to a 3-phase circuit indicated 15 kW and 1.5 kW respectively, the latter reading being obtained after reversing the current coil connections. Calculate the power and pf of load.

$$W_1 = 15 \text{ kW}$$

$$W_2 = -1.5 \text{ kW}$$

$$P = W_1 + W_2 = 13.5 \text{ kW}$$

$$\text{pf} = \cos \theta = \frac{\text{real}}{\text{app}} = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = 0.427$$

- (3) A balanced star-connected load is supplied from a symmetrical, 3-phase, 440V, 50 Hz supply. The current in each phase is 20A and lags behind its phase voltage by 40° . Calculate:

- (i) phase voltage (ii) load parameters (iii) total power
- (iv) reading of 2 wattmeter connected in load circuit to measure total power.

$$V_L = 440 \text{ V}$$

$$I_P = 20 \text{ A}$$

$$\theta = 40^\circ$$

$$(i) V_p = 254.04 \text{ V}$$

$$(ii) Z_p = \frac{V_p}{I_p} = 12.702 \Omega$$

$$\cos 40^\circ = \frac{R_p}{Z_p} \Rightarrow R_p = Z_p \cos 40^\circ = 9.73 \Omega$$

$$\sin 40^\circ = \frac{X_p}{Z_p} \Rightarrow X_p = Z_p \sin 40^\circ = 6.16 \Omega$$

$$2\pi f L = X_p$$

$$L = \frac{6.16}{2 \times 3.14 \times 50} = 25.99 \text{ mH}$$

$$P = 3 V_p I_p \cos \theta$$

$$= 11.675 \text{ kW}$$

$$\omega_1 + \omega_2 = 11.675 \text{ kW}$$

$$\omega_1 = V_i I_i \cos (30 - \theta) = 8.668 \text{ kW}$$

$$\omega_2 = V_i I_i \cos (30 + \theta) = 3.008 \text{ kW}$$

8/2/21 Ch.3 - Magnetic Circuits

$$\int B \, dl = NI$$

$$B = \mu H$$

$$\therefore \int H \, dl = I$$

Magnetic circuit consists of mainly iron paths of specified geometry.


Core \rightarrow ferromagnetic materials \rightarrow high permeability

magnetic

flux

density


$$B = \frac{\phi}{A_c}$$

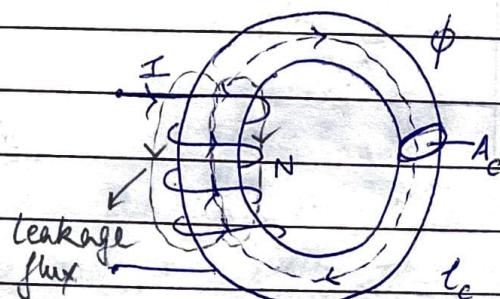

Magnetomotive Force (MMF) \rightarrow

$$MMF = NI = f$$

Amperes turns

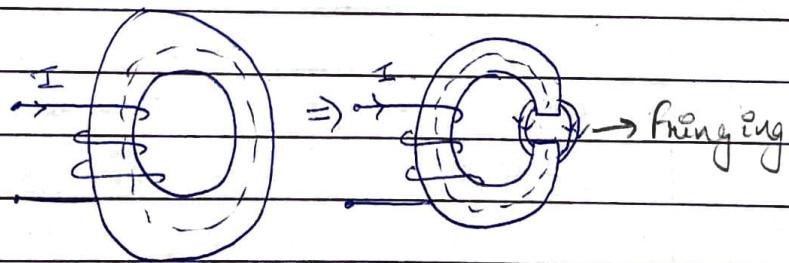

magnetic field

$$H = \frac{mif}{l}$$

No air gap

Air gap

Reluctance \rightarrow

$l_c \rightarrow$ mean circumference

$A_c \rightarrow$ cross-sectional area

$N \rightarrow$ no. of turns

Flux = flux density \times cross-sectional area

$$\phi = BA_c - \textcircled{1}$$

$$\text{MMF} = Hl_c - \textcircled{2}$$

$$B = M\mu$$

$$= M_0 M_u H$$

$$H = \frac{B}{M_0 H_u}$$

$$M_0 H_u$$

$$\text{MMF} = \frac{B}{M_0 H_u} l_c = \frac{\phi l_c}{A_c M_0 H_u}$$

$$\phi = \frac{\text{MMF}}{R}$$

$$\frac{l_c}{A_c M_0 H_u} \rightarrow \begin{array}{l} \text{Reluctance} \\ \text{SIR} \end{array}$$


$$\phi = \frac{f}{R}$$

reluctance R
the opposition offered to the flow of flux

$$R = \frac{l_c}{M_0 N_s A_c}$$

for air gap, $H_u = 1$

$$H_0 = 4\pi \times 10^{-7}$$

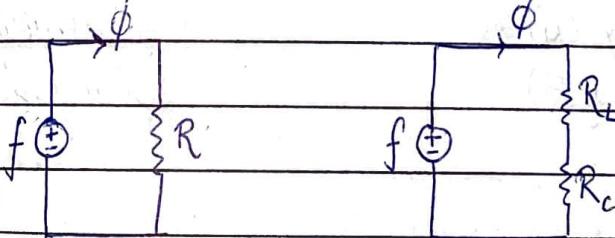


The equivalent
of these is no
air gap

The equivalent
of these is
air gap

* Analogy

Magnetic Circuit

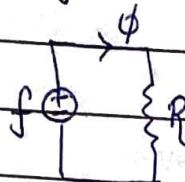

$$\phi = \frac{f}{R}$$

$$R = \frac{l}{A}; M = M_0 H_A$$

Source: Magnetomotive force

Response: flux

Reluctance

Magnetic flux density

$$B = \frac{\phi}{A}$$


Magnetic field (H)

$$B = \mu H$$

Permeability (μ)

Permeance (P)

Electric Circuit

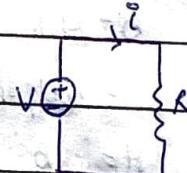

$$i = \frac{V}{R}$$

$$R = \frac{\rho l}{A}$$

Electromotive force

Current

Resistance

Current density

$$j = \frac{i}{A}$$



Electric field (E)


$$j = \sigma E$$

Conductivity (σ)

Conductance (G)

* Air gap

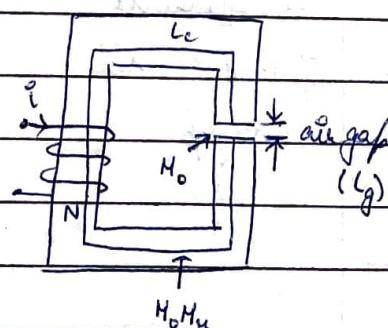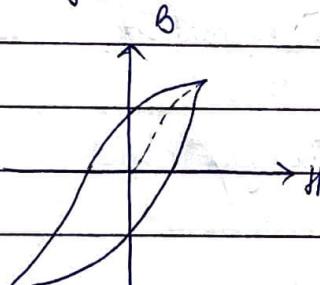

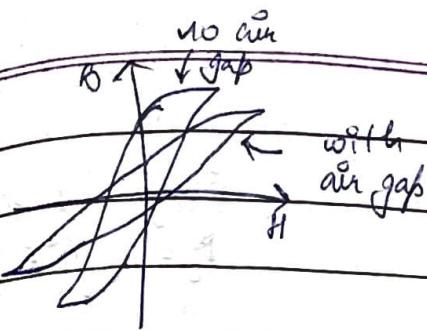

$$f = H_g L_g + H_c L_c$$


$$= \phi R_g + \phi R_c$$

$$= \phi [R_g + R_c]$$

$$R = R_g + R_c$$




$$\phi = \phi_1 + \phi_2$$

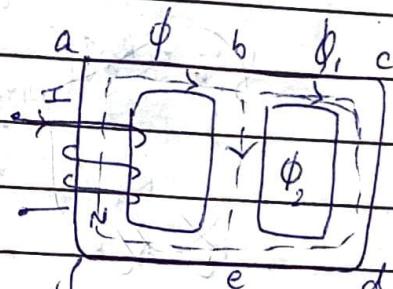

$$R_{refab} \rightarrow \phi$$



$$R_{bc} \rightarrow \phi_2$$

$$R_{bcde} \rightarrow \phi_1$$

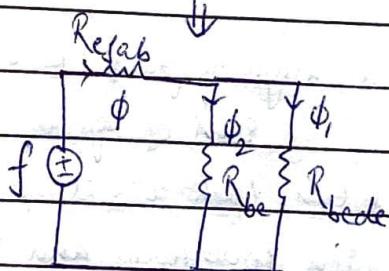

$$f = \phi R_{refab} + \phi_1 R_{bcde}$$

$$f = \phi R_{refab} + \phi_2 R_{bc}$$

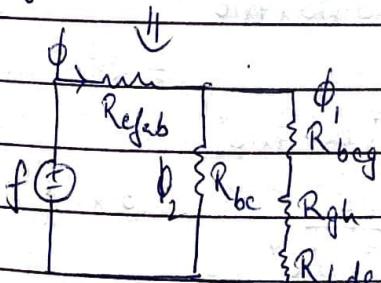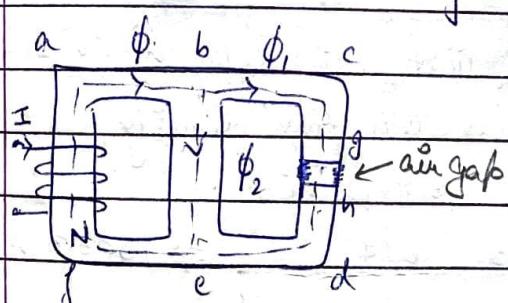

$$f = \phi R_{refab} + \phi_1 [R_{bc} + R_{gh} + R_{hde}]$$

* Core loss

Hysteresis loss \propto Eddy current loss \propto Eman's constant \times Frequency \times Eddy Current loss

$$P_h = k_h f B_m^n \rightarrow \text{max. flux density}$$

$$P_e = k_e f^2 B_m^2$$

$$\text{Frequency } P_o = P_h + P_e$$

$$V = 4.44 f N \phi_m = 4.44 f N B_m A_c$$

$$B_m = \frac{V}{A_c}$$


$$4.44 f N A_c$$

$$P_h = k_h f \left(\frac{V}{4.44 f N A_c} \right)^n$$

$$= K_h f^{1-n} V^n$$

$$P_e = K_e V^2$$

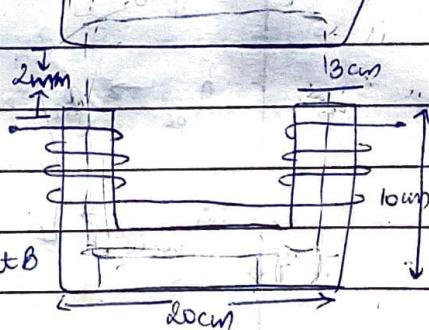$\leftarrow 17\text{cm} \rightarrow$ Part A



Ques. Q) A magnetic frame is built

up of iron of square cross-section. Each coil is wound with 1000 turns and the

exciting current is 1A.

$$H_x (A) = 1000$$

$$H_y (B) = 1200$$

Calculate - (i) R_A (ii) R_B (iii) R_g (both) (iv) total R

(v) MMF (vi) flux (vii) flux density

SOL

$$A_c = 3 \times 3 = 9 \text{ cm}^2 = 9 \times 10^{-4} \text{ m}^2$$

$$(i) R_A = \frac{l}{M_0 H_x A} = \frac{0.17}{4\pi \times 10^{-7} \times 10^3 \times 9 \times 10^{-4}} = 150813 \text{ AT/wb}$$

$$(ii) R_B = \frac{l}{M_0 H_y A} = \frac{0.34}{4\pi \times 10^{-7} \times 1200 \times 9 \times 10^{-4}} = 256521.6 \text{ AT/wb}$$

$$(iii) R_g = \frac{l_g}{M_0 A_c} = \frac{0.1 \times 10^{-3}}{4\pi \times 10^{-7} \times 9 \times 10^{-4}} = 3.5 \times 10^6 \text{ AT/wb}$$

$$(iv) R = R_A + R_B + R_g = 3.94 \times 10^6 \text{ AT/wb}$$


$$(v) mmf = NI = 8000 \times 1 = 8000 \text{ AT}$$

$$(vi) \text{ flux, } \phi = \frac{mmf}{R} = \frac{8000}{3.94 \times 10^6} = 5.08 \times 10^{-4} \text{ wb}$$

$$(vii) \frac{B}{A_c} = \frac{\phi}{A_c} = \frac{5.08 \times 10^{-4} \text{ wb}}{9 \times 10^{-7} \text{ m}^2} = 0.564 \text{ wb/m}^2$$


$\leftarrow 2 \times 50 \rightarrow 2 \times 50 \rightarrow 2 \rightarrow$

Ques. 2

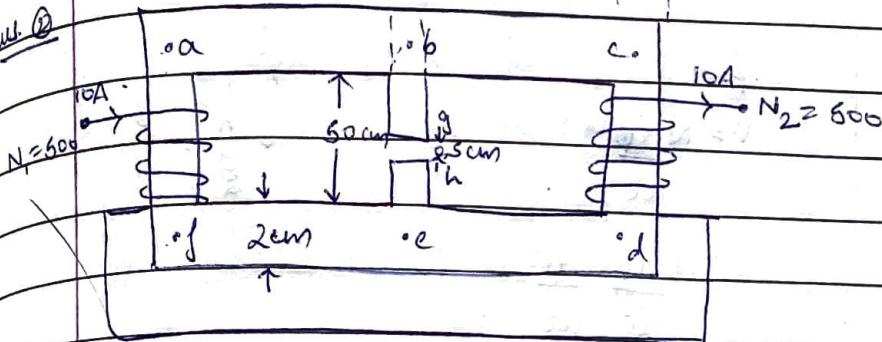

$$M_x = 1200$$

$$\phi, B, H$$

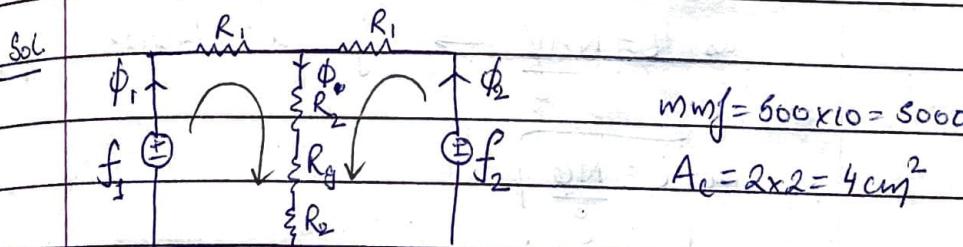

$$R = R_{\text{core}} = R_{\text{back}} = \frac{l}{H_0 M_x A_c} = \frac{156 \times 10^{-2}}{4 \pi \times 10^{-7} \times 4 \times 10^6 \times 1200} = 2.5863 \times 10^6$$

$$R_2 = R_{\text{fg}} = \frac{25.75 \times 10^{-2}}{4 \pi \times 10^{-7} \times 1200 \times 4 \times 10^6} = 5.12 \times 10^{-4} = 4.26 \times 10^5$$

$$R_g = R_{\text{gh}} = \frac{0.5 \times 10^{-2}}{4 \pi \times 10^{-7} \times 1200 \times 4 \times 10^6} = 9.94 \times 10^6$$

$$\phi = \phi_1 + \phi_g$$

$$f_1 = \phi_1 R_1 + \phi_g (2R_2 + R_g) = 5000$$

$$f_2 = \phi_2 R_2 + \phi_g (2R_2 + R_g) = 5000$$

$$\phi = \text{wb}$$

$$B_g = \frac{\phi}{A} = \text{wb/m}^2 \quad H_g = \frac{B_g}{M_0} = \text{AT/m}^2$$

14/1/21

* Electromagnetic Induction

$$V = -N \frac{d\phi}{dt}$$

* Self Inductance

$$\phi \propto i$$

$$V = N \frac{d\phi}{dt}$$

$$= N \frac{d\phi}{di} \cdot \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

as $L = N \frac{d\phi}{dt}$ \rightarrow self inductance

$$\text{or } L = \frac{N\phi}{i}$$



* Mutual Inductance

$$V_1 = V_{1S} + V_{1M}$$


$$V_2 = V_{2S} + V_{2M}$$

$$V_{1S} = N_1 \frac{d\phi_1}{dt} = L_1 \frac{di_1}{dt}$$

$$V_{2S} = N_2 \frac{d\phi_2}{dt} = L_2 \frac{di_2}{dt}$$

$$V_{1M} = N_1 \frac{d\phi_2}{dt} \rightarrow \text{flux produced by } i_2 \text{ linking with coil 1}$$

$$= M_{12} \frac{di_2}{dt}$$

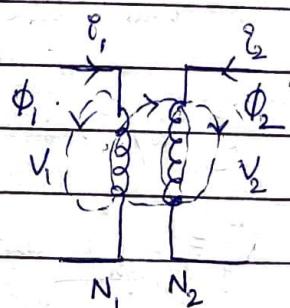

$$M_{12} = N_1 \frac{d\phi_1}{dt}$$



$$V_{2m} = N_2 \frac{d\phi_2}{dt}$$

$$= M_{21} \frac{di_1}{dt} = M \frac{de_1}{dt}$$

$$[M_{21} = N_2 \frac{d\phi_{12}}{dt}]$$

$$\therefore M_{12} = M_{21} = M$$

* Dot Convention

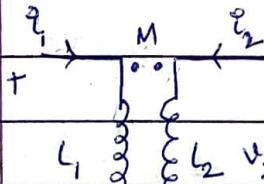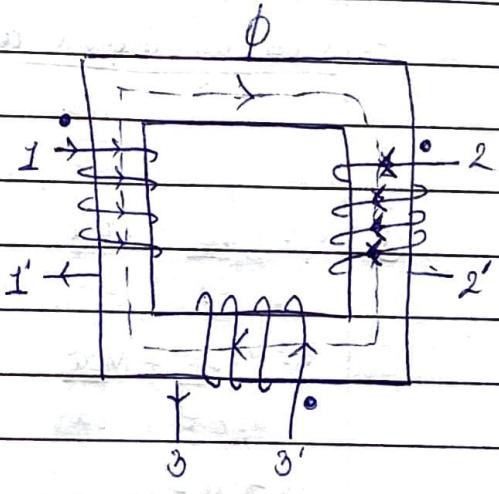


$$v_1 = L_1 \frac{de_1}{dt} + M \frac{de_2}{dt}$$


current
is
entering
the dot

$$v_2 = L_2 \frac{de_2}{dt} + M \frac{de_1}{dt}$$

current
is leaving
the dot

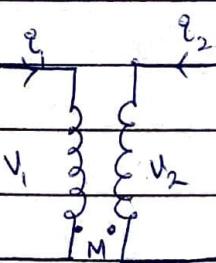

(Same equations)

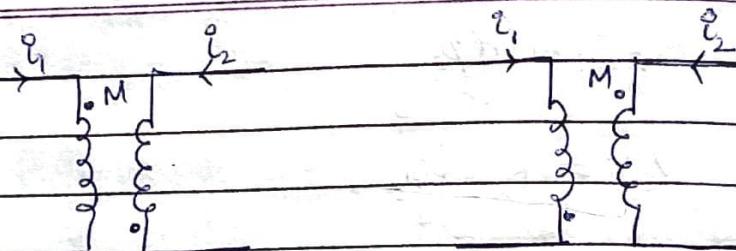

$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

* Mutually Coupled coils connected in series

$$\textcircled{1} \quad v_1 = L_1 \frac{de}{dt} + M \frac{de}{dt}$$

$$v_2 = L_2 \frac{de}{dt} + M \frac{de}{dt}$$

$$v = v_1 + v_2$$

$$= L_1 \frac{de}{dt} + M \frac{de}{dt} + L_2 \frac{de}{dt} + M \frac{de}{dt}$$

$$v = (L_1 + L_2 + 2M) \frac{de}{dt}$$

$$= L_{eq} \frac{de}{dt}$$

$$L_{eq} = L_1 + L_2 + 2M$$

$$\textcircled{2} \quad v = v_1 + v_2$$

$$v_1 = L_1 \frac{de}{dt} - M \frac{de}{dt}$$

$$v_2 = L_2 \frac{de}{dt} - M \frac{de}{dt}$$

$$v = (L_1 + L_2 - 2M) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$

$$L_{eq} = L_1 + L_2 - 2M$$

$$L_{eq} = L_1 + L_2 \pm 2M$$

16/11/21

* Mutually Coupled parallel coils

→ Cumulative


→ Differential

Cumulative


$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

$$\epsilon = \epsilon_1 + \epsilon_2 - ①$$

$$v = L_{eq} \frac{di}{dt}$$

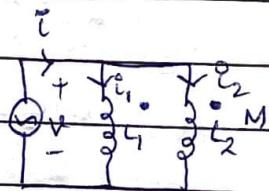
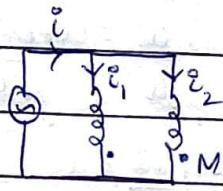
$$v = L_1 \frac{d\epsilon_1}{dt} + M \frac{d\epsilon_2}{dt}$$



$$v = L_2 \frac{d\epsilon_2}{dt} + M \frac{d\epsilon_1}{dt}$$

Differentiating - ①

$$\frac{di}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} - ②$$

$$L_{eq} \frac{di}{dt} = v = L_1 \frac{d\epsilon_1}{dt} + M \frac{d\epsilon_2}{dt} = L_2 \frac{d\epsilon_2}{dt} + M \frac{d\epsilon_1}{dt}$$

$$\Rightarrow L_1 \frac{d\epsilon_1}{dt} - M \frac{d\epsilon_1}{dt} = L_2 \frac{d\epsilon_2}{dt} - M \frac{d\epsilon_2}{dt}$$

$$\Rightarrow (L_1 - M) \frac{d\epsilon_1}{dt} = (L_2 - M) \frac{d\epsilon_2}{dt}$$

$$\Rightarrow \frac{d\ddot{\theta}_2}{dt} = \left(\frac{L_1 - M}{L_2 - M} \right) \frac{d\ddot{\theta}_1}{dt}$$

$$\text{or } \Rightarrow \frac{d\ddot{\theta}_1}{dt} = \left(\frac{L_2 - M}{L_1 - M} \right) \frac{d\ddot{\theta}_2}{dt}$$

$$\text{in (2)} \Rightarrow \frac{d\ddot{\theta}}{dt} = \frac{d\ddot{\theta}_1}{dt} + \left(\frac{L_1 - M}{L_2 - M} \right) \frac{d\ddot{\theta}_2}{dt}$$

$$\Rightarrow \frac{d\ddot{\theta}}{dt} = \frac{d\ddot{\theta}_1}{dt} \left[1 + \frac{L_1 - M}{L_2 - M} \right]$$

$$\Rightarrow \frac{d\ddot{\theta}}{dt} = \frac{d\ddot{\theta}_1}{dt} \left[\frac{L_1 + L_2 - 2M}{L_2 - M} \right]$$

$$\Rightarrow \frac{d\ddot{\theta}_1}{dt} = \left[\frac{L_2 - M}{L_1 + L_2 - 2M} \right] \frac{d\ddot{\theta}}{dt}$$

$$\frac{d\ddot{\theta}_2}{dt} = \left[\frac{L_1 - M}{L_1 + L_2 - 2M} \right] \frac{d\ddot{\theta}}{dt}$$

$$\text{Let } \frac{d\ddot{\theta}}{dt} = L_2 \frac{d\ddot{\theta}_2}{dt} + M \frac{d\ddot{\theta}_1}{dt}$$



$$\text{Let } \frac{d\ddot{\theta}}{dt} = L_2 \left[\frac{L_1 - M}{L_1 + L_2 - 2M} \right] \frac{d\ddot{\theta}}{dt} + M \left[\frac{L_2 - M}{L_1 + L_2 - 2M} \right] \frac{d\ddot{\theta}}{dt}$$

$$\text{Let } \underline{\underline{L_{eq}}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$


$$\therefore \boxed{L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}}$$

Differential

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

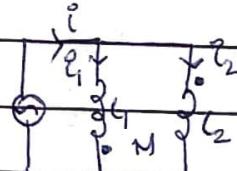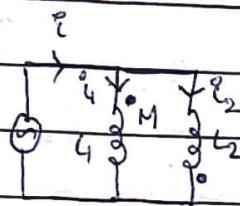* Coefficient of Coupling (k)

$$M_{12} = N_1 \frac{d\phi_{21}}{di_2}$$

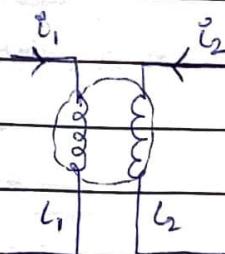

$$\Rightarrow M_{12} = N_1 \underline{\phi_{21}}$$

$$M_{21} = N_2 \frac{\phi_{12}}{i_1}$$

$$\begin{cases} \phi_{21} = k_2 \phi_2 \\ \phi_{12} = k_1 \phi_1 \end{cases}$$

$$M_{12} = N_1 \frac{k_2 \phi_2}{i_2} \quad \textcircled{1}$$

$$M_{21} = N_2 \frac{k_1 \phi_1}{i_1} \quad \textcircled{2}$$

$$M_{12} = M_{21} = M$$

(1) \times (2)

$$\frac{M^2}{L_1 L_2} = \frac{N_1 N_2 k_1 k_2 \phi_1 \phi_2}{L_1 L_2}$$


$$= k_1 k_2 \frac{N_1 \phi_1}{L_1} \cdot \frac{N_2 \phi_2}{L_2}$$

$$M^2 = k_1 k_2 \cdot L_1 \cdot L_2$$

$$[k_1 = k_2 = k]$$

$$M^2 = k^2 L_1 L_2$$

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

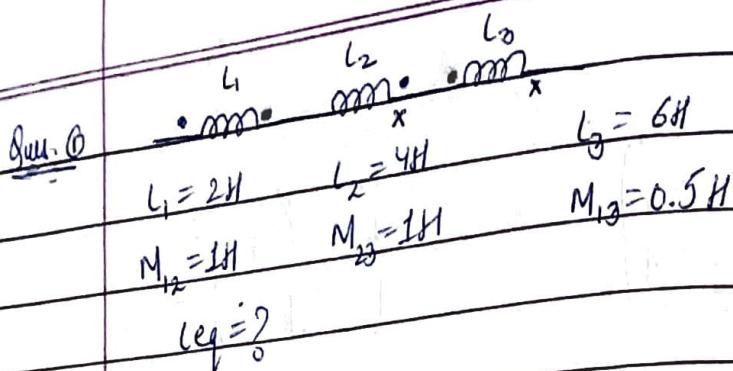Sol.

- ② The combined inductance of 2 coils connected in series is $0.6H$ & $0.4H$ depending upon ^{relative} direction of currents in the coils. If one of the coils, when isolated has self inductance of $0.15H$ then find
- mutual inductance
 - coefficient of coupling

Sol.

$$0.6 = 0.15 + L_2 + 2M$$

$$0.4 = 0.15 + L_2 - 2M$$

$$1 = 0.3 + 2M$$

$$0.35 = L_2$$

$$0.6 = 0.5 + 2M$$

$$M = 0.05H$$

$$k = \frac{0.05}{\sqrt{0.35 \times 0.15}} = 0.218$$


Ch. 4 - Transformers

Transformer


- It is a static device
- Working Principle: Electromagnetic Induction
- Transfer of power from one electric circuit to another.

Winding of Transformer

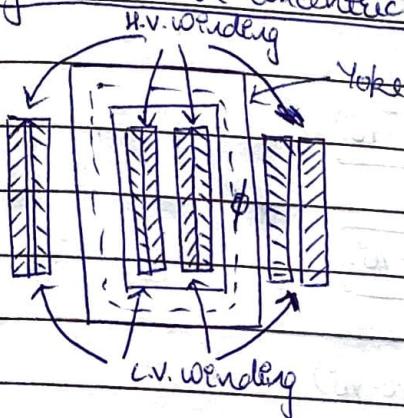Cylindrical or Concentric Winding (Core Type)



Sandwich or Disc Winding (Shell Type)
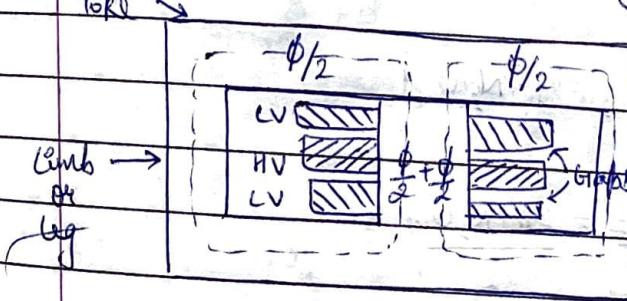
# Ideal Transformer

1. The winding resistances are zero.
2. There is no leakage flux \rightarrow leakage reactance is zero.
3. There is no core loss. [$P_h + P_e \rightarrow$ neglected].

hysteresis loss \downarrow eddy current loss


4. Negligible magnetizing current to establish the working flux. (Permeability = μ_0)

- N due
to Lenz's law

$$e_1 = -N_1 \frac{d\phi}{dt}$$

$$e_2 = -N_2 \frac{d\phi}{dt}$$

$$\boxed{\phi = \phi_m \sin \omega t}$$

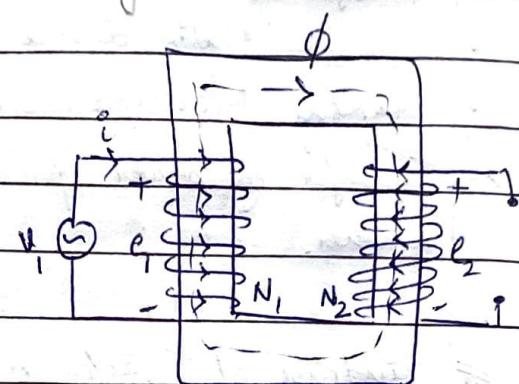

$$e_1 = -N_1 \phi_m \omega \cos \omega t$$

$$e_1 = N_1 \phi_m \omega (-\cos \omega t)$$

$$\boxed{e_1 = N_1 \phi_m \omega \sin(\omega t - 90^\circ)}$$

$$\boxed{e_2 = N_2 \phi_m \omega \sin(\omega t - 90^\circ)}$$

$$e_2 = N_2 \phi_m 2\pi / \lambda m (\omega t - 90^\circ)$$

$$= 2\pi / N_2 \phi_m \sin(\omega t - 90^\circ)$$

$$e_2 = E_{m2} \sin(\omega t - 90^\circ)$$

$$\therefore [E_{max2} / E_{m2}]^{\text{by}} = 2\pi / N_2 \phi_m$$

$$E_2 = E_{max2} = \frac{2\pi / N_2 \phi_m}{\sqrt{2}}$$

$$\boxed{E_2 = 4.44 / N_2 \phi_m}$$

ratio value

$$\boxed{E_1 = 4.44 / N_1 \phi_m}$$

$$\frac{V_1}{V_2} = \frac{E_1}{E_2} = \frac{N_1}{N_2} \rightarrow \text{turns ratio}$$

$$\therefore \begin{cases} V_1 = E_1 \\ V_2 = E_2 \end{cases}$$

* Phasor for Ideal Transformer on No Load

→ magnetizing current

is negligible

$$M_H \rightarrow \infty$$

$V_1 = E_1$ (same magnitude,
opp. dir.)




* Ideal Transformer on Load

$$I_2 \rightarrow \phi_2$$

$$\phi \rightarrow \text{opposing } \phi$$

$$\phi \rightarrow \phi - \phi_2$$

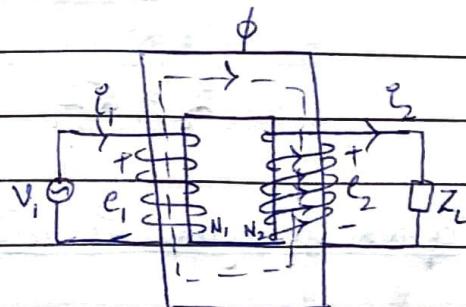

$$I_2 N_2 = N_1 I_1'$$

$$N_1 I_1 \rightarrow \text{magf}$$

$$\phi_2 = \frac{I_2 N_2}{R_c}$$

$$\frac{N_1 I_1}{N_2 I_2} = \phi$$

wire reluctance

$$\frac{I_2}{I_1'} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

$$\phi_n = \phi - \phi_2 + \phi_1$$

equal in magnitude

in ideal cond

but opposite dir

$$I_1' = I_1$$


$$V_1 = -E_1$$

$$I_2' = I_2 \frac{N_2}{N_1}$$

In ideal Transformer,

$$I_2' = I_2$$

$$I_2 = I_2'$$

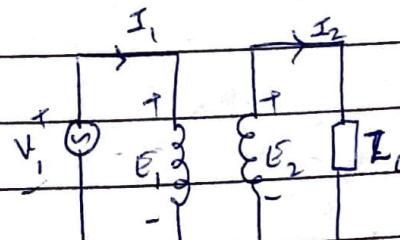

$$\text{loss} = I_2^2 Z_L$$

Equivalent of Ideal
Transformer

Equivalent referred to primary


$$\frac{V_1}{V_2} = a = \frac{I_2}{I_1}$$

$$I_1 = \frac{I_2}{a}$$


$$\text{loss} = Z'_L \times \left(\frac{I_2}{a} \right)^2$$

$$Z'_L \left(\frac{I_2}{a} \right)^2 = Z_L I_2^2$$

$$Z'_L = a^2 Z_L$$

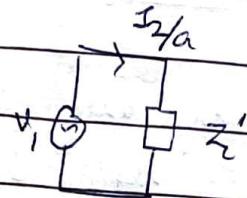


Equivalent referred to secondary

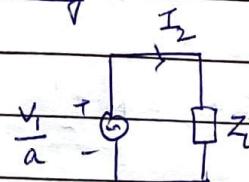

21/1/21

* Practical Transformer

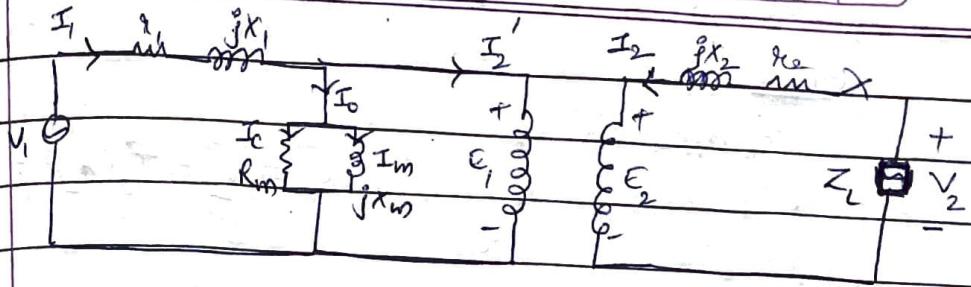- Winding resistance is accounted as ^{series} resistance.
- The effect of leakage flux is accounted through series reactances.
- Core loss will be accounted through shunt resistance.
- Permeability is finite \rightarrow magnetizing current to establish working flux \rightarrow shunt element.



* Phasor of Practical Transformer on no load

$$I_2 = 0$$

$$I_2' = 0$$



$$I_1 = I_0$$

$\phi_0 \rightarrow$ no load pf angle

at no load ϕ is large

as $I_m > I_c$

no load pf of transformer is poor.

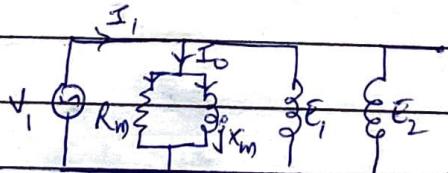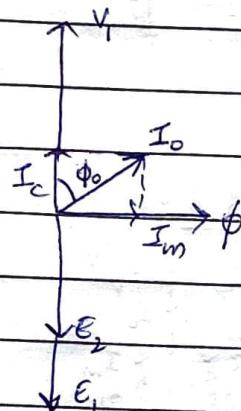

drop across $(R_m + jX_m)$ is neglected as I_0 is just 2.5% of rated I_1 .

* Phasor diagram of Transformer on load

Inductive
↓


Resistive
↓

Capacitive
↓

I_2 lags V_2

$I_2 \& V_2$ are in phase




I_2 leads V_2

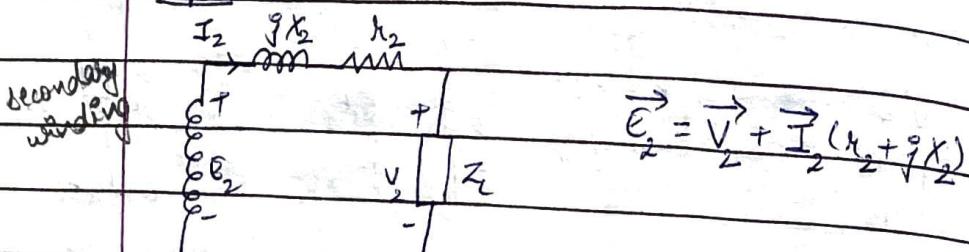Inductive LoadStep 1Step 2


both

$$I_1' = \frac{I_2}{a}$$

$$\frac{E_1}{E_2}$$

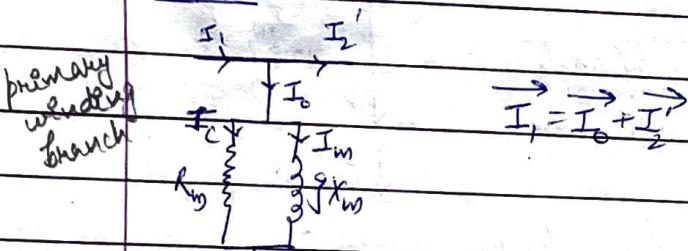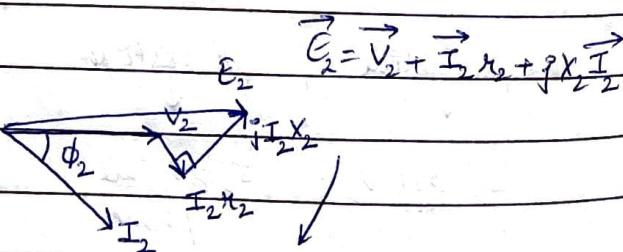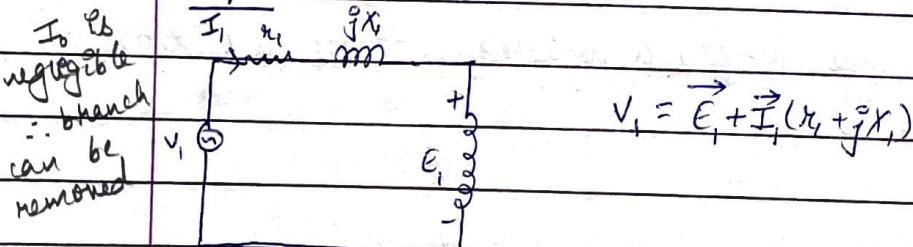Step 3Step 4

I_2 and V_2 have 120° angle b/w them.

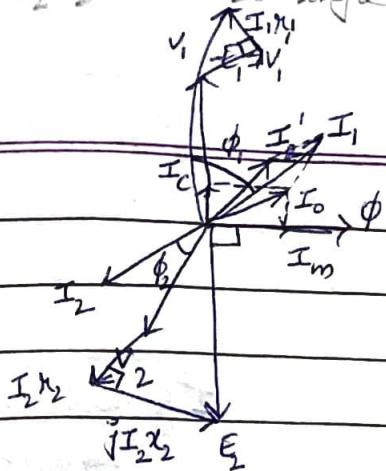


Page No. _____	
Date _____	

$$I_m = I_o \sin \phi$$

$$I_c = I_o \cos \phi$$


Resistive Load

I_2 and V_2 are in same phase.

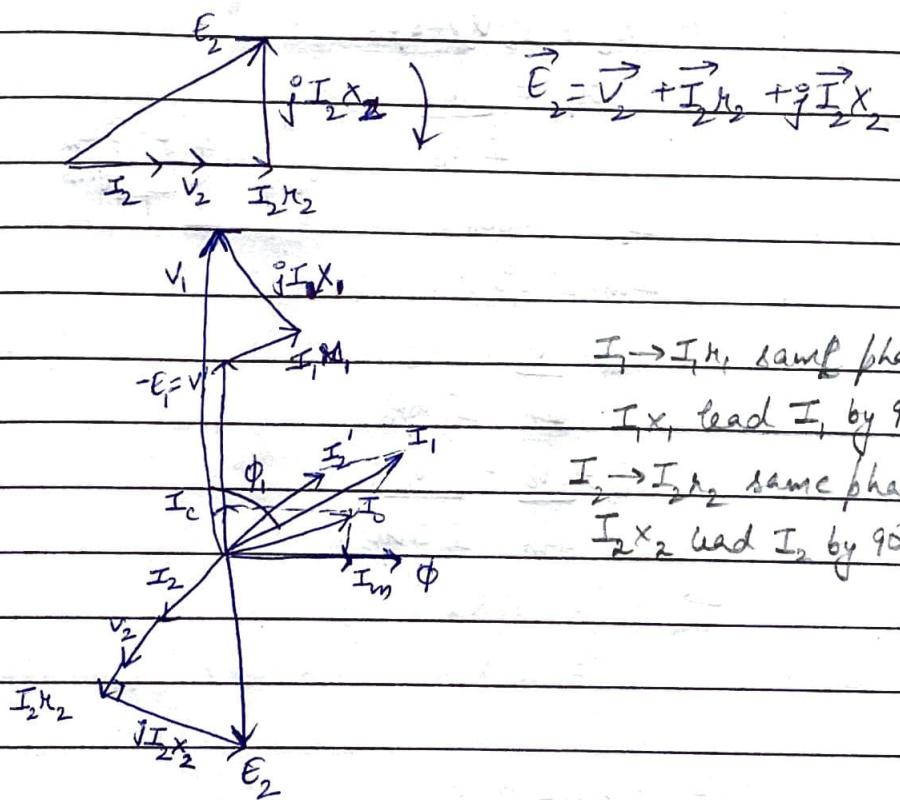

* Tests of Transformer

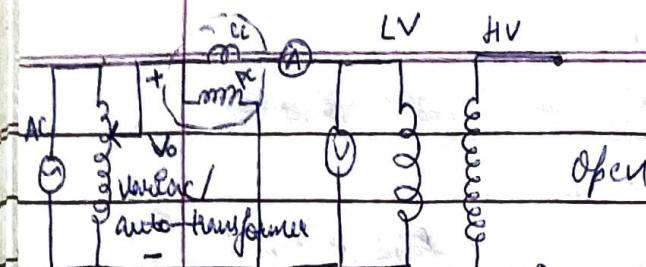- ① Open Circuit Test
- Low Voltage Side
- High Voltage Side is open circuit.
- Performed at rated voltage and frequency.



$I^2 R$ loss are negligible

$$V_o = V_L \text{ rated}$$

Power consumed \rightarrow core loss P_c

$\rightarrow R_m$ & X_m referred to LV (core loss)

$$W_o = I_o V_o \cos \phi_o$$

$$\cos \phi_o = \frac{W_o}{I_o V_o}$$

$$I_c = I_o \cos \phi_o$$

$$I_m = I_o \sin \phi_o$$

$$R_m = \frac{V_o}{I_c} = \frac{V_o}{I_o \cos \phi_o}$$

$$X_m = \frac{V_o}{I_m} = \frac{V_o}{I_o \sin \phi_o}$$

$$\begin{aligned} &\rightarrow R_m^{HV} = a^2 R_m \\ &\quad X_m^{HV} = a^2 X_m \end{aligned} \quad \left. \begin{array}{l} \text{referred to HV} \\ \text{(secondary scale)} \end{array} \right.$$


(2) Short Circuit Test

\rightarrow performed at rated current

$$I_{sc} = I_{fl} = I_{rated}$$

\rightarrow HV side \rightarrow full load

\rightarrow LV side is short-circuited

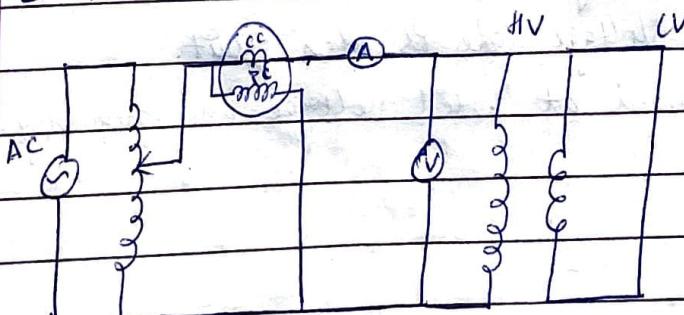

$$P_{Sc} = P_{cv}^{fc}$$

$$P_{Sc} = I_{Sc}^2 R_{Sc}$$

$$R_{Sc} = \frac{P_{Sc}}{I_{Sc}^2}$$

$$Z_{Sc} = \frac{V_{Sc}}{I_{Sc}}$$

$$X_{Sc} = \sqrt{Z_{Sc}^2 - R_{Sc}^2}$$

R_{Sc} & X_{Sc} → referred to HV

$$X_{HV} = X_{cv}' = \frac{X_{Sc}}{2}$$

↓
LV side
resistance
referred to
HV side

Losses \rightarrow Core loss (P_i)

\rightarrow Copper loss / $I^2 R$ loss (P_{cu})

$$P_i = P_c + P_h$$

$$P_{cu} = I_1 R_1 + I_2 R_2$$

$$= I_1^2 R_{c1} = I_2^2 R_{c2}$$

R_{c1} \rightarrow eq. resistance on primary side

R_{c2} \rightarrow eq. resistance on secondary side

Power output $= V_2 I_2 \cos \phi_2$ \rightarrow angle b/w V_2 & I_2

$$\eta = \frac{V_2 I_2 \cos \phi_2}{\text{Total Power}}$$

$$\eta = \frac{V_2 I_2 \cos \phi_2 + P_c + P_{cu}}{V_2 \cos \phi_2 + P_c + I_2^2 R_{c2}}$$

for max. efficiency -

$$\frac{d\eta}{dI_2} = 0$$

$\Rightarrow 0$

$$\Rightarrow P_i = R_{c2} I_2^2$$

Iron loss = full load copper loss
 constant $P_i = P_{cu}$ variable

$$P_{cu}^{fl} = I_{2fl}^2 R_{c2}$$

$$\frac{I_2^2}{I_{2fl}^2} = \frac{P_i}{P_{cu}^{fl}} = k^2$$

$$\therefore k = \frac{I_2}{I_{2fl}}$$

$$k = \frac{I_2}{I_{2fl}} = \sqrt{\frac{P_i}{P_{cu}^{fl}}}$$

$$\eta = V_2 I_2 \cos \phi_2$$

$$\frac{V_2 I_2 \cos \phi_2 + P_i + I_2^2 R_{c2}}{V_2 \cos \phi_2 + P_c + I_2^2 R_{c2}}$$

$$\begin{aligned}\eta &= \frac{V_2 I_2 f k \cos \phi_2}{V_2 I_2 f k \cos \phi_2 + 2P_c} \\ &= \frac{k V_2 I_2 f \cos \phi_2}{k V_2 I_2 f \cos \phi_2 + 2P_c} \\ \eta_{\max} &= \frac{k S_{\text{rated}} \cos \phi_2}{k S_{\text{rated}} \cos \phi_2 + 2P_c}\end{aligned}$$

Rating of Transformer

$$\underbrace{\text{kVA / VA / MVA}}_{\text{Rated VA}} ; N_1/N_2 (V_1/V_2) ; \text{frequency.}$$

(S_{rated})

eg. ^{test}
The following results are obtained on a 20 kVA, 2000/200 V, 50 Hz transformer.

OC Test : 200 V ; 4 A ; 120 W $\rightarrow P_o$ (LV)

SC Test : 60 V ; 10 A ; 300 W $\rightarrow P_{cu}^{fl}$ (HV)

Calculate the efficiency at -

- (i) rated load and 0.8 lagging pf.
- (ii) at half load and 0.8 lagging pf.

Sol. (i) $S_{\text{rated}} = 20 \text{ kVA}$

$$= I_{LV} V_{LV} = I_{HV} V_{HV}$$

$$20 \times 10^3 = I_{HV} \times 2000$$

$$I_{HV} = 10 \text{ A}$$

$$\eta = \left(\frac{20 \times 10^3 \times 0.8}{20 \times 10^3 \times 0.8 + 120 + 300} \right) \times 100$$

$$\eta = 97.44\%$$

(ii) half load $\rightarrow I_2 = \frac{I_{\text{rated}}}{2}$

$$\begin{aligned}
 \eta &= \frac{V_2 I_2 \cos \phi}{V_2 I_2 \cos \phi + P_c + P_{cu}} \\
 &= \frac{V_2 I_2 \cos \phi}{2} \\
 &\quad \frac{V_2 I_2 \cos \phi + P_c + \left(\frac{I_2 R}{2}\right)^2 R_2}{2} \\
 &= \frac{20 \times 10^3 \times 0.8}{2} \\
 &\quad \frac{20 \times 10^3 \times 0.8 + 120 + \frac{P_{cu}}{4}}{4} \\
 &= 97.62\%
 \end{aligned}$$


NOTE: at any fraction of load (x) $\rightarrow I_2 = x I_{2n}$

Output = $x S_{rated}$

Copper Loss = $x^2 P_{cu}$

* Equivalent

Exact eq. referred to primary side -

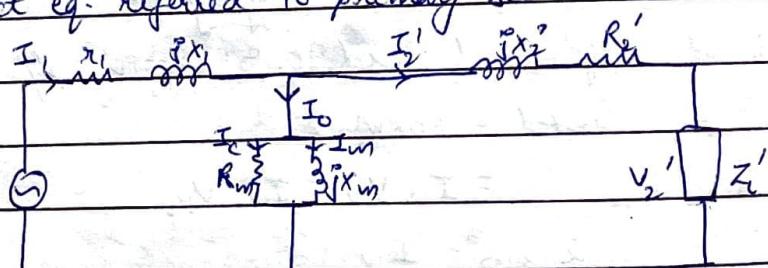

$$a = \frac{N_1}{N_2} = \frac{V_1}{V_2}$$

$$V_2' = a V_2$$


$$I_2' = I_2/a$$

$$R_2' = a^2 R_2$$

$$X_2' = a^2 X_2$$


$$Z_2' = a^2 Z_2$$

Approximate equivalent circuit

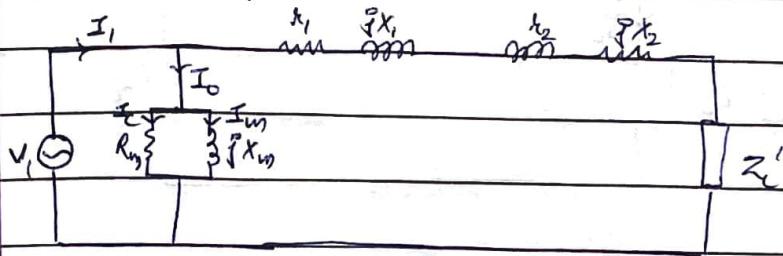


$$R_{eq} = r_1 + r_2' = r_1 + a^2 r_2$$

$$X_{eq} = x_1 + x_2' = x_1 + a^2 x_2$$

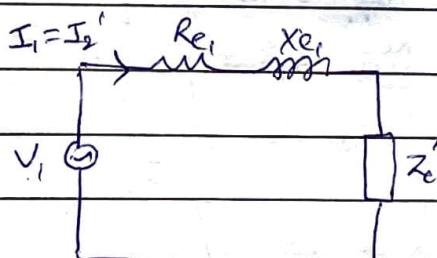

Exact eq. referred to secondary side -

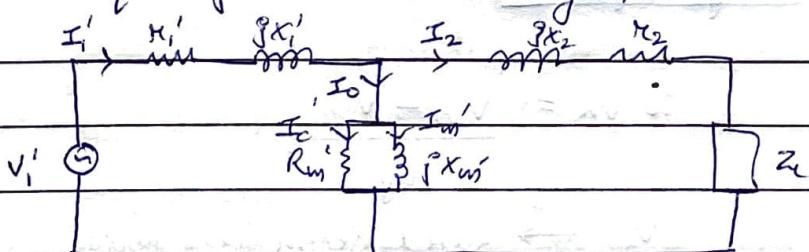

$$\frac{N_1}{N_2} \approx a$$

$$\frac{V_1'}{V_1} \approx a$$

$$I_1' = a I_1$$

$$r_1' = r_1/a^2$$

$$x_1' = x_1/a^2$$

$$R_m' = R_m/a^2$$

$$x_m' = x_m/a^2$$


$$I_0' = a I_0$$

$$I_m' = a I_m$$

$$I_1' = a I_1$$

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{N_1}{N_2}$$

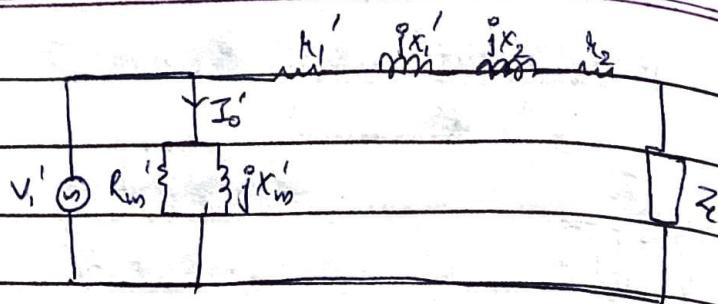
$$\frac{I_1'}{I_1} = \frac{N_1}{N_2} \rightarrow a$$



$$R_{e2} = r_1' + r_2 = \frac{r_1}{a^2} + r_2$$

$$X_{e2} = x_1' + x_2 = \frac{x_1}{a^2} + x_2$$

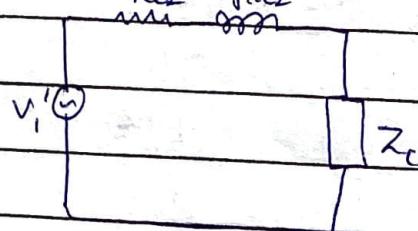Simplified approximate eq. referred to secondary




* Voltage Regulation

$$\% \text{ VR} = \frac{V_{20} - V_{2f1}}{V_{2f1}} \times 100$$

V_{2f1} → rated secondary voltage
 V_{20} → no load secondary voltage

- Use simplified approximate equivalent
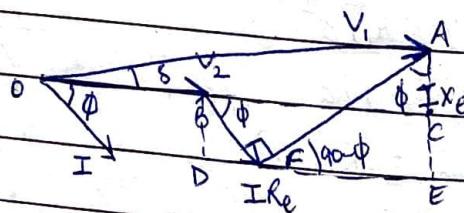
$$\vec{V}_1 = \vec{V}_2 + \vec{I} (R_e + jX_e)$$



Voltage drop across Z_0 is very small as compared to rated V_2 . $S = 0$

$$V_1 \approx V_{OC}$$

$$OC = OB + \Delta f + FE$$

$$V_1 = V_2 + IR_{e \cos \phi} + IX_{e \sin \phi}$$

$$V_1 - V_2 \approx IR_{e \cos \phi} + IX_{e \sin \phi}$$

for lagging $\rightarrow VR = \frac{IR_{e \cos \phi} + IX_{e \sin \phi}}{V_2} \times 100$
 ff (RL load)

for leading $\rightarrow VR = \frac{IR_{e \cos \phi} - IX_{e \sin \phi}}{V_2} \times 100$
 ff (RC load)

Ques. A 100 kVA transformer has -

$$N_1 = 400; N_2 = 100$$

$$r_1 = 0.3 \Omega; r_2 = 0.015 \Omega$$

$$x_1 = 1.1 \Omega; x_2 = 0.055 \Omega$$

Supply voltage is 2400V. calculate

- R_{e1}, X_{e1}
- VR at 0.8 lagging ff; V_2
- VR at 0.8 leading ff; V_2
- ff for zero VR

sol.

- $R_{ef} = r_1 + \alpha^2 r_2$ $\alpha = \frac{N_1}{N_2} = 4$
- $= 0.3 + 16 \times 0.015$
- $= 0.64 \Omega$

$$\begin{aligned} X_{e1} &= x_1 + \alpha^2 x_2 \\ &= 1.1 + 16 \times 0.055 \\ &= 1.98 \Omega \end{aligned}$$

$$S_{rated} = V_1 I_1 = V_2 I_2$$

$$100 \times 10^3 = 2400 \times I_1$$

$$I_1 = 41.67 A$$

$$\text{Lagging} \cdot VR = \frac{41.67 \times 0.54 \times 0.8 + 41.67 \times 1.98 \times 0.8}{2400} \times 100$$

$$= 2.81\%$$

$$\text{Leading} \cdot VR = \frac{41.67 \times 0.54 \times 0.8 - 41.67 \times 1.98 \times 0.8}{2400} \times 100$$

$$= -1.31\%$$

$$\text{Lagging} \cdot V_1 - V_2 = I_e R_{e1} \cos \phi + I_e X_{e1} \sin \phi$$

$$V_2 = V_1 - I_e R_{e1} \cos \phi - I_e X_{e1} \sin \phi$$

$$V'_2 = 2332.99 \quad V = V'_2$$

$$[\text{as } V_1 = V'_2 + I_e (R_{e1} + jX_{e1})]$$

$$V_2 = \frac{V'_2}{a} = 583.12 \approx 583V$$

through

$$\text{(Leading) for } 0 \text{ VR} \cdot \tan \phi = \frac{+R_{e1}}{X_{e1}} = 16.255$$

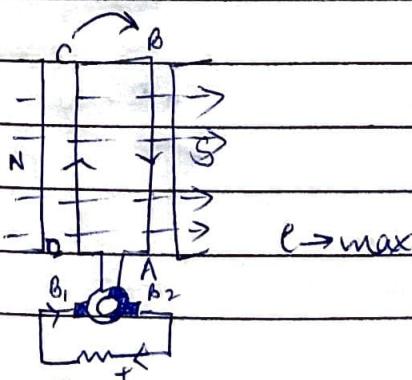
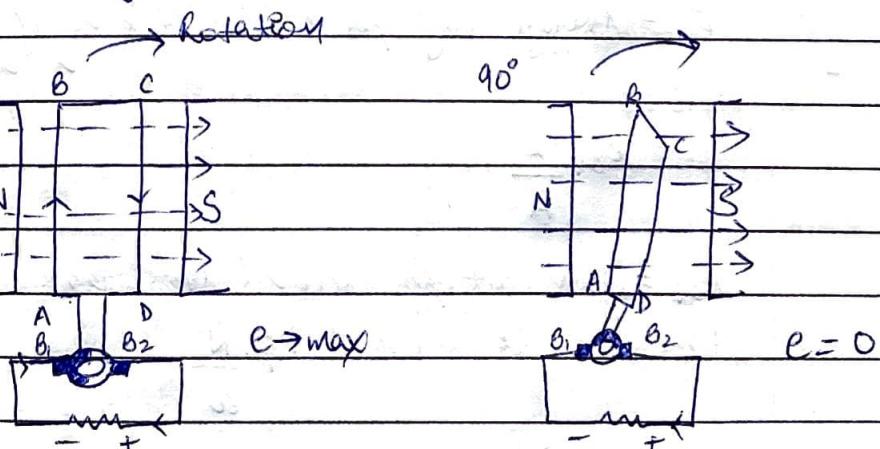
$$\cos \phi = 0.96 \text{ leading}$$

Ch.5 - DC Machines

- Direct-current (DC) machines are divided into DC generators and DC motors.
- DC machines are similar to AC machines.
- DC machines have DC outputs - they have a mechanism converting AC voltages to DC voltages at their terminals.
- This mechanism is called a commutator.
 \therefore DC machines are also called commutating machines.

DC Generator

- Mechanical energy is converted to electrical energy.
- Induced current is found out using Fleming's Right Hand Rule.

* Working Principle


* EMF Equation of DC Generator

Rotor / Armature


- Lap wound $\rightarrow A = P$

- Wave wound $\rightarrow A = 2$

A : no. of parallel paths

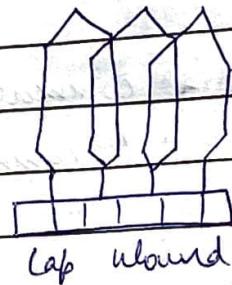

Lap wound

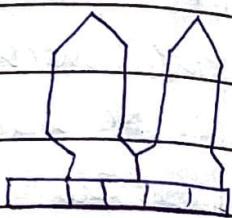

Wave wound

$$e = -\frac{N d\phi}{dt}$$

EMF generated by one parallel path $\rightarrow E_g$

$P \rightarrow$ no. of poles $Z \rightarrow$ total no. of conductors

$\phi \rightarrow$ flux per pole $A \rightarrow$ no. of parallel paths

$N \rightarrow$ speed of machine rpm

$E_g = \text{Average emf per conductor} \times \text{no. of conductors}$
in a parallel path

$$= e_{av} \frac{Z}{A}$$

$e_{av} = \text{flux cut per second (Faraday's law)}$

Flux cut per second = $P\phi \cdot \frac{N}{60}$

$$e_{av} = P\phi \frac{N}{60}$$

$\phi, N \rightarrow$ variable

$P, Z, A \rightarrow$ constant for a machine


$$E_g = \frac{P\phi NZ}{60A} V$$

$$= \frac{PZ}{2\pi 60A} \cdot 2N\phi \pi$$

$$E_g = K_a \phi \omega_m$$

$$\therefore K_a = \frac{PZ}{2\pi \times 60A}$$

* Equivalent of DC Machine

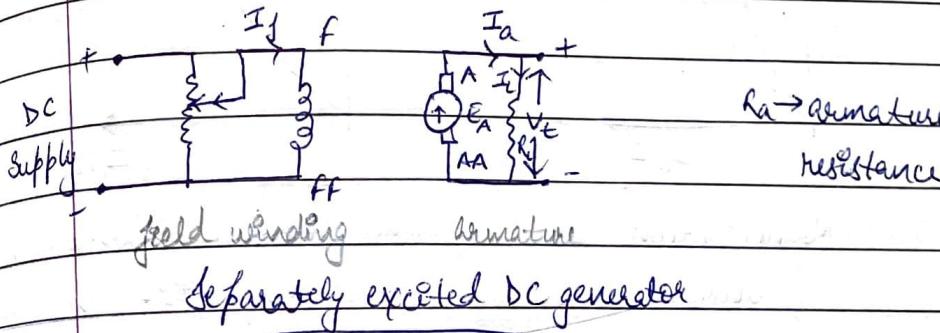

$$I_a = I_f$$


$$I_f = \frac{V_f}{R_f}$$

Shunt generator

$$I_a = I_f + I_L$$

$$I_f = \frac{V_f}{R_{sh}}$$


$$I_L = \frac{V_L}{R_L}$$

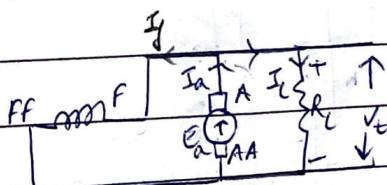

$$V_t = E_a - I_a R_a$$


Series Generator

$$I_a = I_f = I_L$$

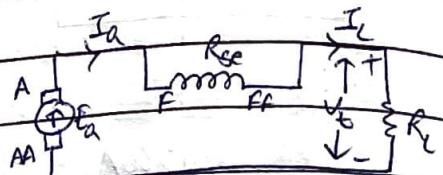

$$V_t = E_a - I_a (R_a + R_{se})$$

26/1/21

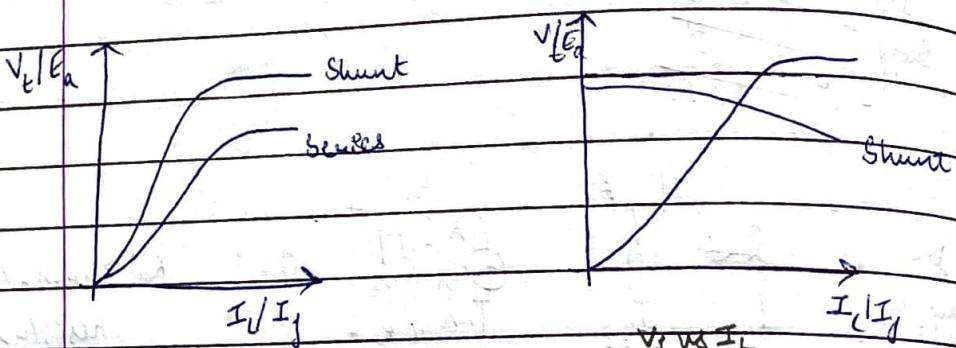Shunt: Magnetization E_a vs I_f

Curve /



Shunt: External Characteristics

Series: Magnetization Curve E_a vs I_f

Series: External Characteristics

 V_t vs I_L # DC Motor

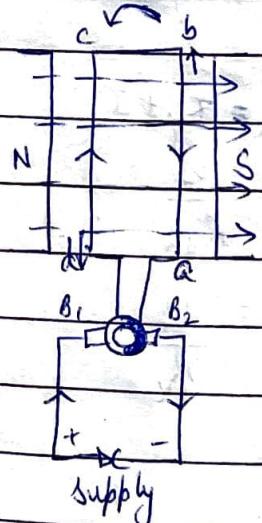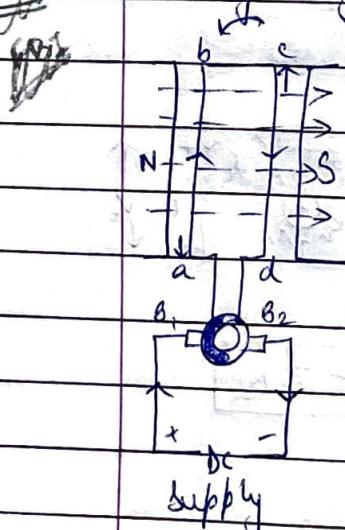- When current carrying conductor is placed inside magnetic field, it will experience a force.
- Fleming's Left Hand Rule is used.




$T_e \rightarrow$ electromagnetic torque is experienced

$E_b \rightarrow$ back emf is introduced produced = $K_a \phi_{w.m.}$

* Electrical Equivalent of Motor

Series

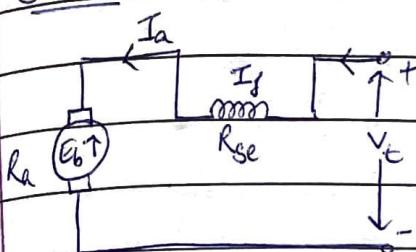


$$I_f = I_a = I_c$$

$$V_t = I_f R_{se} + I_a R_a + E_b$$

$$V_t = E_b + I_a (R_a + R_{se})$$

Shunt

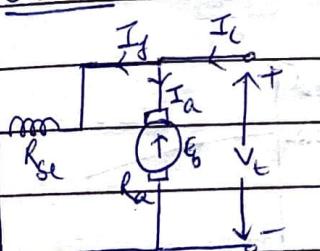

$$I_c = I_a + I_f$$

$$I_f = \frac{V_t}{R_{se}}$$

$$V_t = E_b + I_a R_a$$

* Torque Equation

$$V_t = E_b + I_a R_a$$

$$\text{or } V_t = E_b + I_a (R_a + R_{se})$$

$$V_t I_a = E_b I_a + I_a^2 R_a$$

total electrical power supplied to armature

Copper loss
mechanical power

Power = Torque \times Angular Speed

$$E_b I_a = T_e \omega_m$$

$$T_e = \frac{E_b I_a}{\omega_m}$$

$$\omega_m$$

$$= \frac{K_a \phi I_a}{\omega_m}$$

$$T_e = K_a \phi I_a$$

Series motor

$$\phi \propto I_a$$

$$\phi = C I_a$$

$$T_e = K_a C I_a^2$$

Shunt motor

$$\omega_m = \frac{E_b}{K_a \phi} = \frac{V_t - I_a R_a}{K_a \phi}$$

$$T_e = K_a \phi I_a$$

$$I_a = \frac{T_e}{K_a \phi}$$

Speed

$$\omega_m$$

$$\omega_m = \frac{V_t - T_e R_a}{K_a \phi} \quad (K_a \phi)^2$$

$$\omega_m = \omega_{m_0} - \frac{T_e R_a}{(K_a \phi)^2}$$

no load

Speed

T_e

$$\therefore \omega_m = \frac{V_t - I_a R_a}{K_a \phi} \quad \text{if } I_a \approx 0 \rightarrow \text{no load}$$

$$\omega_{m_0} = \frac{V_t}{K_a \phi}$$

Series Motor

never
operated
at
no load

$$T_e = K_a C I_a^2$$

$$V_t = E_b + I_a (R_a + R_{se})$$

$$E_b = K_a \phi w_m$$

$$\omega_m = \frac{E_b}{K_a \phi}$$

$$= \frac{V_t - I_a (R_a + R_{se})}{K_a \phi}$$

Speed

$$= \frac{V_t}{K_a \phi} - \frac{I_a (R_a + R_{se})}{K_a \phi}$$

$$= \frac{V_t}{K_a C I_a} - \frac{I_a (R_a + R_{se})}{K_a C I_a}$$

$$= \frac{V_t}{K_a C \sqrt{\frac{T_e}{K_a C}}} - \frac{R_a + R_{se}}{K_a C}$$

$$\omega_m = \frac{V_t}{\sqrt{T_e K_a C}} - \frac{(R_a + R_{se})}{K_a C}$$

 T_e