


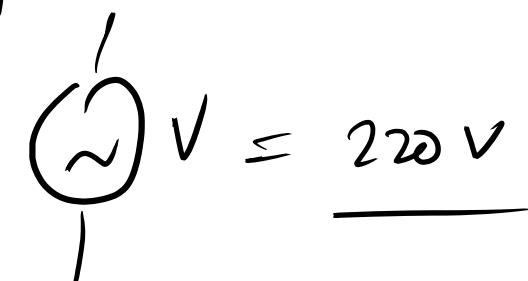
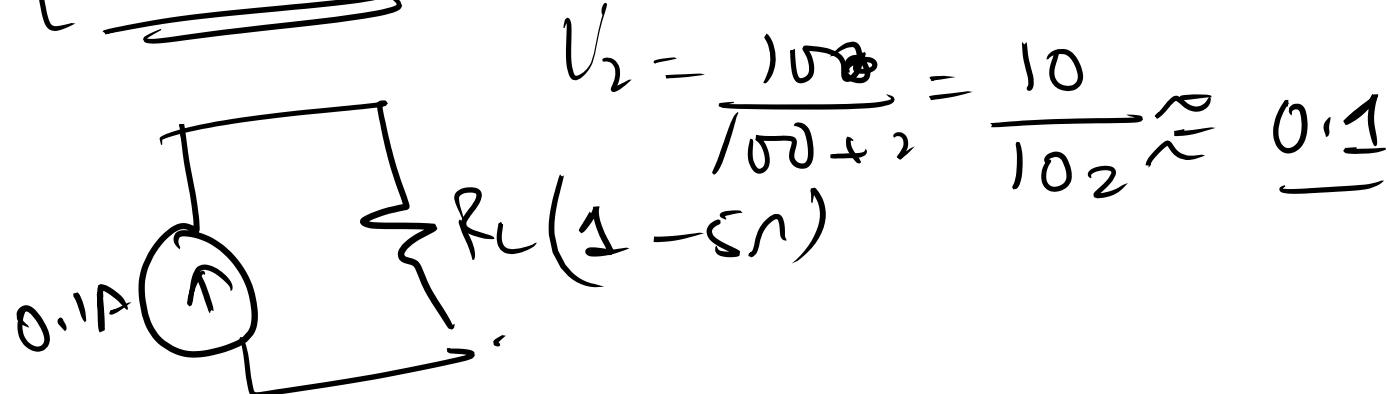
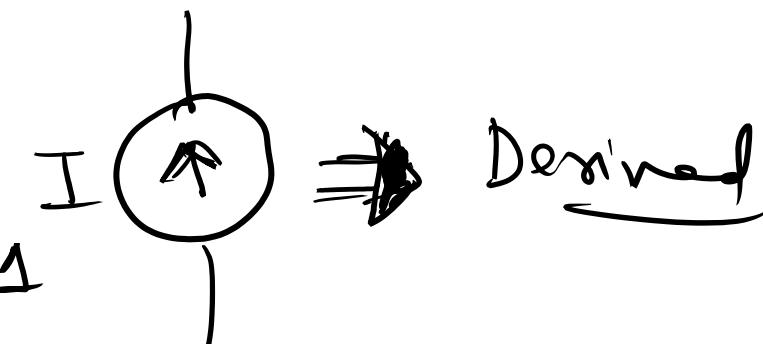
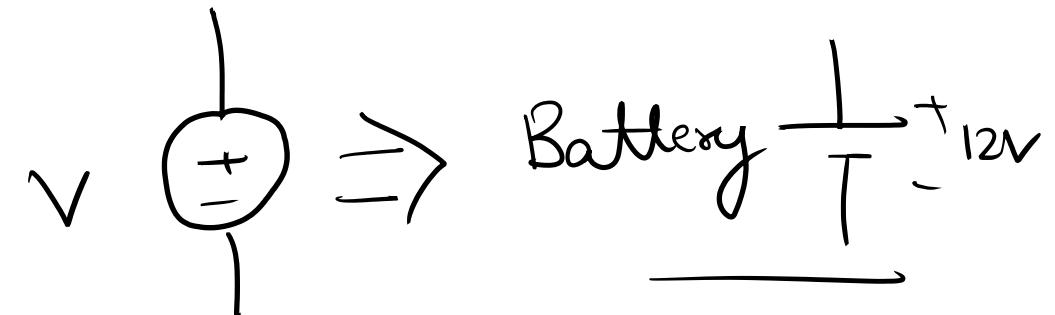
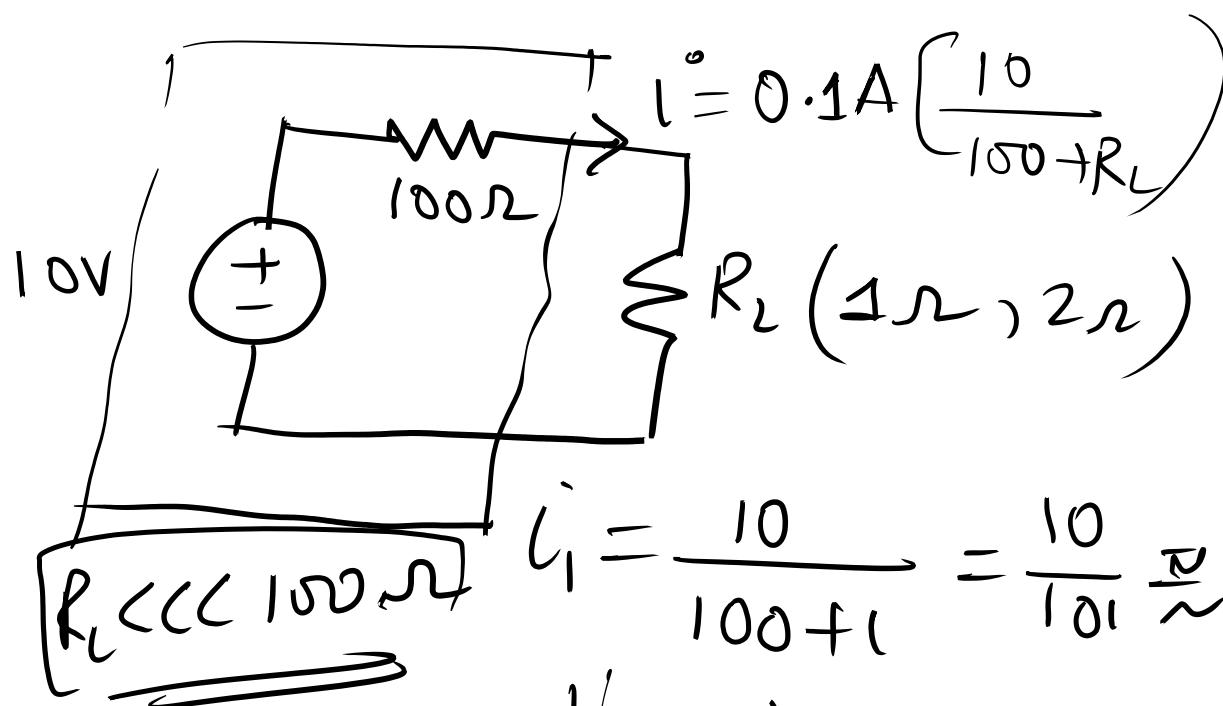


## \* Ideal vs Practical Sources

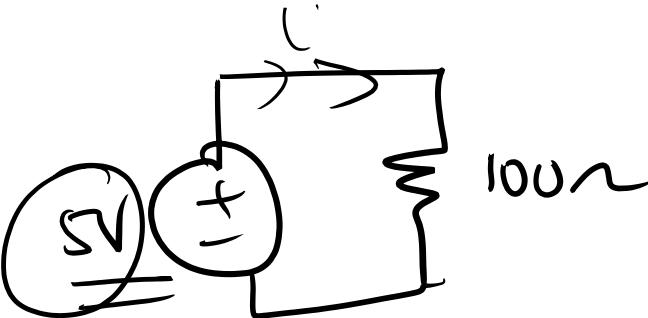


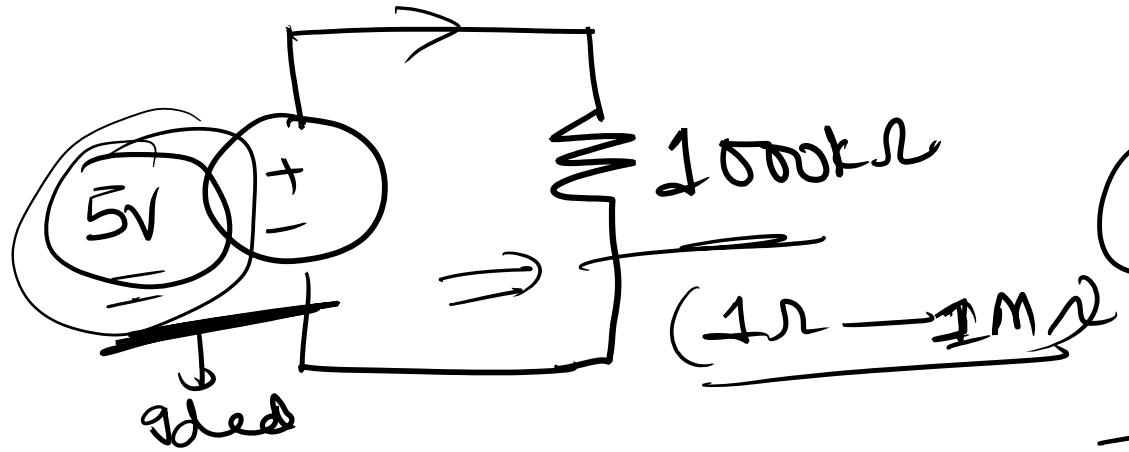




$\Rightarrow$  Cars ignition

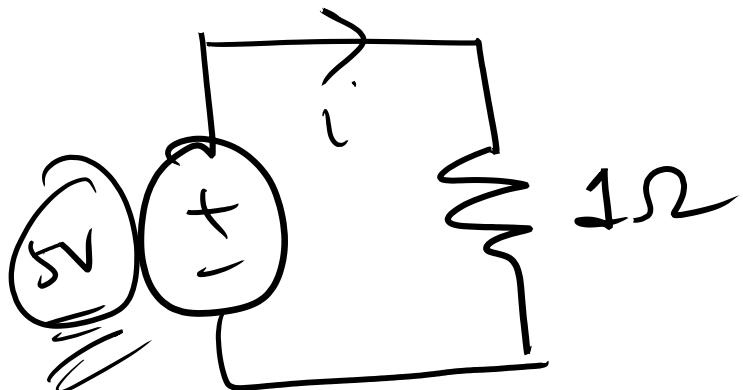

Practical dip in voltage level

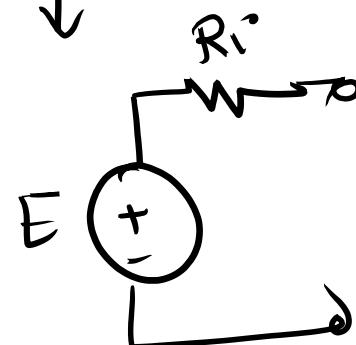


## \* Ideal & Practical Power Sources

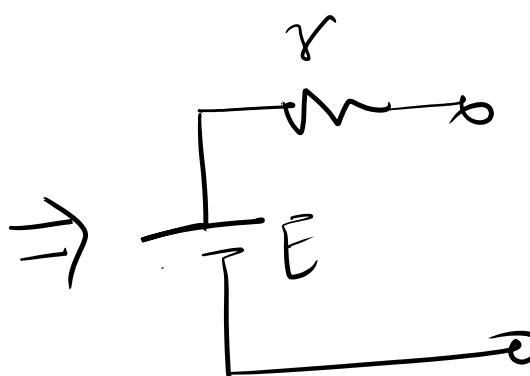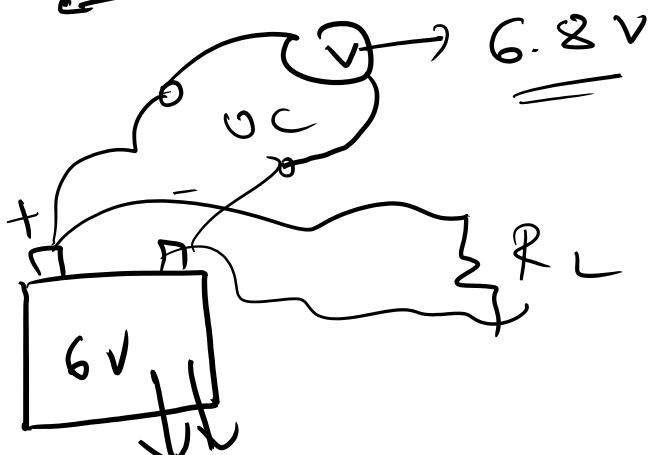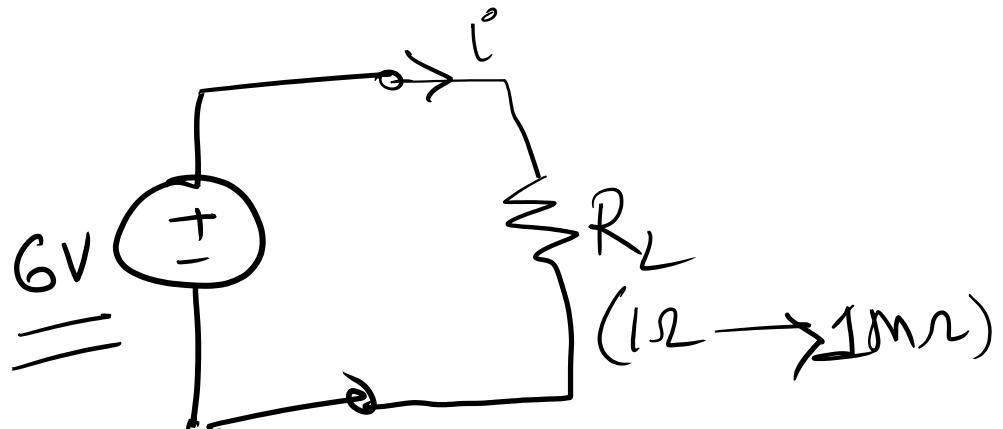



$$(1) 12V \xrightarrow{0A} 12V \\ \xrightarrow{100A} 11V \\ = \underline{\quad} \quad \underline{\quad} \\ 1V$$





Diagram illustrating the effect of internal resistance on terminal voltage. At no load ( $0A$ ), the terminal voltage is  $12V$ . As the load current increases to  $100A$ , the terminal voltage drops to  $11V$ . The internal voltage drop is  $1V$ .

$$r = \frac{V}{I} = \frac{1}{100}$$


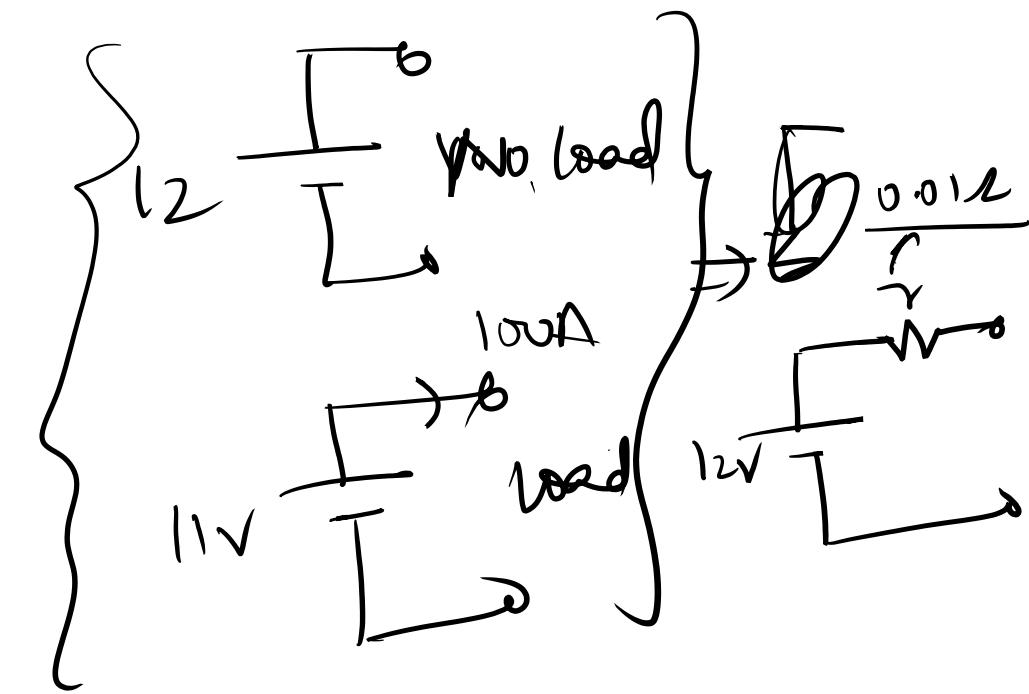


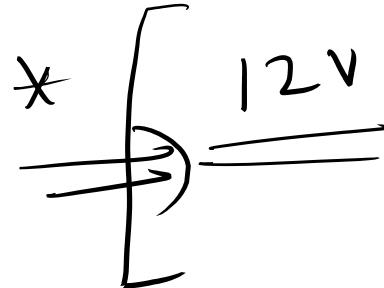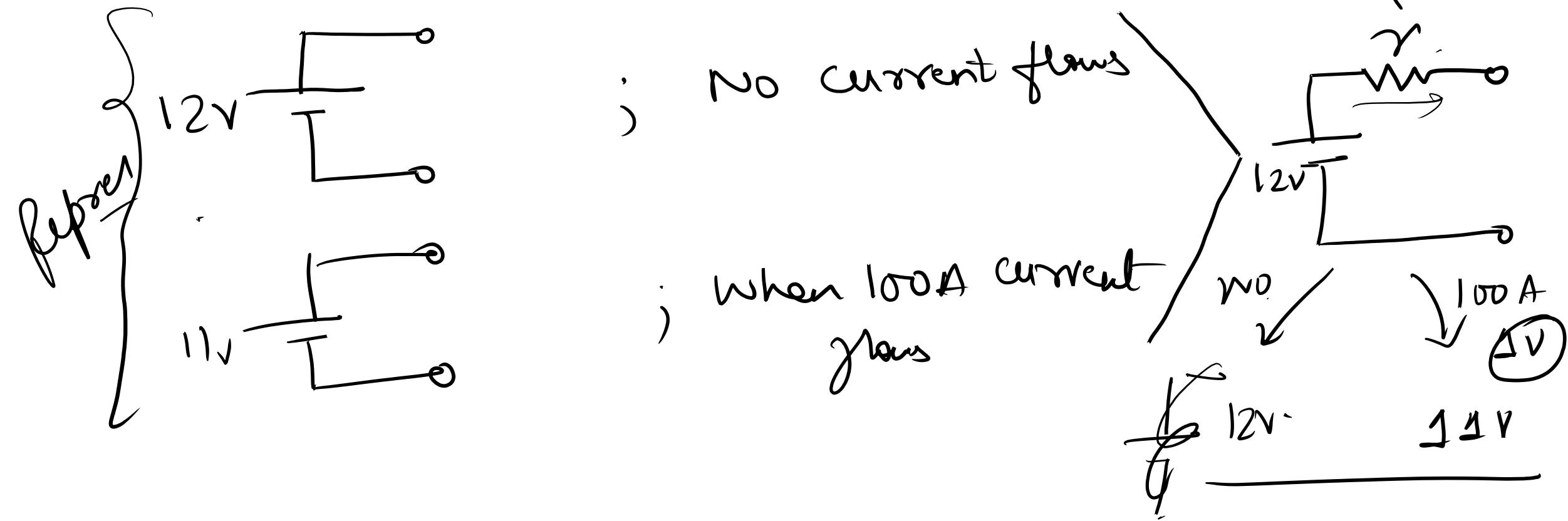\*   $\rightarrow$  When no current flows  $\Rightarrow V = 12V$   
 $\rightarrow$  When 100A flows  $\Rightarrow V = 1V$



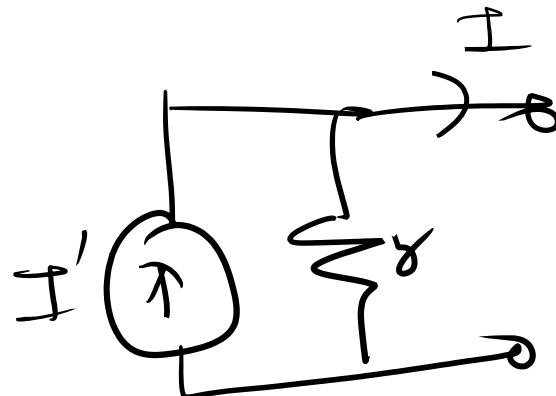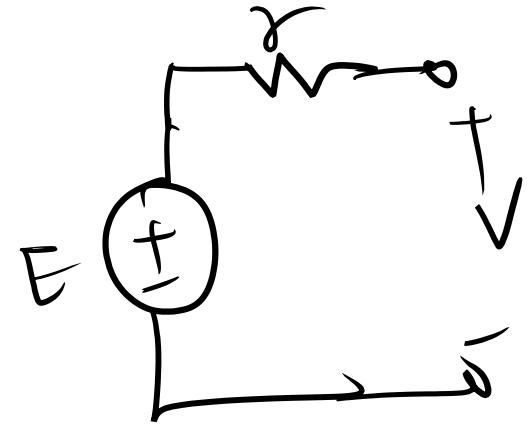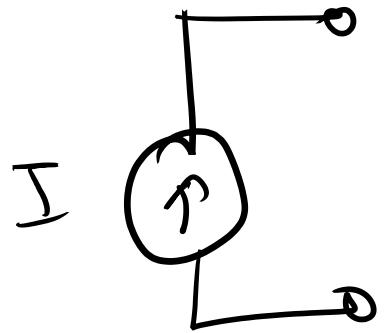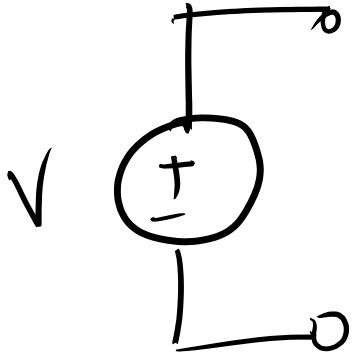


## \* Source Transformation

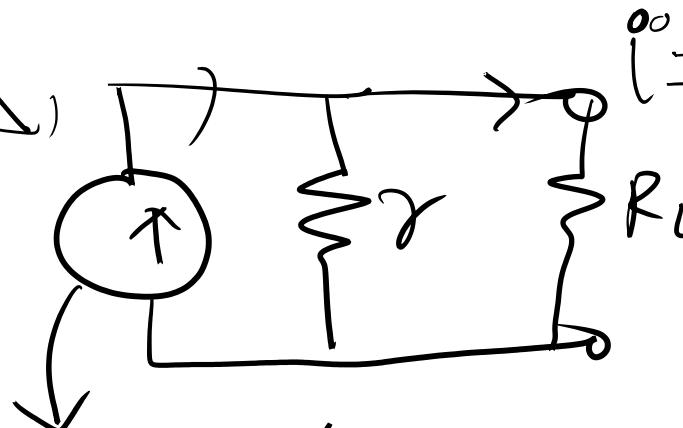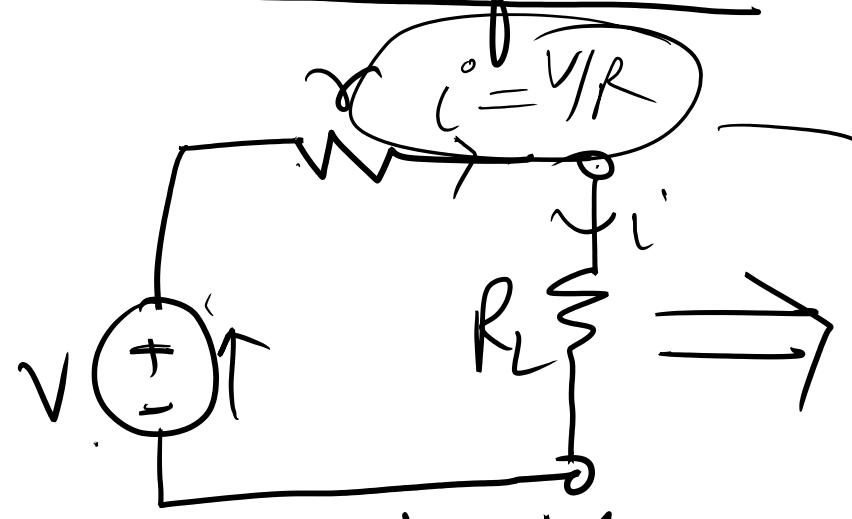


$$i^o = I * \frac{r}{(R_L+r)}$$

$$i^o = \frac{V}{\cancel{r}} \cdot \cancel{\frac{r}{(R_L+r)}}$$


$$= \frac{V}{R_L+r}$$

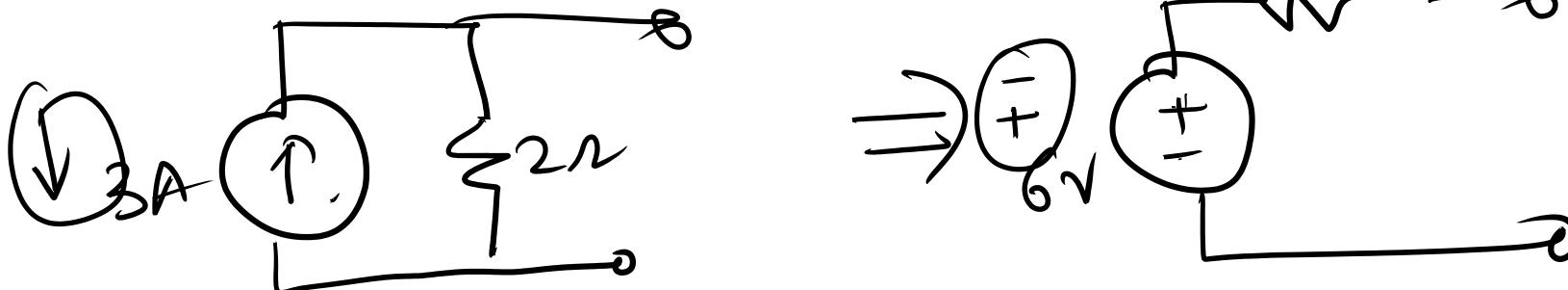

## \* Superposition Theorem

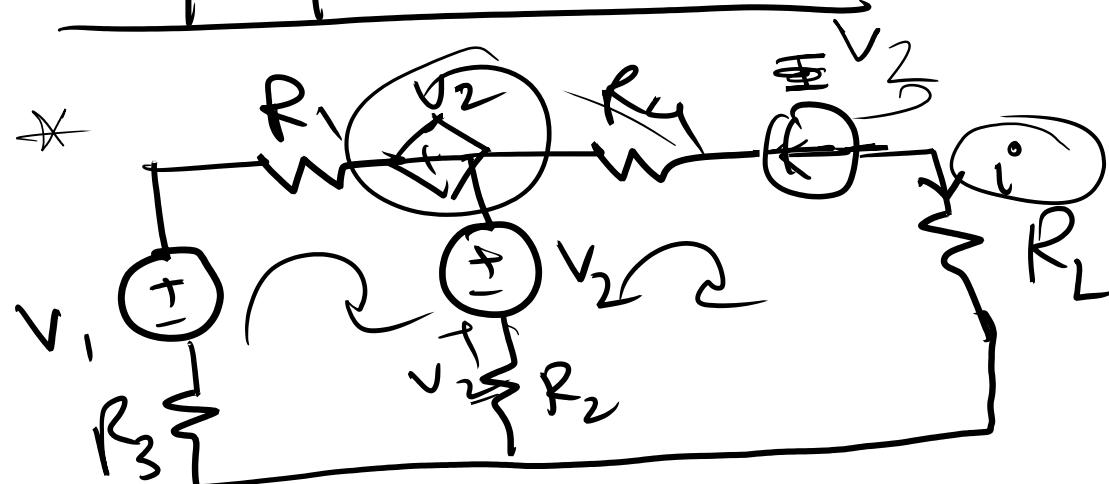


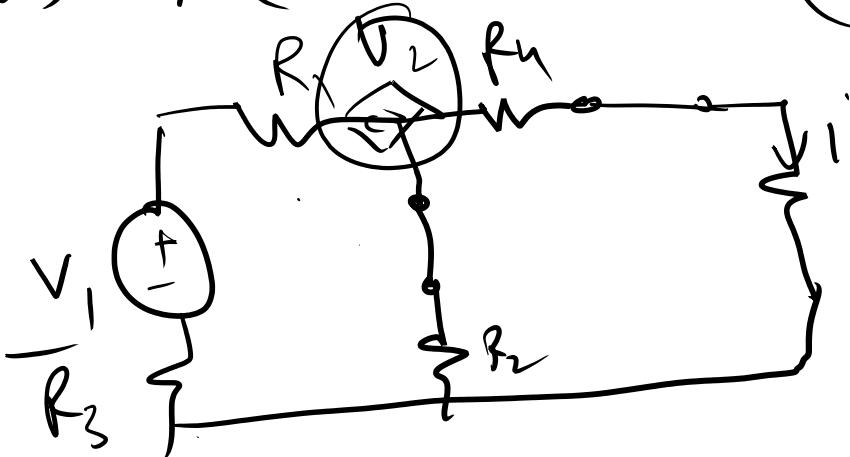(i)  $V_1$  (Kill  $V_2, I$ )  $(i)_V = x \text{ A}$



$i \text{ in } R_L$

(ii)  $V_2 (V_1, I \text{ kill})$

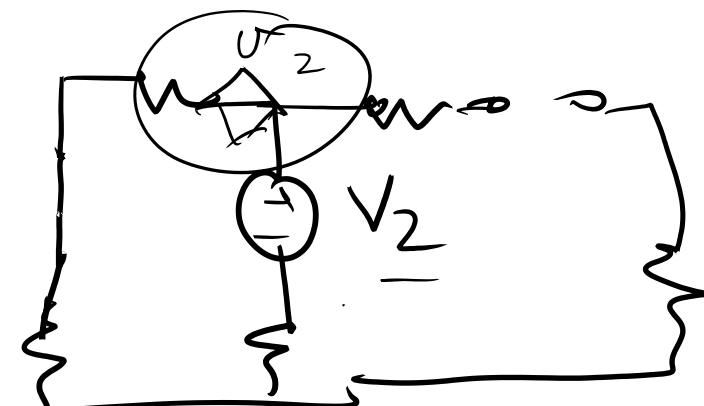

(i)  $V_2 = y A$


(ii)  $I (V_1, V_2)$



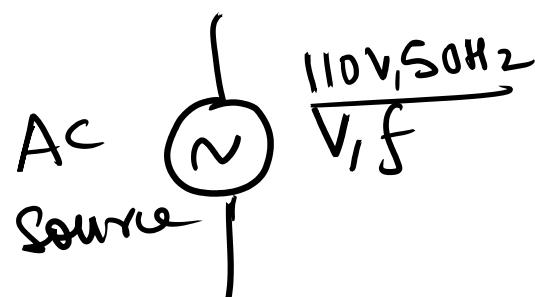(i)  $I = z A$


$$i = x + y + z$$

\* Applicability  $\rightarrow$  Multi freq. sources



Input

(Excitation)

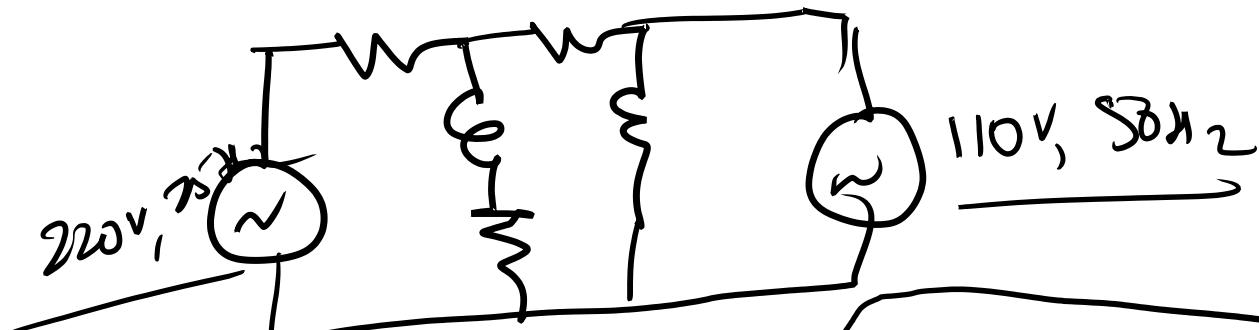

$$V_s = 0.6i_1 - 4V_2$$

$$V_s = 0.6i_1^2 \rightarrow \times \text{not linear}$$

\* Statement:

- Response ( $O/P \Rightarrow$  Output)
- Linear

Ohms law


$V_2$

$V_C V_S$


$2V_1$   $\sim$   $3V_2$

$2V_1$  \*  $2V_2$  \* Not linear

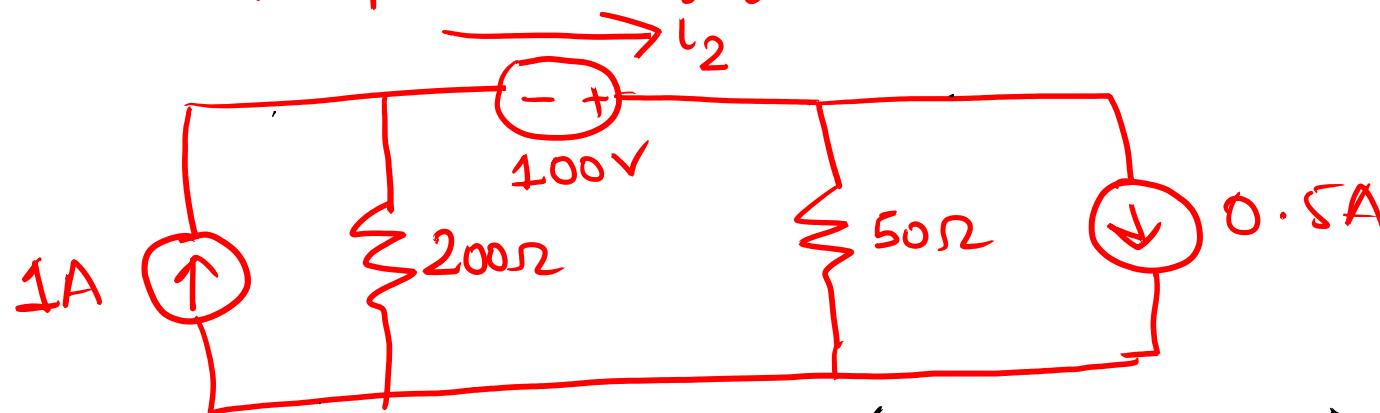
\* Use superposition to find current  $i_2$  in the given circuit.



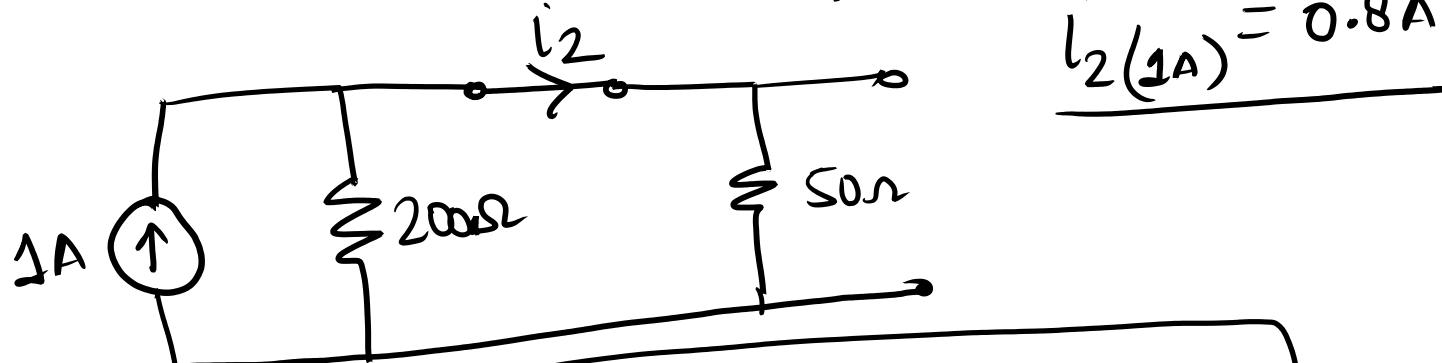(i) Consider 1A source only ( $100V; 0.5A \rightarrow$  killed)




$$i_2 = 0.8 + 0.4 + 0.1 = 1.3A$$

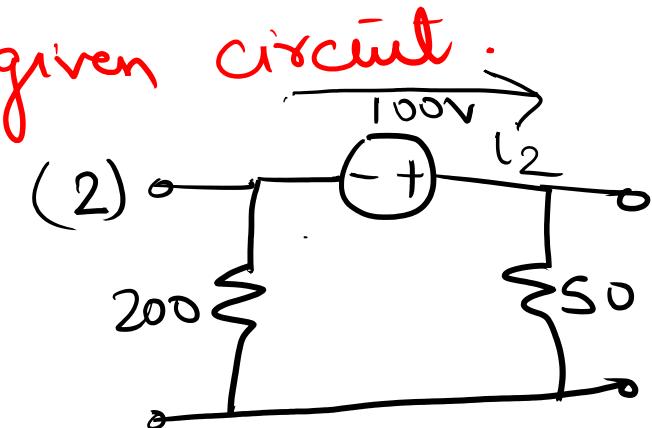



$$i_2(100V) = 0.4A$$

(-3) Consider 0.5A only

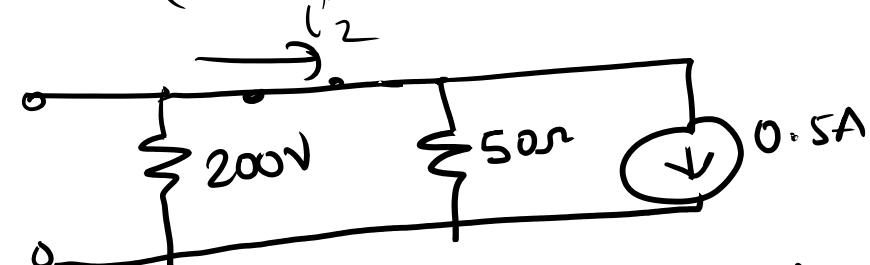


$$i_2(0.5A) = 0.1A$$

\* Use superposition to find  $i_x$

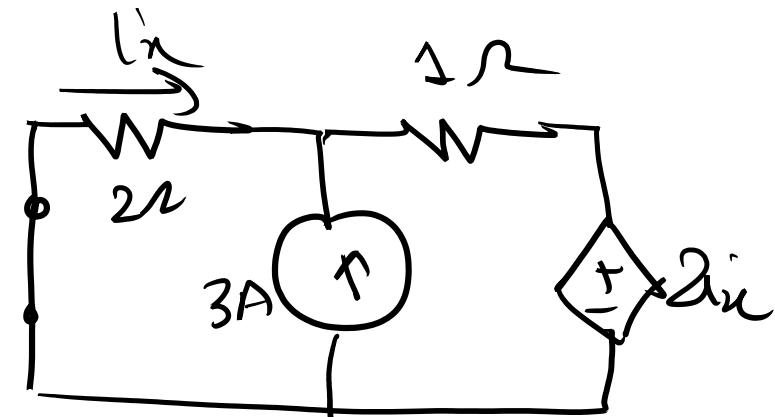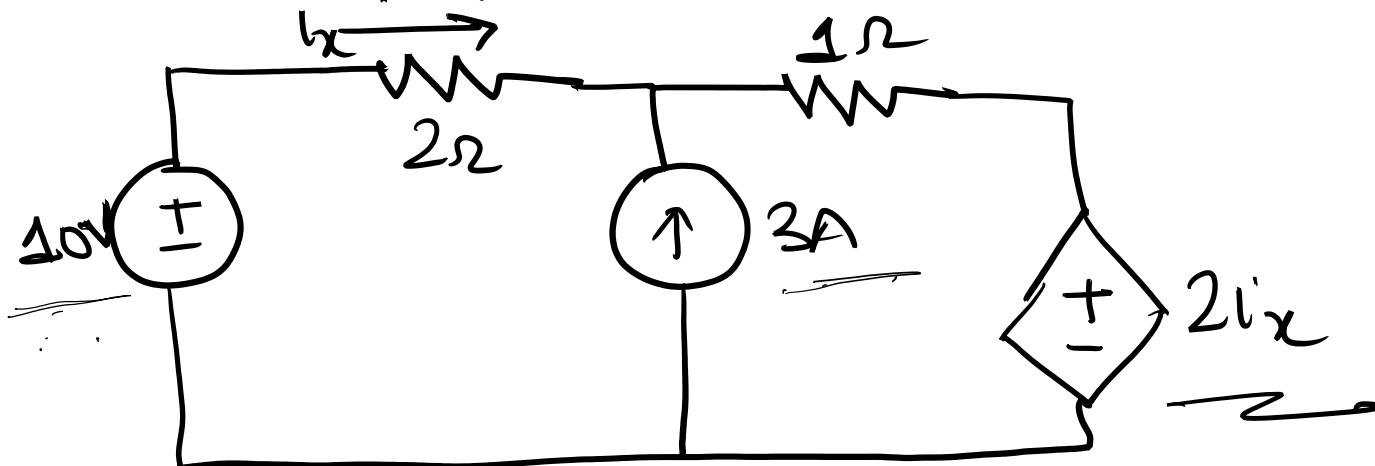

(i) Only 10V

$$i_x(10V) = \underline{2A}$$

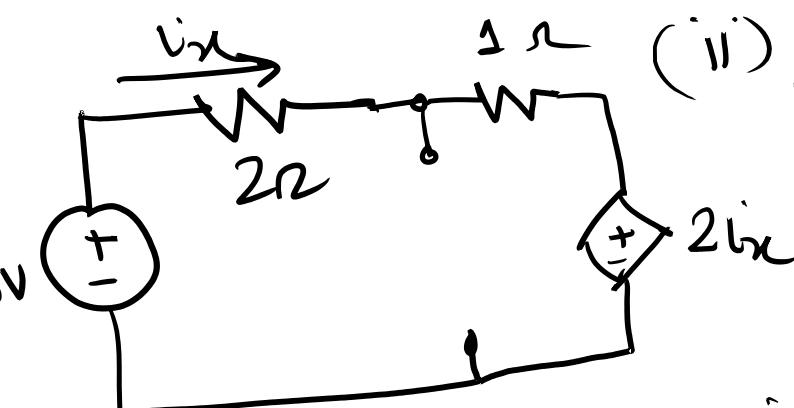


(ii) Only 3A

$$i_x(3A) = \underline{-0.6A}$$


$$i_x = i_x(10V) + i_x(3A)$$

$$= 2 + (-0.6) = \underline{1.4A}$$

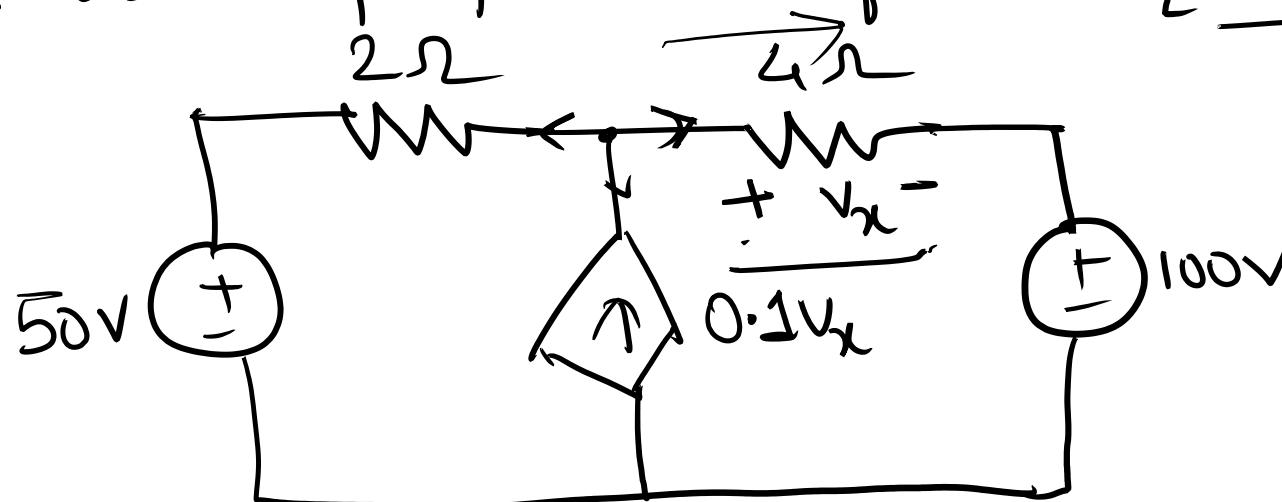\* Use superposition to find  $V_x$  [  $-38.5\text{V}$  ]




~~76.9~~

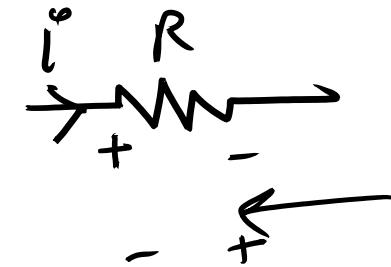

$$V_x(50\text{V}) = +38.461 \text{ V}$$

$$V_x(100\text{V}) = -76.92 \text{ V}$$



## \* Maximum Power Transfer Theorem

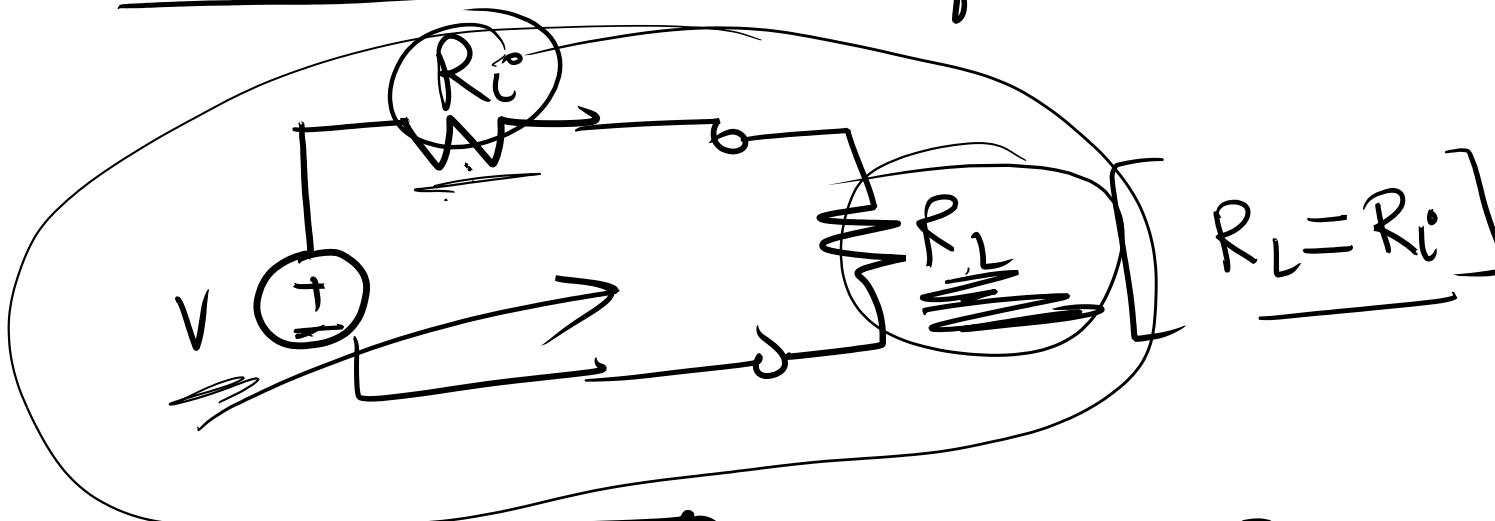


\* Statement:

$$R_L = R_i$$

$\Rightarrow$  Amplifiers

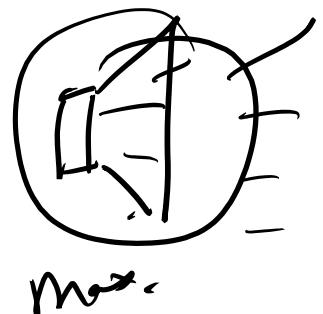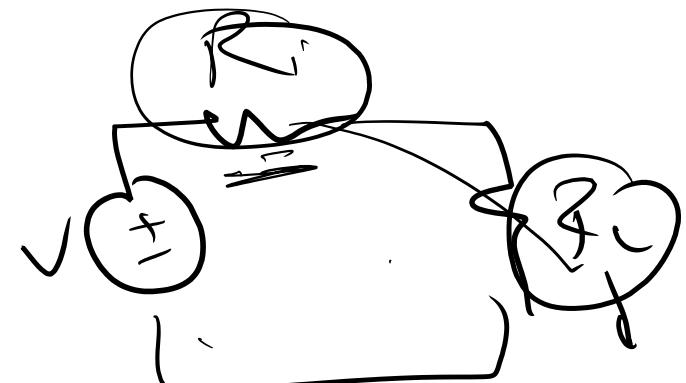

## Max. Power Tf Theorem :-

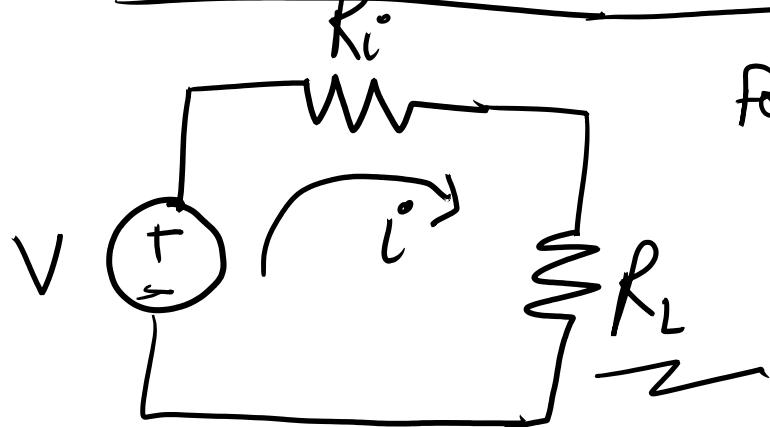

for Max. Power to be delivered to load;

$$R_L = R_i$$

Proof:

$$i^o = \frac{V}{R_i + R_L} \quad \textcircled{1}$$

$$P_L = i^2 R_L \quad \textcircled{2}$$

Put value of  $i^o$  from eq  $\textcircled{1}$  in  $\textcircled{2}$

$$P_L = \frac{V^2}{(R_i + R_L)^2} \cdot R_L \quad \textcircled{3}$$

Differentiate eq  $\textcircled{3}$  w.r.t  $R_L$

$$\frac{dP_L}{dR_L} = 0 \quad ; \Rightarrow ( )$$

$$\left( \frac{d^2 P_L}{d R_L^2} \right)_{( )} < 0 \text{ negative} \rightarrow \text{Maxima}$$

$$\Rightarrow \frac{V^2 \cdot R_L}{4 R_L^2} = \frac{V^2}{4 R_L}$$


$$\frac{dP_L}{dR_L} = \frac{(R_i + R_L)^2 [V^2] - V^2 R_L [2(R_i + R_L)(0+1)]}{(R_i + R_L)^4} = 0$$

$$2R_L = R_i + R_L$$

$$R_L = R_{L^0}$$

For Maxima ;

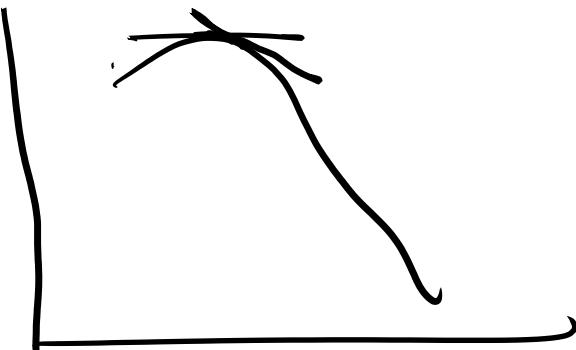
$$\left( \frac{d^2 P_L}{d R_L^2} \right)_{R_L=R_{L^0}} < 0 \quad [\text{Negative}]$$



Max. Power  $\Rightarrow$


$$P_{\max} = \frac{V^2}{4R_L}$$

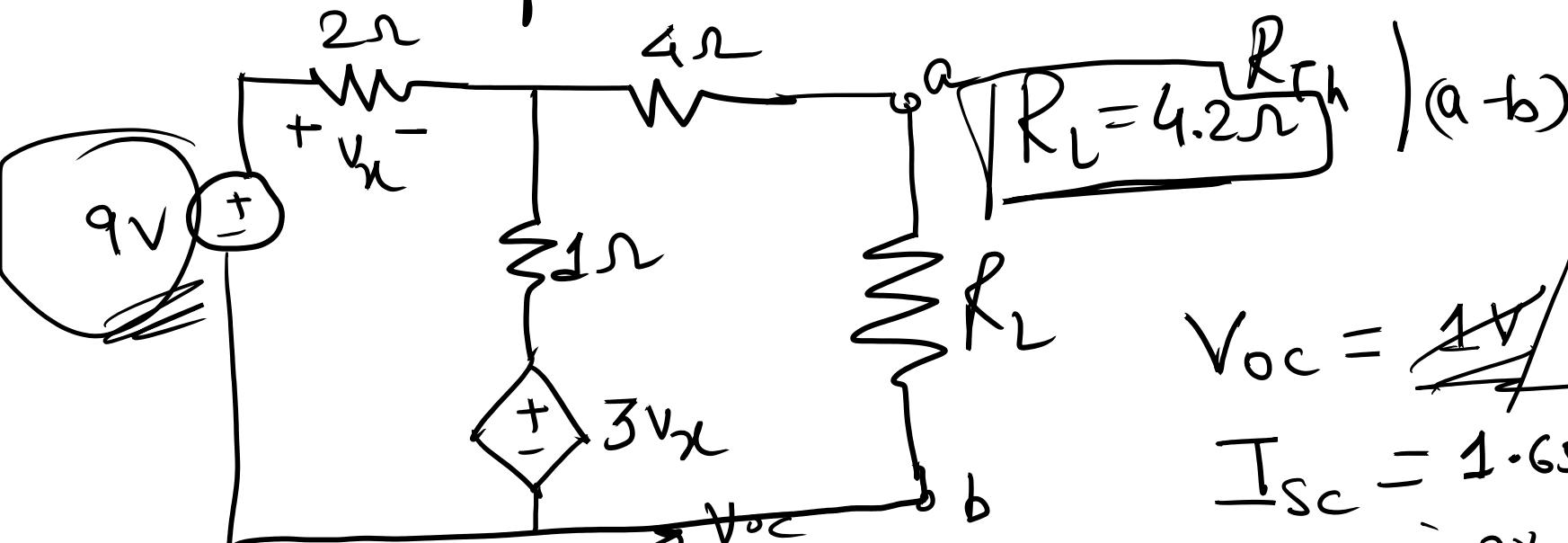\* Determine the value of  $R_L$  that will draw max. power from the rest of the circuit. Also calculate the max. power.



$$V_{oc} = \cancel{1V} / (7V)$$

$$I_{sc} = 1.65A$$

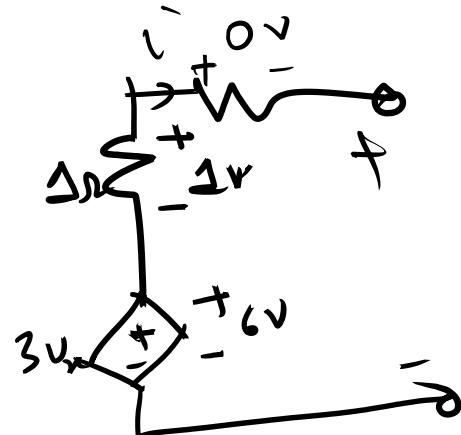

Yes -  $V_{oc}, I_{sc}$


No.  $\frac{V_{oc}}{I_{sc}} \rightarrow R_{eq}$

$R_{Th} = 4.2\Omega$



$$-6 - 1 + V_{oc} = 0$$

$$V_{oc} = 7V$$
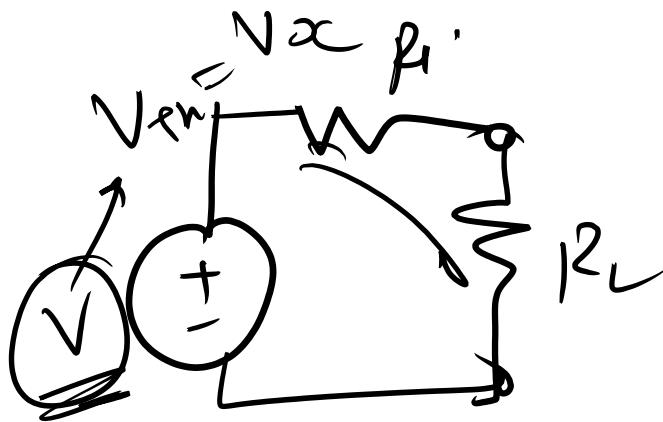
$$P = \frac{V^2}{4R_2} = \frac{7 \times 7}{4 \times 4.2} = 2.9W$$



$$P_L = \frac{V^2}{4R_L}$$

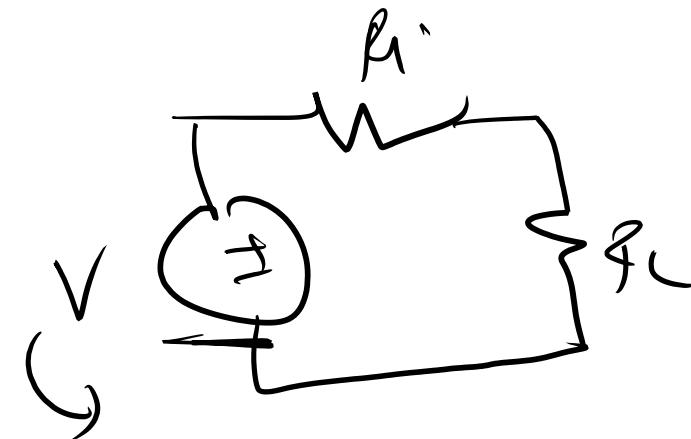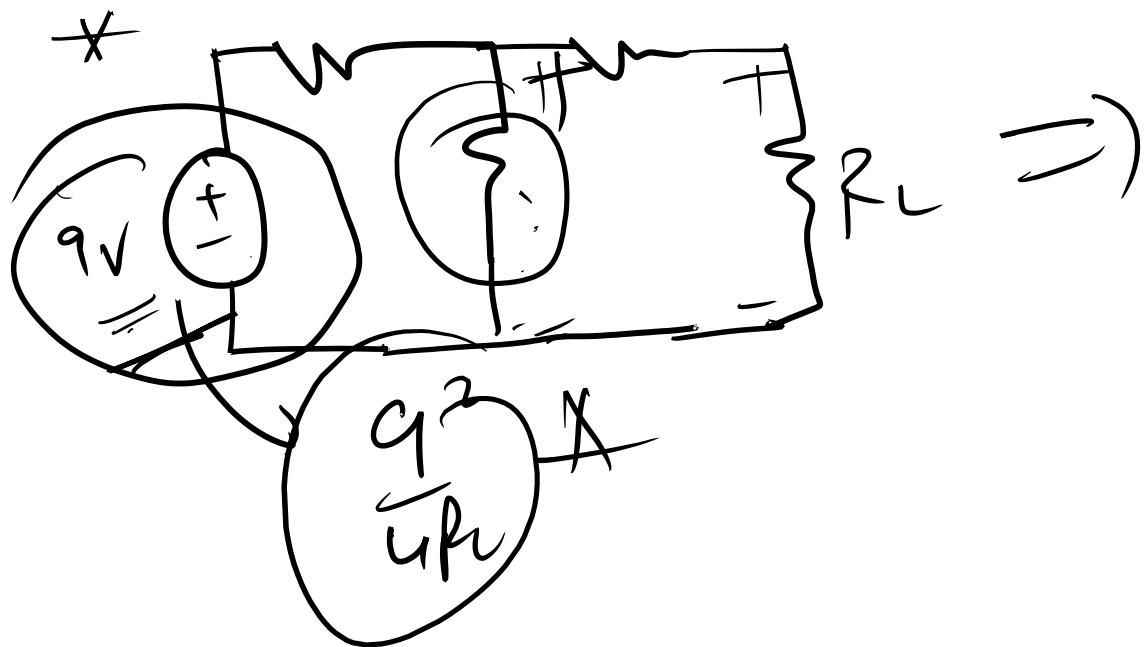


$$P_L = \frac{V^2}{4R_L}$$


## \* Star Delta Transformation




(1) Star ( $\lambda$ )

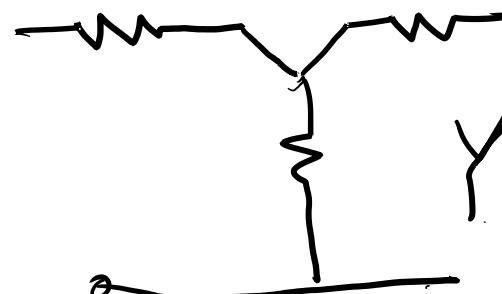

(2) Delta ( $\Delta$ )

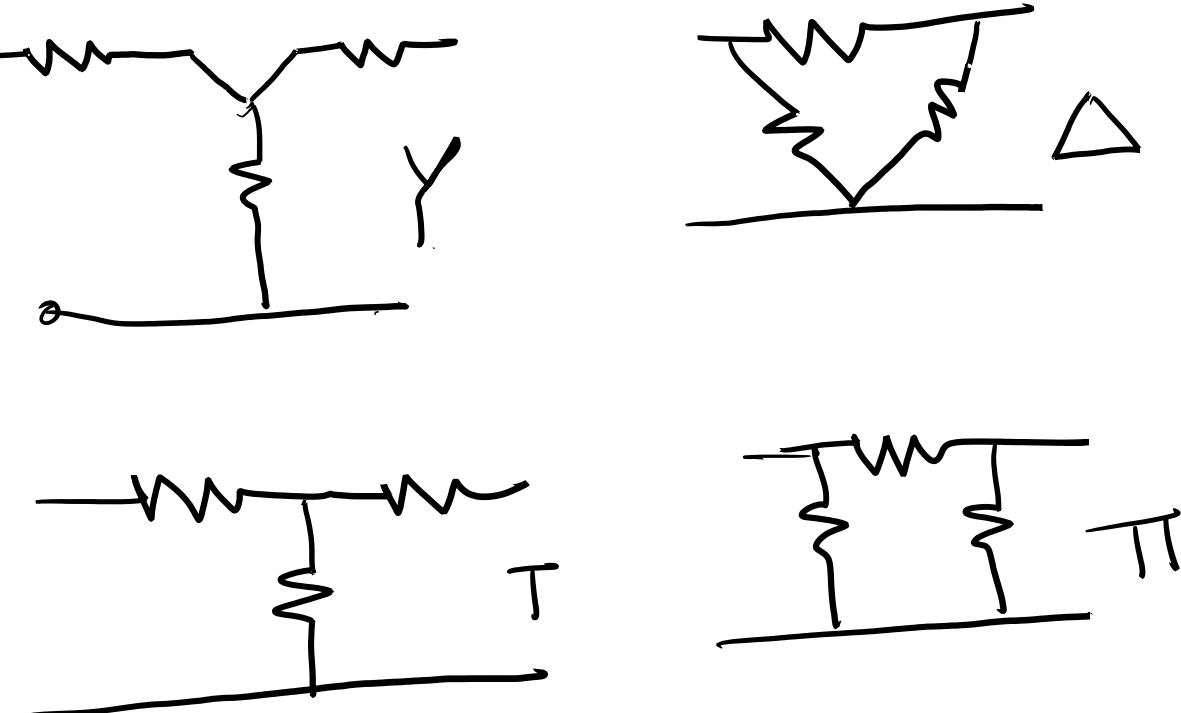


# ① Delta to Star Conversion

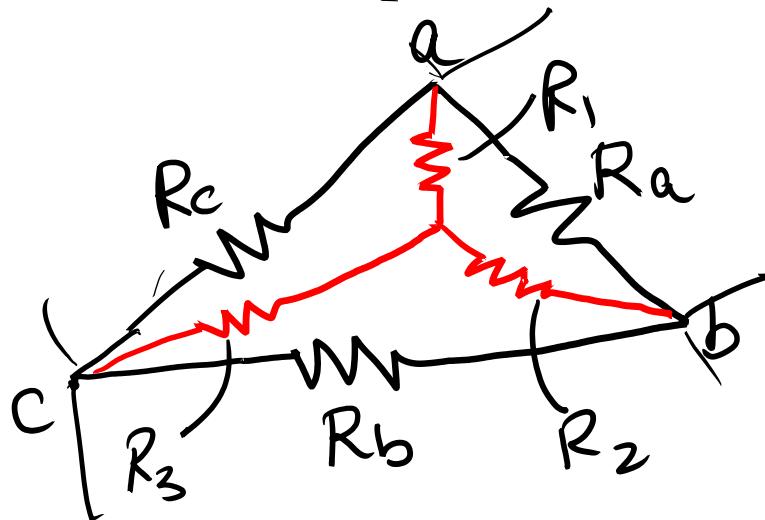

$\Delta \rightarrow \star$


$$(R_{ab})_{\Delta} = (R_b + R_c) \parallel R_a$$

$$(R_{ab})_{\star} = R_1 + R_2$$

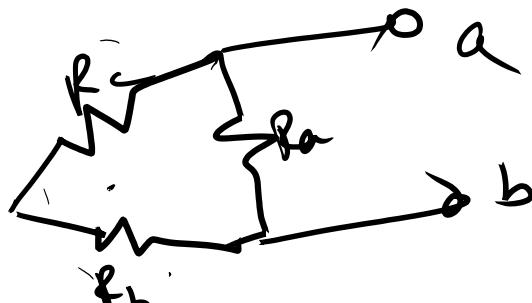

$$(R_{ca})_{\Delta} = (R_{ca})_{\star}$$
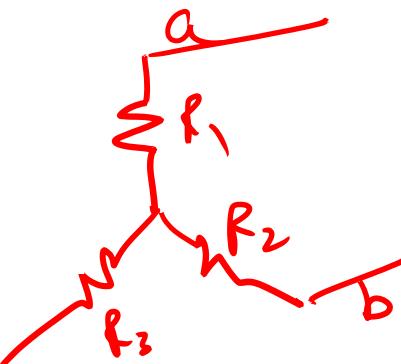
$$R_c \parallel (R_a + R_b) = R_3 + R_1$$



$$(R_{ab})_{\Delta} = (R_{ab})_{\star}$$

$$R_a \parallel (R_b + R_c) = R_1 + R_2 \quad \text{--- ①}$$

Similarly;

$$(R_{bc})_{\Delta} = (R_{bc})_{\star}$$

$$\text{② } R_b \parallel (R_a + R_c) = R_2 + R_3 \quad \text{--- ②}$$

$R_a, R_b, R_c \rightarrow \text{Known}$

$R_1, R_2, R_3 \rightarrow \text{Unknowns}$

$\checkmark R_1 = f(R_a, R_b, R_c)$

$\checkmark R_2 = "$


$\checkmark R_3 = "$

$$R_1 = f(R_a, R_b, R_c) = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_2 = f(R_a, R_b, R_c) = \frac{R_a R_b}{R_a + R_b + R_c}$$


$$R_3 = f(R_a, R_b, R_c) = \frac{R_b R_c}{R_a + R_b + R_c}$$
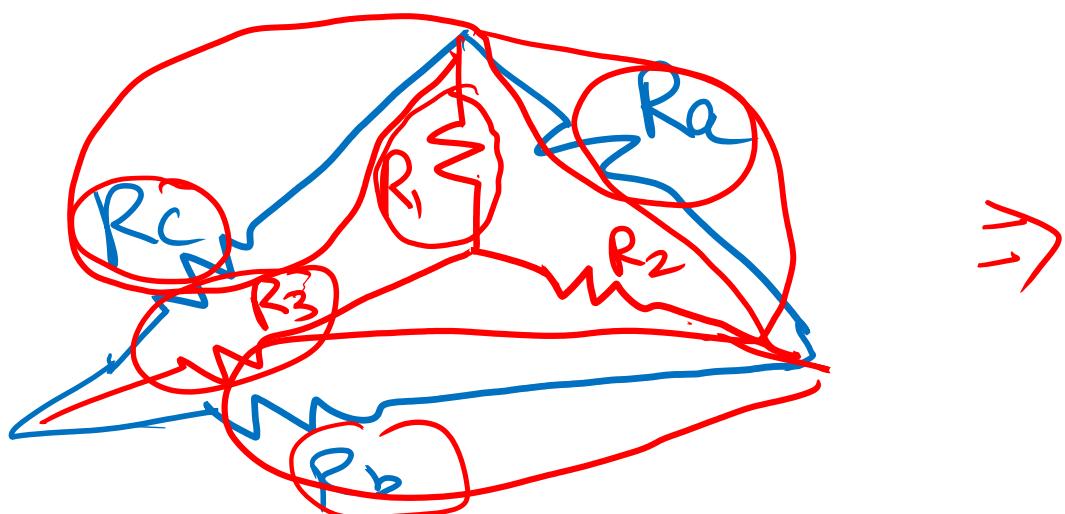
$$R_3 = \frac{R_c \cdot R_b}{R_a + R_b + R_c}$$



$$R_1 = \frac{R_a \cdot R_c}{(R_a + R_b + R_c)}$$
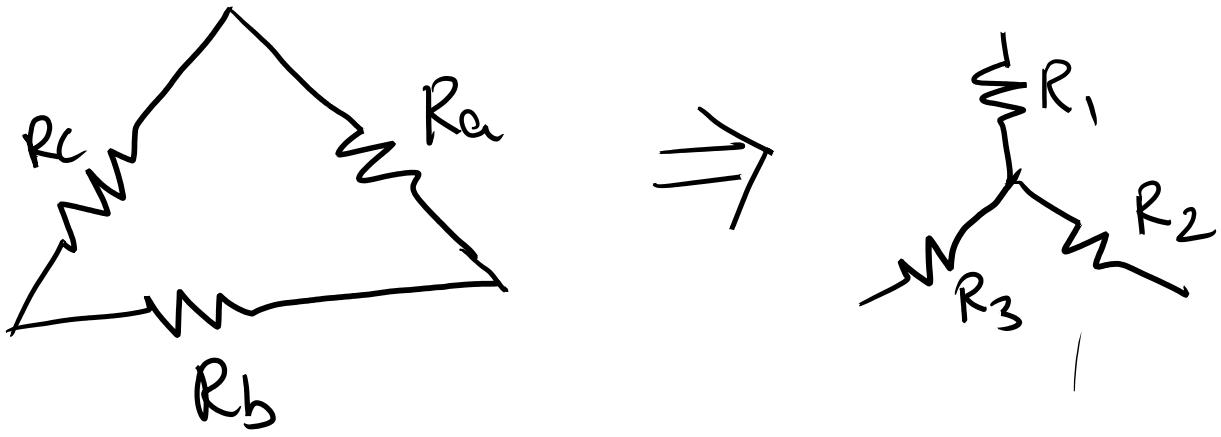
$$R_2 = \frac{R_a \cdot R_b}{(R_a + R_b + R_c)}$$



$$R_1 = \frac{R_a \cdot R_c}{(R_a + R_b + R_c)} \quad \text{--- } ①$$

$$R_2 = \frac{R_a \cdot R_b}{(R_a + R_b + R_c)} \quad \text{--- } ②$$

$$R_3 = \frac{R_b \cdot R_c}{(R_a + R_b + R_c)} \quad \text{--- } ③$$

## \* Star to Delta Conversion



from (1, 2, 3)

$$\Rightarrow R_1 R_2 + R_2 R_3 + R_3 R_1 =$$

Knowns  $\rightarrow R_1, R_2, R_3$

Unknown  $\rightarrow R_a, R_b, R_c$

$$R_a, R_b, R_c = f(R_1, R_2, R_3)$$

$$\frac{R_a^2 R_b R_c + R_b^2 R_a R_c + R_c^2 R_a R_b}{(R_a + R_b + R_c)^2}$$

$$= \frac{R_a R_b R_c (R_a + R_b + R_c)}{(R_a + R_b + R_c)^2} = \frac{R_a R_b R_c}{R_a + R_b + R_c}$$

(4)

Divide eq ④ by  $R_1 \Rightarrow$

$$\frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{R_a R_b R_c}{(R_a + R_b + R_c)} \quad \left| \begin{array}{l} \frac{R_a R_c}{(R_a + R_b + R_c)} \\ \hline \end{array} \right.$$

$$R_2 + R_3 + \frac{R_2 R_3}{R_1} = R_b \rightarrow ⑤$$

Divide eq ④ by  $R_2 \Rightarrow$

$$R_1 + R_3 + \frac{R_1 R_3}{R_2} = R_c \rightarrow ⑥$$

Divide eq ④ by  $R_3 \Rightarrow$



$$R_2 + R_1 + \frac{R_2 R_1}{R_3} = R_a \rightarrow ⑦$$



$$R_1 = \frac{R_a R_c}{(R_a + R_b + R_c)}$$

$$R_2 = \frac{R_a R_b}{(R_a + R_b + R_c)}$$
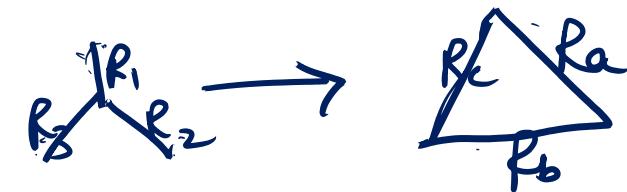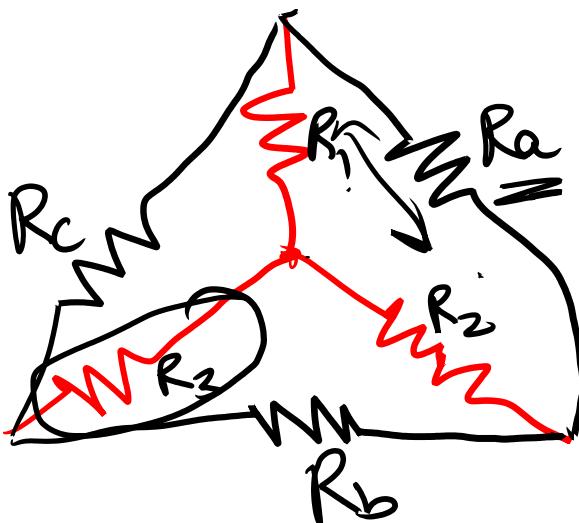
$$R_3 = \frac{R_c R_b}{(R_a + R_b + R_c)}$$




$$R_a = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_b = R_2 + R_3 + \frac{R_2 R_3}{R_1}$$

$$R_c = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$


$$R_a = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$
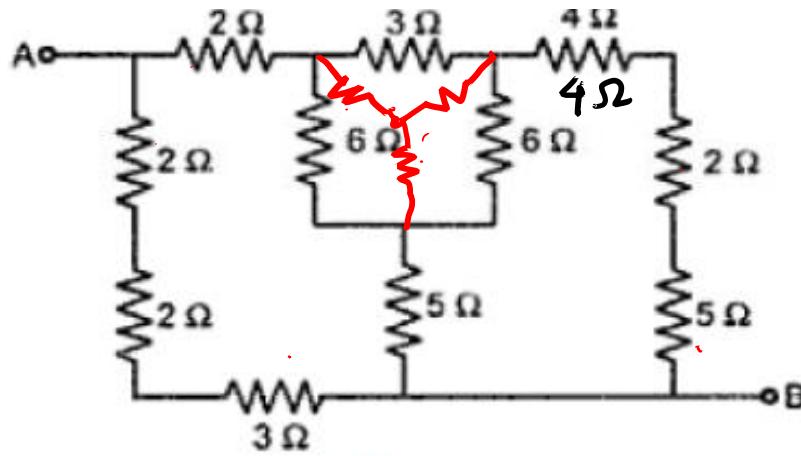
$$R_c = R_1 + R_3 + \frac{R_1 R_3}{R_2}$$



Find eq. Resistance b/w A&B:

$$R_{eq} = 3.69 \Omega$$

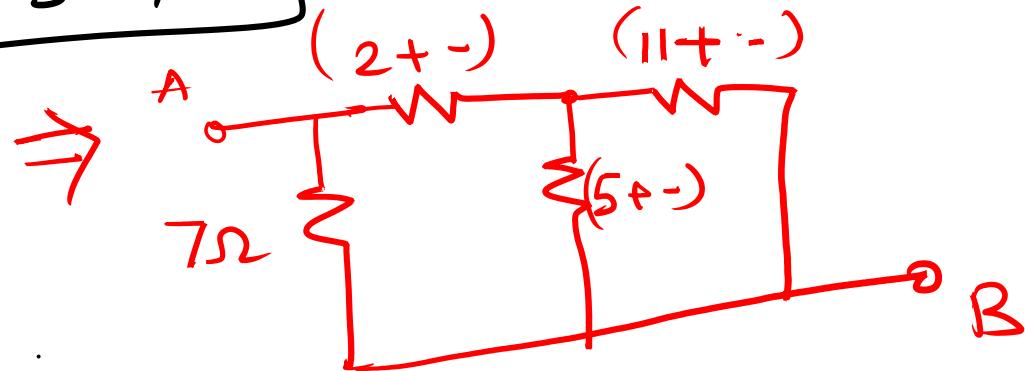

⇒ Transients (L & C)

(super node, mesh)

— KVL, KCL, Nodal, Mesh, Thvenin, Norton, Superposition, Max Power F, Source Transformation,  $\Delta = \lambda$